

10 New Construction Articles!

Underground DX
Page 42

Allband HF Antenna Page 10

73 Reviews Yaesu's FT-980 Page 90

Hamfest Hints

All About Op Amps Page 62

VIC-20 Prefix Program



Amateur Radio's Technical Journal

A Wayne Green Publication



Split Seconds-54

This Antenna Is Too Good To Be True

It's cheap. It works well on all bands.

And it radiates a super signal.

W4HDX 10

Construct the Minuteman Timer

The Secret of Remote Control

Inside those miniature planes lie some sophisticated circuits. WB3BQO 18

Calculate Your FT-101

Here's how to treat your trusty FT-101 to a truly automatic digital display and get a frequency counter in the same box—at the flick of a switch. VK8DE 22

Strictly for FM Deviates

Build a Better Hamfest

These hints from 25 years of experience will help make your event a success.

Housholder

Caveman Radio

With underground inductive transmission, 300 feet is almost DX.... W9MKV 42

Here's the Split-Second Timer

In the darkroom or the shack, this beeper has 1001 uses. Its simplicity makes it the perfect beginner's project.



Peak Your Picture with Home-Brew SSTV Gear

Op Art

Include the ubiquitous op amp in your next circuit. KCØEW tells how.

KCØEW 62

Put the DX World on a Screen

Everything you need to know about a country can be at your fingertips.

All you need is a VIC-20 and this program.

WB7RLX 69

Convert the Oddball Hy-Gain Board

Next Month: In Search of the Shuttle

Share the frustration, fatigue, and fun in the diaries of our special W5LFL correspondents. From Maine to Hawaii, they all gave Owen Garriott their best shots.

Never Say Die—6
73 International—73
Barter 'N' Buy—80
Social Events—83
FCC—83
Awards—84

Ham Help—85, 99 Corrections—85 New Products—86

Products—86 Letters—87 Dr. Digital—88
Fun!—89
Review—90
RTTY Loop—93
Contests—94
DX—96
Reader Service—98
Satellites—101
Dealer
Directory—130
Propagation—130

ICONIC-745

160-10 MTR 100W XCVR / 0.1-30 MHz RCVR



The IC-745 represents a major breakthrough in the ham industry...a full featured HF base station transceiver with a combination of standard features found on no other transceiver in its price range.

Compare these exceptional standard features:

- 100KHz 30MHz Receiver
- 16 Memories
- 100% Transmit Duty Cycle Transmitter with exceptionally low distortion
- IF Shift AND Passband Tuning
- Receiver Preamp
- 10Hz/50Hz/1KHz Tuning Rates with 1MHz band steps
- Adjustable Noise Blanker (width and level)
- Continuously Adjustable AGC with an OFF position
- Full function Metering with a built-in SWR Bridge
- Optional Internal AC Power Supply



Other Standard Features.

included as standard are many of the features most asked for by experienced ham radio operators: dual VFO's, RF speech compressor, tunable notch filter, all-mode squelch, program band scan, memory scan (frequency and modes are stored), receiver and transmitter incremental tuning and VOX.

designs and technology are used in the IC-745 all ham band transceiver which includes SSB, CW, RTTY, AM receive and an optional FM plus a 100KHz to 30MHz general coverage receiver.

ICOM System.

The IC-745 is compatible with ICOM's full line of standard HF accessories.

Accessories available include the IC-PS15 base supply, IC-PS30 system power supply (switching), IC-PS35 internal power supply, the IC-2KL linear amplifier, AT100 automatic antenna tuner, AT500 automatic antenna tuner, HP1 headphones, and HM12 hand or SM6 base microphone.

options. The EX241 marker and EX242 FM module, plus a wide variety of filters for sharp audio reception are available.

-6dB	Center
Width	Freq. MHz
500 Hz	9.000
270 Hz	9.000
2.1 KHz	0.455
500 Hz	0.455
250 Hz	0.455
	500 Hz 270 Hz 2.1 KHz 500 Hz

The IC-745 is the only transceiver today that has such features standard...the number of options and accessories available...and such an affordable price.





5-STORE BUYING POWER!



ETP ALPHA



MODEL LIST SALE 77DX \$5450 \$3775 78 \$2480 \$3495 374A \$2595 \$1860 \$1440 76A \$1985 76PA \$1695 \$2395 76CA \$1930 \$2695

> PRICES F.O.B. FACTORY

KENWOOD Specials

FM "DUAL BANDER"



2M and **70CM** in a single package

TW-4000A FOR \$599.95

and select two of the following items absolutely free!

- 1) VS-1 Voice Synthesizer. \$39.95 value.
- 2) TU-4C sub-audible tone generator. \$39.95 value.
- 3) MA-4000 Duo-band Mobile Antenna. \$44.95 value.

TS-930S



W/ANTENNA TUNER Plus 3 BONUS ITEMS

1) SP-930 SPEAKER

2) MC-60A MICROPHONE

3) YK-88C-1 FILTER

REG. \$2029 VALUE

CALL FOR YOUR LOW PRICES

TS-430S TR-7950





E NEW TON BEEN

NEW DICOM

\$1399 PRICE **INCLUDES FREE \$160 PS-35 POWER SUPPLY**

INVISE TO THE PARTY OF THE PART

(Mounts internally)





IC-271A

IC-471A 2 M • 25W • ALL MODE 430-450 MHz • ALL MODE

CALL FOR YOUR SPECIAL PRICE



W-51 **SALE \$799**

W-36 CALL FOR PRICE

LM-470D **CALL FOR PRICE**

SERVING HAMS

BETTER.

North...south...east...west.

Bob Ferrero, W6RJ

Jim Rafferty, N6RJ

personalized

service.

other well known hams

give you courteous,

KT-34A SALE \$299

KT-34XA **SALE \$459**

PRICES ARE FOB CALIF. **EXCEPT FOR CERTAIN** COMBINATIONS. PLEASE INQUIRE

B-3016 REG. \$239.95 **SALE \$199.95**

B-1016 REG. \$279.95 **SALE \$249.95**

B-108 REG. \$179.95 SALE \$159.95

B-23S REG. \$89.95 SALE \$79.95

B-1010 REG. \$319.95 SALE \$289.95

CALL FOR LOW PRICES

ON HAND-KELDS and all YAESU ITEMS

FT-208R



FT-757GX



FT-726R FT-708R

HAM

RHO)(O)

OUTHANT

UPS (Surface) FREE SHIPM CONTINENTAL U.S.A.

ON MOST ITEMS THAT CAN BE SHIPPED UPS BROWN. THERE ARE SOME EXCEPTIONS IN ALPHA, TRI-EX AND KLM

FREE

9:30AM to 5:30PM PACIFIC TIME.

OVER-THE-COUNTER, 10AM to 5:30PM. MONDAY THROUGH SATURDAY

CALIFORNIA CUSTOMERS PLEASE PHONE OR VISIT LISTED STORES

ANAHEIM, CA 92801 2620 W. La Palma.

(714) 761-3033 (213) 860-2040

Between Disneyland & Knott's Berry Farm

999 Howard Ave., (415) 342-5757 5 miles south on 101 from S.F. Airport

BURLINGAME, CA 94010

VAN NUYS, CA 91401

6265 Sepulveda Blvd., (213) 988-2212 San Diego Fwy at Victory Blvd.

MINI-PRODUCTS * MIRAGE * NYE * PALOMAR * ROBOT * ROHN SHURE * SIGNAL-ONE * STONER * TEMPO * TEN-TEG * TRISTAU VIEWSTAR . VOCOM . YAESU and many more!

OAKLAND, CA 94609

2811 Telegraph Ave., (415) 451-5757 Hwy 24 Downtown. Left 27th off-ramp.

AEA + ALLIANCE + ALPHA + AMECO + AMPHENOL + ARRL + ASTRON AVANTI * BELDON * BENCHER * BERK-TEC * BIRD * B & W BUTTERNUT * CALLBOOK * CDE * COLLINS * CURTIS * CUSHCRAFT SAN DIEGO, CA 92123


5375 Kearny Villa Road (619) 560-4900 Hwy 163 & Clairemont Mesa Blvd

DAIWA . DRAKE . DX EDGE . DX ENGINEERING . EIMAC HUSTLER * HY-GAIN * ICOM * J. W. MILLER * KANTRONICS KENWOOD * KLM * LARSEN * LUNAR * METZ * MFJ * MICRO-LOG

Prices, specifications, descriptions subject to change without notice. Calif residents please add sales lax.

VISA

1984 CALLBOOKS

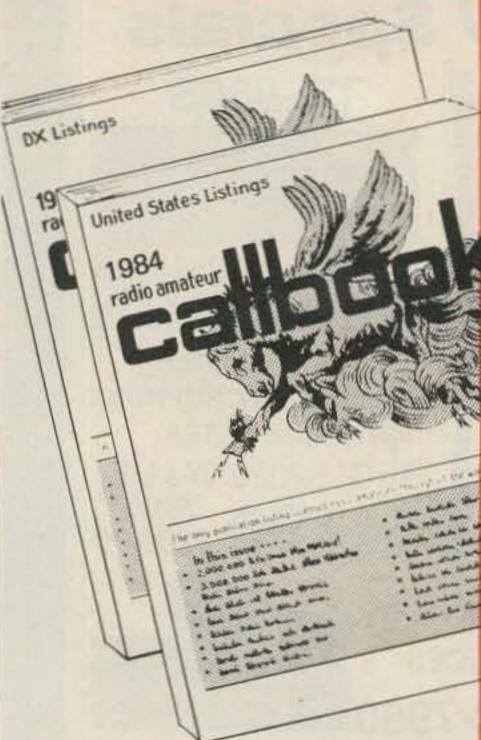

Order today! **NEW 1984 RADIO AMATEUR CALLBOOKS**

Known throughout the world for accuracy, the 1984 Callbooks are a better value than ever before. The U.S. Callbook contains over 433,000 listings; the Foreign Callbook has over 413,000. More than 100,000 changes have been made in each edition since last year. Special features include call changes, Silent Keys, census of amateur licenses, world-wide QSL bureaus, international postal rates, prefixes of the world, and much more. You can't beat this value! Order your 1984 Callbooks now.

Each Shipping Total

DU.S. Callbook \$19.95 \$3.05 \$23.00 □ Foreign Callbook 18.95 3.05 22.00

Order both books at the same time for \$41.95 including shipping within the USA.

Order from your dealer or directly from the publisher. Foreign residents add \$4.55 for shipping. Illinois residents add 5% sales tax.

Keep your 1984 Callbooks up to date.

The U.S. and Foreign Supplements contain all activity for the previous three months including new licenses. Available from the publisher in sets of three (March 1, June 1, and September 1) for only \$12.00 per set including shipping. Specify U.S. or Foreign Supplements when ordering. Illinois residents add 5% sales tax. Offer void after November 1, 1984.


RADIO AMATEUR II BOOK INC.



Dept. B 925 Sherwood Dr., Box 247 Lake Bluff, IL 60044, USA


V61

Tel: (312) 234-6600 WSA

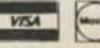



Novices... **Technicians**

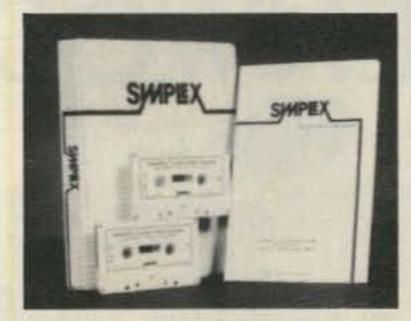

- Don't let Morse code requirement keep you from upgrading
- General Class Code course takes you from 6-16 w.p.m.
- Simple, effective method helps you progress quickly.
- Deluxe album with two 1-hour cassettes and instruction booklet.

P.O. Box 7010, Dept. 73-1 Bismarck, ND 58502

Send \$19.00 plus \$1.00 shipping or write for free information

Prompt Shipping!

DTMF DECODER

The LJM2RK decoder kit converts your receiver into a special receiver or control. When a user-selected timetone combination is received, the output provides a relay control for activating speakers or other devices.

INPUT: Audio from transceiver, scanner, etc. OUTPUT: SPST (N.O.) relay.

FEATURES: Single or dual tones adjustable over the 16 digit Touch Tone range . Adjustable response time . Relay output . Manual or auto reset . Single tone ON latching with different single tone reset OFF . Operates on 12VDC . Interfacing of multiple boards for multi-digit sequential activation and reset.

APPLICATIONS: Call-up system * Repeater or commercial controls . Etc. limited only to your imagination .



Actual Size 3"x3" - Shown Assembled

LJM2RK decoder kit includes all component, relay, and P.C. Board. . . . \$15 plus \$1.50 shipping.

LJM2RC enclosure kit includes molded case, speaker, input cable. . . .\$5 plus \$1.50 shipping.

For information and to order write:

THE METHENY CORPORATION 204 Sunrise Drive, Madison, IN 47250 205

INFO

Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the 73 editorial offices. "How to Write for 73" guidelines are available upon request.

Editorial Offices:

Pine Street Peterborough NH 03458 Phone: 603-924-9471

Advertising Offices:

Elm Street Peterborough NH 03458 Phone: 603-924-7138

Circulation Offices:

Elm Street Peterborough NH 03458 Phone: 603-924-9471

Subscription Rates

In the United States and Possessions: One Year (12 issues) \$25.00 Two Years (24 issues) \$38.00 Three Years (36 issues) \$53.00

Elsewhere:

Canada and Mexico-\$27,97/1 year only, U.S. funds. Foreign surface mail-\$44.97/1 year only, U.S. funds drawn on U.S. bank. Foreign air mail-please inquire.

To subscribe, renew or change an address:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address, include the address label from your most recent issue of 73. For gift subscriptions, include your name and address as well as those of gift recipients.

Subscription problem or question:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. Please include an address label.

73: Amateur Radio's Technical Journal (ISSN 0745-080X) is published monthly by Wayne Green, Inc., 80 Pine Street, Peterborough NH 03458. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Entire contents copyright@ 1983, Wayne Green, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition-University Microfilm, Ann Arbor MI 48106. Postmaster: Send address changes to 73, Subscription Services, PO Box 931, Farmingdale NY 11737. Nationally distributed by International Circulation Distributors.

THE ULTIMATE SCANNER RADIO HAS ARRIVED.

Starting today, we're standing the scanner radio on its ear. Because we've forged ahead—way ahead—in radio frequency and digital technology.

Introducing the Bearcat[®] CompuScan[™] 2100.


It's the first scanner radio designed to put the power of a personal computer to work for you. Now you can scan up to two hundred channels. Stack levels of priority so you'll hear vital calls in order of importance. Automatically search, store and count transmissions for accurate "pictures" of activity within frequency limits you select.


And with automatic video memos you'll know more than you've ever known before. The channel user, special codes, jurisdictions, phone numbers, alternate frequencies—any information you've programmed is automatically displayed when the channel is active.


With ten bands including 70centimeter, 2, 6 and 10 meter FM Amateur, Military Land Mobile, AM Aircraft, plus Low, High, UHF and UHF-T bands.

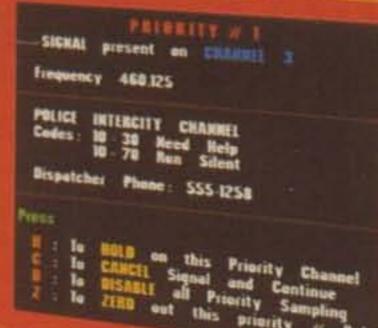For a real earful—and eyeful see your Bearcat scanner dealer. For the name of the dealer nearest you, just call 1-800-S-C-A-N-N-E-R.





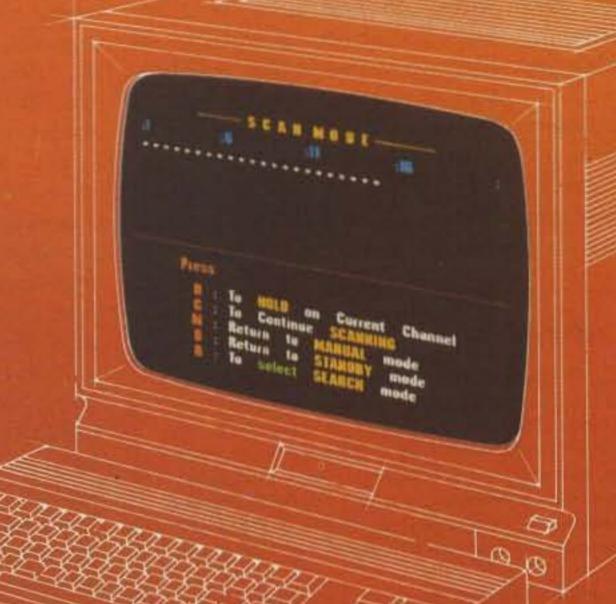

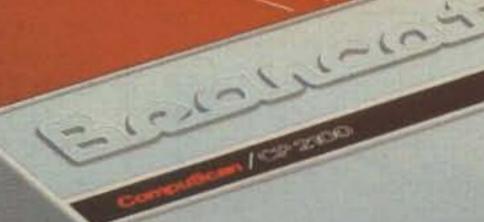

BEARCAT



Electra Company
Division of Masco Corp. of Indiana
300 East County Line Road
Cumberland, Indiana 46229

- 120

© 1983 Masco Corp of Indiana

W2NSD/1 NEVER SAY DIE

editorial by Wayne Green



EGO

Yes, when you write to Wayne Green, I get your letters. Usually I answer, too, much to the surprise of a lot of hams. There is some sort of weird concept that because someone is rich and famous, he is no longer reachable.

Ha! There's that Wayne Green ego again—rich and famous, indeed! Well, golly, I am rich in some ways—and though I've worked a lot harder than most

people to get this way, many begrudge it. I've been writing for how many years now telling you how to get rich? I wrote a booklet on the subject twenty years ago. And fame? Well, I'm well known in a couple of esoteric circles, if that qualifies. Wayne Green is not yet a household term.

Several letters of interest arrived in the last few days. One chap advised me that he was canceling his subscription because my ego is too big and three thanked me for egging them on to become entrepreneurs and making them rich. Well, I don't know what to do about my ego except ask you to live with it and enjoy it the way I do. Without my ego prodding me, I'm not sure where a lot of things would be.

It's a funny thing about "rich." Sure, I have millions to spend just about any way I want, so what am I doing with all of that loot? Well, for the most part, I am using it to help people with ideas bring them to fruit and to make some of my own ideas work. A plane? Nope, I tried that almost 30 years ago, back in '57, and got it out of my system. A big house, right? Tried that in '69 and didn't like it. No, I have a small room over my office which is all I need for the few hours I waste sleeping each day. I've been putting in hundred-hour weeks for years and enjoying it.

A few weeks ago, I attended an evening class in the art of conversation here in Peterborough. Each of us was asked to explain why we'd come to the class. My rationalization was that I really didn't know how to cope with cocktail parties. What in the hell can one possibly talk about when meeting someone for the first time in a noisy room where the meeting will be for only a few minutes? As I explained, I realized that I had exactly outlined one of the big problems with amateur radio-we meet new people under noisy conditions and are expected to provide some entertainment.

I was assured by everyone else in the class that my prob-


Continued on page 100

HELP WANTED

73 is currently seeking a TECHNICAL/INTERNATIONAL EDITOR. The position requires excellent written and oral communications skills, as well as a General-class or higher ticket. Experience with microcomputers would be a help. Responsibilities include participating in manuscript review, organizing and implementing special projects, and supervising our staff of foreign correspondents.

We offer a competitive salary and benefits package and excellent, informal working conditions. As you may know, Peterborough is located 75 miles from Boston in the beautiful Monadnock region of New Hampshire—a state with no sales or income tax.

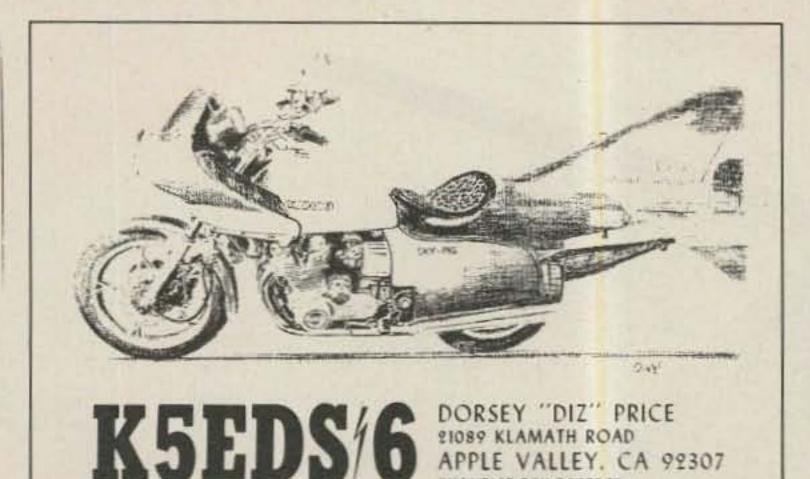Of course, we are an equal opportunity employer. If you are a non-smoker interested in this position, please forward your resume and salary requirements to: Jack Burnett, Executive Editor, 73: Amateur Radio's Technical Journal, Peterborough NH 03458.



QSL OF THE MONTH

We don't know what a "Sky-Pig" is, either, but it sure makes you take a look at Diz Price's card.

To enter your QSL, put it in an envelope along with your choice of a book from 73's Radio Bookshop and mail it to 73, Pine Street, Peterborough NH 03458, Attn: QSL of the Month. Entries not in envelopes or without a book choice will not be accepted.

STAFF

EDITOR/PUBLISHER
Wayne Green W2NSD/1
ASST. EDITOR/PUBLISHER
Jeff DeTray WB8BTH
EXECUTIVE EDITOR

MANAGING EDITOR Susan Philbrick

John C. Burnett

ASST. MANAGING EDITOR Steve Jewett

EDITORIAL ASSISTANTS

Nancy Noyd Richard Phenix

ASSOCIATES

Robert Baker WB2GFE
John Edwards KI2U
Bill Gosney KE7C
Chod Harris VP2ML
Avery L. Jenkins WB8JLG
Dr. Marc Leavey WA3AJR
J. H. Nelson
Bill Pasternak WA6ITF
Peter Stark K2OAW
Robert Swirsky AF2M

PRODUCTION DIRECTOR Nancy Salmon

ADVERTISING GRAPHICS MANAGER

Scott W. Philbrick

DESIGN DIRECTOR Christine Destrempes

PRODUCTION

Lahri Bond
Patricia Bradley
Linda Drew
Michael Ford
Marjorie Gillies
Donna Hartwell
Paula Ramsey
Anne Rocchio
Lynne Simonson
Jean Southworth
Kenneth Sutcliffe
Theresa Verville

PHOTOGRAPHY

Robert M. Villeneuve

Thomas Villeneuve Sandra Dukette Nathaniel Haynes Laurie Jennison Sturdy Thomas

TYPESETTING

Sara Bedell
Darlene Bailey
Marie Barker
Prem Krishna Gongaju
Lynn Haines
Cynthia Letourneau

Kimberly Nadeau Debbie Nutting Lindy Palmisano Heidi N. Thomas Sue Weller

VICE PRESIDENT/GENERAL MANAGER
Debra Wetherbee

ICE PRESIDENTICONTROLLE

VICE PRESIDENT/CONTROLLER
Roger J. Murphy

ASSISTANT TO THE PRESIDENT

Matthew Smith KA1IEI
ACCOUNTING MANAGER

Knud Keller KV4GG/1
CIRCULATION MANAGER

William P. Howard (603)-924-9471

RETAIL AND NEWSSTAND SALES MANAGER

> Ginnie Boudrieau 1-(800)-343-0728

ADVERTISING (603)-924-7138

Jim Gray W1XU, Mgr. Nancy Ciampa, Asst. Mgr. Ross Kenyon KA1GAV Cindy L. Molesky



FM-201A/TM-401A

Iltra-compact and ghtweight, priority, nemory and band scan, 5 watts/TM-201A & 2 watts/TM-401A.

he KENWOOD TM-201A

meter and TM-401A 70-cm

M mobile transceivers are the
mallest and lightest units
vailable, allowing maximum
exibility in automotive
estallation.

TM-201A/TM-401A FEATURES:

- Ultra compact and lightweight Measures 5.6 (141)W x 1.6 (39.5)H x 7.2 (183)D, inch(mm), weighs 2.8 lbs., (1.25 kg.).
- 25-watt output, with HI/LO power switch
 Produces a powerful 25 watts RF output from a surprisingly compact design (TM-201A).
- · Dual digital VFO's built-in
- 5 memories plus "COM" channel, with lithium battery back-up (est. 5 yr. life)

- Memory scan/programmable band scan
- · Priority alert scan
- Highly visible yellow LED frequency display
- High performance receive/transmit
 GaAs FET RF amplifier for high sensitivity with wide dynamic range. Transmit modulation characteristics selected for best sound and minimum distortion.
- External high quality speaker supplied (No internal speaker)
- 16-key autopatch UP/DOWN microphone

Optional FC-10 frequency

May be easily connected to the TM-201A or TM-401A. Convenient control keys for frequency UP/DOWN. MHz shift, VFO A/B. and MR (memory recall or change memory channel). A green, easy-to-read, back-lighted LCD display indicates transmit/receive frequencies, memory channel number, ALERT, and

channel number, ALERT, and SCAN (with blinking MHz decimal). Size: 4.4 (112)W x 1.4 (35)H x 0.9 (22)D, inch(mm). Weight: 3.5 oz. (100 g).

- Repeater offset switch (±600kHz/TM-201A; ±5 MHz/TM-401A; and simplex) and reverse switch
- Audible "BEEPER" confirms operation
- · Easy-to-install mobile mount

TM-201A/TM-401A accessories:

- TU-3 programmable twofrequency CTCSS encoder
- KPS-7A fixed station power supply



FW-4000A

M "Dual-Bander"...
-m & 70-cm in single ompact package, CD, 25 W, optional oice synthesizer.

ENWOOD'S TW-4000A FM
Dual-Bander" provides new
ersatility in VHF and UHF opertions, uniquely combining 2-m
and 70-cm FM functions in a
ngle compact package.

W-4000A FEATURES:

2-m and 70-cm FM in a Compact Package Covers the 2-m band (142.000148.995 MHz), including certain MARS and CAP frequencies, plus the 70-cm FM band (440.000-449.995 MHz), all in a single compact package. Only 6-3/8 (161)W x 2-3/8 (60)H x 8-9/16 (217)D inches (mm), and 4.4 lbs. (2.0 kg.).

- Large, Easy-to-Read
 LCD Display
- 25 Watts RF Power on 2-m/70-cm.
- Opt. "Voice Synthesizer Unit"
 Installs inside the TW-4000A.
 Voice announces frequency, band, VFO A or B, repeater offset, and memory channel number.
- Front Panel Illumination
- 10 Memories with Offset Recall and Lithium Battery Backup

- Programmable Memory Scan
- Band Scan in Selected 1-MHz Segments
- Priority Watch Function
- Common Channel Scan
- Dual Digital VFO's
- 16-Key Autopatch UP/DOWN Microphone
- Repeater Reverse Switch
- High Performance

Receiver/Transmitter
GaAs FET RF amplifiers on both
2-m and 70-cm, high performance MCF's in the 1st IF section,
provide high receive sensitivity
and excellent dynamic range.
The high reliability RF power
modules assure clean and
dependable transmissions on
either band.

- Rugged Die-cast Chassis
- "BEEPER" sounds through speaker.
- Easy-to-Install mobile mount


TW-4000A accessories:


- VS-1 voice synthesizer
- TU-4C programmable twofrequency CTCSS encoder
- KPS-7A fixed station power supply
- SP-40 compact mobile speaker
- SP-50 high quality mobile speaker
- MA-4000 dual-band mobile antenna with duplexor



Blueprint for Success

THE INTERFACE

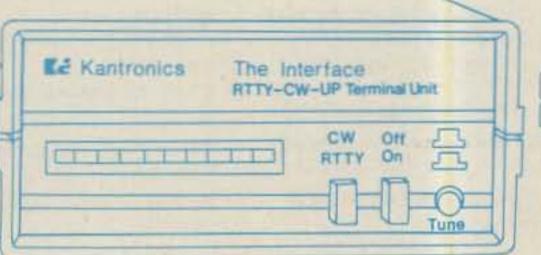

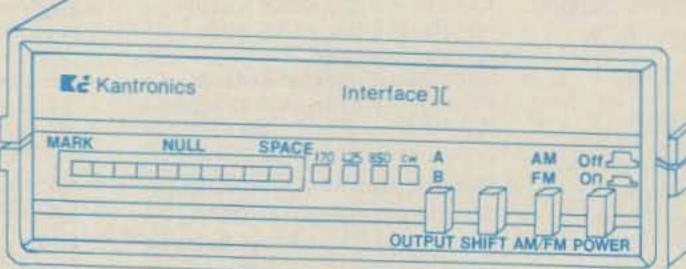

THE INTERFACE 1[

K&Kantronics

TITLE: THE INTERFACE - INTERFACE 1 | PROPOSAL

THE INTERFACE is the original Kantronics terminal unit that broke through the barrier of multi-computer compatibility. THE INTERFACE is an amateur modem for transceiver-to-computer communication. With THE INTER-FACE and Hamsoft or Hamtext for your computer you can send and receive Morse Code, Radioteletype, and ASCII. THE INTERFACE is also compatible with our new software for AMTOR communication, AMTORSOFT. THE INTERFACE is our most popular unit combining active filtering, easy tuning, six-computer compatibility, and low price for an unbeatable package.

INTERFACE It is the new Kantronics transceiver-to-computer interface. INTERFACE It features a new highly sensitive front end with mark and space filtering and a unique new tuning system. Even the most discerning operator will be surprised with the INTERFACE It's ability to dig out signals in poor band conditions, and our new tuning system even displays signal fading.

X-Y scope outputs and dual interface outputs for VHF and HF connections make INTERFACE II compatible with almost any shack. All three standard shifts are selectable and INTERFACE II is compatible with the industry standard Kantronics programs: Hamsoft, Hamtext, and Amtorsoft. Step up to state of the art in computer-amateur communications with INTERFACE II.

Suggested Retail \$269.95

For more information see your Kantronics dealer, or contact:

Kantronics 1202 E. 23rd Street Lawrence, KS 66044

KANTRONICS SOFTWARE Hamsoft,™ Hamtext,™ and Amtorsoft™

MORSE

00:00:00

TRANSMIT SPEED 25 RECEIVE SPEED

ENJOY YOUR MEAL AND WE'LL TALK TO YOU REAL SOON ... 73'S ... WA5RGU WEATHER HERE IS WARM TODAY WITH LOTS OF SUN. . . XYL SAYS TIME FOR DINNER SO 73'S WØXI

Kantronics has led the amateur community in software and total computer communications systems with our original program, HAMSOFT. With five-computer compatibility and reasonable prices HAMSOFT has become the industry standard. HAMSOFT includes split screen display, type ahead buffer, message ports, and complete keyboard control for Morse Code, Radioteletype, and ASCII communications. With THE INTERFACE or INTERFACE 11, HAMSOFT can make any of five computers a complete amateur communications terminal. All programs are on a ROM board, except the Apple diskette.

VIC-20 - \$49.95, ATARI - \$49.95, APPLE - \$29.95,

TRS-80C - \$59.95, TI-99/4A - \$99.95

HAMTEXT is our advanced CW/RTTY/ASCII program for the VIC-20, COMMODORE 64, and APPLE computers. HAMTEXT gives you the ability to store incoming messages in the computer's memory, transmit files directly from tape or disk, and use your computer to its fullest potential. Features like Diddle, Time Transmission, Text Transmission, Printer Outputs, and Word Wraparound, make **HAMTEXT** the program for the serious amateur. HAMTEXT was created with input from our users as guidelines, and with total use of the computer in mind. Suggested Retail\$99.95

00:00:00

PROGRAM OPTIONS

A. RETURN TO BASIC

B. EDIT MESSAGE PORTS

C. SAVE MESSAGE PORTS

D. LOAD MESSAGE PORTS

E. SET XMIT BUFF SIZE

F. EDIT HOLDING BUFFER

G. SAVE HOLDING BUFFER

H. LOAD HOLDING BUFFER

I. SET TIME

00:00:00 KANTRONICS AMTORSOFT COPYRIGHT 29 JUNE 1983

CHOOSE S (AMTOR SLAVE) M (AMTOR MASTER) L (AMTOR LISTENER) P (PROGRAM OPTIONS) T (T/R OPTIONS)

On January 27th, 1983, AMTOR, Amateur RadioTeletype Over Radio, became a legal mode for the amateur service. AMTOR is an essentially error-free radioteletype form of communication. AMTORSOFT, Kantronics' newest software package, gives your computer the ability to become an AMTOR communications terminal when used with The Interface or interface 11. AMTOR-SOFT is currently available for the Apple, VIC-20, and COM-64 computers. AMTORSOFT brings you the newest in computer-amateur communications at an affordable price.

Suggested Retail*89.95

For more information see your Kantronics dealer, or contact: **Kantronics** 1202 E. 23rd Street Lawrence, KS 66044

This Antenna Is Too Good To Be True

It's cheap. It works well on all bands. And it radiates a super signal.



Completed antenna mounted in tree.

ould you like to have an antenna that is capable of working all the HF bands, or any combination of the HF bands including the new WARC bands, with excellent results, at a fraction of the cost of any of the commercially-available multi-band antennas now on the market? Would you also like to have an antenna with an extremely low noise factor? I'm about to describe an antenna that is just what you've been looking for.

This antenna is a combination of the old reliable Zepp with the addition of a balanced, shielded feeder system which has been described in various articles in past years.

This antenna has been in

use at this QTH as well as other locations for over two years and has yielded many fine DX contacts and many good reports stateside.

To determine the comparable merit of this antenna, I erected separate dipoles cut for the center of each band and fed with a single coaxial cable. Then I connected all antennas so they could be switched rapidly to determine the comparable signal strength of each as compared to the Zepp antenna.

In addition to the favorable signal strength comparisons, I also found that the noise level on the Zepp antenna was as much as 5 S-units lower than the noise on the cut-to-frequency dipole with single coax feed. I noticed this particularly on

Desired Bands of Operation	Length of Each Side of Antenna From Center to Each End
160-10 meters	108 feet
80-10 meters	54 feet
40-10 meters	27 feet
30-10 meters	18.7 feet
20-10 meters	13.5 feet
17-10 meters	10.4 feet
15-10 meters	9 feet
12-10 meters	7.8 feet

Table 1.

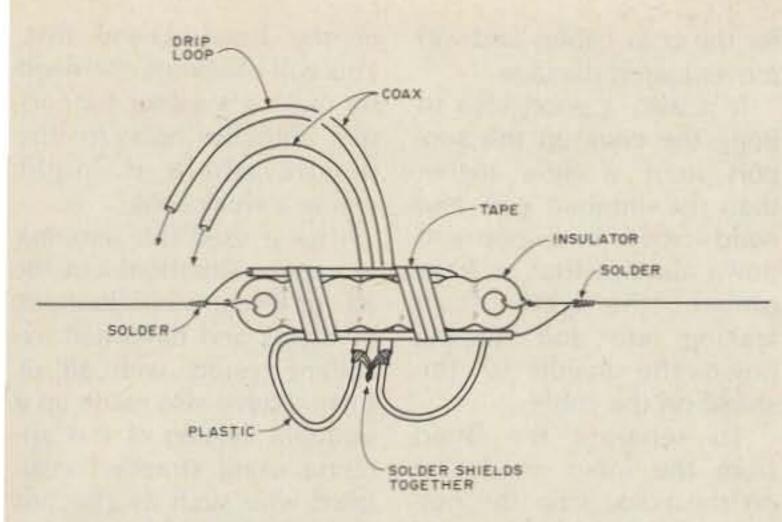


Fig. 1. Method of supporting coax cables.

the model of this antenna which was erected inside the attic of the house in close proximity to the ac wiring of the building, where the noise level dropped from an S-7 on the regular dipole to an S-2 on the Zepp antenna.

To erect this antenna, you simply figure the length of each side of the flat-top from the center to one end by using the figures shown in Table 1.

This antenna can be cut bination of the HF ham bands, including the WARC bands which have not yet been released. For example, if your space is limited, you could put an antenna in the attic of the house, as I did at one location where I had an attic length of only about 30 feet, by figuring the antenna for operation on the bands from 30 through 10 meters, resulting in a length each side of center of 18.67 feet. Then I ran the wire in a Z configuration through the attic to compress it into the available space.

I have used various configurations on this antenna, such as the halo and the inverted vee, and all give good results. If you can get the wire running in a fairly straight line, though, your radiation pattern will be more predictable.

The flat-top portion is designed so that it is non-resonant on all bands of operation, thereby avoiding any extremely high or extremely

low impedance points at the feedpoint. It is designed to be resonant between the one-quarter, half, threequarter, and full-wave points on each band, thereby presenting an impedance to the antenna tuner which is well within range of the tuner on each band and will not cause any loading problems. An antenna tuner is required which has a built-in balun or you must use a 4-to-1 balfor operation an any com- un at the bottom end of the line if you don't have one built in the tuner itself.

> The feedline is made of two runs of RG-8/U cable for powers up to 2 kW PEP, or for low-power operation under 100 Watts output, RG-58/U cable may be used. The lower loss of the larger cable is to be desired, however, even if low power is used.

At the top end of the

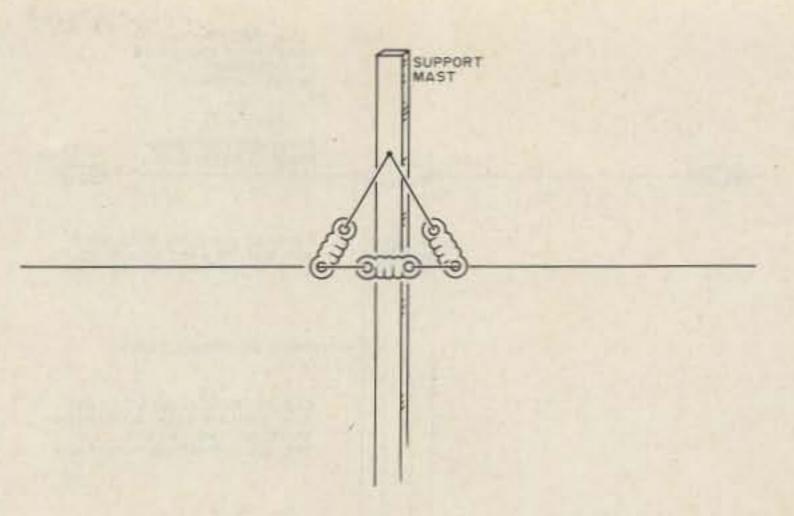


Fig. 2. Method of supporting antenna at center.

feedline, you connect the shields of the two coax cables together but do not connect them to anything else. Then at the bottom end of the line, the shields are tied together and connected to the ground connection in the shack and to the frame of the tuner.

The inner conductors of the coax cables are tied to each leg of the antenna wire at the top of the line, and at the bottom end of the line they are connected to each of the balancedoutput terminals of the antenna tuner.


The feedline can be run anywhere-underground, through metal or vinyl conduit, or in the open. The advantage of this arrangement, however, is that unlike the old open-wire feedline previously used on Zepp antennas, it does not have to be kept clear of surrounding objects and is not

affected by anything it lies against.

There is only one precaution that must be observed, and that is to cut both runs of the cable exactly the same length. They do not have to be run together, however, as the shield on the cables provides exact electrical separation of the inner conductors even if the two cables are widely separated.

As to the length of the feedline, I found that best results were observed with line lengths of a little more than one-quarter wavelength at the lowest frequency of operation (or anything longer than that). Try to avoid making the feedline resonant at any particular frequency you are operating on, particularly the quarter-wave points, or you may have a bit of trouble tuning on this band. Optimum length seemed to be about 55 feet for 80through-10-meter operation.

As for the mechanical construction, it is a good idea to use a long insulator, the same type used on the ends of the antenna, at the center of the antenna. Then slip the end of another insulator of the same type over the wire on either side of the center insulator, coming off at right angles to the wire and tying the support wire to these two side insulators so that equal pull is achieved on either side of the center insulator. Then

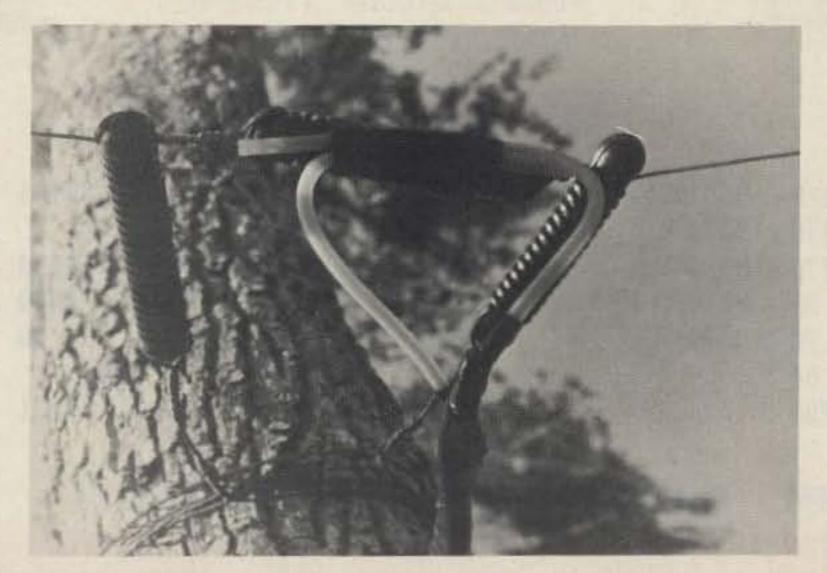

Center support and coaxial connections.

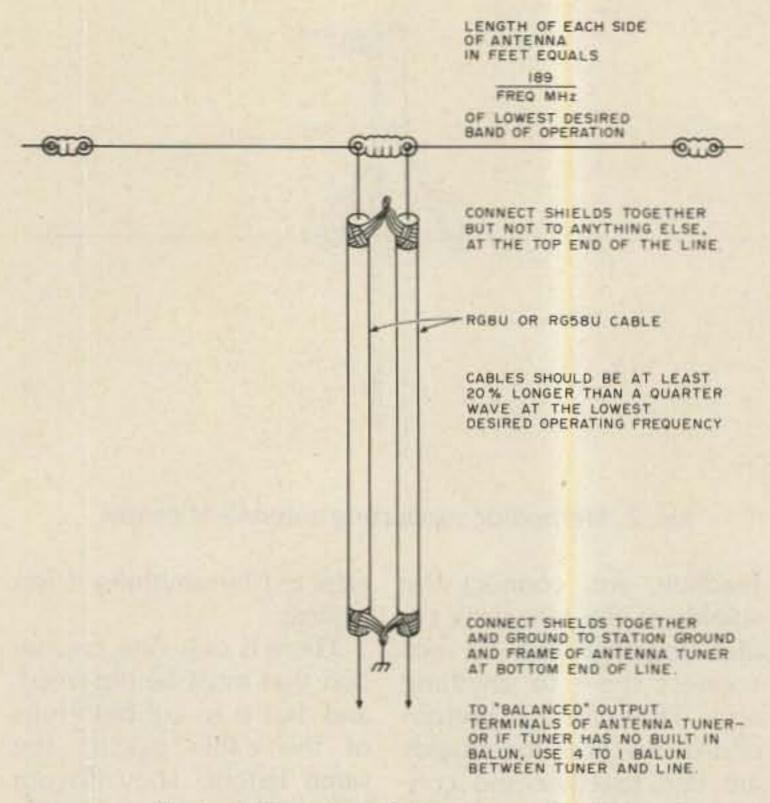


Fig. 3. Allband trapless antenna for HF.

at the point where you need to support the two coax cables, just strip off about 2 feet of the braid, leaving the plastic inner insulation,

and bend this part along the center insulator on each side and tape securely to the insulator. This will make a very solid support for the coax cables and will prevent wind damage.

It is also a good idea to bring the coax up the support mast a little higher than the antenna wire and bend it over in a loop and down about a foot or so to prevent the water from leaking into and running down the inside of the shield on the cables.

To separate the braid from the inner conductor on the coax, strip the outside plastic covering off about two feet from the end, then take the end of the shield and push it down, compressing it so that it becomes larger in diameter. Then take an awl or the tip of a small screwdriver and carefully spread the strands of the braid apart, opening up a hole in one side of the braid. At this point, bend the coax in a U shape and pull the plastic insulated center conductor out through the hole in the side of the braid, U-end first. This will eliminate the need for making a solder connection directly next to the plastic where it might create a weak spot.

I have used this antenna in various situations cut for all different combinations of bands and have had excellent results with all of them. I have also made up a portable version of this antenna using stranded insulated wire such as zip-cord and RG-58/U cables which I use in conjunction with a small antenna tuner for operation on 20 through 10 meters. This one is only 13.5 feet long either side of center with two runs of coax 20 feet long. It is ideal for stringing up in a motel room or apartment by supporting it with nylon fishing line. Just keep the antenna out a foot or so from the wall and support it by anything you can find to tie it to. Try it. You'll like it!

1-800-821-7323

SKENWOOD TS-430S



- All Bands
- Dual VFO's
- General Coverage
- 8 Memories
- 200 Watts

ICOM NEW IC-745



- · General Coverage Receiver 1.8 to 30 MHz
- · Fantastic Buy

YAESU -NEW FT-77




- Extremely Compact
 3.5 to 30 MHZ
- 200 Watts
- Inexpensive

ANTENNA SALE

CUSHCR	RAFT	HY-GAIN TO	WERS	BUTTERNU	IT	HY-GAIN	
A-3	\$215	HG37SS	\$ 649	HF6V	\$109	TH5MK2S	\$318
A-4	\$285	HG52SS	\$ 919	KLM-		TH7DXS	\$378
R-3	\$275	HG54HD	\$1429	KT34A	\$299	TH3MK3S	\$218
AV-5	\$ 98	HG70HD	\$2339	KT34XA	\$449	TH3JRS	\$158
214-FB	\$ 79	HG50MTS	\$ 749	144-148LBA	\$ 69	TH2MKS	\$138
32-19	\$ 94					18AVT/WS	\$ 94
40-2CD	\$285	LARSEN	CALL	AEA	CALL	18HTS	\$335
ANIXTER-	MARK					V2S	\$ 37
HW-3 TRIBAND		Call "TOLL F	REE" For All	Antennas & Acces	sories	EXPLORER 14 30/40 METER KIT	\$275 \$ 79

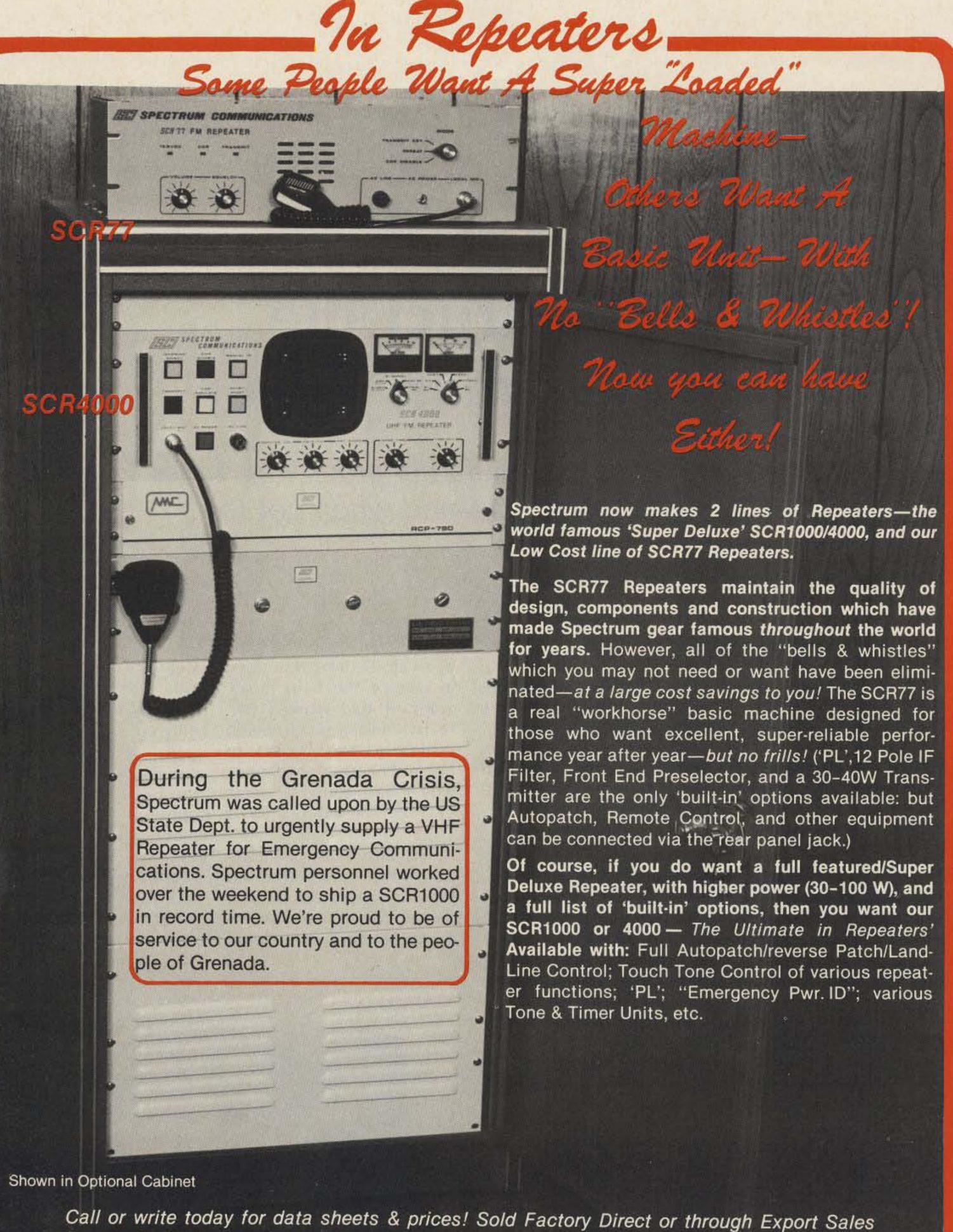2900 N.W. VIVION RD. / KANSAS CITY, MISSOURI 64150 / 816-741-8118 258



Call or write today for data sheets & prices! Sold Factory Direct or through Export Sales Reps only. Get your order in A.S.A.P.!



SPECTRUM COMMUNICATIONS

Construct the Minuteman Timer

As faithful as a grandfather clock, this timer tells when to ID—and when not to.

Gary L. Fait KA8QBQ 302 E. Lexington St. Davison MI 48423

But why do you need another ID timer?"

my wife asked when she saw me trying to sneak yet another Radio Shack bag to the workbench.

The question was no surprise because my very first electronics project had been an ID timer described in one of the ham magazines. It had worked perfectly, and I remembered well how I had shown it to her and carefully explained why I had added a single LED to the circuit for a visual signal.

The answer to her question, however, was that this timer is even better but it is still simple. Using a seven-segment LED, the timer

steps off the minutes beginning with zero.

Many ID timers provide only an audio and/or visual signal when eight or nine minutes have passed. Using this type of timer, the radio operator never knows how much time has elapsed until the signal sounds. I found myself identifying too often because I was never sure when the 10-minute mark would come.

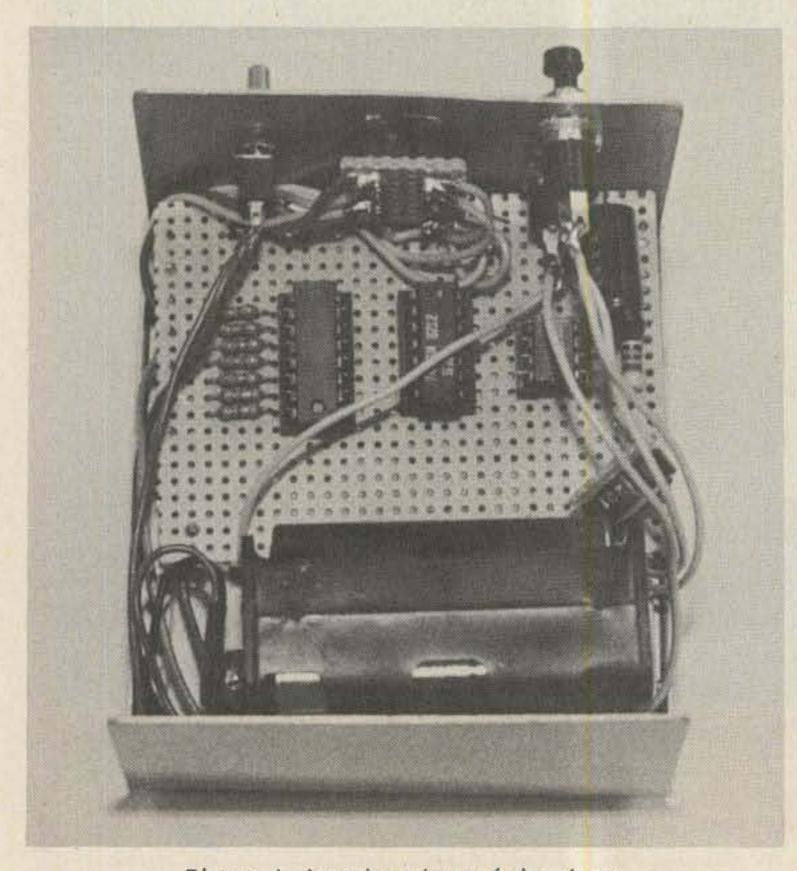


Photo A. Interior view of the timer.



Photo B. Front panel and cabinet for the ID timer.

To solve the problem, I began with a basic timing circuit using three ICs plus the seven-segment LED. I added two push-button switches, one to restart the timer after identifying and one to reset the numeral on the LED.

The 555 timer is controlled by R1, a 1-meg pot. The circuit can be set to time anything from seconds to hours. In this case, obviously, it is adjusted to provide one timing pulse per minute.

Opening S2, a normallyclosed momentary-contact switch, causes the resetting pins on the 7490 to go high. This resets the LED to the numeral nine. S3, a normally-open momentary-contact switch, is then closed. This shorts R1, causing the 555 to pulse, beginning a new timing period and by the way causing the LED to pulse to zero.

After turning on the timer,

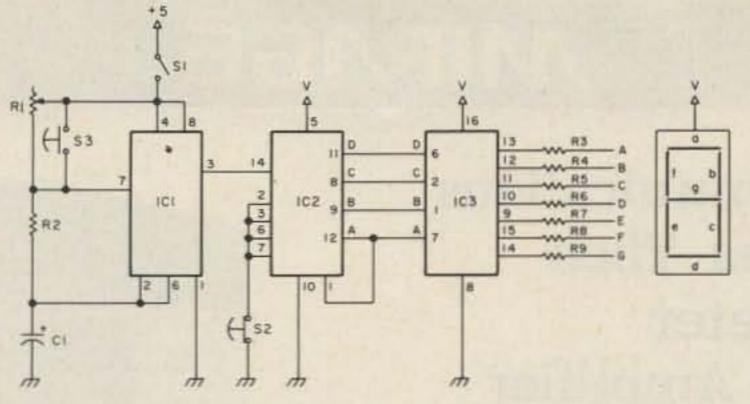


Fig. 1. The LED ID timer schematic.

operation is as simple as one-two. Simply push S2, then S3, to begin at zero. If you identify before the 10 minutes have completely elasped, simply give it the one-two again and the timer is back to zero and counting a full minute.

All parts for the LED ID timer are readily available from Radio Shack. Many parts are probably in any well-stocked junk box, but even if purchased new, the timer will cost less than \$10. It can be housed in any suit-

able enclosure. I used a small, steel-topped cabinet because I wanted to impress my wife, but the extra expense of the cabinet is not necessary.

The circuit is extremely simple and is an ideal project for the beginner, but one note of caution is in order. I suggest the use of IC sockets for mounting the three ICs and the LED, instead of soldering them directly to the circuit board. The entire project can be assembled before the ICs are installed,

	Parts List
C1	100 uF
IC1	555 timer
IC2	7490
IC3	7447
R1	1 megohm pot
R2	1k
R3-R9	330 Ohm
S1	SPST toggle
S2	normally-closed
	momentary
S3	normally-open
	momentary
LED	7-segment
	common anode

reducing the risk of damaging them in the process. The sockets also allow easy replacement for troubleshooting.

My LED ID timer now sits beside my rig, faithfully ticking off the minutes and saving a lot of unnecessary callsign transmissions. Now, if I could just get my wife to stop borrowing the thing to time her daily exercises...



MIRAGE

Mirage Communications Introduces Their 6 Meter Solid-State Amplifier A1015



10 Watts In — 150 Watts Out **\$279.95**

- Built-In Rx Preamp
- All Mode-SSB, CW, FM
- Remote Keying
- DC Power 13.6 VDC at 18 Amps
- FCC Type Accepted
- 5 Year Limited Warranty
- Optional RC-1 Remote Control Available
- Made in the U.S.A.

Available at Mirage Dealers Worldwide

MIRAGE COMMUNICATIONS EQUIPMENT.INC.

P.O. Box 1393, Gilroy, CA 95020 • (408) 847-1857

- ★ TECHNICAL FORUMS
- * ARRL AND FCC FORUMS
- ★ GIANT 3-DAY FLEA MARKET
 Starting Noon Friday
 All Day Saturday and Sunday
- **★** NEW PRODUCTS AND EXHIBITS
- **★** GRAND BANQUET
- **★** ALTERNATIVE ACTIVITIES
- ★ ELECTRICAL SAFETY FORUM
- ★ SPECIAL GROUP MEETINGS
- ★ YL FORUM
- ★ PERSONAL COMPUTER FORUM
- ★ CW PROFICIENCY AWARDS
- * AMATEUR OF YEAR AWARD
- ★ SPECIAL ACHIEVEMENT AWARDS

REMINISH OF THE RESIDENCE OF THE RESIDEN

April 27, 28, 29, 1984

Hara Arena and Exhibition Center — Dayton, Ohio

Meet your amateur radio friends from all over the world at the internationally famous Dayton HAMVENTION.

Seating will be limited for Grand Banquet and Entertainment on Saturday evening so please make reservations early. Harry Dannals, W2HD, Past President ARRL, will be featured speaker.

If you have registered within the last 3 years you will receive a brochure in January. If not, write Box 44, Dayton, OH 45401.

Nominations are requested for Radio Amateur of the Year and Special Achievement Awards. Nomination forms are available from Awards Chairman, Box 44, Dayton, OH 45401.

For special motel rates and reservations write to Hamvention Housing, Box 1288, Dayton, OH 45402. NO RESERVATIONS WILL BE ACCEPTED BY TELEPHONE.

All other inquiries write Box 44, Dayton, OH 45401 or phone (513) 433-7720.

ALL Flea Market spaces will be sold in advance ONLY. NO spaces sold at gate. Entrance for set-up available starting Wednesday. Special Flea Market telephone (513) 223-0923.

Bring your family and enjoy a great weekend in Dayton.

Sponsored by the Dayton Amateur Radio Association, Inc.

ADMISSION

\$7.50 in advance, \$10 at door. (Valid for all 3 days)

BANQUET

\$14 in advance, \$16 at door.

FLEA MARKET SPACE

\$15 in advance. (Valid for all 3 days)

Checks for advance registration to

Dayton HAMVENTION Box 2205, Dayton, OH 45401



And you can see it—in color—again and again when you own the N2NY Ham MasterTapes.

Ever see a cap discharge in slow motion? You will on Ham MasterTapes. Ham MasterTapes can perform the dozens of complicated demonstrations necessary for a beginner's understanding of Ham Radio Theory.

Finally, a step-by-step course in Ham Radio Theory is available on color videotape. The Larry Horne N2NY Ham MasterTapes video course is a unique, effective teaching technique expertly produced by New York's leading professionals in studio and field videotape.

☐ Video Graphics highlight important details.

□ Carefully worked-out demonstrations on video avoid the problem of getting complex gadgets to work on command in front of a class.

☐ Working examples of every ham radio component, device, or system covered in the FCC guide can be clearly understood. The N2NY Ham MasterTapes give you a basic grasp of concepts that build theory background—not only for passing the FCC tests, but for understanding electronics.

The hobby has long needed better, clearer, hightech teaching aids to help newcomers into our wonderful world of Ham Radio.

These six-hour tapes cover completely all the material needed to understand Novice and Tech/General Theory and operations, and include the new 200-question FCC syllabus used beginning September 1983.

Only \$199.95. Order direct and specify Beta or VHS format. Call or write: Larry Horne, N2NY or

Ham MasterTapes

THE N2NY HAM RADIO COURSE ON VIDEOTAPE

Virginia Hamilton, N2EGJ at
Ham MasterTapes
136 East 31st Street
New York, N.Y. 10016 212-673-0680.

© 1983 N2NY Productions, Inc.

The Secret of Remote Control

Inside those miniature planes lie some sophisticated circuits.

The Field House falls quiet as the pilot winds up the rubber-band motor of his scale model of the Porterfield Collegiate. The plane, which is made of lightweight balsa and covered with tissue paper, is held against the pull of the motor by a helper. Then, with the controls checked, the pilot gently tosses the plane toward the far end of the basketball court and steers the plane as it climbs. The pilot guides the Porterfield around the ceiling lights and basketball backboards until the motor winds down and the plane lands on the floor.

The pilot, a member of the State College, Pennsylvania,

Radio Control Club, is an amateur who reworked his Heathkit® radio to reduce its size and weight to fit inside the small Porterfield. By removing the receiver case and using hearing-aid batteries and special small servos, he was able to make a flying machine small enough to fly well inside the confines of an indoor basketball court.

At the other end of the spectrum is the PennFli, an original design of a radio control (R/C) pilot from Indiana, Pennsylvania. The aircraft has a fourteen-foot wingspan and weighs over five pounds. In the warm air of summer, this plane can climb to heights of more

than a quarter mile and fly over an hour without landing. It uses warm air up-drafts to stay aloft without a motor and its flight time is limited by the size of the batteries on board.

The Porterfield and the PennFli, for all their differences in size and weight, share a common guidance-system principle. It's called serial digital data transmission and it links the pilot's hands to the steering controls of the aircraft he's flying.

In Fig. 1, the scope trace shows that a timing or clock pulse initializes the sequence by turning on the decoder chain in the aircraft


receiver. The next pulse in the series is a data pulse of between one and two milliseconds duration, the width of which is controlled by a joystick on the transmitter. The length of the pulse determines what position the servo arm will take. A pushrod connected between the arm and a control surface, in this case the rudder, links the servo to its workload. The receiver detects the transmitter's signal, decodes the serial data, and routes the proper pulse to each servo. In the servo, the pulse is compared to another from the onboard circuits, a function of where the servo arm is positioned. The error dif-



The PennFli, an unlimited class sailplane of fourteen-foot wingspan, weighs about five pounds. Made of balsa and plywood, the plane is covered with a plastic film which shrinks and sticks to the wood when heated with a common clothes iron. Controls are rudder, elevator, spoiler (airbrakes), and releasable tow hook.



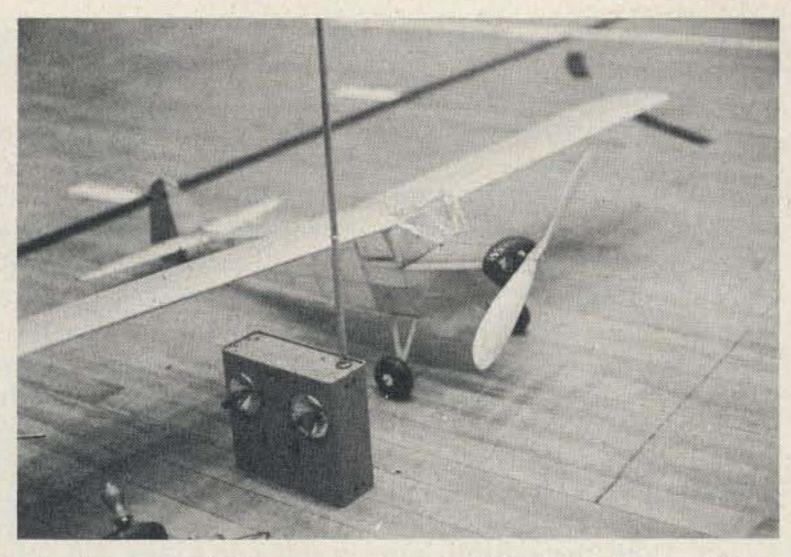
A one-fourth full-sized model of a WWII fighter is started up. Constructed of balsa, plywood, and thin aluminum and covered with fabric, the plane uses a chain-saw engine and two-cycle mix fuel for power. A four-channel R/C rig controls ailerons, rudder, elevator, and engine speed.



The tiny Porterfield at rest. The model is made from a \$5.00 free-flight kit of thin balsa strips covered with lightweight tissue paper and lightly sprayed with model paint.

ference of the two pulses is translated into action through a small dc motor similar to those used as automatic film-winders in cameras. Through a gear train, the motor moves the output arm and also a variable resistor which sets the length of the onboard pulse. When the error ratio of the two pulses is zero, the servo output arm and control surface to which it is connected are in the position called for by the pilot and transmitter. The pulse rate is fast enough so that the net effect is smooth movement of the controls and realistic maneuvering of the plane.

Were all this taking place on the ground where conditions were constant, R/C control would be a fairly simple system. By installing half the control system in an aircraft which at launch is mere inches from the transmitter, then flying the plane so high and far that it looks like a dot in the sky, using simply a length of hookup wire for an antenna, a very special receiver is needed to maintain constant control. As the radio is amplitudemodulated, static or other electrical noise could blank or change the length of one or more data pulses causing steering problems and possibly a crash. A 500-milliwatt rf signal from the transmit-

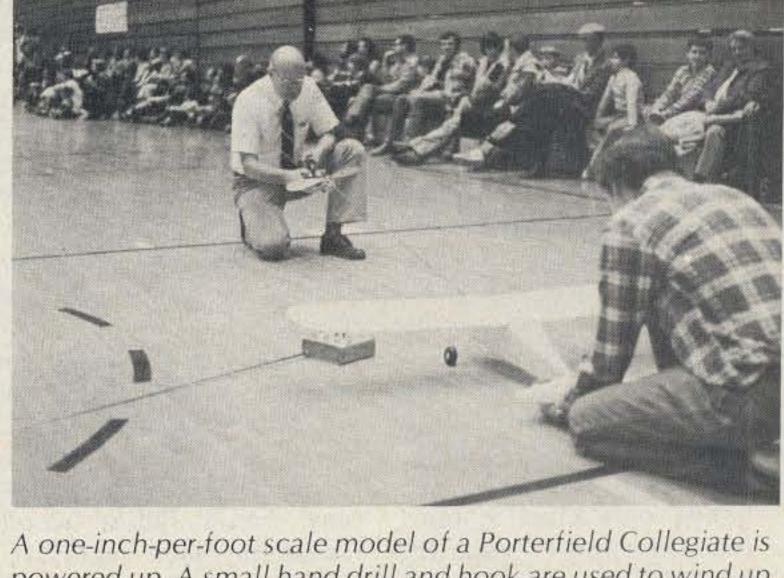

powered up. A small hand drill and hook are used to wind up the large rubber band to full power.

ter is hot enough to provide solid contact out to over a mile depending on the altitude of the aircraft. The receiver is usually triple-tuned at its antenna circuit for adjacent channel rejection while a double-stage agc circuit holds the signal from the single-conversion i-f strip constant no matter how much rf is picked up by the antenna.

All this is performed by a receiver board about the size of a pack of book matches. The decoder board is the same small size and is wired to take power and audio signal output from the receiver. The long clock pulse sets the time sequence for the decoder and helps it to disregard stray noise which does not occur in the proper or expected time frame. The clock also tells the decoder which of the following data pulses are to be routed to the individual servos. The clock does not leave the decoder board while all the following data pulses are fed to their respective servos.

Most systems today are powered by nickel-cadmium rechargeable batteries in both the transmitter and the airborne unit. Airborne battery voltage is normally 4.8 volts from four 500-mAh AA-size batteries wired in series. The transmitter uses

9.6 volts from eight batteries of the same size and rating as the airborne pack. For aircraft which are 1/4-size scale models of full-size planes and have six or eight controls under R/C command, D-cell-size nicad batteries are needed to handle the high net current draw. The added weight of the big pack is also helpful in balancing the model for stable flight.

While most R/C systems are factory built, Heathkit and Ace R/C, Inc., both offer full lines of radios in kit form. As mentioned earlier, the small size and high parts density of the receiver and servos make the building

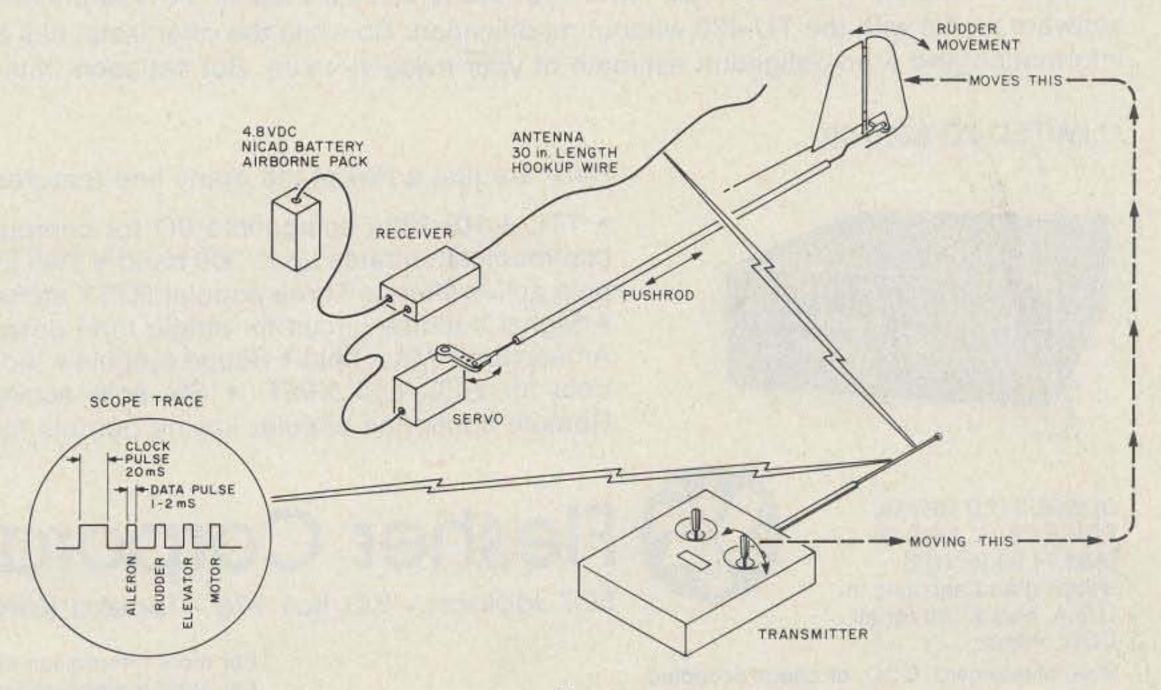


Fig. 1.

task somewhat more critical than wiring an HW-101. While it does call for some high-grade construction skills, most any amateur with some bench time will have no trouble assembling kits from either of these vendors. Both offer operating frequencies in the six-meter band where few interfering signals exist and where there is no crowding, as up in the 72-MHz CB band. While there is no mode restriction for R/C in the amateur bands, only Kraft Systems, Inc., offers an FM-type R/C rig; it is only available factory built. In high rf noise applications such as R/C model helicopters, an FM radio with its higher immunity to static would be a good choice. In most other types of models, the AM type of modulation is very reliable.

Equally as important as the system's electrical specifications is its ability to take physical punishment and be reliable. Whether the aircraft has a large or small engine, each will vibrate the R/C to some degree. If components on the receiver or servo circuit boards aren't mounted close to the board and well soldered, vibration will get them sooner or later. Even gliders, which have no engine, are battered in the landing zone as they have only thin rubber skids on the bottom of the fuselage. The quality of workmanship is very important in R/C rig construction, since almost any circuit failure would cause the plane to crash.

Once an R/C system is built, it can be modified to "fly" many different types of models. Miniature replicas of ocean-going sailboats can be raced in a pond or swimming pool using specially waterproofed gear. Even submarines which have the ability to submerge are available as R/C model kits. The hottest Formula and Indy-type race cars are built from kits and raced us-

ing two-channel radios and either electric motors or glow-type model engines. New military tank models have come out which will climb obstacles, go forward, reverse, go left and right, and swing the turret cannon. Helicopters fly in scale fashion in competition by carrying cargo or flying in formation or firing small solid-fuel rockets at targets.

By far the most popular are the scale models of World War II military aircraft. With the reliable radios available today, anyone can pilot the model of his favorite plane and enjoy the thrill of flying the old war birds.

Adapting the radio system to function in any of these models will allow the amateur to use the same rig in several models. In some cases, extra receivers and servos are built for installation in models and operated from a common transmitter so that two or more planes

can be flown without having to field-change radios from one model to another.

Since there are few of us who can afford to own a Mustang fighter or a B-29 Superfort, a model of these planes is more practical. From biplanes to the space shuttle, R/C radios allow us to build and fly the most exotic flying machines safely and reliably. Imagination is the only limiting factor in choosing which model to operate, and amateur skills at the workbench make the radios as inexpensive as they are reliable.

Kit Manufacturers

Heath Company Benton Harbor MI 49022

Ace R/C, Inc. Box 511, 116 W. 19th St. Higginsville MO 64037

Kraft Sytems, Inc. Box 1268 Vista CA 92083

TRADE IN YOUR OLD RTTY TU FOR A NEW FLESHER TU-470

The Flesher Corporation dares to make an offer you can't refuse. Now you can move up to a high quality FTTY terminal unit without throwing away money you have already invested. Your present name brand RTTY terminal unit is worth up to full retail value* when you trade up to a Flesher TU-470 priced at \$499.95. Most RTTY/CW software works with the TU-470 without modification. So while the offer lasts, call our toll free number for more information and a no-obligation estimate of your trade-in value. But act soon; this offer won't last long.

*LIMITED TO \$200.00



Here are just a few of the many fine features the TU-470 offers:

TTL & RS-232c compatible I/O for computer remote control • RTTY communication rates up to 300 baud • Two tone RTTY detection with six pole active filters • Three popular RTTY shifts • Built-in 20 or 60 mA loop
 • Signal balance circuit for single tone detection • Threshold control • Anti-space • Mark hold • Scope outputs • Independent reverse shift controls for REC and XMIT. • Six pole active filter CW demodulator • Remote controlled bi-polar keying outputs for CW and PTT.

SUGGESTED RETAIL
PRICE ONLY \$499.95
(Add \$4.50 for UPS
shipping and handling in
U.S.A. plus \$1.75 for all
COD orders.



Flesher Corporation

507 Jackson • P.O. Box 976 • Topeka, Kansas 66601

-23

For more information and sales CALL 1-800-HAM-RTTY For service and technical CALL 1-913-234-0198

73 Magazine • February, 1984

PRIVATE PATCH II

THE ULTIMATE SIMPLEX AUTOPATCH


PRIVATE PATCH II is for the discriminating amateur who demands the finest in simplex autopatch performance, features and quality. Our digitally processed VOX and simplex loop create a level of communications quality which is not even closely rivaled. Please ... do not confuse our technique with sampling!! PRIVATE PATCH II has the following major advantages over sampling type autopatches:


- Compatible with every known transceiver—yes, synthesized and relay switched types included.
- No transceiver modifications are ever required!
- Connects only to MIC and external speaker jack-no internal connections to your transceiver required.
- Natural push to talk operation—no need to pause—you may talk the instant the button is pressed.
- Much greater range-noise on your weak mobile signal causes no performance degradation. (Noise sampled autopatches fail to operate when your signal becomes noisy.)
- Private Patch II offers natural "take-turns" style of communications in the manner you are used to. There are no annoying sampling kerchunks and missing syllables punched out of every other word.
- In addition to superb simplex operation, Private Patch II will operate through any repeater from your base location. Yes, any repeater! Tone encoding equipment and repeater modifications are not required.

STANDARD FEATURES

- CW identification—ID ROM chip included.
- Single chip XTAL controlled tone decoder.
- Tone to pulse—compatibility with all telephone systems eliminates critical tone adjustments in the mobile-no wrong numbers, ever! Can be strapped for straight tone dialing.
- Speed dialer compatible—can consume up to 15 digits per second.
- Sophisticated toll restrict logic—user programmable restrict digits.
- Five digit access code—59,049 user programmable code combinations! (Their three digit code beginning with * has less than 196 combinations.)
- Ringback (reverse patch)—alerts you with CW ID.
- Busy channel ringback inhibit-will not send CW ID alert if channel is in use - defeatable.
- · Three/six minute "time-out" timer-resettable from the mobile-four CW ID warnings during final minute.
- Control interrupt timer—assures reliable and positive control.
- Self contained 115VAC supply -230V 50/60 Hz available at slight additional cost.
- Modular phone jack-and seven foot cord.
- 14 day return privilege—when ordered factory direct.
- One year factory warranty.

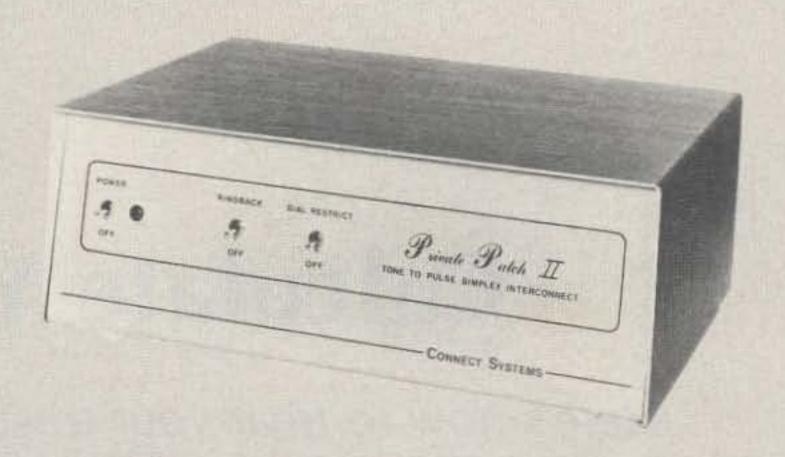OPTION: FCC registered coupler. Inquire about commercial and half duplex models.



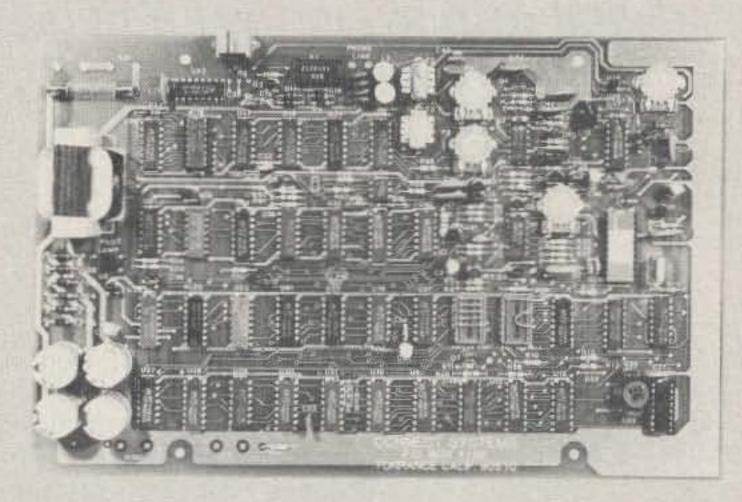

OUR QUALITY GLASS BOARD, SUPERB ENGINEERING AND EXCELLENT COMPONENTS BLEND TOGETHER TO PRODUCE THE FINEST AMATEUR AUTOPATCH AVAILABLE.

CONTACT A LOCAL DEALER TODAY

AMATEUR ELECTRONIC SUPPLY

Milwaukee WI, Wickliffe OH, Orlando FL,

Clearwater FL, Las Vegas NV, Chicago IL

HAM RADIO OUTLET

Anaheim CA, Burlingame CA, Oakland CA, San Diego CA, Van Nuys CA

HENRY RADIO

Los Angeles CA, Anaheim CA, Butler MO

JUNS ELECTRONICS Culver City CA, Reno NV N&G DISTRIBUTING CORP. Miami FL

PACE ENGINEERING Tucson AZ

PIZA ELECTRONICS Ponce, PR

THE HAM SHACK Evansville IN

CANADA:

DOLLARD ELECTRONICS Vancouver, BC

PHILIPPINES: CORONA INTERNATIONAL Cubao, Quezon City



P.O. BOX 4155 TORRANCE CA 90510 23731 MADISON ST. TORRANCE, CA 90505 PHONE (213) 373-6803

Calculate Your FT-101

Here's how to treat your trusty FT-101 to a truly automatic digital display and get a frequency counter in the same box at the flick of a switch.

D. N. Ellis VK8DE 57 Memorial Avenue Alice Springs, N.T. 5750 Australia

he FT-101 series of HF transceivers has been one of the most popular in amateur radio history. One models through the "E"

series, however, was the lack of a true calculating digital display. While Yaesu did offer the YO-601 digital lingering criticism of the display, it counted only the vfo and required operator adjustment for correct frequency display with any band or mode changes.

The "VK8DE Calculating FT-101 Display" is a "handsoff" calculating counter giving true zero-beat frequency readout on all modes and bands. It is inexpensive and straightforward to build and requires only a simple passive interface to the FT-101. It can also serve as a 50-MHz bench frequency counter, and also sports a switchable calibration output signal. The implementation used is LSTTL (Lowpower Schottky), available worldwide at low cost. An accurate, automatic digital display is a necessity on the crowded bands, and this project is a convenient and economical upgrade for FT-101 owners.

The counter performs the following frequency calculation formula according to the FT-101 oscillator mixing scheme: F = bfo + LO vfo, where F = the displayed frequency, bfo = modeswitched Beat Frequency Oscillator (LSB, USB, and



Photo A. Front view. Note that many ventilation holes were drilled oversize for more effective convection cooling of the internally-mounted LM323K voltage regulator and heat sink (photo by R. Campbell).

CW/AM), LO band-= switched Local Oscillator (1 crystal per band), and vfo = dial-tuned Variable Frequency Oscillator.

General Description

Reference to the block diagram of Fig. 1 will be helpful for a general description. The three oscillator signals are routed from the FT-101 external vfo octal socket (J13) on three previously unused pins through coax to the display box.

Isolation amplifiers buffer the signals and then perform a TTL level conversion for the digital processing. A crystal-referenced oscillator feeding a decade divider chain provides necessary timing for the control section. The control section directs up-down counters to follow the frequency determination formula and finally to store and display the information in 7-LED numerical displays. The FAST/ SLOW switch offers the operator a choice between 80- or 800-ms-display updates with 100- and 10-Hz resolution, respectively.

The FT-101/external switch allows the unit to function as a normal frequency counter using the LO jack as the input source. The bfo-detect circuit is used to provide a preset substitute value in the absence of bfo signal, such as in AM receive mode. This feature also gives zerobeat CW frequency when the FT-101 mode switch is moved from CW to AM. The "normal" CW presentation is offset low by 800 Hz if tuned properly, which happens to be the difference between the FT-101's USB oscillator of 3.1785 MHz (used in CW receive) and the CW/AM oscillator of 3.1793 MHz (used in CW/AM transmit). A regulated +5-volt source supplies the necessary power for the counter, displays, and isolation amplifiers.

Circuit Details

References to the timing diagram (Fig. 2), and the four

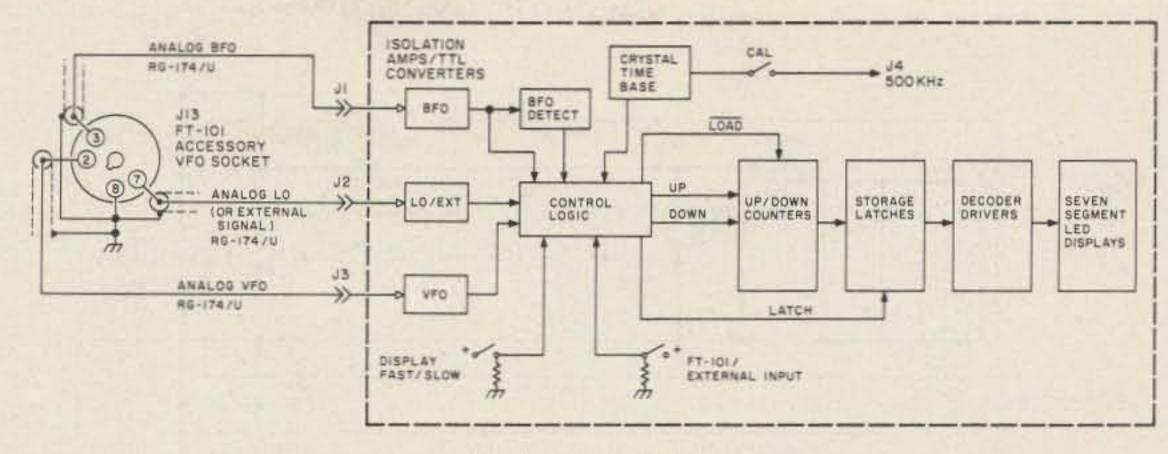


Fig. 1. Block diagram.

sections of the schematic (Figs. 3, 4, 5, and 6) will be made in this section. Fig. 3 shows the raw analog bfo, LO, and vfo cables routed to the BNC jacks J1, 2, and 3, respectively. With the exception of a single input resistor change in the bfo isolation amplifier, the three buffer-converters are identical. One description will, therefore, serve for the three circuits.

Because of the JFET input and the 1-megohm bias resistors, each of these amplifier's input impedance is essentially the value of the input resistor. For high sensitivity it is 1000 Ohms for the LO and vfo, and 10,000 Ohms for the bfo. These impedances do not appreciably load the oscillator signals with 1-meter connecting lengths of RG-174/U coax from the FT-101.

The JFET then feeds an NPN driver which emittercouples via a large value capacitor to a linearly-biased 74LS04. The IC wired in this

manner, as a dc-coupled multistaged amplifier, produces a TTL level (HIGH ≥ 2.7 V, LOW < .8 V) pulse output from the sinusoidal input. This cheap but utilitarian dc 50-MHz analog-to-TTL amplifier has been used so often by so many that it must nearly be "public domain."

Fig. 4 shows the bfo, LO, and vfo TTL signals as inputs to the timing and control section. In order to guarantee the successful use of low-cost LSTTL, the signals are each prescaled (divided) by a factor of 2. This forces the maximum LO input of 35.52 MHz (used in the 29.5-30-MHz band of the FT-101) to a value of 17.76 MHz after passing through U8, a 74S74 flip-flop.

The guaranteed specification of 30 MHz for a 74LS74 flip-flop, or for that matter, the 74LS192 up/down counters, is thereby never tested. The penalty for prescaling by two is a corresponding extension of the counting time by the same factor.

The control-section activity is directed by a fourstate counter made up of U18, a 74LS74. Besides creating a specific counting interval for the bfo, LO, and vfo, the state counter provides a fourth interval to display the resultant frequency calculation and then prethe machine pare for another cycle. The timing diagram of Fig. 2 shows the succession of these states and the ensuing events. The state names of 00, 10, 11, and 01 are derived from the successive logical conditions of U18 pins 5 and 9, called QA and QB. The 1-MHz crystal oscillator of U6 is divided down to provide a continuous stream of state clock pulses as shown in Fig. 2.

Three state clock pulses cause the machine to count up the bfo, count up the LO, and count down the vfo, or add, add, and subtract, in accordance with the F=bfo +LO-vfo equation. The fourth state, called 01, causes a LATCH command to store the frequency value

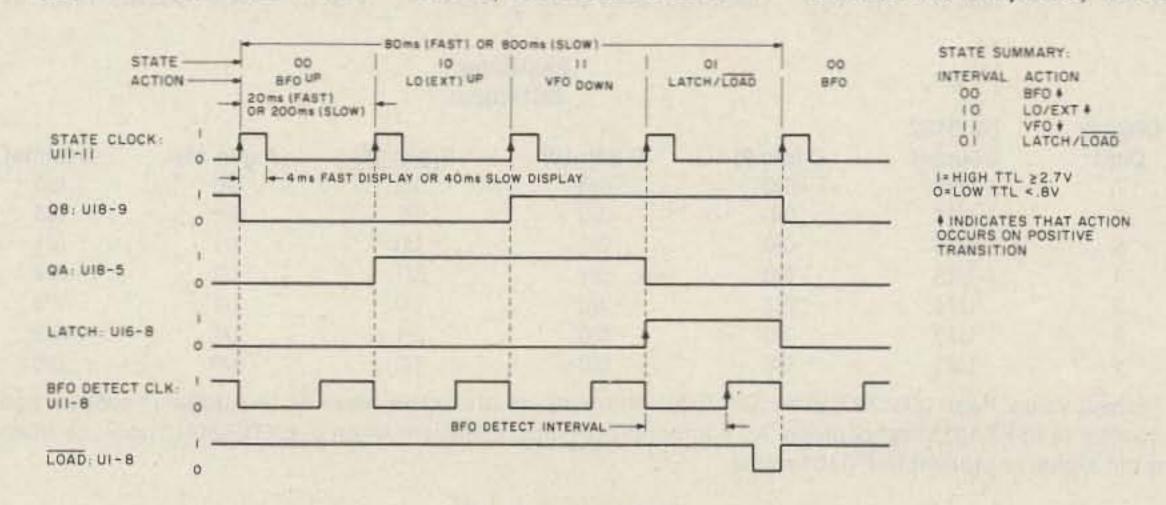


Fig. 2. Timing diagram.

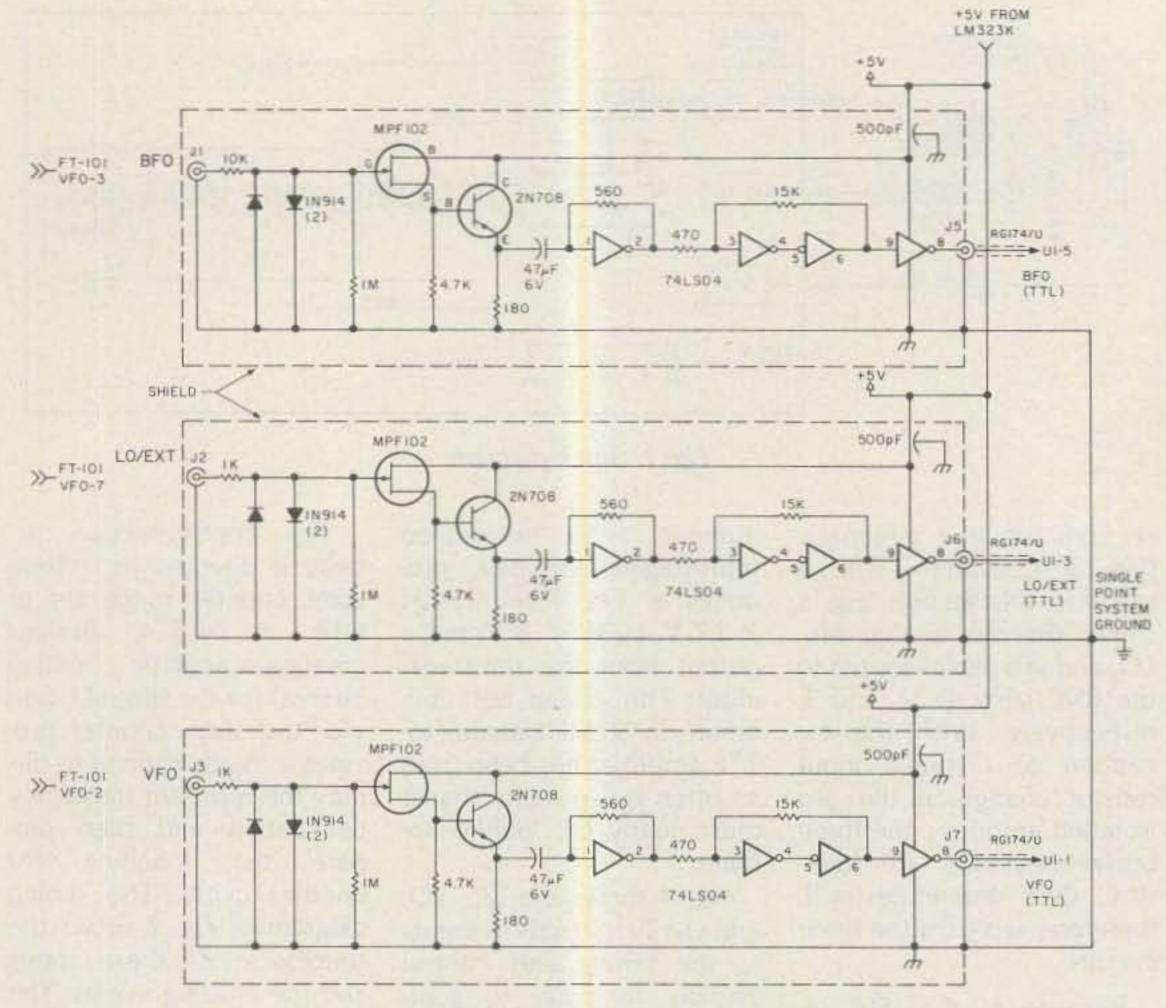


Fig. 3. Isolation amplifiers/TTL converters.

for display viewing and a when QA is a logical 0 (less LOAD pulse to prepare the 74LS192 up/down counters for the next display cycle. A bfo-detect interval is also defined that will determine whether the counter chips are to be loaded with zero or whether, in the absence of a bfo signal, the preset value of 031793 (the CW/AM oscillator frequency) is substituted for the bfo.

The two UP clock signals (bfo and LO) are multiplexed by U15, a 74LS158. The QA (U18-5) line selects the bfo than .8 volts), and the LO signal when it's a logical 1 (at least 2.7 volts). During the vfo (11) and Latch/Load (01) states, U15 is disabled, producing a solid logical 1 output. The vfo flip-flop, U9, is similarly disabled during the bfo, LO, and Latch/Load states. This action was necessary to properly condition the 74LS192 counters for up/down counting. Thus, for UP counting of the bfo and LO, the DOWN line is disabled, and during DOWN

counting, the UP line is disabled.

The occurrence of the 01 state produces the LATCH command at U16-8, which stores the counter bits into 74LS175 quad flip-flops. U17 is the bfo detector, and if bfo activity was present during the bfo-detect interval, U17-8 will go to a logical 1, disabling U3. The disabled outputs of U3 will be all zeros and will be jammed into the 74LS192 counters (U22 through U28) when the LOAD pulse occurs later in

the 01 interval. U17 is enabled only during the Latch interval (01 state) and, because of U10, only when the machine is in the FT-101 display mode. The extra U16 gates are used as a delay to ensure U3 output stability during activity of the LOAD signal.

The presence of two display times, together with the bfo-detection concept, was responsible for the inclusion of U3 and its strangelyoutputs. Table 1 named shows how U3 (when wired as shown in the schematic) will (when no bfo signal has been detected) inject into the seven 74LS192 counters the value 0031793 when in the FAST mode (80-ms display update), and 0317930 when in the SLOW mode (800-ms update).

Fig. 4 shows the 74LS192s, the 74LS175 storage flipflops, the 74LS247 decoderdrivers, current-limiting resistors, and common-anode right-hand decimal-point displays. The direct-drive approach was chosen to minimize the chance of display-driver RFI, which often is an unwanted result of the more efficient method of display-digit multiplexing.

Two decimal points are lit for each display mode: one to distinguish megahertz from kilohertz and one to separate kilohertz from Hertz. The FAST position illuminates decimal points on digits 5 and 2 while the SLOW setting drives digits 6 and 3. The decimal point switching and driving derive from a gate of U1 and an open collector-inverter, U2. The seven digits plus the four decimal points require 53 180-Ohm, 1/4-W resistors. The displays are 8mm red 5082-7731 units, but any common-anode right-hand decimal-point displays will work.

Fig. 6 shows the power supply. An LM323K in a 15-Watt heat sink is ample for the maximum 2.1-Ampere current requirement. About 1.5 Amps is used by

Fast/Slow* RCD Input

			DCD	nput		
Display	74LS192 Counter	D (pin 9)	C (pin 10)	B (nin 1)	A (nin 15)	Decimal
Digit	Counter	D (bill a)	C (pill 10)	B (pin 1)	A (pin 15)	Decimal
7	U28	0/0	0/0	0/0	0/0	0/0
6	U27	0/0	0/0	0/1	0/1	0/3
5	U26	0/0	0/0	1/0	1/1	3/1
4	U25	0/0	0/1	0/1	1/1	1/7
3	U24	0/1	1/0	1/0	1/1	7/9
2	U23	1/0	0/0	0/1	1/1	9/3
1	U22	0/0	0/0	1/0	1/0	3/0

^{*}Preset value: Fast: 0031793; Slow: 0317930. Above inputs are active when no bfo signal is present and counter is in FT-101 display mode. All counter-preset inputs are zero when in EXTERNAL mode, or when a bfo signal is present in FT-101 mode.

Table 1. Preset counter bit values.

The small dish that captures all the entertainment.



Only Wilson Microwave Systems can give you the versatility of hand-held control of the total satellite television spectrum at such a remarkably low price.

Total System Design.
From the solid steel antenna to the

From the solid steel antenna to the state-of-the-art electronic receiver and hand-held control unit, Wilson gives you the most complete, integrated system you can own.

At Wilson Microwave Systems, we put the world of entertainment in the



BUILT BY YAESU

1 year warranty on receivers
4 year limited warranty on dish

NOW ONLY

\$1695.00 F.O.B. Nampa, ID

Includes: 110° LNA - Polarizer I - 100' Cable Wilson MD9 Dish - YM1000 Receiver

> Dealerships Available

Antenna is shown with optional LNA cover.

Distributed by

NAMPA SATELLITE SYSTEMS

312 12th Avenue South • Nampa, Idaho 83651 (208) 466-6727

In State Wats 1-800-654-1319 • Out of State Wats 1-800-654-0795

138

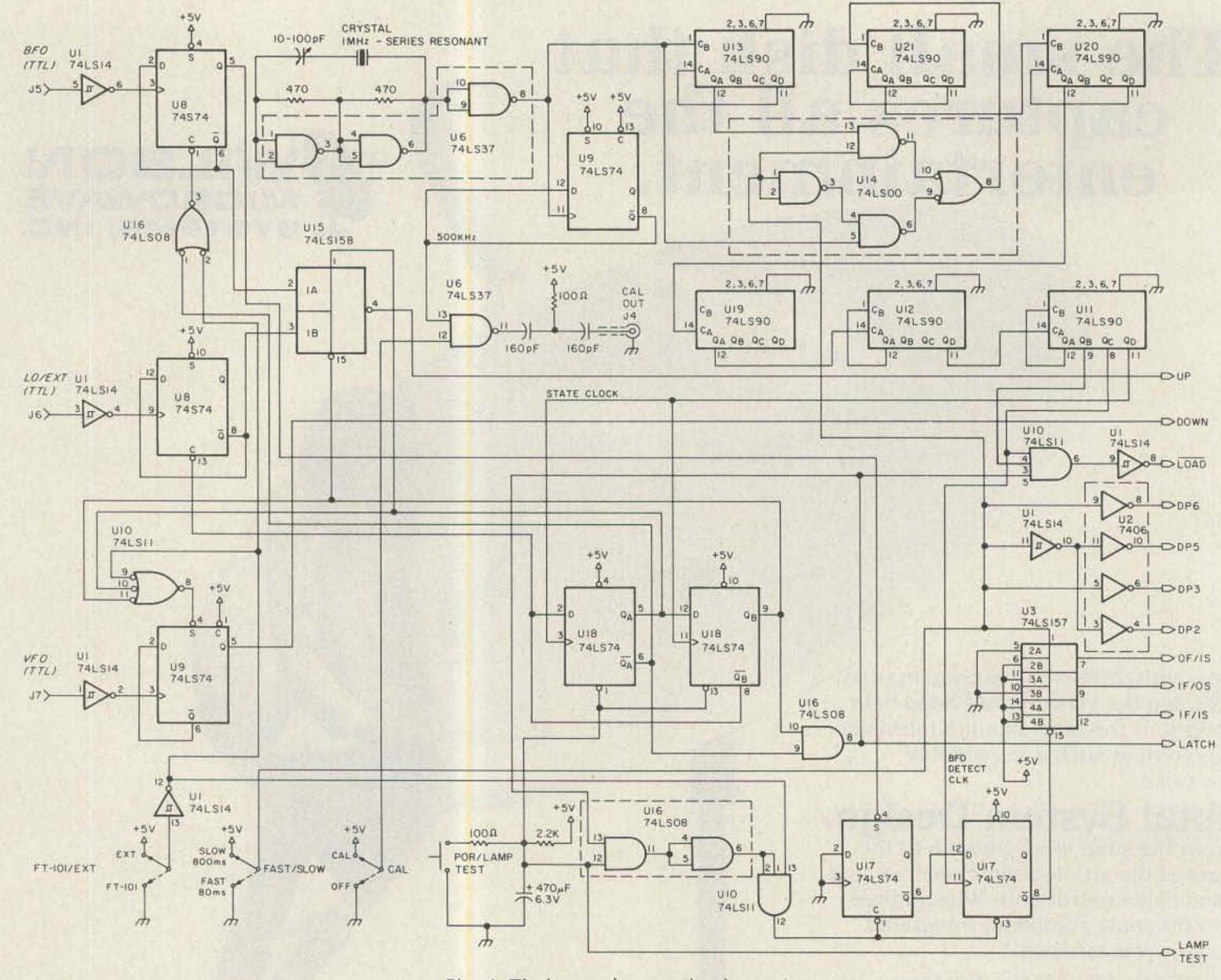


Fig. 4. Timing and control schematic.

the display during a lamp test, when all digits show eights. A 15-V center-tapped, 3-Amp transformer in a full-wave configuration was used. The ac primary is double-pole switched and fused for safety. A single-point ground system was employed to minimize the chances of ground loops.

The time base for the project is conventionally implemented from a 1-MHz TTL crystal oscillator (U6) and a cascaded string of 74LS90 decade dividers. U14 is wired as a 1-of-2 selector to change the frequency of final divider U11's outputs by a factor of 10 for the FAST/SLOW display presentation. An unused portion of U9 divides the 1-MHz oscillator signal by 2, then a

remaining U6 gate buffers it and feeds a CRC differentiation network. When the CAL switch is activated, a 500kHz harmonically rich signal is routed to the 14



Photo B. Rear view. Shown are the FT-101 inputs, the 500-kHz CAL output, and the operating controls. For frequency counter use, the toggle switch is set to EXT and the signal of interest connected to the LO/EXT input (photo by R. Campbell).

output jack. This easily allows band-edge checks and frequency station-standard checks against WWV, JJY, CHU, etc.

Construction and Checkout

The project was built in stages. The FT-101 interface was wired first. Many thanks to KH6BK (March, 1977, QST) for this simple but effective method of accessing the three FT-101 oscillator signals.

FT-101 interface instructions: The objective is to capacitively couple the bfo, LO, and vfo via small sections of RG-174/U coax routed through the underside of the chassis to the vfo accessory socket (J13) at pins 3, 7, and 2, respectively.


812-422-0231






808 N. Main Evansville, IN 47711

HAM SHACK

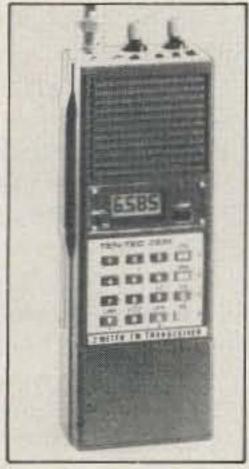



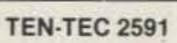

SANTEC 142



YAESU 726R	
AEA	
CP-1/C-64 or VIC-20 Software Package	\$235.00
MP-20 or MP-64 Interface Package	129.00
Software for C-64 or VIC-20	69.00
Amtor Text	69.00
ARRL	
US Call Directory	\$15.75
1984 Handbook	12.00
Antenna Book	8.00
ALLIANCE	
HD73 (10.7 sq ft) Rotator	\$99.00
ASTRON	
RS7A 5-7 Amp Power Supply	
RS10A 7.5-10 Amp Power Supply	
RS12A 9-12 Amp Power Supply	
RS20A 16-20 Amp Power Supply	
RS20M 16-20 Amp w/meter	
RS35A 25-35 Amp	
RS35M 25-35 Amp w/meter	
RS50A 37-50 Amp	225.00
RS50M 37-50 Amp w/meter	225.00
AZDEN	2000.00
PCS4000 2M mobile rig	\$280.00
BENCHER	
BY-1 Paddle/BY-2 Chrome	\$36.00/45.00
BUTTERNUT	
HF6V 80-10 Meter Vertical	\$119.00
CUSHCRAFT	
A3 Tribander 3EL	\$215.00
A4 Tribander 4EL	270.00



	THE OWNER OF THE PARTY OF
_88	00000
	TEN-TEC CORSAIR

55 = . = . ISB145	
=:():200d)	
3=-000 / E	
The second second second	13.8

ICOM 745

R3 Motor Tuned Vertical	279.00
R3 Motor Tuned Vertical	75.00 each
32-19 Super Boomer 19EL 2M	89.00
ARX-2B Ringo Ranger II 2M	
DAIWA	
CN-520 1.8-60 MHz SWR/Pwr Mtr	\$63.00
CN-620B 1.8-150 MHz SWR/Pwr Mtr	
CN630 140-450 MHz SWR/Pwr Mtr	
CN720B 1.8-150 MHz SWR/Pwr Mtr	
CHTZOD I.O TOO MITZ SWITE WI MIT	150.00
DRAKE	
TR7A Xcvr w/PS7	\$1,495.00
ENCOMM (SANTEC)	
ST-142, 222, 442	
The Handhelds Still Offering the Most	Features
Call for Your Discount Price	
HAL	
DS3100/MPT/ST6000	
CT2200/KB2200	
CWR6850 Telereader	749.00
HIN CAIN	
TH7 DXS 7EL Tribander	6275.00
TH5 MK2S 5EL Tribander	
Explorer 14 Tribander	
5/8 Wave 2M Mag Mt	
CD45 8.5 sq ft Rotator	
HDR 300 25 sq ft Rotator	
Ham IV 15 sq ft Rotator	7 7 8 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7
T2X 20 sq ft Rotator	249.00
Free Shipping on all crank-up towers	
ICOM	
IC-02AT Now Available	Call
751 Ultimate Transceiver	
745 Amazing New Transceiver	Call
730 Super Buy	
IC-2ATNo	225.00
3AT/4AT Handhelds	235.00
27A 2M Xcvr	
271H new 2M 100W Amp	
45A 440 MHz	
R70 Receiver	
KLM	
OSCAR antennas in stock	call for prices
	EL PER SERVICE
KANTRONICS	
The Interface II. The brand new computer	interface for
CW, RTTY, ASCII. Software Available for	
APPLE, ATARI, TR80C, TI99	1020, 0.04,
Amter Celtuere New Available	

MFJ	Call
1224 New Computer Interface	
422 Keyer/BENCHER Paddle combo	
313 VHF Conv for HT	
989 3KW Tuner	
940B Tuner/Meter/Ant. Switch	
900 Tuner	
401 Econokeyer	
722 Filter w/notch	
812 VHF Meter	
816 HF Meter	
1040 Deluxe Preselector	
103 New 24hr Clock	
MIRAGE	
B1016 10/160 Preamp	\$245.00
B3016 30/160 Preamp	
D24N 440 MHz Amp	
SHURE	
444D Desk Mic	\$ 55.00
	00.00
TEN-TEC	3 1000000
New 2M Handheld (Model 2591)	
Argosy II Digital	
2KW Tuner Kit	
The Fantastic Corsair	
TOKYO HY-POWER	
HL30V 2/30W Amp	\$63.00
HL160V 3 or 10/160W Preamp	
HC2000 2KW Tuner	
HL82V 10/80W Preamp	
HL20U 2/20W UHF Amp	
HL45U 10/45W UHF Amp/Preamp	
HL90U 10/80W UHF Amp/Preamp	305.00
YAESU	
FT-726R Tri-band Xcvr	699.00
FT-980 Computer Aided Xcvr System	Call
FT-102 160-10M w/WARC Bands Xcvr	889.00
FT-208R 2M Handheld	
FT-757GX Gen'l Coverage Xcvr	call
OSCAR HEADQUARTERS	
Transceivers - Call for Special Package Price	9
ICOM 271A/471A Deluxe Base Transceivers	2055
ICOM 290H/490A Affordable Mobile Transce	ivers

ICOM 402 432 MHz Transceiver YAESU 726R/432 MHz/Duplexer

Antennas & Amplifiers KLM 14C, 18C, CS2 & Stacking Frames......Call MIRAGE D1010N 432 MHz Amp/Preamp \$279.00 TOKYO HY-POWER HL90U Amp/Preamp......305.00 KEN-PRO UHF/VHF Preamplifiers Call ALLIANCE U110 Small Elevation Rotator......... 49.00

Send SASE for our new & used equipment list. MON-FRI 9AM-6PM . SAT 9AM-3PM

NLA-150-MM 5/8 Wave 2M Mag Mt......\$39.00

Prices and Availability Subject to Change

Amtor Software Now Available

LARSEN

Merry Christmas from Dan, Sandi, Laura, Rick, Mary, Marconi, Dave, The Q & Harold.

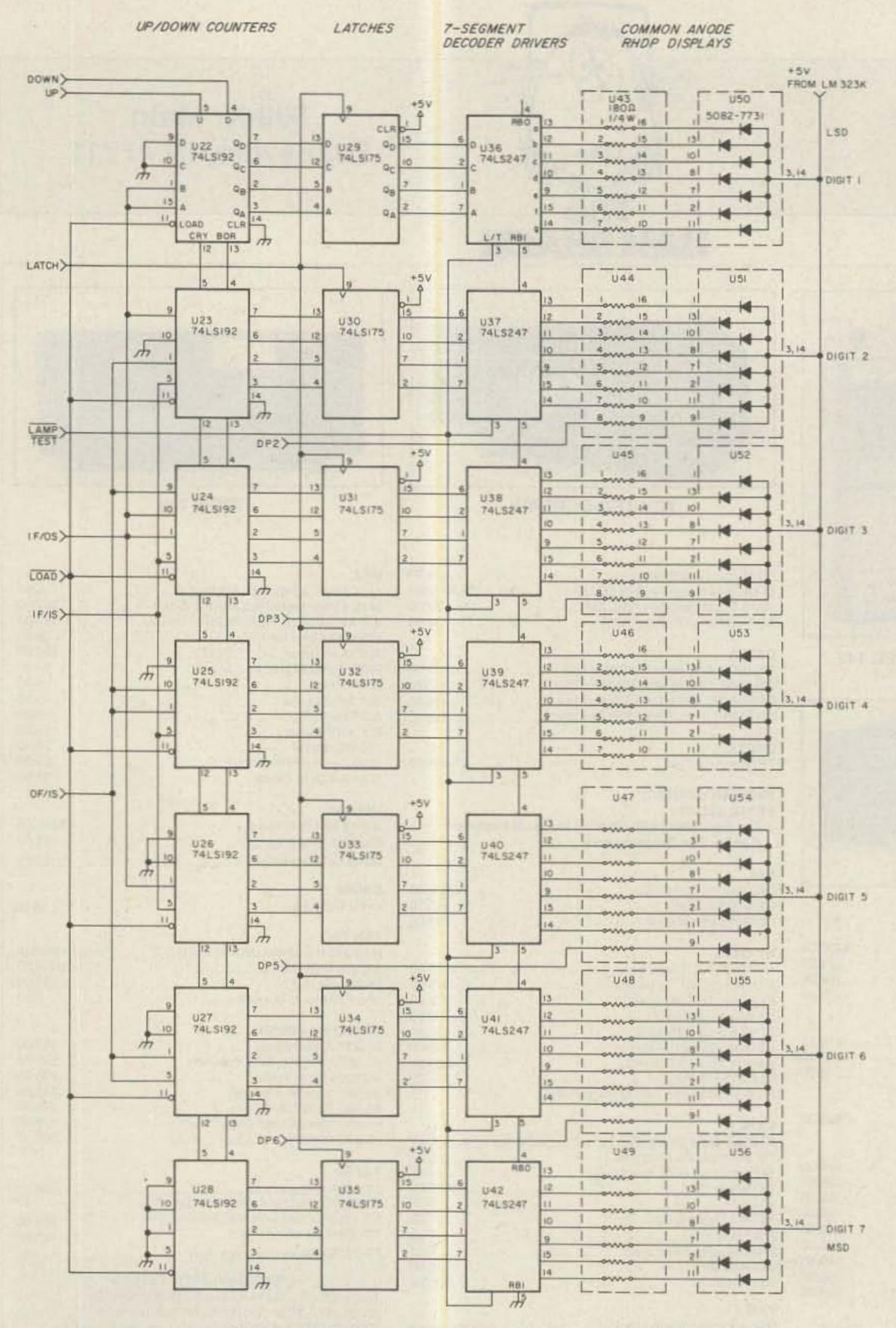


Fig. 5. Up/down counters and display schematic.

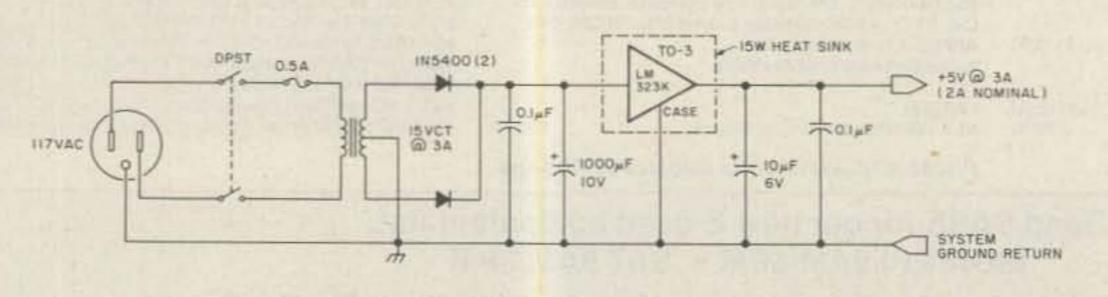


Fig. 6. Power supply.

The shields will be soldered to J13, pin 8. Dress and tin the leads for neatness.

(1)Bfo: Prepare a suitable length of coax and solder the inner conductor to one side of a .01-μF capacitor. Solder the other end of the capacitor to pin 6 of PB 1184A connector. Solder the shield to pin 7 (gnd). Route the cable to the octal vfo socket and solder the inner conductor to pin 3. Solder the shield to pin 8.

(2) LO: Prepare a length of coax and solder the inner conductor of one end directly to pin 15 of the PC connector for PB 1181A. Solder the shield to pin 18 (gnd). After routing the cable back to the vfo socket, solder the inner conductor to pin 7 and the shield to pin 8.


(3) Vfo: Prepare a length of coaxial cable. Solder the inner conductor to one end of a .01-μF capacitor. Solder the other end of the capacitor to pin 11 of the PC connector for PB 1180A (mixer). Solder the shield to pin 10. Route the cable to the vfo socket, soldering the inner conductor to pin 2 and the shield to pin 8.

(4) Remove PB 1181A. Solder a .01-μF capacitor between test point TP and pin 15. Replace PB 1181A.

The interface cable from the FT-101 to the VK8DE Calculating FT-101 Display consists of an octal plug, three equal sections of RG-174/U coax up to 1m in length, and three plugs. The plugs used in the prototype were BNC, but RCA shielded phono plugs would work. Prepare the plug ends of the cables, check for shorts, then solder the inner conductors to octal plug pins 2, 3, and 7. Label the cable to pin 2 "VFO," the pin 3 cable "BFO," and the pin 7 cable "LO," and solder the three shields to pin 8.

Plugging and unplugging the cabled octal plug at the external vfo socket will probably shift the receiver frequency a few Hertz. This is normal and merely re-

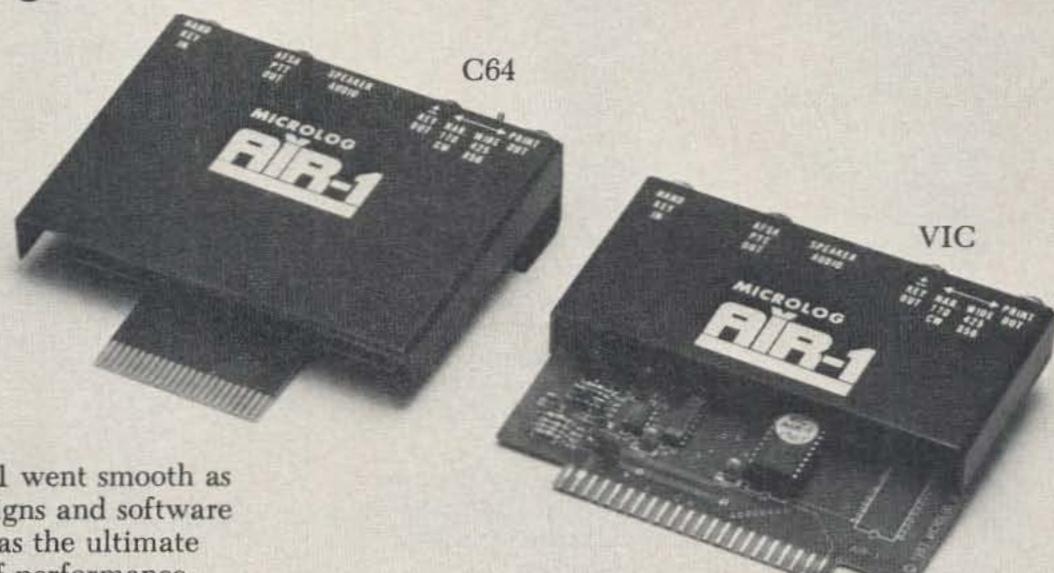The Evolution of a Superior Terminal for RTTY and CW



AIR-1 Past

As an R & D project, the AIR-1 went smooth as silk. By using our proven TU designs and software that's been refined on units such as the ultimate ATR-6800, we obtained a level of performance only found in much more expensive dedicated systems. Compare it for yourself or ask an AIR-1 owner. They work great!

AIR-1 Present

Along with great performance, the AIR-1 boasts an impressive list of features, some of which are exclusive to Microlog.

- Computer enhanced detection means extensive use of software digital filtering techniques for noise and bandwidth that track the operating speed and code.
- Full speed RTTY 60 to 132 WPM, CW to 150 WPM, & 110/300 Baud ASCII.
- Choice of full or split-screen display with large type ahead text buffer and programmable memories.
- On screen tuning indicators mean you never have to take your eyes off the video for perfect copy tuning. RTTY "scope" cross hatch and "red-dot" signal acquisition monitor right on the screen.
- Keyword or manual control of VIC or Parallel printer and receive buffer storage.
- Convenient plug-in jacks for all connections.
- Single board design contains TU & ROM software that does not require external power.
- · Full one year warranty.
- WRU, UNshift On Space, Word wrap-around, Test "Quick Brown Fox" & "RYRY" in ROM.
 Break buffer, Random Code generator, Handkey input, Real-time clock, sturdy metal cover and more.

The optional on-board 4 mode AMTOR includes these exciting extras:

- ARQ mode A (chirp), Time Diversity mode B (Selective & Collective Broadcast), and Listen (eavesdrop) for mode A.
- Word processor mode for full editing of transmit and receive text.
- The unprecedented ability to transmit BASIC programs over the air directly from memory!!! Just load your program normally by hand, disc or tape, jump to AIR-1 to establish communications, and type a special control command. The AIR-1 does the rest. All standard Commodore Basic and screen control commands are transmitted/received intact, just as you typed them, for immediate RUN/SAVE. Share BASIC programs with your friends around the world without tedious "two-step" re-typing or mailing fragile discs and tapes.

AIR-1 Future

There's room for expansion and adaptability with some really "neat stuff" planned for the AIR-1. But then, why tip off the competition? Now you understand how we live up to the title "Innovators in Digital Communications." The complete AIR-1 for VIC-20 or C-64 is \$199 (with AMTOR, \$279). See it at your local dealer or call Microlog Corporation, 18713 Mooney Drive, Gaithersburg, Maryland 20879. TELEPHONE (301) 258-8400, TELEX 908153.

MICROLOG _51
INNOVATORS IN DIGITAL COMMUNICATION

Commodore and VIC 20 are registered trademarks of Commodore Electronics, Ltd. Copyright © 1983 MICROLOG CORPORATION

Parts List FT-101 Interface 1 7406 3 .01-µF disc capacitors 1 74LS14 3 45-cm pieces RG-174/U 1 74874 1 74LS11 Interface Cable 74LS08 1 Octal plug 3 74LS74 3 1m sections RG-174/U 6 74LS90 3 RG-174 BNC plugs 7 74LS192 **Isolation Amplifiers** 7 74LS175 3 Metal boxes1 7 74LS247 3 5 x 2.5 cm fiberglass 7 5082-7731 red CA perfboard displays 3 BNC chassis jacks 1500 cm wire-wrap wire 2 1kΩ resistors **Power Supply** 10kΩ resistor 1 15 V CT @ 3 A 3 1 M resistors transformer 3 4.7kQ resistors 2 1N5400 diodes 3 180Ω resistors .5-Amp fuse 560Ω resistors fuse holder 3 470Ω resistors **DPST** switch 15kΩ resistors 1 1000-μF @ 25-V 1N914 diodes capacitor 3 MPF102 JFETs 1 10-μF @ 6-V capacitor 3 2N708 NPN 15-Watt TO-3 heat sink 3 47-µF, 6-V capacitors 1 LM323K 5-volt, 3-A 3 74LS04 regulator 3 14-pin solder-tail IC

Counter Board

sockets

3 RCA phono jacks

- 1 1-MHz series-resonant crystal
- 1 10-100-pF (nominal) ceramic trimmer cap
- 12 .1-µF disc ceramic caps
- 3 RCA shielded phono plugs
- 3 15 cm RG-174/U
- 1 2.2k, 1/4-W resistor
- 53 180Ω, 1/4-W resistors
- 2 100Ω, 1/4-W resistors
- 2 470Ω, 1/4-W resistors
- 2 160-pF caps
- 1 20 cm × 12 cm glass epoxy board2
- 31 16-pin DIP wire-wrap sockets
- 23 14-pin DIP wire-wrap sockets
- 8 16-pin DIP component carriers (headers)
- 1 74LS37
- 1 74LS157
- 1 74LS158

bezel

- 1 9 cm x 2 cm red display
- 3 SPDT toggle switches

1 LMB CO-4A cabinet

1 rubber grommet for power cord

2 .1-μF @ 50-V disc

capacitors

1 3-wire ac cord

Chassis

- 1 SPDT momentary switch3
- 1 100Ω, ¼-W resistor


Misc.

- 4 3-cm metal standoffs
- 4 2-cm metal standoffs
- 4 1.5-cm metal standoffs Screws, washers, bolts, wires, hand tools, solder, etc.
- 1. About 7.5 cm x 4.5 cm x 2 cm, similar to Bud 2100. 2. 2.54mm-spaced holedrilled, similar to Vector 84P44WE.
- Lamp test/power-on-reset.

flects the small change in oscillator loading.

The next step suggested is the construction of the three isolation amplifiers. Compact layout, either by printed-circuit etching Or point-to-point wiring, called for. A reasonable example layout for the amplifier from WA2FPT can be found in the September,

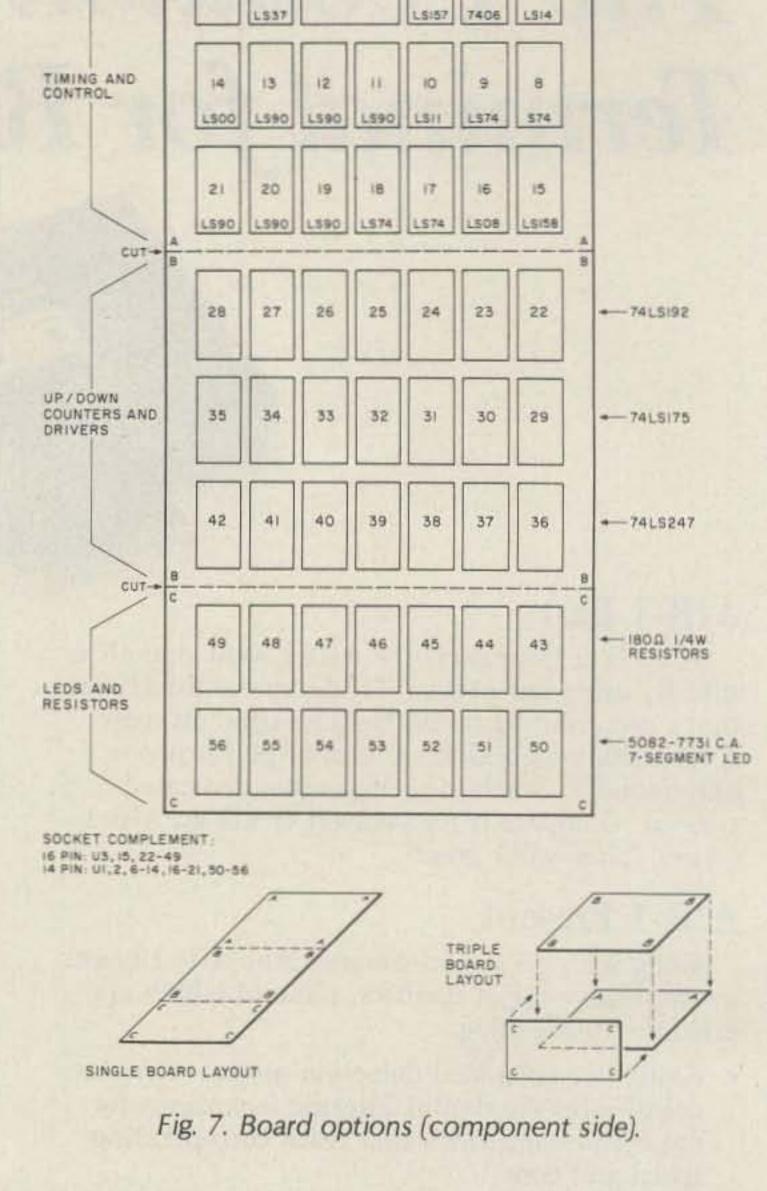1982, 73, on page 44. The three amplifiers were mounted in small metal boxes for shielding, with BNC inputs (J1, 2, and 3) and RCA phono-output jacks (J5, 6, and 7). RCA phono connectors could be used instead of BNC jacks to save a couple of dollars. The boxes were positioned at the rear of the cabinet so that J1, J2,



CRYSTAL OSC

MISC R.C

and J3 would protrude into the enclosed compartments.

The board layout shown in Fig. 7 allows a choice of packaging. Using the single-board approach minimizes interconnections between pieces but requires a larger cabinet and right-angle sockets for the display LEDs. Cutting the larger board into three smaller sections, as shown by dotted lines, allows for a more compact chassis but more board-to-board wires. The prototype employed the three-board approach, mainly for aesthetics. Either way will work. Liberal use of .1-µF bypass capacitors is recommended—about one to every four ICs.

After the isolation amplifiers are built and working. the power supply should be built to allow checkout of

succeeding sections. Then the 1-MHz oscillator and decade divider chain can readily be wired. This prototype used wire-wrapping on a 2.54mm drilled fiberglass board (similar to the Vector 84P44WE), but it is not required. Years of home-brewing, however, point to a higher success rate with wire-wrapping despite the extra cost. Point-to-point construction would be somewhat cheaper and will definitely work but would probably require a larger layout. The choice is yours.

Power and ground wires to all ICs should be wired next. Use of a TTL data book is helpful, remembering that the wiring side is a mirror image of the component side.

The control section was wrapped next, and the timing diagram of Fig. 2 should

WE SHIP WORLDWIDE

SOFF BECCE CONICS COFF WORLD WIDE AMATEUR RADIO SINCE 1950 Your one source for all Radio Equipment!

For the best buys in town call: 212-925-7000

Los Precios Mas Bajos en Nueva York...

142151 60



Join us for our G.W. "whale of a sale."

We are now an Authorized

KENWO

Dealer

R-600, R-1000, R-2000, TS-930S/AT, TS 430S, TR 2500/3500, TR 7930, TR 7950, TW-4000A.

Kenwood Service/Repair.

ROCKWELL/COLLINS KWM-380

VoCom/Mirage Tokyo Hy-Power Amplifiers & 5/8 \ HT Gain Antennas IN STOCK



AEA CP-1, Kantronics

Big Ham Clock/Ham Tags KANTRONICS Field Day 2, Mini-Reader, Interface, Software & Code Tapes

AEA 144 MHz AEA 440 MHz ANTENNAS

EIMAC 3-500Z 572B, 6JS6C 12BY7A & 4-400A

BIRD T'Wattmeters & Elements In Stock

KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK. Saturday & Sunday 10 to 5 PM

Monday-Friday 9 to 6:30 PM Thurs. to 8 PM Come to Barry's for the best buys in town. For Orders Only Please Call: 800-221-2683



I ICOM

IC-R70, IC-751, IC-730, IC-745, IC-27A, IC-37A IC-47A, IC-271A/H, IC-2KL, IC-471A, IC-290H, IC-120

YAESU

FT-ONE, FT-980, FT-102, FT-77, FT-230R FT-757GX FT-726R, FT-720RU, FT-290R, FRG-7700, FT-203R

ICOM YAESU IC2AT FT-208R IC3AT FT-708R IC4AT FTC-1903 IC02AT

Land-Mobile H/T Midland Wilson Mini-Com II Yaesu FTC-2203, FT-4703 Icom IC-M12 (Marine) Tempo M-1



DRAKE TR-5, TR-7A, R-7A, L-7, L-75, Earth Satellite Receiver ESR-24, THETA 9000E & 500. EARTH SATELLITE STATION ESS-2250



SMART PATCH

CES-Simplex Autopatch 510-SA Will Patch FM Transceiver To Your Telephone. Great For Telephone Calls From Mobile To Base, Simple To Use - \$319.95

SANTEC ST-222/UP ST-142/UP ST-442/UP NEW IMPROVED

MURCH Model MFJ UT2000B

Repeaters in Stock: Spectrum SCR-1000, 4000, & 77 ICOM IC-RP 3010 (440 MHz) ICOM IC-RP 1210 (1.2 GHz)

DIGITAL FREQUENCY COUNTER

Trionyx-Model TR-1000 0-600 MHz Digimax Model D-510 50 Hz-1GHz



Models

HAM MasterTapes-

Beta or VHS Tapes

900, 940B, 941C, & 951D

Tri-Ex Towers

ty-Gain Towers and Rotors

will be shipped direct to you FREE of shipping cost.

Telephone for export in stock **BENCHER PADDLES &**

Long-range Wireless

Vibroplex Keys In Stock!! New TEN-TEC 2591 HT, Corsair In Stock

Complete Butternut Antenna

Inventory In Stock!

ROBOT 450C-800C-1200C

Color Mod Kits

DENTRON IS BACK IN STOCK!

MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.

LARGEST STOCKING HAM DEALER **New York City's** COMPLETE REPAIR LAB ON PREMISES

"Aqui Se Habia Espanol"

BARRY INTERNATIONAL TELEX 12-7670 TOP TRADES GIVEN ON USED EQUIPMENT STORE HOURS: Monday-Friday 9 to 6:30 PM Parking Lot Across the Street

Saturday + Sunday 10 to 5 p.m. (Free Parking) AUTHORIZED DISTS. MCKAY DYMEK FOR SHORTWAVE ANTENNAS & RECEIVERS.

IRT/LEX-"Spring St. Station" Subways: BMT-"Prince St. Station" IND-"F" Train-Bwy. Station"

Bus: Broadway #6 to Spring St.

ORDER LINE CALL 800-221-2683

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astatic, Astron, B & K, B & W, Bash, Bencher, Bird, Butternut, CDE, CES, Collins, Communications Spec. Connectors, Covercraft, Cubic (Swan), Cushcraft, Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Eimac, Encomm, Hell-Sound, Henry, Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics, Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini-Products, Mirage, Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook, Robot, Rockwell Collins, Saxton, Shure, Swan, Telex, Tempo, Ten-Tec, Tokyo Hi Power, Trionyx TUBES, W2AU, Waber, Wilson, Yaesu Ham and Commercial Radios, Vocom, Vibroplex, Curtis, Tri-Ex, Wacom Duplexers, Repeaters, Phelps Dodge, Fanon Intercoms, Scanners, Crystals, Radio Publications.

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED.

COMMERCIAL RADIOS stocked & serviced on premises.

Amateur Radio & Computer Courses Given On Our Premises, Call Export Orders Shipped Immediately, TELEX 12-7670

be referenced for verification. Access to a dual-tracetriggered sweep oscilloscope would be extremely helpful if substantial troubleshooting is anticipated (or necessary!). The last section connected is circuitry from Fig. 5, consisting of the 74LS192 up/down counters, 74LS175 latches, 74LS247 decoder drivers, the 180-Ohm resistors, and the displays. The front of the prototype contains only the display bezel to emphasize the "hands-off" design concept. The FAST/SLOW switch is a long "bat handle" type on the upper-rear center panel that is easily accessed by a finger flick. For even easier access, it could as readily mount on the front, centered beneath the display.

Operational checks are made by watching the display as the FT-101 is tuned. Upon the application of power, the display will briefly flash all 8s. When display-

ing frequency, the last digit will be plus or minus a digit, and will change at either the 80-ms fast rate, or every 800 ms, the slow rate. The 80-ms (12.5 Hz) updates will track any tuning rate generated by human hands. Moving the FT-101/EXT switch to the EXT position with the unit cabled to the FT-101 will display the particular LO crystal-oscillator frequency.

The bfo-detect circuit is checked by noting the difference in frequency as the FT-101 is switched from CW to AM. The AM position should read about 800 Hz higher than the CW display. When the CAL signal is input into the LO/EXT jack (J2) and the EXT switch activated, the counter should read exactly .500.00 in the SLOW position, and .500.00 in the FAST position. A short wire inserted into the CAL jack (J4) and placed near the FT-101 antenna input will couple the CAL signal into

the FT-101, allowing bandedge checks. The 1-MHz oscillator can be trimmed WWV against in this manner.

Although any suitablesized, well-ventilated metal cabinet could be used to house the display counter, those in the LMB CO series of two-tone gray cabinets are particularly appealing. The prototype is housed in the CO-4A model (20×18× 10cm) which required careful, dense packaging. This line of cabinetry has a convenient sub-chassis that allows all the ac wiring to lie under the sub-chassis plate. A source for LMB cabinets is Tri-Tek, Inc., 7808 N. 27th Ave., Phoenix AZ 85021.

The VK8DE Calculating FT-101 Display can be built all-new purchased from parts for about US\$100. A little scavenging can reduce that figure substantially, however. Areas of cost reduction are cabinetry and

point-to-point wiring avoid wire-wrap construction.

The project was conceived, designed, and built sporadically over a two-year period, allowing for some refinement, circuit and, admittedly, for economical parts acquisition. An "asbuilt" parts list appears in the box. My only regret is that it was not built sooner.


A display counter such as this one is well worth the effort for the home-brewing FT-101 owner. Variations on the conventional design themes used are quite feasible and are to be encouraged for the adventurous experimenter.

As the one and two "kilobuck" price barriers are regularly burst by new HF transceivers, investing a modest sum and a little work to modernize the venerable FT-101 seems a rather attractive alternative.

Happy digitizing!

TUCSON AMATEUR PACKET RADIO

Complete Packet Radio Controller Kit!

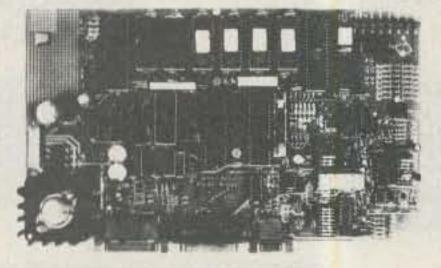

- Simple hookup and commands for the newcomer to packet!
- On-board modern designed for optimum performance with standard, unmodified
- · Retains over 60 user adjustable parameters (including call sign, terminal characteristics, etc.) - even with power removed!
- · Full AX.25 and VADCG protocols built inl
- · Simultaneous operation as packet station and digital repeater built in!
- Full duplex operation (perfect for Oscar 10) built in!
- RS-232C (to 19.2 kboud) and Parallel Interfaces—built in!
- Parallel port optionally configurable for link status monitoring built in!
- 32K ROM and 8K RAM included! (expandable to 64K without modification).
- . On board frequency calibration circuitry for modem built in!
- · Regulated power supply built in!
- · PC board electronically tested to assure quality!
- 200+ page manual with 50 page, heavily illustrated construction section—included!
- · Hundreds of TAPR TNCs are in the field NOW!
- For background, see Ham Radio (July and Rugust, 1983) and 73 Magazine (September and October, 1983).
- Support through PSA, TAPR's bi-monthly newsletter serving a membership of over 500. amateurs worldwide!
- Introductory price \$240 (plus \$7 S&H) in the US and Canada (Arizona residents add 5% tax.)
- Manual available separately for \$18 (plus \$2 S&H) in the US and Canada (manual price) creditable towards kit purchase)

- 136 Send a deposit of \$25 to secure your delivery position to: Tucson Amateur Packet Radio (TRPR) P.O. Box 22888, Tucson, RZ 85734 (A Non-Profit Research and Development Group)

Note: Due to heavy demand, allow up to 90 days for delivery. Prices and specifications subject to change without notice.

ALL NEW H.F. 10/160 METER SOLID STATE P.L.L. TRANSCEIVER



Model 10/160 M

USB-LSB

4 Memories 3 Way Auto-Scan Includes New Bands 3-Step Tuning Speed IF Tune ± 1 KHZ Built-in Dual VFO Narrow CW filter optional CW-W CW-N

200 W. PEP (160M-12M) 100 W. PEP (10M) **Built-in Power Supply** AC-120 VAC DC-13.8 V -Ground External ALC & Relay RTTY, FAX, ASCII



JUST SLIGHTLY AHEAD

1275 N. GROVE ST. ANAHEIM, CA 92806 Cable: NATCOLGLZ

TO ORDER OR DLR INFO. CALL (714) 630-4541

-254

NOTE: Price, Specifications subject to change without notice and obligation

Try an AEA Breakthrough

ADVANCED ELECTRONIC APPLICATIONS, INC. was the first company to introduce a single chip microcomputer-based product (the AD-1 Auto Dialer) to the consumer market back in 1977. Since that time, AEA has developed a reputation for engineering design excellence (in both hardware and software), high manufacturing quality, outstanding customer service and prices that are competitive with products providing much less value. If you have never owned an AEA product, ask others who have and you will find a real pride in ownership resulting from years of reliable and enjoyable service.

MICROPATCH™ Low-Cost/High-Performance Interface with Software



The MICROPATCH™ computer interface is our latest example of engineering excellence bringing you superb value at a low, low price. The MICROPATCH is a COMPLETE RTTY/CW/ASCII PLUG-IN HARDWARE/SOFTWARE PACKAGE for either the Commodore 64 (model MP-64) or VIC-20 computer (model MP-20). The MICROPATCH includes MBATEXT™ software which is currently the most extensive and most user-friendly communications software available for the VIC-20 or C-64 computers. The hardware outperforms any competitive unit we have tested under \$200, but is easily up-gradeable to the CP-1 Computer Patch™ without sacrificing \$90 worth of software. You can also use it with any other computer by making use of the MICROPATCH hardware and procuring new software. The MICROPATCH is extremely easy to integrate into your station by simply wiring a mating microphone connector onto a cable pre-wired to the MICROPATCH and by providing audio to the 3.5 mm jack on the MICROPATCH from your receiver external speaker jack. The MICROPATCH comes complete with keyboard overlay prompting aid and operator's manual. Operates from 12VDC (power supply not included). For more information, see your dealer or use the coupon below.

COMPUTER PATCH™ Deluxe Interface

The COMPUTER PATCH™ interface has earned a solid reputation for outstanding performance at a very reasonable cost. The COMPUTER PATCH features dual-channel Mark and Space filtering with a sophisticated Automatic Threshold Correction (ATC) circuit that allows for good copy even when either one of the tones is totally obliterated. The COMPUTER PATCH has become the new standard of excellence for computer interfaces. 117VAC wall adapter supply is included. AEA now has software available for most popular computers, including AMTORTEXT™ for the C-64 when used with the CP-1 or MICROPATCH.



MORSEMATIC™ Advanced Keyer/Trainer



AEA has developed the most sophisticated line of automatic microcomputerized Morse keyers and trainers in the world. AEA keyers and trainers are the standard against which all others have been judged and have fallen short. Two of our trainers (Model BT-1 and KT-3) are designed for people who have never learned the Morse Code. The BT-1 and KT-3 utilize our basic training program which actually teaches the code at 18 or 20 WPM character speed and allows you to go to 99 WPM. The proficiency training programs in the MM-2 and KT-2 are designed for the person who already knows the Morse Code, but wants to upgrade in the shortest time possible. All AEA keyers operate from 12VDC (power supply not included).

The ISOPOLE™ patented antenna has caused more excitement in innovative VHF antenna design than any antenna in recent history. Initially called a "gimmick" antenna by our competitors, all the laughter has long since subsided as the ISOPOLE has proven to be a high performer, rugged yet sleek appearing, and easiest of all to assemble, with little chance for installation or tuning errors.

In the same vein, the AEA Hot Rod" antenna is shorter, lighter and less bulky than competitive 5/8 wave two meter handheld whips. Equally important, the Hot Rod does not have an out-of-phase current at the base that distorts the pattern as in the case of the 5/8 wave competitors. This means actual on-thehorizon gain for the Hot Rod relative to the 5/8 wave. In spite of the fact that a tuning network to match an end fed half-wave is far more difficult to achieve than for a 5/8 wave, the Hot Rod is priced to compete.


Please Send:

Since our beginning in 1977 with one unique and innovative product, our product line has grown to over 30 catalog items. For your free catalog describing all our fine products in detail, please fill out and return the attached coupon or better yet, see your dealer.

AEA Brings you the Breakthrough!

☐ Catalog	☐ Dealer List	☐ Price List	□ Other
Name			
Address			
Telephone			

ANTENNAS

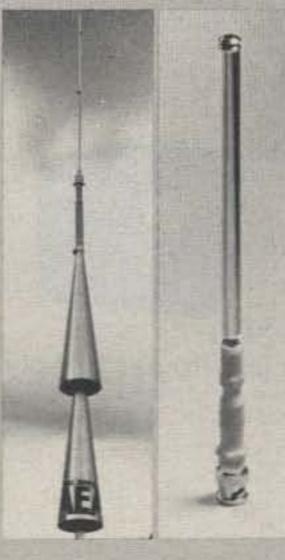

Advanced Electronic Applications, Inc. P.O. BOX C-2160 • LYNNWOOD, WA 98036 • (206) 775-7373 • Telex: 152571 AEA INTL



BE HEARD! GIVE YOUR HAND-HELD THE BOOST IT NEEDS!

The New Daiwa LA-2035 two meter linear amplifier.

A compact amp at a compact price Only \$79.95 Suggested Retail.

This amplifier is designed for use with hand-held transceivers in either mobile or fixed station configurations.

Because of its light weight and compact size, the LA-2035 can be mounted under the dash, under the seat, or in any other convenient location.

The LA-2035 is equipped with RF activated stand by circuitry. Easy operation. Simply connect your antenna and your hand-held to the LA-2035. Connect the LA-2035 to a suitable power supply and go.



Specifications Band: 144-148 MHz Mode FM/CW/SSB Input power: 1-3 watts

Maximum output power: 30 watts plus. Power consumption: 13.8VDC at 5A. Max. Dimensions: 100W × 35H × 125Dm/m Weight: 500 grams

Coaxial input cable supplied with a BNC connector Output connector: S0 239

CN-520/CN-540/CN-550 Cross Needle Meters

Daiwa cross needle convenience in a compact case Get SWR and Power readings in a single glance.



CW is both communication and art. Sharpen your "fist" with Daiwa precision!

PS-300 30A DC Power Supply

9-15 V variable 30A Max., 22A continuous Overload protected multiple terminals



DK-200/DK-210

Electronic Keyers



All Mode Active Filters Luxurious selectivity at an affordable price!

AF-606K/AF-406K

858 E. Congress Park Dr. Centerville, Ohio 45459. Phone 1-513-434-0031 Exclusive U.S. Agents for these DAIWA products. Dealer inquiry invited.

HIGH PERFORMANCE PRESELECTOR-PREAMP

The solution to most interference, intermod, and desense problems in AMATEUR and COMMERCIAL systems.



Typical rejection:

±600 Khz@144 Mhz: -28dB

±1.6 Mhz@220 Mhz: -40dB

±5 Mhz@450 Mhz: -50dB

. 40 to 1000 Mhz - tuned to your frequency

5 large helical resonators

· Low noise - High overload resistance

• 8 dB gain - ultimate rejection > 80 dB

. 10 to 15 volts DC operation


Size - 1.6 x 2.6 x 4.75" exc. connectors


FANTASTIC REJECTION!

Price - \$79.95 bipolar w/RCA jacks Connector options: BNC \$5, UHF \$6. N \$10

SUPER HOT! GaAs Fet option \$20

AUTOMATIC IDENTIFIERS

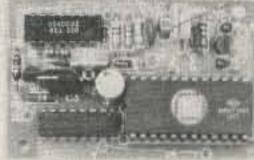

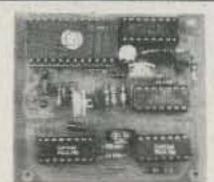

10-2

- For transceivers and repeaters AMATEUR and COMMERCIAL
- Automatic operation adjustable speed and amplitude
- . Small size easy installation 7 to 15 volts DC
- · 8 selectable, reprogrammable messages each up to 2 min. long
- · Wired, tested, and programmed with your message(s) Model ID-1 - \$39.95 Model ID-2 w/2 to 10 minute timer - \$59.95

We offer a complete line of transmitter and receiver strips and synthesizers for amateur and commercial use. Request our free catalog. Allow \$2 for UPS shipping - Mastercard and VISA welcome

1952 Clinton St. Buffalo, NY 14206 716-824-7936, 9 to 4

143

WORK THE U.H.F. BANDS

Add a transverter or converter to your existing 10m, 6m or 2m equipments. Choose from the largest selection of modules available for DX, OSCAR, EME, ATV.

TRANSVERTERS



MMT 50-144 \$189.95 MMT 144-28 \$179.95 MMT 432-28 (S) \$269.95 MMT 439-ATV \$349.95 MMT 1296-144 \$339.95 OTHER MODELS AVAILABLE write for details

POWER AMPLIFIERS

all models include RF VOX & Low Noise RX Pre-Ampl. (no pre-amp in MML432-100)

100W output MML144-100-LS 1W or 3W in \$254.95 2 Meters: 100W output MML144-100-S 10W input \$264.95 50W output MML144-50-S 10W input \$214.95 30W output MML144-30-LS IW or 3W in \$109.95 25W output MML144-25 3W input \$114.95 432 MHz: 100W output MML432-100 10W input \$399.95 50W output MML432-50 10W input \$239.95 30W output MML432-30-L 1W or 3W in \$199.95 1268-1296 MHz: Coming soon. Watch for details.

ANTENNAS (incl. 50 ohm balun) 2 Meter J-Beams: 12.3 dBd gain

8 over 8 Horizon'l pol D8-2M \$63.40 8 by 8 Vertical pol D8-2M-vert 1250-1300 MHz Loop-Yagi 1296-LY


70 cm/MBM 88

\$76.95 \$44.95 70 cm/MBM 48 \$75.75

70/MBM 48

Send 36¢ stamps for full details \$105.50 of all our VHF/UHF items Pre-selector filters Pre-amplifiers Antennis

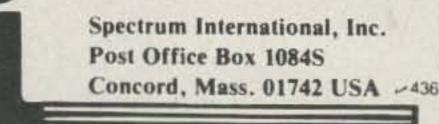Low-pass filters Transverters Varactor triplers Converters





Crystal Filters

-82



HF Transceivers
IC-740 9-band 200w PEP Xcvr w/mic \$1099.00 94995
plus FREE PS-740 internal power supply &
S50 Factory Rebate - until gone!

Sou Factory Repate	unun g	one:
PS-740 Internal power supply *EX-241 Marker unit *EX-242 FM unit *EX-243 Electronic keyer unit *FL-45 500 Hz CW filter (1st IF)	\$159.00 20.00 39.00 50.00 59.50	
*FL-54 270 Hz CW filter (1st IF) *FL-52A 500 Hz CW filter (2nd IF) *FL-53A 250 Hz CW filter (2nd IF) *FL-44A SSB filter (2nd IF) SM-5 8-pin electret desk microphone HM-10 Scanning mobile microphone MB-12 Mobile mount *Options also for IC-745 below	47.50 96.50 96.50 159.00 39.00 39.50 19.50	8995
*Options also for IC-745 below. IC-730 8-band 200w PEP Xevr w/mic EL-30 SSR filter (passband tuning)		599 ⁹⁵
FL-30 SSB filter (passband tuning) FL-44/A SSB filter (2nd IF) FL-45 500 Hz CW filter EX-195 Marker unit EX-202 LDA interface; 730/2KL/AH-1 EX-203 150 Hz CW audio filter EX-205 Transverter switching unit SM-5 8-pin electret desk mic HM-10 Scanning mobile microphone MB-5 Mobile mount IC-720A 9-band Xcvr/.1-30 MHz Rcvr \$ FL-32 500 Hz CW filter FL-34 5.2 KHz AM filter SM-5 Desk microphone MB-5 Mobile mount	59.50 159.00 59.50 39.00 27.50 39.00 39.00 39.50 19.50 49.50 39.00 19.50	
PS-35 Internal power supply CF5-455K5 2.8 KHz wide SSB filter HM-12 Hand microphone SM-6 Desk microphone See IC-740 list above for other opt	\$999.00 160.00 TBA 39.50 39.00	14495



IC-751 9-band Xcvr/.1-30 MHz Rcvr \$	1399.00	1229
PS-35 Internal power supply	160.00	THE R. P. LEWIS CO., LANSING, MICH.
FL-52A 500 Hz CW filter	96.50	8995
FL-53A 250 Hz CW filter	96.50	8995
FL-33 AM filter	31.50	1
HM-12 Hand microphone	39.50	
SM-6 Desk microphone	39.00	
RC-10 External frequency controller	35.00	
CR-64 High stability reference xtal	56.00	
Options: 720/730/740/745/751	Regular	SALE
PS-15 20A power supply	\$149.00	13495
EX-144 Adaptor for CF-1/PS-15	6.50	
CF-1 Cooling fan for PS-15	45.00	
PS-20 20A switching ps w/speaker	229.00	19995
CC-1 Adapt. cable; HF radio/PS-20	10.00	1

ICOM

(miles a parties and a second	The Contract of the Contract o
Options - continued	Regular SALE
Options - continued CF-1 Cooling fan for PS-20	45.00
EX-310 Voice synthesizer for IC-751	
SP-3 External speaker	
Speaker/Phone patch - specify radio	100 mm (40)
BC-10A Memory back-up	
EX-2 Relay box with marker	
AT-100 100w 8-band automatic ant tuner	
AT-500 500w 9-band automatic ant tuner	449.00 39995
MT-100 Manual antenna tuner	
AH-1 5-band mobile ant w/tuner	
PS-30 20A systems power supply	
GC-4 World clock	
14.61	Regular SALE
HF linear amplifier	The state of the s
IC-2KL 160-15m/WARC solid state linear	1795.00 1295
VHF/UHF base multi-modes	-740 00 54005
IC-251A* 2m FM/SSB/CW xcvr	\$749.00 54933
*\$50 Factory Rebate -	until gone!
	The second second second
IC-551D 80w 6m Xcvr	\$699.00 59995
PS-20 20A switching ps w/speaker	
EX-106 FM adaptor	
BC-10A Memory back-up	100 0000
SM-2 Electret desk microphone	
	100 Television (1995)
IC-271H 100w 2m FM/SSB/CW Xcvr	
PS-35 Internal power supply	
IC-271A 25w 2m FM/SSB/CW Xcvr	699.00 629 95
IC-451A 430-440 SSB/FM/CW Xcvr/ps	
IC-451A/high 440-450 Xcvr/ps	899.00 769 95
AG-1 15 db preamp for IC-451A/45A	89.00 79 95
IC-471A 10w 430-450 SSB/CW/FM Xcvr	799.00 71995
PS-25 Internal power supply	
EX-310 Voice synthesizer	17 T T T T T T T T T T T T T T T T T T T
HM-12 Hand microphone	
SM-6 Desk microphone	10.00
VHF/UHF mobile multi-modes	55.00
	549.00 489 95
IC-290H 25w 2m SSB/FM Xcvr, TTP mic	
IC-560 10w 6m SSB/FM/CW Xcvr	
IC-490A 10w 430-440 SSB/FM/CW xcvr	649.00 579 95
VHF/UHF/1.2 GHz FM	000 00 0400
IC-22U 10w 2m FM non-digital Xcvr	
EX-199 Remote frequency selector	35.00
IC-25A 25w, 2m, grn leds, up-dn-TTP mic	359.00 319 95
IC-25H as above, but 45 Watts	389.00 349 95
IC-27A 25w 2m mobile Xcvr	
IC-45A 10w 440 FM Xcvr, TTP mic	
EX-270 CTCSS encoder	
BU-1 Memory back-up	120 200 E
RP-3010 10w 440 MHz FM repeater	
KT-3010 TOW 440 MITE THE TEPERATE	333.00 033
Buy (10) IC-45A's at one time	at our SALE
PRICE & get an RP-3010 at 50%	OH OI LIST.
IC 100 1 TO CITE EM Vere	¢400 00 44095
IC-120 1w 1.2 GHz FM Xcvr	A STATE OF THE PARTY OF THE PAR
RP-1210 10w 1.2 GHz FM repeater	
Cabinet for RP-1210 or RP-3010	
VHF/UHF portables	Regular SALE
IC-505 3/10w 6m port. SSB/CW Xcvr	\$449.00 39995
BP-10 Internal nicad battery pack	79.50
BC-15 AC charger	
EX-248 FM unit	
LC-10 Leather case	THE PARTY NAMED IN COLUMN TWO IS NOT THE PARTY N
IC-402 432 MHz portable SSB xcvr	The state of the s
SP-4 Remote speaker for portables	
IC-3PS Power supply for portables	
IC 201 2m 3/10w PEP or FM amp	98 00 8995



Accessories for hand-helds

Hand-held transceivers: Regular SALE Deluxe models IC-02A for 2 meters \$ 319.00 28995 IC-02AT w/DTMF.... 349.00 31495 IC-04A for 440 MHz TBA IC-04AT w/DTMF..... Standard models Regular SALE IC-2A for 2 meters ... 239.50 21495 IC-2AT with TTP 269.50 21995 IC-3A for 220 MHz ... 269.95 23495 IC-3AT with TTP 299.95 23995 IC-4A for 440 MHz ... 269.95 23495 IC-4AT with TTP 299.95 23995

Regular

riceessories for fluire fieres
BC-25U Extra wall charger \$ 10.00
BC-30 Drop-in rapid charger 69.00
BP-2* 425ma 7.2v 1w long life battery 39.50
BP-3 Extra 250ma 8.4v 1.5w battery 29.50
BP-4 Alkaline battery case
BP-5* 425ma 10.8v 2.3w high power batt 49.50
*BC-30 required to charge BP-2/5
CA-2 Telescoping 2m antenna
CA-5 5/8-wave telescoping 2m ant
CP-1 Cig lighter charger (for BP-3) 9.50
DC-1 DC operation module
FA-2 Extra 2m flexible antenna
HM-9 Speaker/microphone 34.50
LC-2A Leather case without TTP cut-out 34.95
LC-2AT Leather case w/TTP cut-out 34.95
ML-1 2m 2.3w/10w amplifier (use BP-5) SALE 79.95
ML-25 2m 20w amplifier SALE 179.95
3A-TTN 16-button TTP front; 2A/3A/4A 39.50
CommSpec SS-32M 32-tone encoder 29.95
CA-3 Extra 220 flexible antenna 9.12
CA-4 Extra 440 flexible antenna 9.12
M-12 12 ch marine hand-held SPECIAL 269.95
S 55" THE PERSON OF THE PERSON

Shortwave receiver	Regular SALE
R-70 100 KHz-30 MHz digital receiver	
EX-257 FM unit	
IC-7072 Transceive interface, 720A	112.50
FL-44/A SSB filter (2nd IF)	
FL-63 250 Hz CW filter (1st IF)	
SP-3 External speaker	49.50
EX-299 (CK-70) 12v DC option	
MB-12 Mobile mount	

Use your Credit Card!





HOURS: Mon. thru Fri. 9-5:30; Sat. 9-3 Milwaukee WATS line 1-800-558-0411 answered evenings until 8:00 pm, Monday thru Thursday.

Please use WATS line for Placing Orders.
For other information, etc. please use Regular line.

Order Toll Free: 1-800-558-0411

In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195

AMATEUR ELECTRONIC SUPPLY ING

IC-20L 2m 3/10w PEP or FM amp

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES.

WICKLIFFE, Ohio 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside 1_800-321-3594 ORLANDO, Fla. 32803 621 Commonwealth Ave. Phone (305) 894-3238 Fla. WATS 1-800-432-9424 Outside 1-800-327-1917 Florida

CLEARWATER, Fla. 33575
1898 Drew Street
Phone (813) 461-4267
No In-State WATS
No Nationwide WATS

LAS VEGAS, Nev. 89106 1072 N. Rancho Drive Phone (702) 647-3114 No In-State WATS Outside 1-800-634-6227

98.00 8995

CHICAGO, Illinois 60630 ERICKSON COMMUNICATIONS 5456 N. Milwaukee Avenue Phone (312) 631-5181 Outside 1-800-621-5802

Associate Store

Strictly for FM Deviates

Ever wonder how the modulation is on your FM rig? Try this simple deviation meter and find out.

Rudolf E. Six KA8OBL 30725 Tennessee Roseville MI 48066

Unlike AM-SSB, FM modulation monitoring on most rigs simply is not available. It's unusual to see audio-modulated transmitters without some indicator to monitor modulation. The opposite is true of FM transceivers. The only indication

that your talk power is too high is distortion at the receiving end.

The FM deviation meter I built can be used for monitoring modulation, frequency offset between transmitters, etc. Its most attractive features pay off when, in conjunction with an audiofrequency generator, the transmitter is bench-checked for equal deviation on

both sides of the carrier, maximum deviation, and audio distortion.

Amateur FM uses narrow-band FM, ±5 kHz maximum deviation from the carrier. The instrument can measure ±10 kHz deviation at 146.52 MHz, the common direct 2-meter frequency. An audio output with 750-µsec de-emphasis is available for scope monitoring. Most parts

are available from Radio Shack, coils and variable cap were purchased from Radio Kit, and the crystal from Sentry Manufacturing.

The heart of the deviation meter is a 565 PLL FM demodulator listed as having a high linearity of demodulated output (0.2%). Calibration proved this out, better than 1% at the meter. The circuit uses the heterodyne method. A crystal-controlled local oscillator beats with the incoming signal and the resulting lower frequency FM is demodulated by the phase-locked loop. After filtering, a peak detector displays the maximum positive or negative frequency excursion of the incoming signal.

How It Works

The internal frequency generator starts with FET local oscillator Q2 at 14.655 MHz. The ouput tank circuit is tuned to the 5th harmonic; it drives doubler circuit Q1. The output is thus 146.55 MHz. The incoming signal with a carrier of 146.52 MHz and the local oscillator are lightly coupled into the mixing diode, D1, resulting in a beat frequency of 30 kHz. This signal has the modulation of the incoming signal. To minimize capacitive loading of the diode, the signal first goes through highfrequency choke L5 and

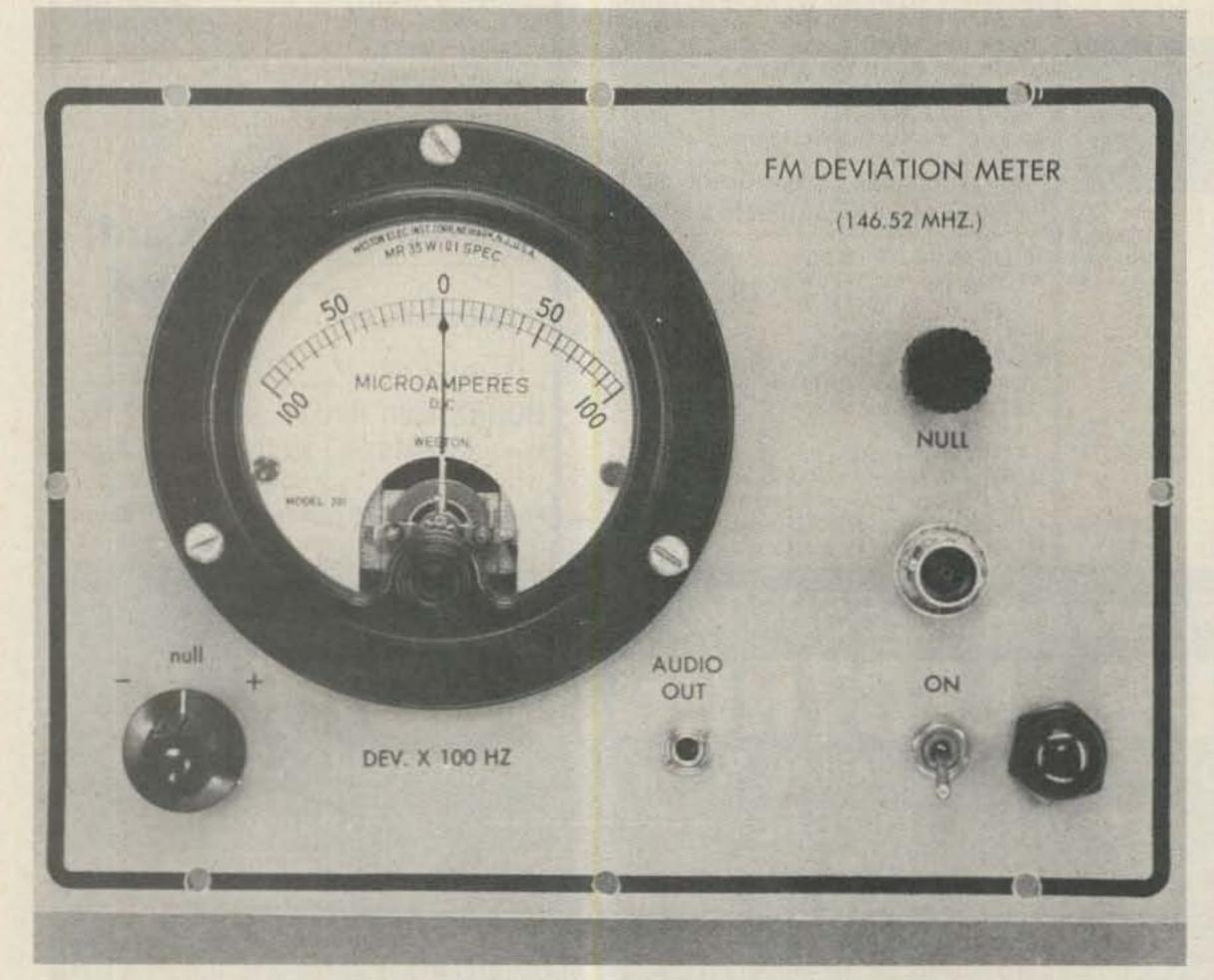


Photo A. Two-meter FM deviation meter.

then low-pass filter L6-C24. Amplifier Q3 boosts the signal approximately 10 times.

The 565 PLL has a voltagecontrolled oscillator centertuned to 30 kHz with C16-R13-R14. Basically, the incoming signal is compared with this oscillator and a dc voltage is generated which is directly proportional to the frequency of the input signal. As the input frequency shifts, it is this output signal which causes the vco to shift its frequency to match that of the input. The peak voltage occurs at peak frequency deviation.

This demodulated audio signal is available at pin 7 of IC1 and is connected to the low-pass filter and to the audio output jack through deemphasis network R15-C21. Low-pass filter IC2a filters some 30 kHz noise generated within the PLL. The peakdetecting circuit, IC2b, charges C23 to either the positive or negative peak, selectable with switch S1. M1 essentially shows the peak voltage across C23.

The null mode of S1 is used

for adjusting the difference between the unmodulated carrier and local oscillator to 30 kHz. The output voltage from the PLL at pin 7 is a dc voltage since there is no modulation. Amplifiers IC2a and IC2b works as straightforward dc amplifiers and M1 is calibrated at 30 kHz for zero reading with R16, an offset potentiometer. During use, zero adjust is made by changing the local oscillator frequency with C9, the null control.

Construction

A 7"×5"×3" aluminum box is used for the enclosure. The oscillator is mounted on a separate board and is shielded from the rest of the circuitry. Feedthrough capacitors for power to the oscillator and the PLL input signal are used to prevent rf leakage. The shielding extends wall to wall of the enclosure; slits were filed in the box lip to let the shields slide through. Both oscillator coils were close-wound with #22 enamel wire. The top of the coil connects to

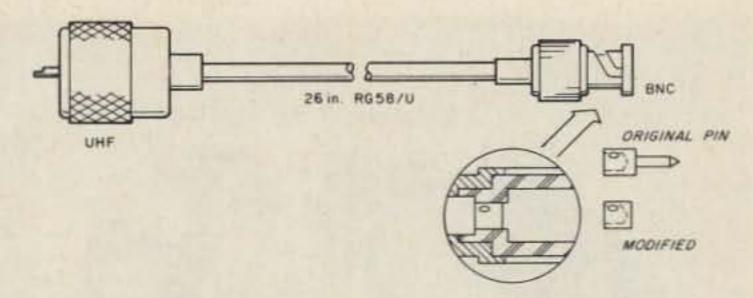


Fig. 1. Cable connectors.

the collector and the bottom end to the power supply. Tuned-circuit caps should be temperature-stable NPO discs or silver micas and are mounted at the coil with the shortest leads possible. The rest of the parts are mounted thorough the perfboard, bent over and soldered. The complete oscillator mounts on a 1.5" x 1.75" surface with 3/4"-long spacers.

The mixing diode, D1, is mounted right behind the BNC connector. C1 reaches from the oscillator board, and L5 leads the signal to the PLL circuitry. D1 works best with a minimum of parallel capacitance. The PLL and meter circuitry together with the power supply also are mounted on perfboard. The parts are soldered to flea clips and are wired at the rear with a Vector wire pencil. All variable pots face the back for easy adjustment when the instrument is out of the enclosure. The meter is shielded from all the circuitry since rf could enter through its face.

The calculated value of the resistors used in the lowpass filter are shown on the schematic. The nearest standard value is listed in the parts list. I used a borrowed LCR bridge to select C19-C22-R18-R19-R20 to within 1% of the calculated value. If this is not possible, use standard values and check the low-pass filter for flat response with an audio generator. With 1% parts, the response curve is flat to 2 kHz, drops to approximately

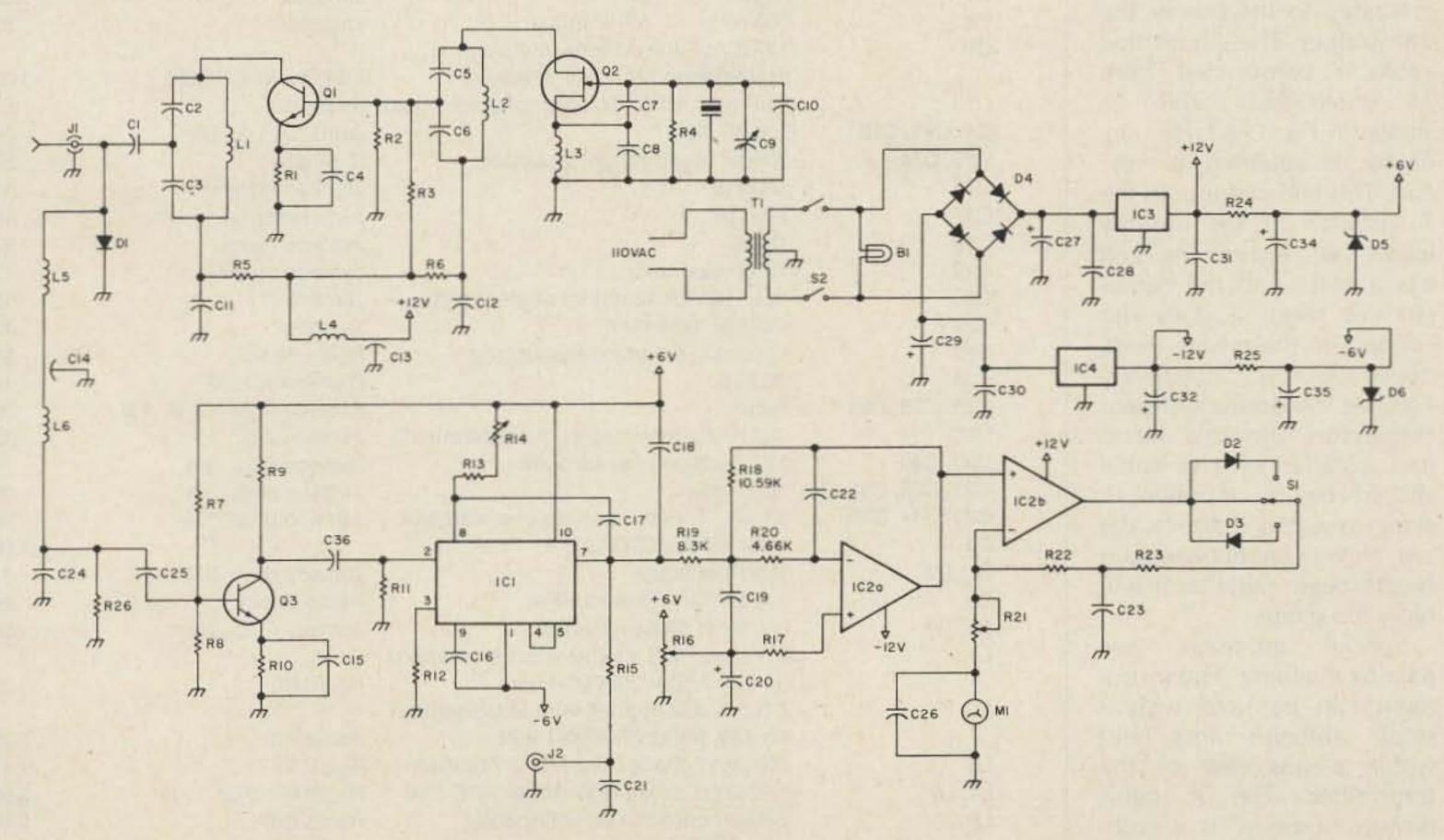


Fig. 2. Schematic.

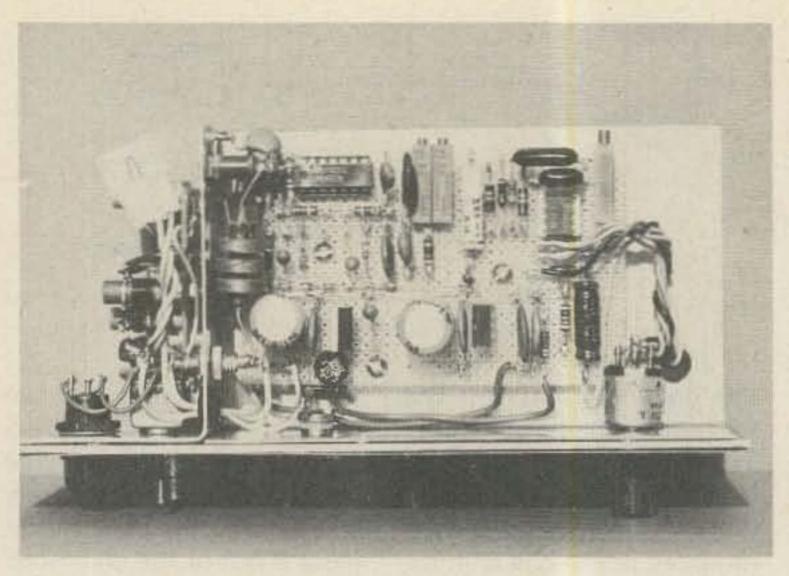


Photo B. Bottom view. Signal enters through C14 feedthrough. PLL circuitry and power supply are mounted on one board.

94% at 3 kHz, and 70% at 5 kHz. For accurate measurements of deviation, an audio tone of less than 2 kHz should be used. I used a 1.8-kHz "Sonalert" piezobuzzer right into the microphone. These units output a clean sine-wave tone, easy for a quick test.

The power-supply transformer is mounted in the back of the box, oscillator section, and is connected with a 3-pin molex® connector. The center tap is grounded to the box at the transformer. The connecting cable is constructed from 26" of RG-58/U cable. As shown in Fig. 1, a UHF connector is soldered to one end. This will connect to the T installed at the dummy load. The instrument end has a BNC with the center pin cut short; it does not connect to the mixing diode directly but is capacitively coupled. Mounting different connectors prevents incorrect installation. The cable should be 1/2 wavelength since, as a stub, it affects the swr. Never connect a regular feedthrough cable as it will blow the diode.

Special attention was paid to shielding. The instrument can be used with a small antenna and held within a few feet of the transmitter. The rf noise pickup, however, is a problem and can cause unpre-

dictable meter readings. The best way is to use a tapped dummy load with coax connections and good shielding practices.

The microammeter is a 100-0-100 movement liberated from a local surplus store for \$3.50. It is an accurate movement and originally came from a General Radio instrument. An off-center scale movement can be used but extra contacts will be needed on \$1 to reverse the meter.

The parts are readily available. D1 is a UHF mixer diode purchased from a local Radio-TV supply firm. The negative voltage regulator and 10-turn pots are available from mail-order electronic parts suppliers. Coils, chokes, and caps are available from Radio Kit, Box 411S, Greenville NH 03048. They have a small catalog listing radio parts which are almost impossible to obtain elsewhere. Radio Shack fills

out the remainder of the parts list.

Calibration and Use

The PLL was calibrated with an audio generator monitored by a frequency counter. A 30-kHz audio tone of approximately 40-mV p-p output is fed into amplifier Q3 at R26. L6-C24 is disconnected. Pin 7, IC1 is monitored with a dc voltmeter and R14 is adjusted to a point where there is no change in voltage between the audio tone connected and disconnected. This establishes the internal vco of the PLL at 30 kHz. Switch S1 is turned to center position, or null, and R21 is adjusted at approximately the midpoint of its resistance range. M1 is now adjusted for zero, or null, with R16.

	Parts List		
B1	24-V power-on indicator	Fair Radio—Holder	
		6210-617-0934 and lamp	
		(#327)	.78
C1	3.3-pF disc	Radio Kit	.20
C2	5 pF (May	Radio Kit	.50
C3	50 pF be	Jameco	.35
C5	15 pF disc,	Jameco	.35
C6	33 pF NPO,	Jameco	.35
C7	25 pF or	Jameco	.35
C8	100 pF silver mica)	Jameco	.35
C9	1.8-8.7-pF air variable, null control		
	(Hammarlund MAC-10 or equiv.)	Fair Radio 228-6085	1.25
C10	5-pF disc, NPO, or silver mica (see text)	Radio Kit	.50
C4, C11, C12	500-pF disc	Jameco (3 @ .08)	.24
C13, C14	100-pF feedthrough capacitor	(2 @ .25)	.50
C16	.0022 μF	Jameco mylar TM .	.12
C17	1000 pF	Jameco mylar	.12
C18	.01 µF	Jameco mylar	.12
C19	.01 µF (see text)	Jameco mylar	.12
C20	1-μF, 16-V-dc tantalum or electrolytic	Jameco	.15
C22	.0022 µF (see text)	Jameco	.12
C23	10-μF non-polarized electrolytic	Radio Shack	.99
C24	.003 μF	Digi-Key M1332	.14
C15, C25, C36	.02 µF	Jameco mylar (3 @ .13)	.39
C26	.1-µF disc, mounted at meter terminals	Jameco disc	.12
C27, C29	220-μF, 25-V-dc electrolytic	Jameco (2 @ .39)	.78
C21, C28, C30, C31	1.05-µF disc	Jameco (4 @ .09)	.36
C32, C34, C35	4.7-μF, 16-V-dc tantalum or electrolytic	Jameco (3 @ .15)	.45
D1	1N84 diode (ECG 112)		1.00
D2, D3	1N914 or equiv.	Jameco (2 @ .07)	.14
D4	1-A, 50-piv bridge rectifier	Radio Shack	.89
D5, D6	6-V zener diodes 1N4735	Jameco (2 @ .25)	.50
L1	41/2 turns, #22 enamel wire close-wound		
	on J.W. Miller 20A000-4 core	Radio Kit	3.30
L2	7 turns, #22 enamel wire close-wound		
	on J.W. Miller 20A000-4 core	Radio Kit	3.30
L3	100-µH rf choke (J.W. Miller 74F104A1)	Radio Kit	1.45
L4, L5	1.72-µH rf choke (J.W. Miller RFC-144)	Radio Kit (2 @ 1.75)	3.50
L6	2-mH rf choke (J.W. Miller 4666)	Radio Kit	2.40

Vary the audio generator above and below 30 kHz and note the meter movement. An increase in frequency should show an increase in meter movement, a frequency decrease, a decrease in meter movement. If it is the reverse, interchange D2-D3 wires to S1.

Set the audio generator at 35 kHz and adjust the meter reading to 5 kHz with R21. Turning S1 to + deviation should not have any effect on the meter reading. Conversely, adjust for 25 kHz and note a negative meter reading of 5 kHz in null, or -, deviation. Slowly decrease the frequency to 20 kHz. The meter should come close to 10-kHz deviation and then suddenly return to zero. The PLL has lost control at that point.

Set the audio generator 1 kHz below the point the PLL loses control and now slowly decrease the input voltage. Again at some input level the PLL will lose control. Carefully note this voltage; it is the minimum voltage required to give fullscale indication. It could be as low as 5-mV p-p. For reliable operation, the voltage from the mixing diode, D1, should be at least four times this minimum level. I checked the meter in 1-kHz steps and found the calibration better than 1%.

Reconnect the L6-C24 filter to R26 when the calibration is completed. The local oscillator is tuned up by first turning the tuning slugs all the way in. R26 is monitored with a dc volt-

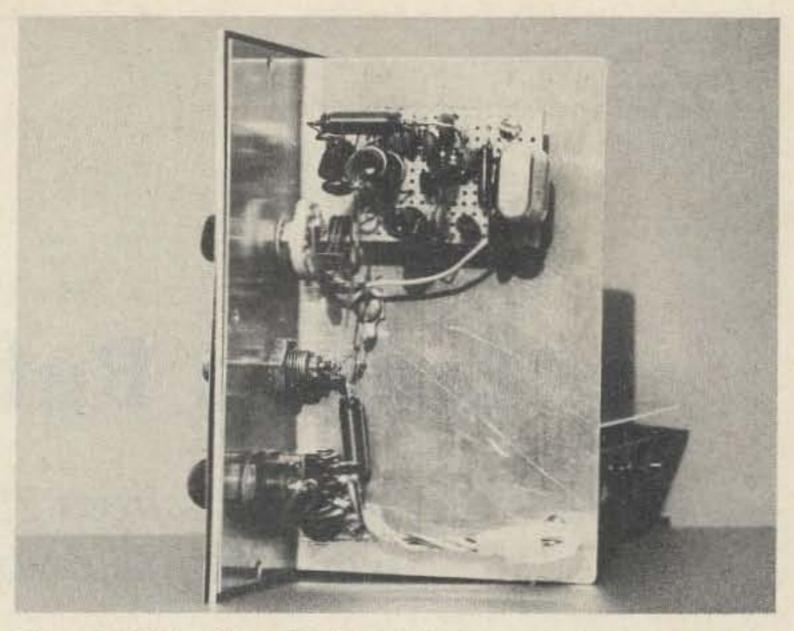


Photo C. Right side—the internal frequency generator. C1, D1, and L5 are shown connected to the BNC connector. L4 at the left top supplies power through feedthrough C13. The molex connector at the bottom connects to the transformer.

meter, and L2, L1 is tuned for a peak reading of approximately ¼ volts dc. Make sure the output is the 10th harmonic or 146.55 MHz, with a wavemeter or such, and not the 11th or 9th harmonic.

The transceiver is now connected to the dummy load with a T connector. Attach the special cable and tune the transceiver to 146.52 MHz direct. Set C9. the null control, at half capacitance. Attach a scope to resistor R26. The scope, during transmit, should display a sine wave of approximately 40-mV p-p amplitude and a frequency above 30 kHz. A value of 5 pF for C10, installed across C9, should bring the frequency to about 30 kHz. The idea is to have C9 in the middle of its operating range.

At this point, we are ready to try measuring deviation. I tested a 10-Watt unit and a 2-Watt hand-held in high and low power. With the deviation meter switched to null, push to transmit and zero the meter with the null control. Turn to + deviation and hum loudly into the microphone. The meter will show maximum positive deviation. Turn to - and repeat for negative deviation. The reading should be the same, and at 5 kHz.

Q1	MPS 918	Radio Shack	.89
Q2	MPF 102	Digi-Key	.54
Q3	2N3904 or equiv.	Digi-Key (2 @ .20)	.40
IC1	LM565 PLL	Jameco	1.19
IC2	1458 dual 741	Jameco	.59
IC3	LM340T12	Jameco	.79
IC4	LM7912CT	Jameco	.89
R1	470-Ohm, 1/4-Watt resistor, 10%	Jameco	.06
R2, R10	1k	Jameco (2 @ .06)	.12
R3, R17	10k	Jameco (2 @ .06)	.12
R4	150k	Jameco	.06
R5, R6	100	Jameco (2 @ .06)	.12
R7	33k	Jameco	.06
R8	8.2k	Jameco	.06
R9	6.8k	Jameco	.06
R11, R12, R13	4.7k	Jameco (3 @ .06)	.18
R15	15k	Jameco	.06
R22	47k	Jameco	.06
R23	100	Jameco	.06
R24, R25	390	Jameco (2 @ .06)	.12
R14	5k 10-turn pot, PLL frequency adjust	Jameco 43P	1.19
R16	5k 10-turn pot, meter null adjust	Jameco 43P	1.19
R21	20k 10-turn pot, meter calibrate adjust	Jameco 43P	1.19
R18	10k (see text)	Jameco	.06
R19	8.2k (see text)	Jameco	.06
R20	4.7k (see text)	Jameco	.06
T1	24-30-V-ac c-t transformer	Radio Shack	3.99
Xtal	14655.00-kHz crystal (parallel	Sentry Mfg.,	
	resonance, 32 pF)	Chickasha OK 73018,	
		Ref. 289590	8.00
Chassis	BUD AC-429		6.10
S1	SP-3T miniature rotary switch	Radio Shack #275-1386	1.19
S2	DPDT miniature toggle switch	Radio Shack #275-626	1.99
J1	BNC connector, chassis mount, female	Radio Shack #278-105	1.59
J2	1/8" miniature phone jack	Radio Shack #274-251	.45
M1 -	100-0-100-μA dc meter*	Radio Shack 0-50-µA	
		meter	8.95

^{*}Fair Radio lists several 0–50-μA or 0–100-μA movements. Meter-reversing switch arrangement is needed. Switch S1, Radio Shack 275-1386, can be used.

Build a Better Hamfest

These hints from 25 years of experience will help make your event a success.

After over a quarter of a century of hamfest attendance as a spectator, retail exhibitor, manufacturer, and hamfest committee member, I have been asked numerous times to put down a few thoughts as to what I and other exhibitors liked and disliked. I will comment mostly from the point of view of exhibitors, as they probably have the least input to a hamfest committee.

Every committee wants to do the very best job, and most put in lots of effort and time with the very best of intentions. I can remember several hamfests that really bent over backwards to give the exhibitors maximum exposure to the public. We could set up all day Friday, open the exhibits Friday night, 6:00 to 10:00 pm, open Saturday, 8:00 am to 6:00 pm, have a Saturday night party, and be open on Sunday from 9:00 am to 5:00 pm.

The committees in these instances really did mean well and had good intentions, but if an exhibitor has to fly in or drive many hours Friday to set up, the last thing he needs is to open the exhibit area Friday night. He is ready to collapse for awhile and get ready for Saturday and/or

Sunday. After all, he probably worked the last 5 days also. Saturday 9:00 am to 3:00 or maybe 4:00 pm is enough for one day of standing around trying to be alert and cheerful!

Several hamfests have a Saturday night cocktail party with a free bar for the first hour for the exhibitors only, then open it up for the rest of the attendees with a cash bar. This has worked quite well in most cases and is certainly a good way to show appreciation to the exhibitors. And best of all, key members of the committee can be there to get information as to what the exhibitors like and dislike about the hamfest and get suggestions of how to make next year's better.

Now here is something which could be very important: A few small exhibitors may have only one person in the booth and it is very difficult for them to take coffee or rest breaks. Some hamfests have local Boy or Girl Scouts or C.A.P. squadron members to help out. Such local community groups often are looking for things to do and would be happy to help man a booth and watch things for a few minutes - or go and get coffee, donuts, or a sandwich.

Some committees ar-

range to have coffee and donuts for the exhibitors and bring them to the booth or have it available in a central location; some even have a room where exhibitors can sit down and relax for a few minutes.

I certainly do not mean to imply that all or any committees should do all of the things mentioned here. They are things that I have observed over the years and are meant only as food for thought. And some of these ideas are more important than others. For example: It would be a very useful and desirable thing if all hamfest organizers provided some means for exhibitors to be reached in an emergency situation. A telephone situated in the display area or, at the very least, near the PA system would be one possibility. Another possibility would be a telephone located near the person who is running the radio talk-in operation. Perhaps both locations could be covered. In any case, there have been emergencies at almost all hamfests where exhibitors had to be reached quickly. Some thought should be given to this problem.

Hamfest Dates

There are times when it is difficult or impossible to coordinate your event with others on the same date. You could be locked into a date by the facilities that you use. Last year there were several hamfests that had the same dates as others that we wanted to attend as exhibitors. I am sure that situations like this will continue as it is very difficult to arrange no-conflict dates. It helps, however, if you get your date out and announced ASAP. Keep plugging this date in publications and on the air if it is a large affair that you want the big manufacturers and dealers to attend. Make sure that they know the date of the next one ASAP after the last one. Some commitments (such as ARRL national conventions) are made more than a year in advance by exhibitors.

Security is a major concern with many exhibitors, and rightly so since some have many tens of thousands of dollars worth of equipment on display. During setup times, I have observed many people walking around convention areas without benefit of any ID (committee, exhibitor, or general public). I think this is a real no-no, for two reasons. First, when you are trying to set up your area, the last thing you need is a distraction, especially by curious committee members or

other exhibitors who probably are not customers. They may mean well, but as I said before, an exhibitor may have left before the chickens got up that morning and perhaps drove or flew many hours before arriving for a weekend hamfest. He may also have worked the week before and maybe the last several weekends in the hamfest season.

Second, it seems that over the last few years the need for more and better security has increased drastically. I'm not sure why; maybe it's just the economy, or maybe, with our lack of ability to enforce our laws and prosecute shoplifters, more people are willing to take a chance. Anyway, could it be time to need a bill of sale on your person for your newlooking HT as you walk in and out of the exhibit area? Time for a bill of sale for any package, box, or equipment that you carry in and out of the exhibit area? I certainly hope not, but the Consumer Electronics Show and others have had to take this approach, with guards on the doors doing briefcase inspections, etc.

Last year I went to numerous hamfests that had equipment stolen right off displays during show hours. At the Cedar Rapids national ARRL convention last summer, a sharp-eyed and concerned attendee witnessed an HT slide off a display and into the wrong person's possession. He reported it to the exhibitor who immediately gave chase and ran the person right into the arms of a policeman. I don't know if there was a prosecution or not, but the name and call of the individual were known by a lot of exhibitors in very short order.

In your flyers or exhibitor packages, a map of your location with respect to the local airport, expressways, and major landmarks is cer-

tainly nice-along with approximate times and mileages from them. A list of local motels, hotels, and nice restaurants along with any 800 numbers and local numbers, rates, and specialty menus would make it easier for a stranger to make a choice to meet his needs or desires. Quite often, you can arrange a block of rooms, especially in a dead season, and you can really get a price break.

SAROC used to hold its convention the first week after New Year's Eve-the slowest weekend in Las Vegas-and got super room and exhibit-area rates. (Now CES has taken this time slot for the very same reasons.) So don't overlook the expensive convention areas if you can use them in their slow times; a little income for them is better than zero. But be careful of union-contract areas. The exhibit area may be inexpensive, but the electricians and dray people may turn out to be very expensive.

An absolute must for good rapport with the commercial exhibitors is a thankyou-for-coming letter sent no later than 30 days after the hamfest. It also gives you the excellent opportunity to include a questionnaire: How did you like the hamfest? What could stand improvement? What services or functions would you like to see added or dropped? Was there anything exceptionally good or bad? Did you like the location and facilities? The list can go on and on.

If you use a form letter that requires only a check mark () for yes or no and includes space for comments, you will get a better response. If you ask only for written comments, don't expect very many to answer you. Make it easy for the busy exhibitor to respond.

It is certainly appreciated when at least one person from the committee takes time and comes around



terfering signals in the 80-216 and 400-512 MHz VHF/UHF bands up to 40 dB. Size 4" x 2" x 3". Only '41.00 includes UPS shipping.

Guaranteed for one year; 15 day return policy.

CALL TODAY to place your order on Mastercard or Visa or send check or money order. No COD.

MONITORING TIMES, the most informative accurate periodical written exclusively for the serious listener to the spectrum. Equipment reports, frequency information and schedules for military, government, broadcasters, public safety, satellites, smugglers, pirates...everyone on the airwaves! 28-page tabloid newspaper. Only 19.50 per year. Write for free sample.

order and UPS ship-FAST and DEPENDABLE Your order processed

for the prompt

response to orders

(8 days total using

the mails money

within 24 hours from receipt.

GROVE ENTERPRISES, INC.

140 Dog Branch Road, Dept. D , Brasstown, NC 28902 Business Hours: 9-5 EST weekdays

CALL NOW

for your free catalog. 1-800-438-8155 (cont.US) 1-704-837-2216 (NC.HI,AK)

once or twice, minimum, to each booth and asks if there is anything needed or wanted to make it a better show. Such visits should not interrupt a sale or a serious conversation. Committee members should wear some kind of ID to let exhibitors know who they are. And they should try to talk with the boss, if possible; all such good efforts might be for naught if only the hired help is seen when the boss might have something he feels is important to chat about.

Make sure, in all correspondence to exhibitors, that there is a phone number, name, and address of a responsible person who can make commitments for the event or at least will follow up with a prompt response. If you have a large event, supply a committee list of chairpersons complete with phone numbers and addresses and their responsibilities.

Booth fees at some

events are negotiable, and at some they are not. Almost all hamfests need door prizes that have to come from someplace, and trading for them with booth space is probably one of the best ways to stretch a hamfest budget. I think that most dealers or manufacturers would rather trade merchandise than pay cash for a booth. There are bookkeeping problems on both sides sometimes in doing this, so play this one by ear to satisfy both sides.

In conclusion, I'd like to add that hamfests are fun for all concerned, and a little more attention to some of the details can turn a mediocre hamfest into a spectacular show satisfying to exhibitors, committee members, and hams alike. I hope that some of these ideas and comments will help your hamfest become the most successful and talked-about one this year and for years to come.

Caveman Radio

With underground inductive transmission, 300 feet is almost DX.


Frank S. Reid W9MKV PO Box 5283 Bloomington IN 47402 Magnetic-induction equipment which transmits signals through the ground is a valuable aid to cave-mapping and under-

ground rescue. Even more useful than its communication ability is its ability to accurately find a spot on the surface above an underground transmitter. It can also determine depth within a few percent, using field-geometry measurements.

It's legal! Magnetic induction is not real radio—it's simply very-loosely-coupled transformer action. The FCC does not define equipment operating below 10 kHz as "radio frequency devices."

How It Works

Inductive communication is a very old technique (see "Who Really Invented Radio?-The Twisted Tale of Nathan B. Stubblefield," 73, December, 1980). When amateur radio was banned during World War II, many hams communicated by "ground wave," i.e., magnetic induction and earth-current. ("Earth-current" is transmission of audio-frequency signals through the ground between pairs of widely-spaced ground rods connected to amplifiers.) Ranges greater than one mile were claimed.

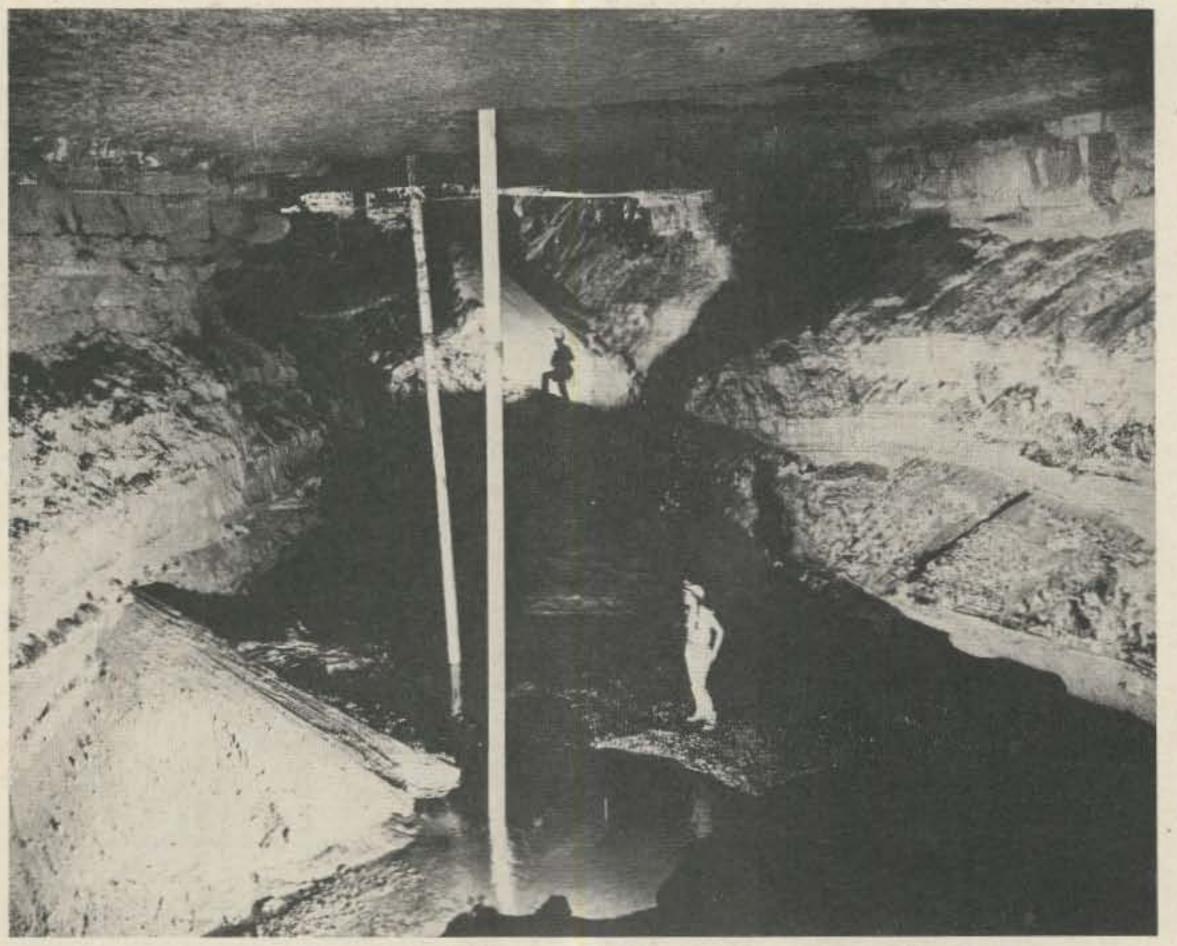

120-foot-deep wells near Park City, Kentucky, penetrated cave within two feet of radio targets. Drill drift caused error. Pipes contain hydrological instrumentation. (Photo by Samuel S. Frushour)

Skin effect, which causes rf currents to travel only on the surfaces of conductors, normally prevents radio waves from penetrating ground or water more than a few feet. The depth of the "skin" increases as frequency is lowered; thus, submarines can receive transmissions from very powerful VLF stations. Experimenters have reported successful cave-to-surface communications on 160 meters. Others report positive but unpredictable results on higher frequencies.

Audio-frequency magnetic fields penetrate most geologic structures easily. There are methods for locating ore bodies, using magnetic-induction equipment as a sort of giant metal-detector (see QST, June, 1928).

Inductive communication is inherently short-range because magnetic dipole field strength decreases as the cube of the distance from the source, unlike radio waves which obey an inverse-square law. Conductive overburden will absorb the signal, but the inversecube attenuation is so predominant that absorption is rarely noticeable. Generating true radio (electromagnetic) waves at audio frequencies would require enormous antennas.

E. R. Roeschlein suggested using the directional properties of magnetic fields to map caves in an article in Electronics, September 23, 1960. Cavers, notably William Mixon and Richard Blenz, refined the equipment and developed depthmeasuring techniques which are independent of signal strength (several articles appear in Speleo Digest, 1964).

Equipment

It's easy to get 300-foot range with very simple equipment. Longer ranges are more challenging.

A transmitter is just an audio oscillator driving an amplifier which is driving a coil. Impedance matching is important for maximum coil current. Perhaps the most important part of the transmitter is the keyer - a circuit to make it go "beep... beep... beep." In addition to the advantage of saving battery power, a pulsed signal is much easier for the receiver operator to distinguish against a background of interference than is a steady tone.

A simple resonant coil connected to an audio am-

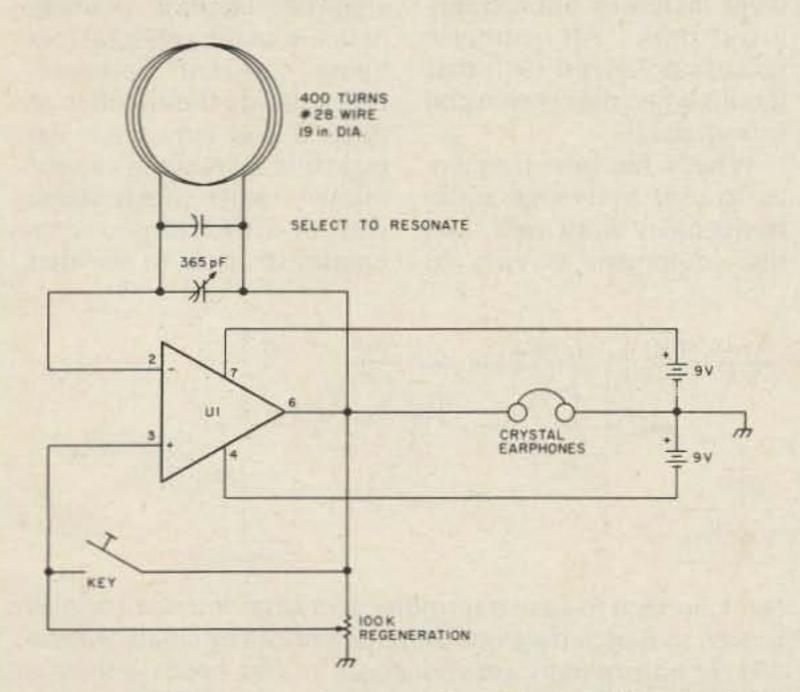


Fig. 1. One-chip transceiver uses Q-multiplier effect for high sensitivity and selectivity. Antenna needs no electrostatic shield. U1 is any 741-type op amp.



WB9TLH operates underground transmitter on 3500-Hz CW, using microswitch for telegraph key.

plifier will work for a receiver. Use crystal earphones, because magnetic phones will cause feedback.

The circuit of Fig. 1 is a Q-multiplier. The resonant circuit is in negative feedback instead of being simply connected to the amplifier's input. The Q (regeneration) control taps some of the output and feeds it back to the noninverting (+) input.

The amplifier forms a negative resistance which cancels the resistance of the coil. As the Q control is advanced, sensitivity and selectivity get higher and higher until the circuit goes into oscillation (infinite Q). Since it will oscillate, the circuit can also be used as a very-low-powered transmitter.

A 60-Hz notch filter will not get rid of power-line in-

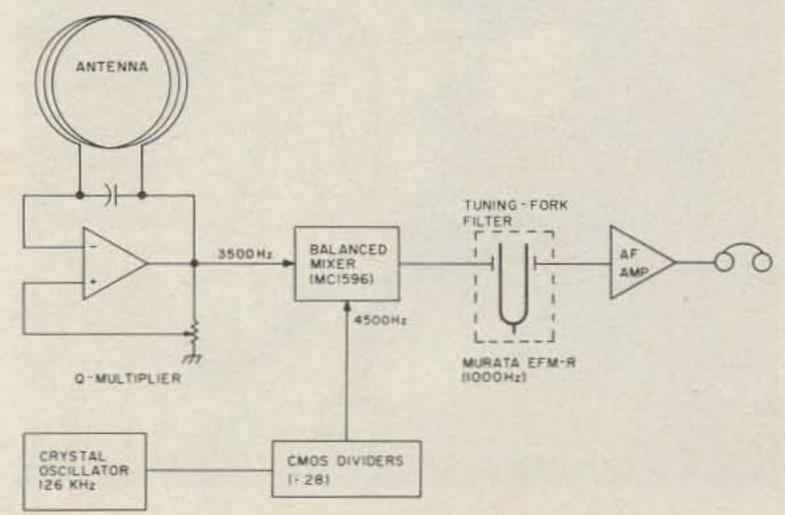


Fig. 2. Receiver with frequency conversion allows very high gain without feedback problems.

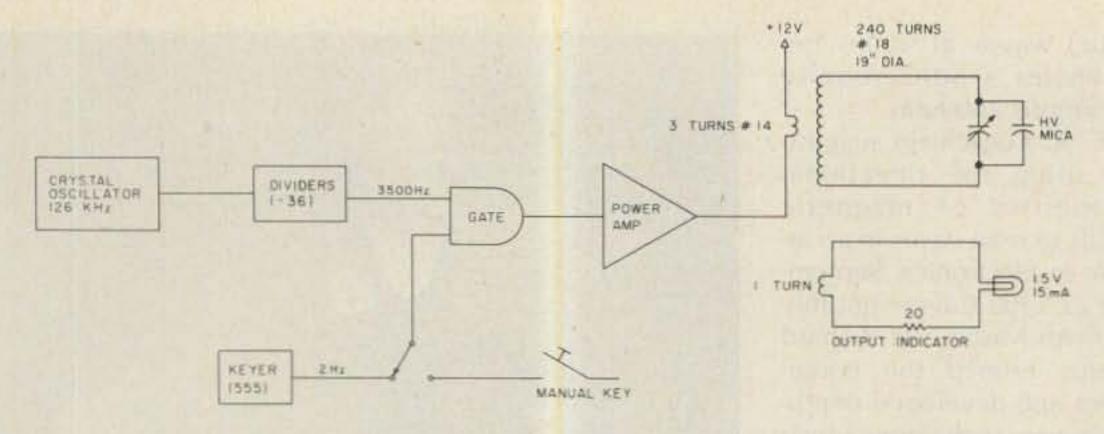


Fig. 3. A cave-radio transmitter. Precise frequency control is necessary if receiver uses verynarrow-bandwidth filters.

terference, which is not just 60 Hz but many harmonics. Don't use active filters indiscriminately. Very strong interference can intermodulate with the desired signal in an active filter, creating even worse interference.

Even with crystal earphones, receiver gain cannot be increased indefinitely. After a certain point, no amount of shielding and decoupling will prevent feedback. You can keep the antenna far from the amplifier, but then it's not portable. A balanced mixer and local oscillator can convert the input frequency to some other frequency, which can then be filtered and greatly amplified without feedback problems. Fig. 2 is a block diagram of one such receiver.

Interference

Power lines are the major source of interference, even in isolated areas. Harmonics of 60 Hz extend well into the ultrasonic frequencies. Powly directional and can be partially nulled out by the receiving antenna. To minimize interference, choose an operating frequency in between a pair of power-line harmonics and use a receiving filter narrow enough to reject the adjacent signals. Resonant-reed or tuningfork filters of the type used in radio pagers can provide the necessary selectivity. Such extremely narrow bandwidths require precise frequency control and very slow CW speeds. Atmospheric noise from distant thunderstorms can

er-line interference is usual-

Atmospheric noise from distant thunderstorms can be a problem in summer. Daytime atmospheric noise is minimal around 3.5 kHz (National Speleological Society Bulletin, vol. 32, no. 1, January, 1970). The noise level increases appreciably after dark. Atmospheric noise is polarized such that it nulls when the receive coil is horizontal.

What's the best frequency to use? Mid-range audio frequencies work well, and the equipment is easy to

build. I use 3500 Hz. 3276.8 Hz would be a good frequency because it is easy to generate from a 32.768-kHz wristwatch crystal. 3276.8 Hz falls in between harmonics of both 50- and 60-Hz power lines, and so could be used in any country. At higher frequencies, ground absorption increases and audio amplifiers become less efficient. Some experimenters have tried SSB on ultrasonic frequencies, but have found no advantages to justify the complexity of the equipment. Below 2 kHz, atmospheric noise and power-line harmonics are very strong. Subaudible frequencies below 60 Hz have been used, with very complex receiving equipment.

The OMEGA navigation system transmits very strong signals on several frequencies between 10 and 14 kHz. OMEGA stations make good beacons for testing receivers. Each station transmits for one second in a sequence that repeats every ten seconds.

Antennas

For best performance, maximize the magnetic moment of the coils. Magnetic moment is Ampere-turns multiplied by the coil's area.

Doubling the range of an inductive system requires an eightfold increase in magnetic moment, other factors being constant. Self-resonance limits the number of turns a coil may have. An eightfold increase in current implies either much larger wire or a 64-fold power increase. It's easy to see that



Surface location and depth of transmitter are found by nullseeking with directional antenna and by measuring shape of magnetic field.

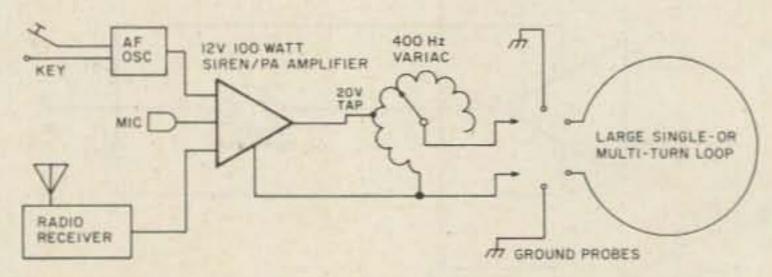


Fig. 4. Surface-to-cave transmitter uses large antenna and high power, so that underground equipment can be small. Surplus 400-Hz transformers are very cheap or free because there is little demand for them. (Caution—possible shock hazard between chassis and earth grounds if amplifier has no internal output transformer.)

IRON POWDER and FERRITE PRODUCTS

AMIDON.

Fast, Reliable Service Since 1963

Small Orders Welcome

Free 'Tech-Data' Flyer

Toroidal Cores, Shielding Beads, Shielded Coil Forms Ferrite Rods, Pot Cores, Baluns, Etc.

12033 OTSEGO STREET, NORTH HOLLYWOOD, CALIFORNIA 91607

2 METER RADIOS

AZDEN PCS-300 FM HANDHELD, 3W, 8 MEM259.95
AZDEN PCS-4000 FM MOBILE, 25W, 16 MEM 265.95
KDK-2030 FM MOBILE, 25W. 11 MEMORY259.95
SANTEC ST-144 FM HANDHELD, 3.5W, 10 MEM 262.95
TEMPO S-15 FM HANDHELD, 5W, 3 MEM242, 95
TEMPO S-15T S-15 WITH 16 KEY TONE PAD 265.95
TENTEC 2591 FM HANDHELD, 2.5W, 10 MEM 262.95

TEMPO S-1 FM HANDHELD, 1.5W
TEMPO S-1T S-1 WITH 12 KEY TONE PAD 199.95
PRICE ON S-1 & S-1T INCLUDE 5/8 WAVE SUPER
STICK II & RUBBER DUCK WHILE SUPPLY LASTS

2 METER HANDHELD **ACCESSORIES**

HT-BAT SPARE BATTERY FOR PCS-30024	. 95
HT-ESM SPEAKER MIKE FOR PCS-30026	
HT-LC LEATHER CASE FOR PCS-30026	
ST 500B3 SPARE BATTERY FOR ST-14422	
5M-3 SPEAKER MIKE FOR ST-14431	. 95
ST-LC LEATHER CASE FOR ST-14431	
ST-4QC AC QUICK CHARGER FOR ST-14461	. 95
ACH-15 AC QUICK CHARGER FOR S-1552	
CC-15 LEATHER CASE FOR S-1521	. 95
BP-15 SPARE BATTERY FOR S-1525	. 95
HM-15 SPEAKER MIKE FOR S-1530	. 95
OTHER ACCESSORIES AVAILABLE PLEASE CALL	

2 METER BASE ANTENNAS
BUTTERNUT 2MCV 5/8 WAVE TROMBONE29.95
BUTTERNUT 2MCV-5 5/8 SUPER TROMBONE34.50
CUSHCRAFT ARX2B RINGO RANGER II34.00
CUSHCRAFT A144-11 11 ELEMENT BEAM44.25
CUSHCRAFT A147-11 11 ELEMENT BEAM44.25
CUSHCRAFT A144-20T 20 ELEMENT TWIST67.95
CUSHCRAFT A147-20T 20 ELEMENT TWIST81.95
CUSHCRAFT 214B & 214FB 14 ELEMENT BEAM74.95
CUSHCRAFT 32-19 19 ELEMENT BEAM

2 METER MOBILE ANTENNAS

AVANTI	AP151.36 1/2 WAVE "ON GLASS"29.5
CUSHCRAFT	AMS-147 MAGNET MOUNT27.5
CUSHCRAFT	ATS-147 TRUNK MOUNT27.9
HUSTLER	SF-2 5/8 WAVE 3DB GAIN10.5
HUSTLER	CG-144 5/8 WAVE 5.2DB GAIN27.9
VALOR	CX-144 5/8 WAVE 3DB GAIN9.9

2 METER AMPLIFIERS

MIRAGE	B23 FM/SSB 2W IN 30W DUT75.0
MIRAGE	B10B FM/SSB 10W IN BOW DUT151.0
MIRAGE	B1016 FM/SSB 10W IN 160W DUT 235.0
MIRAGE	B3016 FM/SSB 30W IN 160W DUT 201.0
VJ PROD.	90L-PA FM/SSB 10W IN 90W DUT 128.9
VJ PROD.	160L-PA FM/SSB 20W IN 160W DUT279.9
TEMPO	S-30 FM 2W IN 30W DUT79.9
T. 200 T. 100	W. W. T. S. W. W. S.

HF/10M/6M RADIOS

THE PROPERTY OF THE PARTY OF TH
TENTEC ARGOSY 100W, SSB/CW, 10-BOM510.0
TENTEC CORSAIR 200W, SSB/CW, 10-160M999.0
TENTEC DMNI-A 200W, SSB/CW, 10-160M799.9
AZDEN PCS-4800 10M, FM MDB., 10W, 16 MEM., 269.9
AZDEN PCS-4500 6M, FM MOB., 10W, 16 MEM 279.9
KENWOOD TS-600 6M ALL MODE W/VOX (USED) .350.0

HE ANTENNAS

LIL WIN	CIVINAS
BUTTERNUT	HF6V 10-BOM & 30M VERTICAL106.75
BUTTERNUT	HF6VX AS ABOVE IN SMALL BOX 121.75
	AV-3 10-20M TRAP VERTICAL47.95
	AV-4 10-40M TRAP VERTICAL88.95
	AV-5 10-BOM TRAP VERTICAL94.95
	10-4CD 10M 4 ELEMENT BEAM101.95
CUSHCRAFT	15-3CD 15M 3 ELEMENT BEAM108.95

(continued)

CUSHCRAFT 20-3CD 20M 3 ELEMENT BEAM183.95
CUSHCRAFT 20-4CD 20M 4 ELEMENT BEAM257.95
CUSHCRAFT 40-2CD 40M 2 ELEMENT BEAM271.95
MINI-PROD HQ-1 6M-20M MINI QUAD129.50
MINI-PROD B-24 6M-20M 2 ELEMENT BEAM95.50
MINI-PROD C-4 6M-20M VERTICAL54.50
WILSON (MACO) SY-33 10-20M 3 ELE. BEAM 193.95
WILSON (MACD) SY-36 10-20M 6 ELE. BEAM 258.95
WILSON (MACO) 33-6MK 40M ADD ON KIT67.95
WILSON (MACO) WV-1A 10-40M TRAP VERTICAL.68.95
WILSON (MACO) GR-1 GROUND RADIAL KIT26.95
507050 0 0451 50

HD-73	ALLIANCE HEAVY DUTY ROTOR99.00
U-110	ALLIANCE LIGHT DUTY ROTOR 45.00
HDR-300	HYGAIN SUPER HEAVY DUTY ROTOR, 400.00
8610	B CONDUCTOR ROTOR CABLE. PER FT. 0.17
9091	MINI RGB (RGBX) COAXPER FT.0.16
9095	RG-BU SUPERFLEX CDAXPER FT.0.28
4063	RG-213 MIL-SPEC CDAXPER FT.0.28

ANTENNA SWITCHES & SWR/WATT METERS

MILLER	CS-201 2 POSITION COAX SWITCH 19.95
MILLER	CS-401 4 POSITION COAX SWITCH61.95
MILLER	CN-520 1.8-60MHZ SWR/WATT58.95
MILLER	CN-620B 1.8-150MHZ SWR/WATT102.95
MILLER	CN-720B 1.8-150MHZ SWR/WATT144.95
MIRAGE	MP-1 1.8-30MHZ SWR/WATT99.95
MIRAGE	MP-2 50-200MHZ SWR/WATT99.95
WELZ	SP-10X 1.8-150MHZ POCKET SIZE34.95
WELZ	SP-45X 140-470MHZ SWR/WATT79.95

POWER SUPPLIES BY MACO

		, _,,		400000000000000000000000000000000000000	
2006	BAMP	SURGE, 6AMP	INT.	4AMP	CONT 46.00
		SURGE, 10AMP			
		SURGE, 20AMP			
2030	36AMP	SURGE, 30AMP	INT., 1	BAMP	CONT. 100.00

ANTENNA TUNERS

MFJ-900 ECONO TUNER 1.8-30MHZ 200WATTS39.	95
MFJ-901 AS ABOVE WITH 4:1 BALUN49.	95
MFJ-941C ANTENNA TUNER/SWR METER 1:48AL.75.	95
MFJ-962 1.5KW, ANT. SWITCH, METER, BALUN179.	95
MFJ-982 3KW, ANT. SWITCH, METER, BALUN156.	95
MILLER CNAIGOIA AUTOMATIC TUNER 200W294.	95

COMPUTER ACCESSORIES

×	KANTRONICS	HAMSOFT	FOR APP	LE		. 24.	95
8	KANTRONICS	HAMSOFT I	FOR ATA	RI		.39.	95
ĕ	KANTRONICS	HAMSOFT	FOR VIC	-20		.39.	95
	KANTRONICS	HAMTEXT I	FOR COM	MODORE &	54	.82.	95
h	KANTRONICS	HAMTEXT	FOR VIC	-20		.82.	95
ł	KANTRONICS						
ħ	KANTRONICS	MINI-TER	MINAL C	W/RTTY/	ASCII.	269.	95
1	MFJ-1200 C	ONLY CO	MP. INT	ERFACE		.59.	95
	MFJ-1224 C	W/RTTY/AS	CII COM	P. INTER	REACE.	.88.	95

CLOSEOUTS

•	
5	PRICES GOOD WHILE SUPPLY LASTS
5	HY-BAIN TH7DXS 10-20M 7 ELEMENT BEAM 335.00
	HY-BAIN TH3JRS 10-20M 3 ELEMENT BEAM 140.00
0	HY-GAIN HQ-2S 10-20M QUAD234.00
	HY-GAIN 66-BS 6M 6 ELEMENT BEAM90.00
	HY-GAIN 5DBQ 10-BOM TRAP DOUBLET87.00
	HY-BAIN 153BA 15M 3 ELEMENT BEAM66.00
3	HY-GAIN 18V 10-80M VERTICAL21.00
3	HY-GAIN 25B 2M 5 ELEMENT BEAM18.00
	HY-GAIN 288 2M B ELEMENT BEAM24.00
	HY-GAIN 2148 2M 14 ELEMENT BEAM28.00
3	HY-GAIN HB-144 2M MAGNET MOUNT12.00
9	INNERSPACE 20 AMP POWER SUPPLY
3	INNERSPACE ZO HAP HETERED FOWER SUPPLY. 121. 00

Amateur)

COD Available

Hours: 8:30 a.m. to 5:00 p.m. Monday thru Friday 9:00 a.m. to 2:00 p.m. Saturday - CST Prices subject to change without notice.

CALL FRANK WD5GZU OR JOE KA5ROQ FOR QUOTES ON OTHER RELATED PRODUCTS FOB ORIGIN.

Amateur Equipment, Accessories & Antennas. **Export Anywhere**



VISA

2317 Vance Jackson Rd. San Antonio TX 78213

(512) 733-0334

(Toll free number 800-531-5405)



has more gain, less windload, and more mechanical integrity than other 2 meter an-

tennas. You'll find F.M. simplex or repeater operation more satisfying with this amazing antenna.

5.5 d Bd Gain 7.0 dB Ref. 1/4Z Whip Complete Ham Band

Coverage Low Angle Radiation DC Ground For Lightning Protection Stainless Steel

Hardware Mounts Easily With Other Antennas Slim Profile Design Easy to Assemble 6063-T832 Aluminum

Tubina Delivers The Performance You Expect Adjustable For Marine Commercial, Public

Vinyl Connector Boot ARX-220B 220-225MHz ARX-450B 435-450MHz





YOUR DEALER

R & L ELECTRIC

575 MAIN STREET HAMILTON, OH 45013 TEL. 1-513-868-6399

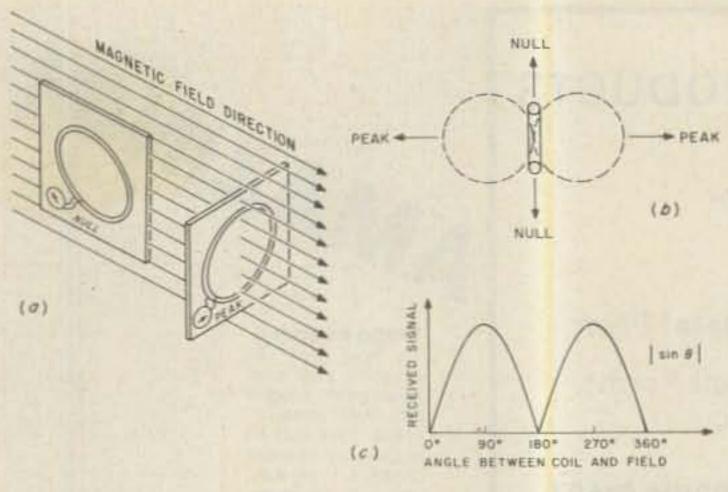


Fig. 5. (a) Received signal disappears when coil is parallel to magnetic field. (b) Note that magnetic-induction receiver coil's sensitivity pattern has null directions in the plane of the coil, unlike radio loop antennas. (c) Nulls are much sharper than peaks, but with very weak signals you may have to seek peaks instead of nulls.

the brute-force approach soon reaches limitations.

For a given length of wire, the optimum antenna is a single huge circular turn. Very large loops are OK for fixed locations, but coils for direction-finding must be rigid, flat, and portable. Transmitting coils must be small enough to fit through tight cave passages. In any case, the easiest route to long range is with coils of the largest manageable diameter. Build a transmitter of a few Watts, carefully match it to the coil, and concentrate the rest of your effort on a good receiver.

should perform well if properly designed. Ferrite cores can introduce problems of temperature instability, microphonics, and magnetic saturation. Doug DeMaw's recent book, Ferromagnetic-Core Design and Applications Handbook, published by Prentice-Hall, is an excellent reference.

Nathan B. Stubblefield may have discovered the interesting interaction between the magnetic-induction and earth-current modes of communication: Current injected into the ground between a pair of widely-spaced rods flows around a large underground area, creating a large magnetic moment. An inductive

receiver will detect the signal. Likewise, a pair of ground probes can detect voltage induced by a distant current-carrying coil. Some cave-radio experimenters have built equipment which operates in either mode, allowing greater flexibility in varying conditions of ground conductivity.



Receiving antenna has inclinometer made from vernier radio dial and spirit-level for measuring vertical angles.

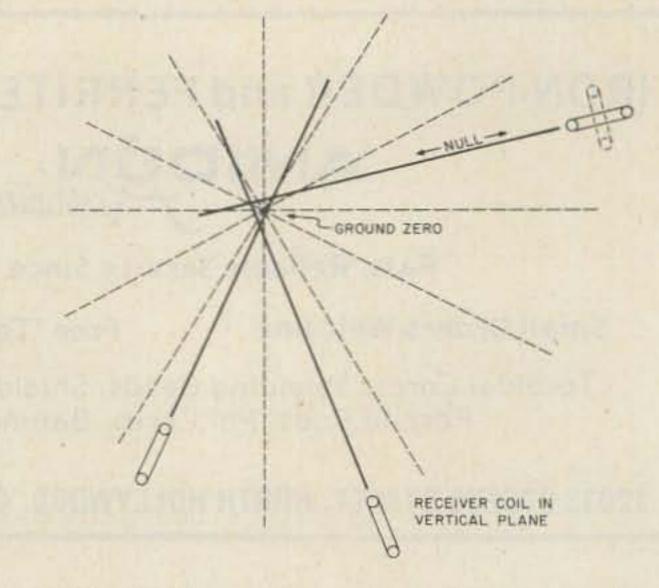


Fig. 6. Finding the approximate surface point above the transmitter (plan view).

Voice Operation

My own equipment was designed primarily for direction-finding and minimum weight. It can transmit from cave to surface by CW, but it does not transceive. Two-way communication is not essential for surveying operations, but it can be very useful. (People who don't know Morse code can usual-

ly send it intelligibly if provided with a code list and a few minutes of instruction on lengths of dots, dashes, spaces, letter and word spacing, and abbreviations.)

For a "downlink" I use a 12-volt-operated, 100-Watt police siren/PA amplifier driving either a large loop of wire lying on the surface or a pair of ground rods. A surplus 400-Hz variable autotransformer matches the amplifier to different loads. The underground voice receiver has a ferrite-core coil connected to an audio amplifier through a highpass LC filter which cuts off at 600 Hz, with 70 dB of rejection below 300 Hz. The filter rejects the strongest power-line harmonics. A band of voice energy called the first formant is lost, resulting in loss of the qualities that distinguish individuals' voices, but intelligibility remains. The female voice works best here.

Magnetic Direction-Finding

Someone must take the transmitter into the cave to the point of interest and turn it on at an appointed time. The transmit coil must be horizontal and very accurately level.

Received signal strength depends on how much magnetic flux passes through the coil. With the plane of the coil parallel to the field, no

WACOM DUPLEXERS

Our Exclusive Bandpass-Reject Duplexers With Our Patented



provides superior performance, especially at close frequency separation.

Models available for all commercial and ham bands within the frequency range of 40 to 960 MHz.

TELEPHONE 817/848-4435



P.O. BOX 7127 • WACO, TEXAS 76710 • 817/848-4435

TS830/TS930S IMPROVED!

Yes, spectacularly! By simply adding a Matched Pair of top-quality Fox Tango Filters. Here are a few quotes from enthusiastic users:

- ... makes a new rig out of my old TS830S ...
- ... VBT now works the way I dreamed it should ...
- ... Spectacular improvement in SSB selectivity
- Completely eliminates my need for CW filters... ... Simple installation ... excellent instructions ...
- ... Switched filters to new 930S when I traded my old

830 ... same solid improvement! ...

The 2.1KHz bandwidth Fox Tango SSB filters are notably superior to both original 2.7KHz BW units but especially the modest ceramic second IF; our substitutes are both 8-pole discrete-crystal construction. Compare the test results-Fox Tango Filters vs. Kenwood's:

On SSB with VBT Off-RX BW: 2.0 vs 2.4: Shape Factor: 1.2 vs 1.34; 80dB BW: 2.48 vs 3.41; Ultimate Rejection:

On CW with VBT set for 300Hz BW-Shape Factor: 2.9 vs 3.33; Insertion Loss: 1dB vs 10dB! Chances are you won't need them but a new 400Hz CW pair is now available for those who insist on the very best CW reception.

COMPLETE KITS Only \$170 each FTK830 or FTK930 (2.1KHz BW for SSB/CW)

FTK830 or FTK930 (400Hz BW for CW Only) Each includes a Matched Pair of Fox Tango Filters, all

needed cables, parts, detailed instructions. Specify rig and bandwidth desired when ordering. Shipping: \$3 (COD) +\$1, Air +\$2, Overseas +\$5). Florida residents: add 5% Sales Tax. ONE YEAR WARRANTY



GO FOX-TANGO-TO BE SURE! Order by Mail or Telephone.


AUTHORIZED EUROPEAN AGENTS Scandinavia, MICROTEC, Makedien 25. 3200, Sandefjord, NORWAY Other INGOIMPEX, Postfach 24 49. D-8070, Ingolstadt, W. GERMANY

FOX TANGO CORPORATION Box 15944S, W. Palm Beach FL 33416 (305) 683-9587

CALL LONG DISTANCE ON 2 METERS

Only 10 watts drive will deliver 75 watts of RF power on 2M SSB, FM, or CW. It is biased Class AB for linear operation. The

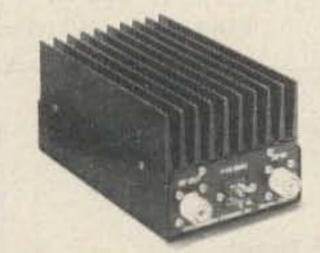current drain is 8-9 amps at 13.6 Vdc. It comes in a well constructed, rugged case with an oversized heat sink to keep it cool. It has a sensitive C.O.R. circuitry, reliable SO-239 RF connectors, and an amplifier IN/OUT switch. The maximum power input is 15 watts.



Our products are backed by prompt factory service and technical assistance. To become familiar with our other fine pro-

ducts in the amateur radio market, call or write for our free product and small parts catalog.

Model 875 Kit \$109.95 Wired & Tested \$129.95



Communication Concepts Inc.

2648 North Aragon Ave. + Dayton, Ohio 45420 + (513) 296-1411 14




DIRECTION FINDING?

- * Doppler Direction Finding
- * No Receiver Mods
- * Mobile or Fixed
- * Kits or Assembled Units
- ★ 135-165 MHz Standard Range



- * Circular LED Display
- * Optional Digital Display
- * Optional Serial Interface
- * 12 VDC Operation
- * 90 Day Warranty

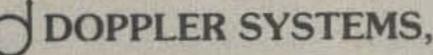New Technology (patent pending) converts any VHF FM receiver into an advanced Doppler Direction Finder. Simply plug into receiver's antenna and external speaker jacks. Use any four omnidirectional antennas. Low noise, high sensitivity for weak signal detection. Kits from \$270. Assembled units and antennas also available. Call or write for full details and prices.



5540 E. Charter Oak, Scottsdale, AZ 85254

(602) 998-1151

¥ 425

HI-Q BALUN

- · For dipoles yagis inverted vees & doublets
- · Replaces center insulator
- · Puts power in antenna
- Broadbanded 3-40 MHz · Small lightweight and
- weatherproof
- 1 1 Impedance ratio
- For full legal power and more
- Helps eliminate TVI
- With SO 239 connector

only \$13.95

HI-Q ANTENNA CENTER INSULATOR



Small rugged lightweight weatherproof

HI-Q

Balun

Replaces center insulator Handles full legal power and more

\$6.95 With SO 239 connector

HI-Q ANTENNA **END INSULATORS**



Rugged, lightweight, injection molded of top quality material, with high dielectric qualities and excellent weatherability. End insulators are constructed in a spiral unending fashion to permit winding of loading coils or partial winding for tuned traps.

May be used for

· Guy wire strain insulators End or center insulators for

 Construction of antenna load ing coils or multiband traps

		PRICE	WITH	WITH HI-Q
MODEL	BANDS LENGTH		THE PERSON NAMED IN COLUMN TWO IS NOT THE PERSON NAMED IN COLUMN TWO IS NAMED IN COLUMN TW	NSULATOR
Dipoles				
D-80	80,75	130	\$31.95	\$27.95
D-40	40,15	66	28.95	24.95
D-20	20	33	27.95	23.95
D-15	15	22	26.95	22.95
D-10	10	16	25.95	21.95
Shortened d	ipoles			
SD-80	80,75	90	35.95	31.95
SD-40	40	45	32.95	28.95
Parallel dipo	des			
PD-8010	80,40,20,10,15	130	43.95	39.95
PD-4010	40,20,10,15	66	37.95	33.95
PD-8040	80,40,15	130	39.95	35.95
PD-4020	40,20,15	66	33.95	29.95
Dipole short	eners - only same as in	cluded in	SD model	

S-80 80,75 \$11.95 pr \$10.95 pr S-40

All antennas are complete with a HI-Q Balun or HI-Q Antenna Center insulator, No. 14 antenna wire, ceramic insulators, 100 nylon antenna support rope (SD models only 50) rated for full legal power. Antennas may be used as an inverted V and may also be used by MARS or SWLs.

Antenna accessories—available with antenna orders Nylon guy rope 450# test 100 feet Ceramic (Dogbone Type) antenna insulators \$1.50 pr SO-239 coax connectors

All prices are postpaid USA 48 Available at your favorite dealer or order direct from

Dealer Inquiries Invited Van Gorden Engineering

BOX 21305 B, SOUTH EUCLID, OHIO 44121

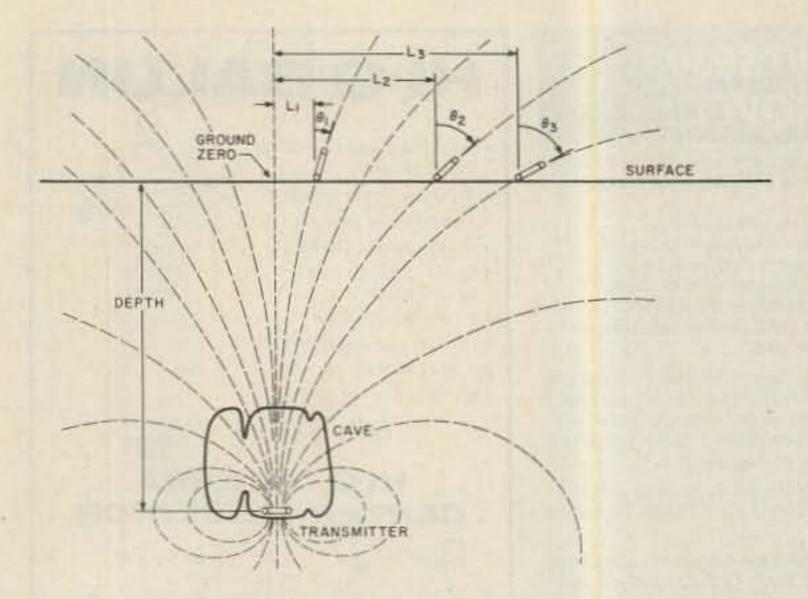


Fig. 7. Ground zero is pinpointed by finding the spot where the field is vertical. Then, distances (L) and vertical angles (⊖) are used in calculating depth of transmitter.

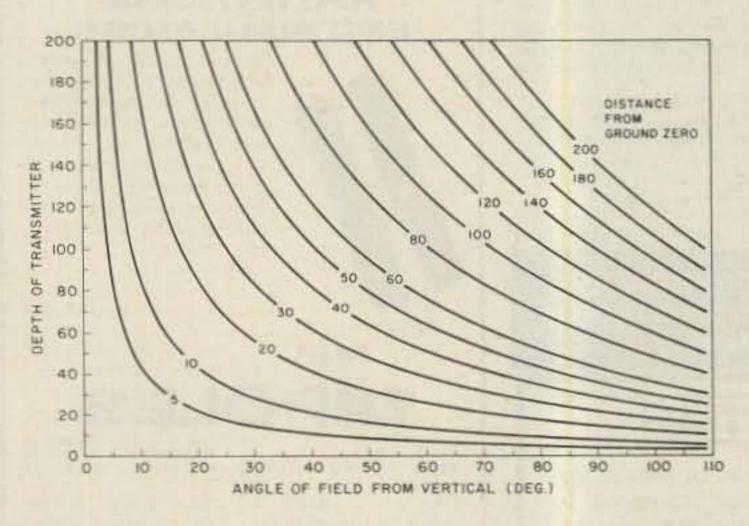


Fig. 8. Cave Radio Depth Chart (after W. Mixon). Each curve is depth vs. field angle for a different horizontal distance from ground zero. Use any distance units: feet, meters, etc. Example: For distance 50' and angle 40°, depth is 102'. Thanks to Robert F. Blakely for providing this HP-85 computer plot.

flux passes through the center and the signal disappears in a very sharp null (Fig. 5).

Viewed from above, the field of the transmit coil looks like straight lines radiating from the center (Fig. 6). The receiver operator can home in on the area of the underground transmitter by a technique similar to that of normal hidden-transmitter hunting: Hold the coil in a vertical plane and rotate to find the null direction, then "triangulate."

Once the approximate site has been found by horizontal nulls, the location can be refined to within a few inches, using vertical nulls. Fig. 7 shows a side

view of the curved shape of the field. Point the coil toward maximum signal, then tilt it back and forth to find a null which indicates the direction of the field coming up out of the ground. Move in the direction of decreasing vertical angle to find a place where the null direction is straight down. Turn 90° horizontally and repeat the procedure, getting closer to the center of the field each time. "Ground zero" is the point where the vertical null is straight down, no matter what horizontal direction you point the coil's axis. An experienced operator can usually find ground zero in about ten minutes and de-

CALCULATOR METHOD

Finding depth by calculator is fast, easy, eliminates plotting errors, and provides wider range than the graph. (The graph still has the advantages of low cost and easier error detection.) A programmable pocket calculator with nonvolatile memory, such as the Hewlett-Packard HP-29C, is ideal for calculating depth while on location.

HP-29C Program for Depth of Cave Radio

Equation solved for depth:

$$D = L(3 + \sqrt{9 + 8 \tan^2 \Theta})$$

$$4 \tan \Theta$$

0°<0<90°

01 15	5 13 00	g LBL 0
02	15 34	g DEG
03	14 54	f TAN
04	31	ENTER
05	15 63	g x²
06	08	8
07	61	X
08	09	9
09	51	+
10	14 63	f√x
11	03	3
12	51	+
13	21	x≷y
14	04	4
15	61	X
16	71	+
17	61	X
18	15 12	g RTN

To use: Key in L. ENTER Key in Θ (in degrees). GSB 0

Example: L = 50', $\Theta = 45^{\circ}$: Depth = 89.04'

termine depth in another ten.

Finding Depth

The receiver antenna should be mounted on a rigid, flat board or framework and must be equipped with some type of inclinometer, such as a carpenter's protractor. Estimate vertical angles to the nearest 1/10 degree when taking data for depth.

Mark ground zero with a stake or rock. Stretch a measuring tape horizontally away from ground zero and measure the vertical angle of the field at several different distances away. Use the distance-and-angle data in the calculator formula above or plot the data on the fami-

ly of curves in Fig. 8. Average the results of several pairs of data. The depths should be consistent, falling near the average value and randomly either side of the average. An increasing or decreasing trend indicates an error in ground zero location or an unlevel transmit coil. Most of the error can be recovered by taking another set of data in the opposite direction away from ground zero and averaging the results of both sets.

Note that the slope of the depth function (Fig. 8) is very steep for small angles, i.e., a small error in measuring the angle will produce a large depth error. For best results, use only angles between 12° and 75°. (At vertical angles

near and greater than 90°, the null is less distinct and, of course, the signal is weaker at greater distances from ground zero.)

The depth chart (Fig. 8) derives from the formula: $tan \Theta = 3LD/(2D^2 - L^2),$ where: 0 = angle of field (measured from vertical =0°), L = horizontal distance from ground zero, and D = depth. The formula is an approximation which assumes that the transmit coil is very small relative to depth.

Note that the closed curves of the magnetic field are ellipses, not circles. Simple triangulation cannot be used to determine depth (D = L when $\Theta = 71.57^{\circ}$, not 90°). An 8 1/2" × 11" working copy of the depth chart is available from the author for an SASE.

The Future

Extending the range of underground communication makes a fine project for


hams, especially VLF enthusiasts. Experiments on 1750 meters should be especially interesting.

Correlation, signal-averaging, and other sophisticated techniques for weak-signal recovery are becoming increasingly attractive to amateurs with new developments in integrated circuits. Very-long-range cave radio could, of course, be accomplished by interfacing shortrange cave-to-surface links with conventional amateur radio equipment. Future technology may allow communication through the entire Earth on modulated beams of neutrinos!

The National Speleological Society is an organization promoting safety and conservation in the sport and science of cave exploring. Their address is Cave Avenue. Huntsville, Alabama 35810.

T.V.I. problems?

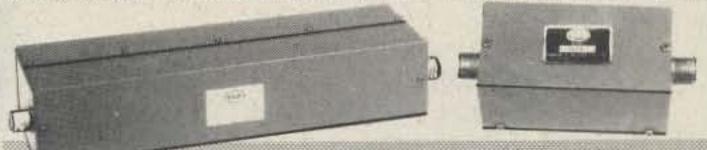Low pass T.V.I. filters from Barker & Williamson



427 425

424 423

Model	Power (Watts)	Cut Off Frequency	Frequency of Maximum Attenuation	Minimum Attenuation	Frequency Range	Price
425	1000	34 MHz	52 MHz	70 db	1.8 - 30 MHz	\$29.50"
424	100	44 MHz	57 MHz .	60 db	1.8 - 30 MHz	\$22.50
427	1000	55 MHz	63 MHz	70 db	6 meter	\$36.00*
423	100	55 MHz	63 MHz	50 db	6 meter	\$25.00°

All above to match 50 ohm transmitters and antennas.

*Add \$2 shipping and handling

ALL OUR PRODUCTS MADE IN USA

Quality Communication Products Since 1932 At your Distributors write or call

10 Canal Street, Bristol PA 19007 (215) 788-5581




TRIONYX INC MANUFACTURER OF ELECTRONIC LEST

COMPLETE SYSTEMS

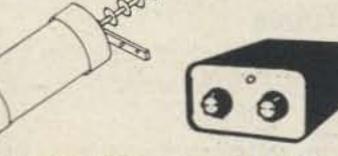1.9 TO 2.5 GHZ

BUILT ANTENNA AND VARIABLE TUNER **OPERATES ON TV** CHANNELS 2 THRU 6



\$59.95

ALL SYSTEMS INCLUDES DETAILED INSTRUCTION

DOWN CONVERTER **BOARD & PARTS KIT**



9.95

\$36.80

BOARD & PARTS KIT



ALUMINUM CABINET ALL HOLES PRE-PUNCHED \$6.95

VARIABLE POWER SUPPLY


MICROWAVE ANTENNA KIT \$9.95 EDOWN CONV KIT \$9.95 POWER SUPPLY KIT \$9.95 CABINET \$6.95


ALL RG59/U COAX CABLES COME WITH CONNECTOR ATTACHED

\$15.95	E
\$13.95	TER
\$10.95	
\$2.50	5
	- 00
	\$13.95 \$10.95

TRIONYX

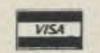6219 COFFMAN RD. INDIANAPOLIS, IN 46268 ADD \$3.50 FOR SHIPPING



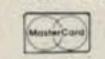

PHONE OR MAIL

(317) 291 7280



ANTENNA \$ 12.95 RUBBER DUCKS FORM \$6.95 TO \$7.95


coaxial R.F. antenna switches



Heavy Duty switch for true 1 Kw POWER - 2 Kw P.E.P.

Single Pole, 3 Position. Desk or wall mount All unused positions grounded

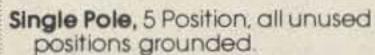- #593-UHF connectors / \$27.25
- #596-BNC connectors / \$36.50 '
- 2 Pole, 2 Position, bypasses linears, reflectometers, antenna tuners, etc.
- #594 UHF connectors / \$34.25



- #595 UHF connectors / \$32.00° #597 - BNC connectors / \$46.50°
- * Shipping and handling for any item add \$2 each.

ALL OUR PRODUCTS MADE IN USA



Quality Communication Products Since 1932

At your Distributors write or call 10 Canal Street, Bristol PA 19007 (215) 788-5581



Introducing The SRT-3000 A High Performance RTTY Communications Send-Receive Terminal

Built-in demodulator & AFSK modulator for 170,425,850 Hz shifts, high and low tone pairs • 60,66,75,100,132 WPM Baudot, 110,300 Baud ASCII, 5-99 WPM Morse • 1000 character text buffer with BREAK feature • Ten 80 character message memories with battery backup •

Selectable display formats, 24 lines x 72 characters (2 pages), 24 lines x 36 characters (4 pages), 16 lines x 36 characters (6 pages) • Split screen operation • On screen status line displays a tuning bar, mode, speed, shift, tone pair, normal/reverse, USOS, WRU, SELCAL, buffer mode and buffer count • Cassette interface for long "Brag Tapes" or unattended message storage • Baudot and ASCII printer outputs • Built-in audio monitor • Built-in 110 VAC power supply • Other features—PTT control, WRU, SELCAL, sync idle, CW ID, USOS, autostart, full or half duplex, scope outputs, weight control, intercharacter spacing, reverse video, RS-232, word wrap around • Compact size only 13.3 x 10.3 x 4 inches • Made in USA.

Send For Free Information



787 BRIAR LANE, BELOIT, WISCONSIN 53511 (608) 362-0410





The SLINKY DIPOLE® Antenna

A broadband, low SWR dipole that really works in apartments, small yards, attics, anywhere a small antenna is a must. Indoors or out, you can work ANY HF BAND, including 10 MHz. No gimmicks or add-ons. Imagine 80M in as little as 24 ft.! Complete kit and instructions, plus 50 ft. of coax. Easy to set up and adjust. More information available - just call or write.

Blacksburg Group

Box 242 Suite 500 Blacksburg, Virginia 24060 703/951-9030 Money Back Guarantee
Virginia residents
add 4% sales tax

Your Ham Tube Headquarters!

TUBES BOUGHT, SOLD AND TRADED SAVE \$\$\$—HIGH \$\$\$ FOR YOUR TUBES

Call Toll Free 800-221-0860 Tubes

SRT-3000

3-400Z \$85	5.00 7360 \$10.00	
3-500Z 85		
4-400A 80		
4CX250B50		
572B 48		
811A 12	2.00 884426.50	
81335		
6146B 6		
6360 4	1.25 8877450.00	
6883B 6	5.75 8908 12.50	
0	to a second seco	

Semiconductors

MHF 245/SD	1416.\$30.00	MRF 644/SD1088.	. 19.95
MRF 454	18.95	2N3055	95.00
MRF 455	12.50	2N6084	
	DE Con	nootoro	

RF Connectors

	11001010	
PL259 10/\$4.95	M3582.50	ea.
PL258 10/8.95	M3591.75	ea.
UG175/176 10/1.60	Type "N" Twist on	
UG255/u2.50 ea.	(RG8/u)\$4.75	ea.
UG273/u2.25 ea.	Minimum Order \$25.00	

Color Salow \$3.00 min. for UPS charges
Communications, Inc.

2115 Avenue X Brooklyn, NY 11235

SERVING THE INDUSTRY SINCE 1922 Phone (212) 646-6300

Call CECO For Your CCTV Security And Color Production Requirements



THESE COULD BE THE KEYS TO YOUR FUTURE

Unlock *all* the potential of your Commodore 64 and VIC-20* with RUN.

Explore...Experiment...Enjoy...

Beginner and expert alike will be taken beyond the manual to the limits of their abilities. Enter your own game programs. Construct a simple hardware add-on. Broaden your scope with unique applications...And...get a 13th issue FREE!

Enjoy key features like these:

- Games for fun & strategy.
- Programming tips help you learn short cuts.
- Candid reviews help you make money-saving decisions.
- Programs to add to your library.
- Instructions & tutorials to increase your skills.
- Hardware & software modifications help your machine work smart.
- Unique applications broaden your scope.

Here's a system-specific magazine written with you in mind. Written by and for the reader to give time-saving, money-saving hints. You'll get instructions and tutorials to increase your skills, and candid reviews to help you make the right decisions. Most of all though, you'll have fun.



Commodore 64 and VIC-20 owners are one of the largest groups of computerists today. Enjoy the benefits of this with your own magazine. Be in control like never before. Order RUN today and get a 13th issue free with your prepaid order (check or credit card) of only \$17.97. Send in the coupon or call toll free 1-800-258-5473. In N.H. call 1-924-9471.

Send me a subscription to RUN for only \$17.97 per year. I understand that with payment enclosed or credit card order I will receive a FREE issue making a total of 13 issues for \$17.97. Save \$2.00 off the basic rate!


card #	exp. date
signature	
name	
address	
city	state zip

Canada & Mexico \$20.97; Foreign Surface \$37.97, 1 year only, US funds drawn on US bank. Foreign airmail, please inquire. Please allow 6 to 8 weeks for delivery.

RUN • Box 954 • Farmingdale, NY 11737

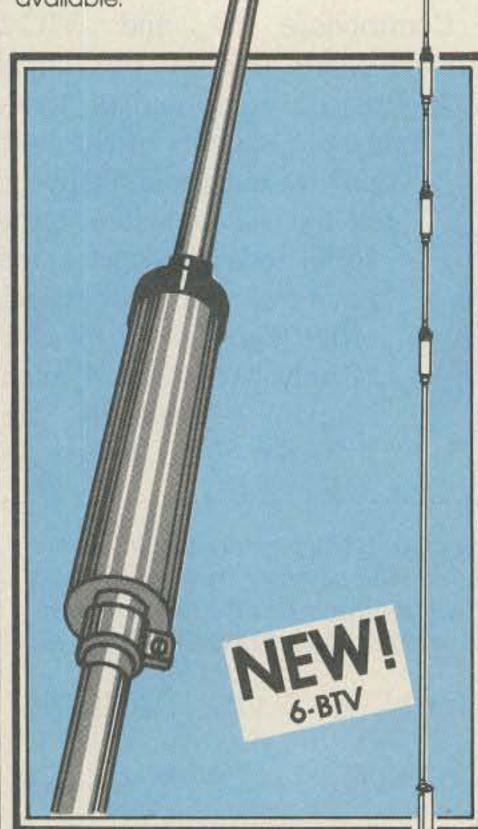*Commodore 64 and VIC-20 are registered trademarks of Commodore Business Machines, Inc.







Don't miss our 30 meter excitement. HUSTLER -STILL THE STANDARD OF PERFORMANCE.



Kissimmee, Florida 32741

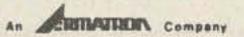

-123

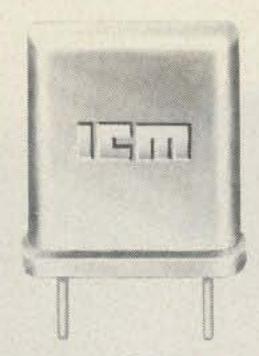

THE PRINTS A DIFFERENCE IN QUARTZ CRYSTALS.

International's leadership in crystal design and production is synonymous with quality quartz crystals from 70 KHz to 200 MHz. Accurately controlled calibration and a long list of tests are made on the finished crystal prior to shipment.

That is why we guarantee International crystals against defects, material and workmanship for an unlimited time when used in equipment for

which they were specifically made.

Orders may be placed by Phone: 405/236-3741. TELEX: 747-147. CABLE: Incrystal · TWX: 910-831-3177 · Mail: International Crystal Mfg. Co., Inc., 10 North Lee, P.O. Box 26330, Oklahoma City, OK 73126.

Write for Information



INTERNATIONAL CRYSTAL MFG. CO., INC. 10 North Lee, P.O. Box 26330, Oklahoma City, OK 73126

\$17.85

APPLIED INVENTION THE SOURCE FOR SOLID STATE / STATE-OF-THE-ART (37)

GaAs

MGF 1100 Dual Gate GaAs FET 2.5dBNF @ 4GHz \$ 7.35 MGF 1202 (1402 chip in a 1200 package) MGF1404 GUARANTEED 0.65dBNF @ 4GHz \$66.60 MGF1402 - 0.4 dBNF @ 432, 1.1 dBNF @ 4GHz MGF1412 GUARANTEED 0.8, 0.9 or 1.0 dBNF @ 4GHz \$21.-\$34.75 MGF1801 10GHz linear PO 150mW \$40.75

MITSUBISHI X BAND Hybrid Integrated Circuits with tuneable Dielectric Resonator (0.12MHz/°C) GaAs FET Oscillators

F0-1010X - 10.4 GHz, 15mw out, UER100 Flange \$39.37 \$39.37 F0-1210Y - 11.5 or 12.0 GHz, UER120 Flange \$36.22 F0-UP11KF - Complete Heterodyne Rx, 10.468 GHz LO Can be used for 12.5 GHz terrestrial and DBS \$43.05 F0-DP13KF Doppler Module 10.525 GHz UER100 Flange

GaAs FET Preamp 1.7-2.1 GHz, 2.0-2.35 GHz, 2dBNF \$49.00 At: THE SOURCE for RETICON Universal Audio Active Filters NEW R5620 digitally programmed switched capacitor audio filter \$ 7.85 R5621 dual section resistor programmed SCF \$ 6.51

X-Band 15 dBG die cast horn antenna (UER100)

R5622 quad section resistor programmed SCF \$11.07 \$ 2.00 Out performs National MF-10! Application notes OPTOELECTRONICS from MITSUBISHI and SIEMENS

CALL CW LASER DIODES, HIGH OUTPUT IRLEDS, PIN PHOTO DIODES. MITSUBISHI BIPOLAR POWER TRANSISTORS FOR 900/1296 CALL 2SC2931, 2, 3, 4 (1.4 to 30 Watts P0)

MRF 901 Substitute 2SC2876, Ft=7GHz, 2.2dBNF @ 1GHz \$ 1.50 NEC 64535 direct replacement: Siemens BFQ 74 \$ 9.66 LEADLESS DISK CAPS 100, 220, 470, 680, pF 10/\$ 2.50 MICROWAVE CHIP CAPS - Very low loss VITRAMON P7800 series GO2(0.7-1.4 GHz) GO4(1.3-2.6 GHz) GO1(2.6-4.2GHz) \$ 1.25 5/\$ 2.50 VITRAMON VHF/UHF NPO chips: 10, 100, 1000 pF. A-B type FW5N 1000pF discoidal Feedthru \$ 0.75

STRIPLINE SHUTTLE TRIMMERS (VOLTRONICS) 0.1-2.5, 0.5-9.0pF \$ 3.34 HI-Q SEALED CERAMIC PISTON TRIMMERS (VOLTRONICS) 0.6-9.0pf \$ 3.58 SAPPHIRE TRIMMERS Johanson 0.4-2.5pF \$ 9.47 For WA2GFP preamp Sprague 0.6-4.5pF \$ 9.47 Thermo Electric Heat Pumps & Sub-Miniature Cryogenic Refrigerators CALL

3M GX250 glass/tte board, Er=2.55 @ 10GHz 0.031 0.062 \$0.52 sq. in. Sq.flange female \$3.50, E.F. JOHNSON SMA's: Male cable \$ 2.88 PROMPT SERVICE. SEND FOR CATALOG. MINIMUM ORDER \$5.00

VISA/MASTERCARD Accepted. CASH prepay take 5% discount. S&H * ITEMS (UPS) \$3.75 - ALL OTHER ITEMS \$2.50 (1st CLASS) NY STATE RESIDENTS ADD 7% SALES TAX

ROUTE 21 HILLSDALE, NY 12529 518-325-3911



IF YOU HAVEN'T HEARD OUR BEEPERS YOU'RE NOT LISTENING!

What's a BEEPER? Sometimes called a "courtesy beep," both Faxscan BEEPERS add a gentle high frequency beep automatically to the beginning of each transmission and a low beep at the end. "Talk-over" is a thing of the past! INTRODUCING BP-4 "The PRO" BEEPER. The PRO is state-of-the-art beeping! Includes a digitally-programmable timer (use it for ID or timeput warnings), an automatic "Slumber Mode" for long battery life (9V battery required-not included), and programmable volume control of the unique double 4-beep timeout warning. No speaker! Uses a piezo-transducer!

Hook-up's a snap with either model! Interfaces to virtually all modern gear. Manual supplied with each BEEPER. Available in three versions:

"A" versions are complete with case, cable, industrystandard 4-pin connectors

"B" versions are the same as above but without connectors. Add your own

"C" versions are circuit-board models for custom installations. Perfect for repeaters or building INTO your rig

BEEPERS ARE A FAXSCAN EXCLUSIVE!

BP-3 "The Original" BEEPER BP-4 "The PRO" BEEPER

A- \$79 All units are assembled, tested,


B- \$49 B- \$69 carry a 90-day limited warranty. and shipped pre-paid in US. C- \$29 C- \$49

Ohio residents add 6% sales tax



3148 Dorf Drive . Dayton, Onio 45418



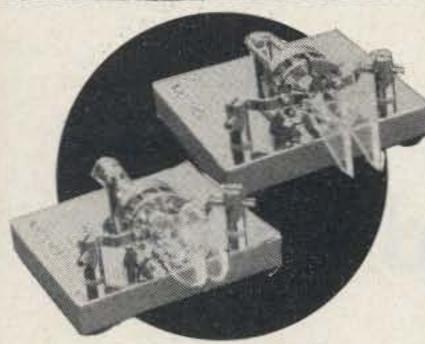

Is CW important to you? If so, there's no better investment in operating pleasure than a Bencher paddle. Offered in both single and dual lever models, quality built Bencher paddles are world famous for flawless keying and responsive ness; unmatched at any price.

Write; or see your dealer for full details-a legend from \$46.95.



"PUBLIC DOMAIN" - SOFTWARE -

Supporting all COMMODORE computers Written by users, for users * GAMES * UTILITIES * EDUCATIONAL *

VIC 20"

collection #1 - collection #2 - collection #3 collection #4 - collection #5 - collection #6 70+ programs per collection - Tape/Disk - \$10.00 VIC COLLECTION #6

A or An Quiz @ Alarm Quiz @ Alpha Sort Amortiza @ Banner @ Big So: @ Bio Printer @ Breakout [J] Budget-Mgr @ Bumblebee @ Buzzword @ Cascades CBuff Peak & CBuff Save & Colour Proball & Computer Fix Coverage Predict @ Craps @ Crytogram @ Dee Density @ Easter Dates @ Electric Cost @ F.I.C.A. Tax Fast Sort @ FFT Calc. @ Firing Tank @ Freq. Copnt. Geog. Spell Game @ Guardian @ Hi-Res @ Job Jar L Pad Design @ Labrinth @ Latter Reco @ Marston City Rvd. Match the Number & Math Dice & Math Fact Drill Math Test @ Math Time @ Maze Maker @ Merry Christmas Millionaire & Mosaic & Multiply Tables & National Parks Nicoma @ PCB Printer @ Pl Network Desig @ Quartic Quiz @ R-S-P @ Rebound Hockey @ Revenge Inst. Revenge Prog. ® Rnd. Graphics ® Rolling Sticks ® Rom Aid Shopping List ® Simon ® Slide Voice ® Snoopy Hires Spelling Aid @ Stopwistch @ Sunrise/Sunset @ Sym T Atten Tennis 3 @ Too High-Too Low @ Typing Tast @ Vectors Vehicle Cost @ VIC Orbit @ VIC Symphony @ Wumpus Inst. Wumpus Prog. @ Zero Formula

COMMODORE 64"

64 collection #1 - 64 collection #2 - 64 collection #3 64 collection #4 - 64 collection #5 25+ programs per collection - Tape/Disk - \$10.00

COMMODORE 64 COLLECTION #5 GAMES — Alien Capture @ Auto Rally @ Dominoes @ Explore Lost Gold Adv. @ Niche @ Owen @ superman. @ Zone X UTILITIES — Accounting Test @ Annuity @ Average Growth Building Costs @ Buy/Sell @ Change Disk Name Cross Word @ Data Search @ Elec. Use @ Finance @ Growth fir. Cash Flow @ Load Calc. @ Real Estate cost @ Rent or Buy EDUCATIONAL - A or An @ Arrow Facts @ Big Math @ Element Chart Eliza ® Europe ® Hang Math ® Linear Prog. ® Loops Marblestat ® Math Facts ® Number Match ® World Quiz

PET® / CBM®

5 Utility - Tapes/Disks - \$10.00 each 11 Game - Tapes/Disks - \$10.00 each 6 Educational - Tapes/Disks - \$10.00 each

DINSET": Reset Switch

Works on Vic 20 or Commodore 64 - \$5.00 All prices include shipping and handling.

CHECK, MONEY ORDERS, VISA and MASTERCARD accepted.

For A Free Catalog Write:

Public Domain, Inc. 5025 S. Rangeline Rd., W. Milton, OH 45383 10:00 a.m. - 5:00 p.m. EST - Mon. thru Fri. (513) 698-5638 or (513) 339-1725

VIC 20" CBMF and Commissions 64" are Trademarks of Commission Electronics Ltd. PET* a a Registered Trademark of Commission Suprises Machines. Inc.

Homebrew



KIT \$49.95 Plus \$2.50 Shipping & Handling "SMART" SQUELCH FOR SSB

73 MAGAZINE 8/82

Detects human voice but ignores noise, steady tones and Russian woodpecker

Works for voice signals below noise level

Ideal for net activities Audio operated - no receiver modification Connects between audio output and speaker

1983-84 CATALOG 50c

Other Kits:

R-X Noise Bridge (hr 2/77) General Coverage Reception Drake R-4C Receiver (QST 5/81)

2 Meter Converter (73 4/82)


40 Meter QRP Transceiver (hr 1/81)

Fun-Mitter (73 2/81) Fun-Ceiver (73 7/81)

Fun-Oscillator (73 2/82) Fun-Amp (73 5/82) and others

Box 411S, Greenville, NH 03048 (603) 878-1033

PACKET RADIO

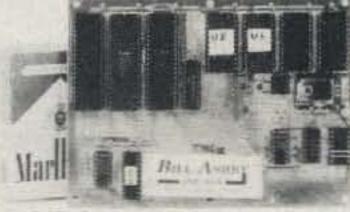

ASCII—USA/AX.25 HDLC CONVERTER

USA/AX.25 is the AMRAD approved digital format STANDARD used on amateur packet radio networks.

\$80.00 PAC/NET board only Assembled/Tested, NoICs, 90day warranty

Package of all ICs except 2-2716 **EPROMs**

\$80.00

PAC/NET SYSTEM

PAC/NET SYSTEM \$240.00 System Tested 4.5 × 6" board complete with all ICs and programmed EPROMs

personalized for each purchaser. Requires only single 8-10 volt 1/2 amp power. 1 year guarantee of hardware/software/AX.25 standard RS232 serial ASCII at any user baud rate. RS232 HDLC for 202 modem used for AFSK or direct to RF equipment for FSK.

Custom Systems Custom Programming

BILL ASHBY

AND SON K2TKN-KA2OEG 201-658-3087 **BOX 332 PLUCKEMIN N.J. 07978**



Fox Tango proudly presents the ultimate sequential data base for Commodore's VIC 20 and 64K computer users.

VERSATILE

Instantly ready to organize records as soon as you turn on your computer, MINI JINI is a cartridge that plugs into the slot in the back of the VIC 20 or 64K. Designed for maximum versatility and general use, it serves anyone with records to keep: the professional, the student, the educator, the collector, the small business man, the investor, the housewife, and the radio amateur who may be any of these. MINI JINI is ideal for those who want to harness the speed and power of their sophisticated units for more than RTTY communications and game playing.

POWERFUL

MJ Electronic Filing Cabinet can:

- Alphabetize/sort up to 500 records
- Add, delete, or change records
- · Search and find records from a bit of information
- · Provide data for printing reports and labels
- · Record data on tape or disk
- · Perform arithmetic operations

ADAPTABLE

Besides keeping electronic logs, contest records, and similar amateur functions, the MINI JINI Record Keeper is being used right now for Club and Church rosters, Real Estate listings, Class and School records, Stock and Bond portfolios, Business and Personal Inventories, Bank and Budget matters, Amway and Avon distributors, Bookstore and Library records, - even Newspaper routes! While such files can be prepared easily by the user, many are available in time-saving form on tape cassettes and disks.

EASY TO USE

Best of all, MINI JINI is quickly learned in 20 minutes for most users. The secret is simplicity - from the plain-language Manual written in tutorial form, to the single letter commands. Order yours today and put your computer to WORK.

NOW AVAILABLE

MJ Record Keeper for VIC 20 . . . \$89.95 MJ Record Keeper for 64K \$89.95 Optional Ham Radio Packages: Shipping \$3, Florida Sales Tax 5%

Order by Mail or Telephone. We accept VISA/MC, Checks, and COD Orders.

- 151 FOX TANGO CORPORATION Box 15944, W. Palm Beach, FL 33416

Telephone (305) 683-9587

Tom Bowman WA3REY 4 Judy Drive, RD #3 Annville PA 17003

Bruce Long WA3PTU c/o Ionospheric Research Lab Room 224, EE East University Park PA 16802

Here's the Split-Second Timer

In the darkroom or the shack, this beeper has 1001 uses. Its simplicity makes it the perfect beginner's project.

Editor's Note: This article, although not exclusively amateur radio oriented, so impressed us at 73 that we are presenting it here. The author has come up with a nifty audible clock circuit. The timer could be used in a photography darkroom, as suggested by the author, or in the ham shack to time your exposure of circuit boards. The timer is simple enough to build as a first-time project. We hope you enjoy this project as much as we did.


ike many hams that I've -talked to, I have a second and maybe more expensive hobby-photography. Inflation has made my photo darkroom even darker with paper costs climbing to over 25 cents a sheet.

Chemicals spiral upward along with paper prices while freelance jobs dwindle. The result is that I'm very money-conscious each time I open my bright yellow box of printing paper. I even scrawled "25¢ a


sheet" on top of the box, but that didn't seem to cut back on the mountain of wasted paper.

With rising paper costs in mind, I decided that the cure might be a new darkroom timer. Too many prints ended up in the wastebasket because of bad dodging and burning. What I needed was a timer that would help me be more accurate, print after print. But the new digital timers cost more than I was willing to spend.

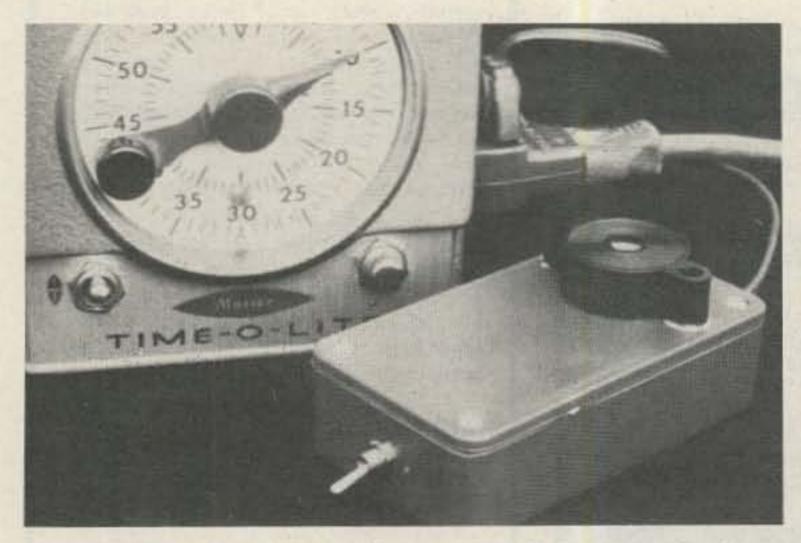My old mechanical timer worked fine as long as I left



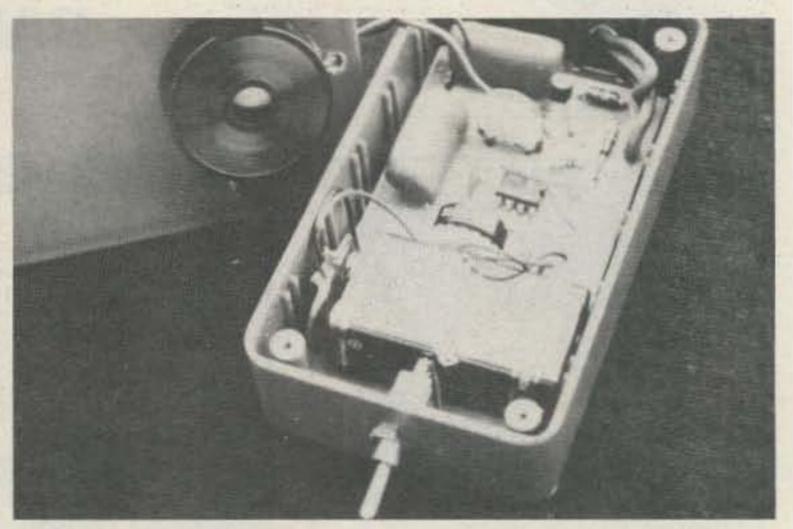Here's how to interface the beeper. A cube tap is pushed into the enlarger outlet of the mechanical darkroom timer. The red wire from the cube tap goes to my photo enlarger and the brown wire to the beeper. When the timer cycles line voltage to the enlarger outlet, both the beeper and the enlarger lamp come on together.



Close-up detail of parts placement inside plastic case. The piezo buzzer is glued to the top of the case. The switch in the foreground is used to turn off the beeper while focusing under the enlarger.

it set on one particular time. The problem crept in when I needed to reset the timer to a new time to burn in part of the print. When I returned the pointer to the original time to make another print, that new print never looked the same as the first print.

Enter Bruce WA3PTU

I talked over my problem with Bruce Long WA3PTU. We reasoned that an audible beep sounding each second coupled to my present timer would permit me to set the timer for, say, 10 seconds and then never move it again. To add or subtract printing time would be easy. All I would have to do would be to count the seconds that ticked by, then block the enlarger's light path with my hand when the correct time was reached.

Dodging and burning prints could be done more accurately since I would hear the passing seconds as I worked over each print. All that was needed was an inexpensive add-on beeper (and, of course, the circuit from WA3PTU).

I built the beeper for about \$11. The handful of parts came from the local Radio Shack store and fit into a plastic box. Calibration was simple using only my wristwatch. The beeper was interfaced with my darkroom timer by plugging it into a cube tap shared with my photo enlarger. The addon beeper has made darkroom life more enjoyable and cost-efficient—so, let's build one.

How It Works

The beeper is simple. A piezo buzzer sounds each second that the enlarger lamp is on. Line voltage is also routed to the add-on beeper through a cube tap. That line voltage turns on a 2N2222 transistor switch in the beeper. The 2N2222 switches on the 555 timer circuit by grounding an in-

ternal 9-volt battery. When the mechanical darkroom timer shuts off the line voltage, the enlarger lamp and the beeper turn off, for practical purposes, simultaneously.

Part of the 555 timer circuit was borrowed from Don Lancaster's TTL Cookbook. I won't repeat Lancaster's very complete description of why the circuit works. All that's necessary is to note that the combination of R1 and C1 produces a beep about .1 second long. The 5k pot adjusts the beep's volume.

The 500k pot calibrates the timing cycle. This pot is carefully adjusted until 61 beeps are timed in 60 seconds. That's right, 61 beeps. When the enlarger lamp and the beeper are first turned on, a beep sounds. That's the extra beep. I really wasn't sure that I could live with that first beep coinciding with the enlarger lamp turning on. Now, after 7 months of use, I expect that first beep and compensate for it. Look at it this way: When you have 20 identical prints to make of the family reunion, it doesn't matter if you remember 5 beeps or 6 beeps as the time for burning in Aunt Lydia's face. What counts is that you consistently give her face that same extra exposure on each of the 20 prints if you don't want to waste paper. Whether or not you count that extra first beep is your decision.

Building the Beeper

Now let's build the beeper. My beeper shown in the photos was built on a printed circuit board. However, a 2"×2" square of perfboard or an etched and drilled Radio Shack IC board, catalogue number 276-024, makes construction simple. The important thing is to make certain that you

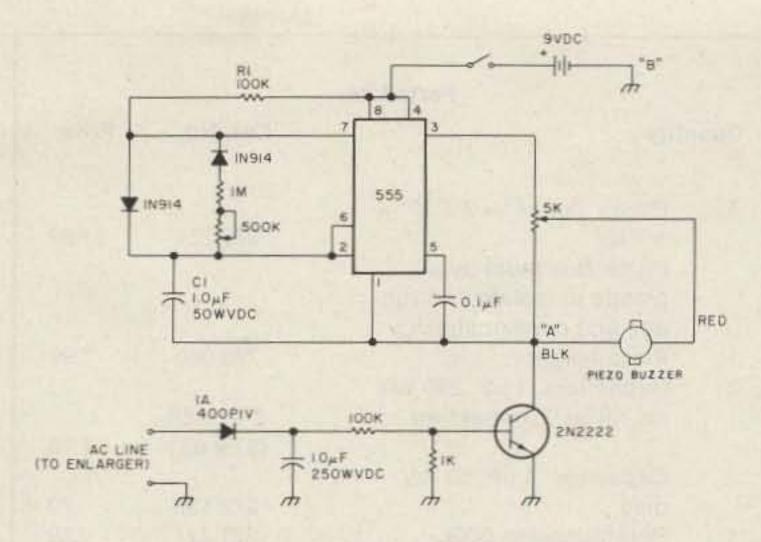


Fig. 1. Add-on beeper schematic.

assemble the parts in an all plastic box. That's a plastic box with a plastic panel. Do not substitute any of the multitude of boxes available with aluminum panels. The 110-volt-ac line is quite safe as long as it remains isolated inside the case. Aluminum panels could provide a dangerous path outside the box.

The circuit board and battery are friction-fit inside my case. Don't use metal screws to fasten the board to the box because of the shock hazard. Instead, glue the battery and board to the case with a few well-placed dabs of silicone rubber cement.

A word about parts. No, 1 don't manage a Radio Shack store or have stock in Tandy Corporation. The parts list has Radio Shack catalog numbers to help beginning builders. I'm certain that these commonly available parts can be found in most any ham junk box. Parts layout isn't critical, either. Observe the polarity of the piezo buzzer. The schematic is marked to show placement of the red and black leads.

Operation

I included a switch to turn off the beeper while focusing or composing under the enlarger. When you are ready to make that first print, turn on the beeper. Set the mechanical darkroom timer for your average print-

ing time. I've standardized on 10 seconds. Never move the mechanical timer off the time you selected—in my case, 10 seconds. If you have a dense negative and must burn in parts of the print, simply press the mechanical timer's button again for another 10-second cycle and count off the extra time. You will probably find that the old mechanical timers are sufficiently accurate when used this way. Inaccuracies creep in when changing the time setting back and forth. For this reason it is much more accurate to set the timer and print as I described than it is to print for 10 seconds then reset the timer for another 5 seconds to burn in part of the print. Consistent dodging can be done by counting the beeps as you hold back underexposed parts of the negative.

Consistency and repeatability result from using the beeper and the "hands-off-the-timer" method. If you don't believe me now, wait until you finish that print order of 20 reunion pictures. Aunt Lydia will look the same on each print—guaranteed.

An Extra Added Bonus

Now that you've built the add-on beeper and love it, let's take it out of the dark-room. Remember that picture you tried to take last December of the Christmas tree and lights after dark in

¹⁷TL Cookbook, Don Lancaster, Howard W. Sams and Co., p. 174.

	Parts List		
Qua	ntity	Cat. No.	Price
1	Plastic box, 4" × 2-7/16" ×		
	1-1/16"	270-221	\$1.89
	(Note: Box must be all		
	plastic to isolate line volt-		
1	age and prevent shock.) Piezo buzzer	273-060	2.99
2	Capacitors, 1 uF, 250 WV	210 000	2.00
	dc, mylar TM metal film	272-1055	
		(\$.89 ea.)	1.78
1	Capacitor, .1 uF, 50 WV,		
	disc	272-135	.79
1	Potentiometer, 500k	271-221	.59
2	Potentiometer, 5k Resistors, 100k,	271-217	.59
-	1/4 Watt, 5%	271-1347	.16
1	Resistor, 1k, 1/4 Watt, 5%	271-1321	.08
1	Resistor, 1 meg,		
	1/4 Watt, 5%	271-1356	.08
2	Diodes, silicon switching		
	1N914	276-1122	.20
	Diode, 1 Amp, 400 piv	276-1103	.69
1	Timer IC, 555	276-1723	.99
N. I	Transistor, 2N2222	276-2009	.79
		Total	\$11.62

Catalog numbers from 1982 Radio Shack Catalog No. 354.

the front yard? The Kodak Professional Photoguide suggests that with ASA 64 film and your camera lens set at f/8, a starting exposure is 5 seconds. Now, you could count "one-one-thousand, two-one-thousand." or you could build a second add-on beeper to time that long exposure.

All you need is a PC cord to interface the beeper with your camera. Build another beeper without the ac line cord and transistor switching circuit. Cut off the end of the PC cord that mates with a flash unit and solder one PC cord wire to point A on the schematic and the other PC wire to point B. Plug the PC cord into the camera, set the shutter to Bulb, and hold open the shutter for an audible 5 seconds or 6 beeps.

Bracketing is just as easy as counting more or less beeps either side of the recommended starting exposure. Think you can count 5

seconds pretty accurately to yourself in your head? Well, the beeper might come in handy when making a picture of, let's see, a "moonlit snowscape." According to the *Professional Photoguide*, that's about 70 seconds at f/4, with Kodachrome 64 film.

Hmmm Now if I want to bracket, that's 140 seconds and 35 seconds, but then I have to take into account reciprocity failure, so. Or was that 141 beeps and 36 beeps? Anyway, the important thing is to build a second beeper without line cord and interface it with your camera. That way there won't be any shock hazard.

The circuit is simple but the beeper works quite well. Build one and stop filling your darkroom wastebasket with printing paper. Instead, start thinking about where you're going to put that new tribander with all the money you save.

HAL-TRONIX, INC.

HAL 2304 MHz DOWN CONVERTERS (FREQ. RANGE 2000/2500 MHz) 2304 MODEL #1 KIT BASIC UNIT W/PREAMP LESS HOUSING & FITTINGS. \$19.95 2304 MODEL #2 KIT (with preamp). \$29.95 2304 MODEL #3 KIT (with High Gain preamp). \$39.95
MODELS 2 & 3 WITH COAX FITTINGS IN & OUT AND WITH WEATHER-PROOFED DIE CAST HOUSINGS
BASIC POWER SUPPLY



2100-2500 MHZ

*AMR-II COMPLETE UNIT COMPLETE SYSTEM AS SHOWN, NOT A KIT, INCLUDES A PC BOARD, POWER SUPPLY, CABLES & CONNEC-TORS—PRE-ASSEMBLED AND TESTED, 24dB GAIN OR GREATER.

> BUY YOUR FIRST UNIT AT \$99.95 3 OR MORE UNITS AT \$89.95 ea.

*HAM MICROWAVE RECEIVER

PRE-AMPLIFIER

HAL-PA-19 WIDE BAND PRE-AMPLIFIER, 2-200 MHz BANDWIDTH (-3dB POINTS), 19dB GAIN FULLY ASSEMBLED AND TESTED \$8.95

HAL-PA-1.4 WIDE BAND PRE-AMPLIFIER, 10 MHz TO 1.4 GHz, 12dB GAIN

FULLY ASSEMBLED AND TESTED \$12.95

HAL-PA-2.1 GHz 2 STAGE PRE-AMPLIFIER, DESIGNED FOR 2304 DOWN CONVERTER.

MADE TO PIGGIE-BACK ON THE 2304 BOARD. OFFERS 20dB GAIN. ALSO HAS AN IMAGE REJECTION FILTER.

FULLY ASSEMBLED AND TESTED \$34.95


SHIPPING INFORMATION: ORDERS OVER \$25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25, PLEASE INCLUDE ADDITIONAL \$2.50 FOR HANDLING AND MAILING CHARGES. SEND 20¢ STAMP FOR FREE FLYER.

HAL-TRONIX INC.

P.O. BOX 1101 SOUTHGATE, MICH. 48195 PHONE (313) 285-1782



"HAL" HAROLD C. NOWLAND W8ZXH

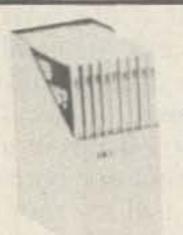

MAKE IT EASY TO SAVE your copies of



73 Magazine

Your magazine library is your prime reference source—keep it handy and keep it neat with these strong library shelf boxes. They are made of white corrugated cardboard and are dust resistant. Use them to keep all your magazines orderly yet available for constant reference.

Self-sticking labels are available for the following:

80 Micro 73 Magazine Radio Electronics
Microcomputing QST Personal Computing
inCider CQ HOT CoCo
Desktop Computing Ham Radio Interface Age

Interface Age es (BX1001) are \$1.50 each

One box (BX1000) is \$2.00, 2-7 boxes (BX1001) are \$1.50 each, and 8 or more boxes (BX1002) are \$1.25 each. Be sure to specify which labels we should send.

Call TOLL-FREE for credit card orders:

1-800-258-5473

73 Magazine

Attn: Book Sales, Peterborough, NH 03458

☐ SHIPPING AND HANDLING CHARGES \$2.00 per order, up to and including a quantity of eight. 25¢ for each additional box ordered.

TS430S FILTERS

For superior performance at lower cost, use toprated 8-pole Fox Tango crystal filters to fill the optional spots in your rig. For example, our 1800 Hz FT2808 equivalent of the YK88SN has 60/6dB shape factor of 1.7 compared with 2.0, a price of \$55 vs \$60, and squarer shoulders at the top with steeper skirts all the way down to more than -80dB!

For more pleasant audio use our 2100Hz for SSB and/or our 6000Hz for AM. For CW, our 400Hz unit is better than the YK88C, while our 250Hz is sharper than the YK88CN.

BIGGER IS BETTER!

Fox Tango filters are better because of their discrete crystal (not monolithic) construction. This makes them slightly larger than YK filters so they are patched into the circuit with short lengths of coax. Installation is easy—no drilling or circuit changes. Order with confidence.

COMPLETE FILTER KITS - \$60 EACH

AM—FT2811 (6000Hz Bandwidth) SSB—FT2808 (1800Hz); FT2809 (2100Hz) CW—FT2801 (250Hz); FT2802 (400Hz)

Kits include all needed cables, parts, detailed instructions. Specify the type(s) desired:

Shipping \$3 per order, (\$5 air). FL Sales Tax 5%.



ONE YEAR WARRANTY
GO FOX-TANGO—TO BE SURE!
Order by Mail or Telephone.

AUTHORIZED EUROPEAN AGENTS Scandinavia: MICROTEC, Makedien 26, 3200, Sandefjord, NORWAY Other: INGOIMPEX Postfach 24 49, D-8070, Ingolstadt, W. GERMANY

FOX TANGO CORPORATION Box 15944T, W. Palm Beach, FL 33416

Phone: (305) 683-9587

RF TRANSISTORS


FRESH STOCK - NOT SURPLUS

FRE	24 2	IUCK	- 1101 9	UNF	LUS
		2.30	MHz		
P/N	Net N	latch/Pr	P/N	Net	Match/Pr
MRF412	\$18.00	\$39.00	MRF455	\$13.50	\$30.00
MRF421	27.00	58.00	MRF455A	13.50	30.00
MRF450	12.50	28.00	MRF458	18.00	40.00
MRF450A	12.50	28.00	MRF492	20.00	43.00
MRF453	15.00	33.00	SRF2072	15.00	33.00
MRF435A	15.00	33.00	SRF2769	15.00	33.00
MRF454	16.50	36.00	CD2545	18.50	40.00
MRF454A	16.50	36.00	CD3424	19.00	41.00
STATE OF LICENSES, NO.	High Gain	Matched P	airs & Quads /	a vallable	22.00
P/N	ng	Net	P/N		Net
MRF406		\$14.50	MRF475		\$ 5.00
MRF422		39.50	MRF476		3.50
MRF433		14.50	MRF477		13.00
MRF435		42.00	SD1407		37.00
MRF449		14.50	SD1487		28.00
MRF449A		14.50	S10-12		14.50
444.35.37.37.37.37	VI	HF & UHF	TRANSISTORS		*******
Type	Mount	Rating	MHz		Net/ea.
MRF238	(5)	30W	145-175		\$13.00
MRF240	(a)	40W	145-175		15.00
MRF245	(F)	W08	130-175		27.00
MRF247	(F)	80W	130-175		27.00
MRF492	(F)	70W	27-50		20.00
SD1416	(F)	80W	130-175		29.50 37.00
SD1477	(F)	125W	130-175		83.50
SD1441	(F)	150W	130-175		7.75
2N6081	(5)	15W	130-175		9.75
2N6082	(s)	25W	130-175		9.75
2N6083	(s)	30W	130-175		12.00
2N6084	(8)	40W	1,15,000,000,000		15.00
2SC1955	-	1W	130-175		20.00
2SC2289	-	5W	430-470		18.00
MRF641	(F)	15W	430-470		21.50
MRF644	(F)	25W	430-470		24.50
MRF646	(F)	45W	430-470		33.50
MRF648	(F)	60W		roce-r	eference
Technic	al As	sistance	and o	0 0	D D/Al'a
informat	ion on	CD, PI	RF, SRF	& S	D PINS,
Call our	Enginee	ering Dep	t.	(619) /	44-0728
WE SHI	SAME	DAY	0.01	or VI	SA/M.C.
					Shipping
Minimur	n Order	\$20,00	OFH & CH	entitu C	incounts

Minimum Order \$20.00 Add \$3.50 Shipping
RF Parts Catalog Avail. OEM & Quantity Discounts
ORDERS ONLY: 800-854-1927

1320 Grand Ave.

California 92069

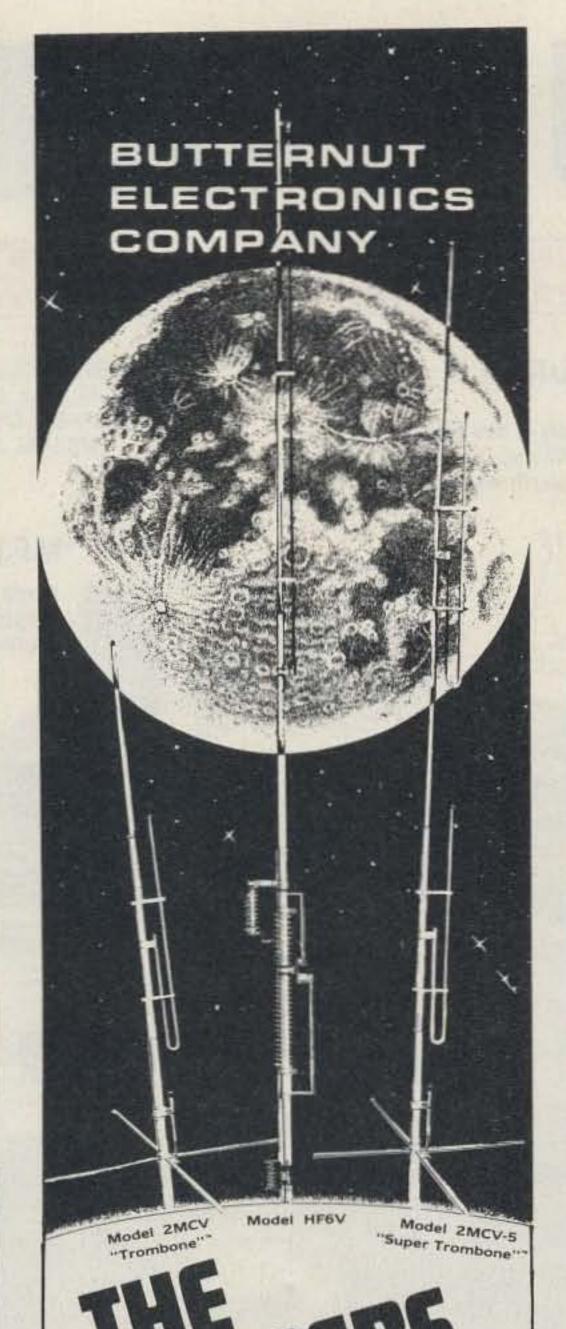

Model HF6V—Completely automatic bandswitching 80 through 10 plus 30 meters. Outperforms all 4- and 5-band "trap" verticals of comparable size. Thousands in use worldwide since December '811 160 meter option available now; retrofit kits for remaining WARC bands coming soon. Height: 26 ft/7.8 meters; guying not required in most installations.

Model 2MCV "Trombone" — omnidirectional collinear gain vertical for 2 meters having the same gain as "double-%λ" types, but the patented "trombone" phasing section allows the radiator to remain unbroken by insulators for maximum strength in high winds. No coils "plumber's delight" construction and adjustable gamma match for complete D.C. grounding and lowest possible SWR. Height: 9.8 ft/2.98 meters

Model 2MCV-5 "Super-Trombone" — Same advanced features as the basic 2MCV but a full wavelength taller with additional gain. Height: 15.75 ft/4.8 meters

All BUTTERNUT ANTENNAS use stainless steel hardware and are quaranteed for a full year. For further information on these and other BUTTERNUT products write for our FREE CATALOG!

BUTTERNUT
ELECTRONICS
405 E. Market St. Lockhart, TX 78644



Electronics Supply

1508 McKinney Houston, Texas 77010 713-658-0268 TOLL FREE - ORDERS ONLY 1-800-231-3057

QUALITY TUNERS THAT DELIVER MORE PERFORMANCE, MORE FEATURES, MORE VALUE FOR YOUR MONEY.

MFJ-941D 300 WATT VERSA TUNER II

0095 MFJ's fastest selling tuner packs in plenty of new features. New styling! Brushed aluminum front. All metal cabinet. New SWR/Wattmeter! More accurate. Switch selectable 300/30

watt ranges. Read forward/reflected power.

New antenna switch! Front panel mounted. Select 2 coax lines, direct or through tuner, random wire/ balanced line or tuner bypass for dummy load.

New airwound inductor! Larger more efficient 12 position airwound inductor gives lower losses and more watts out. Run up to 300 watts RF power output.

Matches everything from 1.8 to 30 MHz: dipoles, inverted vee, random wires, verticals, mobile whips, beams, balanced and coax lines.

Built-in 4:1 balun for balanced lines. 1000 V capacitor spacing. Black. 11 x 3 x 7 inches. Works with all solid state or tube rigs. Easy to use anywhere.

MFJ-949B 300 WATT **DELUXE VERSA** TUNER II

(+4)

C12095 MFJs best 300 watt Versa

Tuner II. Matches everything from 1.8 - 30 MHz, coax, randoms, balanced lines, up to 300W output, solid state or tubes.

Tunes out SWR on dipoles, vees, long wires, verticals, whips, beams, quads.

Built-in 4:1 balun. 300W, 50-ohm dummy load. SWR meter and 2 range wattmeter (300W and 30W).

6 position antenna switch on front panel, 12 position air-wound inductor; coax connectors. binding posts, black and beige case. 10 x 3 x 7 in. MFJ-940B, \$79.95, 300 watts, SWR/Wattmeter, antenna switch on rear. No balun. 8 x 2 x 6 in. eggshell white with walnut grained sides. MFJ-945, \$79.95, like MFJ-940B with balun, less antenna switch. MDJ-944, \$79.95, like MFJ-940B with balun, antenna switch on front panel, less SWR/Wattmeter. Optional mobile bracket for 940B, 945, 944, \$5.00.

MFJ-900 200 WATT VERSA TUNER

Matches coax, random wires 1.8-30 MHz. Handles up to 200 watts output; efficient airwound inductor gives more watts out.

(+\$4)

5x2x6 in. Use any transceiver, solid state or tube. Operate all bands with one antenna. OTHER 200 WATT MODELS: MFJ-901, \$59.95, like 900 but includes 4:1 balun for use with balanced lines. MFJ-16010, \$39.95, for random wires only. Great for

apartment, motel, camping operation. Tunes 1.8-30 MHz.

MFJ-962 1.5 KW **VERSA TUNER III**

to 1.5 (+\$10)KW PEP

and match any feedline continuously from 1.8 to 30 MHz; coax, balanced line or random wire. Built-in SWR/Wattmeter has 2000 and 200 watt ranges, forward and reflected power. 2% meter movement. 6 position antenna switch handles 2 coax lines (direct or through tuner), wire and balanced lines, 4:1 balun 250 pf 6 KV variable capacitors. 12 position inductors. Ceramic rotary switch. All metal black cabinet and panel gives RFI protection, rigid construction and sleek styling. Flip stand tilts tuner for easy viewing. 5 x 14 x 14 inches.



MFJ-989 3 KW ROLLER INDUCTOR VERSA TUNER V

\$329% Meet "Versa Tuner V". It has all the features you asked for, including the new smaller size to match new smaller rigs only 10 3/4"W x 4 1/2"H x 14 7/8"D.

Matches coax, balanced lines, random wires - 1.8 to 30 MHz. 3 KW PEPthe power rating you won't outgrow (250 pf-6KV caps).

Roller Inductor with a 3-digit turns counter plus a spinner knob for precise inductance control to get that SWR down to minimum every time. Built-in 300 watt, 50 ohm dummy load, built-in 4:1 ferrite baiun.

Built-in 2% meter reads SWR plus forward and reflected power in 2 ranges

(200 and 2000 watts). Meter light requires 12 VDC. Optional AC adapter MFJ-1312 is available for \$9.95.

6-position antenna switch (2 coax lines, through tuner or direct, random/ balanced line or dummy load). SO-239 connectors, ceramic feed-throughs, binding post grounds.

Deluxe aluminum low-profile cabinet with sub-chassis for RFI protection, black finish, black front panel with raised letters, tilt ball. MFJ-981, \$239.95. 3 KW, 18 position switched dual inductor. SWR/Wattmeter, 4:1 balun.

ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO OBLIGATION. IF NOT DELIGHTED, RETURN WITH-IN 30 DAYS FOR PROMPT REFUND (LESS SHIPPING)

- One year unconditional guarantee
 Made in USA.
- · Add shipping/handling shown in parenthesis
- . Call or write for free catalog, over 100 products.

MFJ ENTERPRISES, INC. Box 494, Mississippi State, MS 39762

TO ORDER OR FOR YOUR NEAREST DEALER, CALL TOLL-FREE 800-647-1800. Call 601-323-5869 in Miss. and outside continental USA Telex 53-4590 MFJ STKV



ASCII / MFJ AMTOR CW

RTTY/ACSII/AMTOR/CW

INTERFACE CARTRIDGE FOR VIC-20/C-64

Most versatile RTTY/ ASCII/AMTOR/CW Interface cartridge available for VIC-20 and Commodore

MFJ-1228 **GO** 95

64. Gives you more features, more performance, more value for your money than any other interface cartridge available.

Same Interface cartridge works for both VIC-20 and Commodore 64. Plugs into user's port.

Choose from wide variety of RTTY/ASCII/CW. even AMTOR software. You are not married to one on-board software package. Use MFJ, Kantronics, AEA plus most other software cartridge, tape or disk.

850 Hz and 170 Hz shifts on receive and transmit. Has mark and space outputs for scope tuning. Normal/Reverse switch eliminates retuning.

True dual channel mark and space active filters and automatic threshold correction gives good copy when one tone is obliterated by QRM or selective fading.

Easy, positive tuning with twin LED indicators. Narrow 800 Hz active CW filter. Automatic PTT. Exar 2206 sine generator for AFSK output. Shielded XCVR AFSK/PTT Interface cable provided. Plus or minus CW keyed output. FSK out.

Powered by computer (few mA.), no power adapter to buy or extra wire to dangle or pick up/radiate RFI. Glass epoxy PCB. Aluminum enclosure. 41/2x41/2x1".

MFJ INTERFACE plus MFJ SOFTWARE CARTRIDGE

for VIC-20 or Commodore 64. MFJ-1228 PLUS MFJ-1250 or MFJ-1251 for one low price

Save \$20.00

SOFTWARE CARTRIDGE FOR VIC-20/C-64 MFJ-1250/MFJ-1251

Powerful MFJ software cartridge for VIC-20 (MFJ-

\$ 10 95

MFI COMPUTER INTERFACE FILTER


1250, \$49.95) and Commodore 64 (MFJ-1251,\$49.95). Plugs into expansion port. Developed by MFJ.

Features RTTY/ASCII/CW send and receive, split screen display, type ahead buffer, message ports, status display, automatic CW speed tracking, parallel and VIC serial printer compatibility plus much more.

SUPER RTTY FILTER


\$ 39 95 NEW MFJ-725

Super RTTY filter greatly

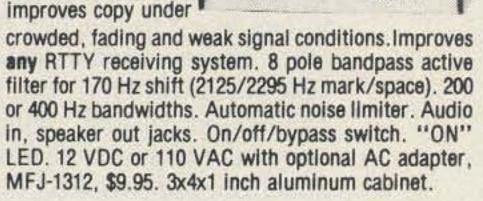

GENERAL PURPOSE RTTY/ASCII/ AMTOR/CW COMPUTER INTERFACE

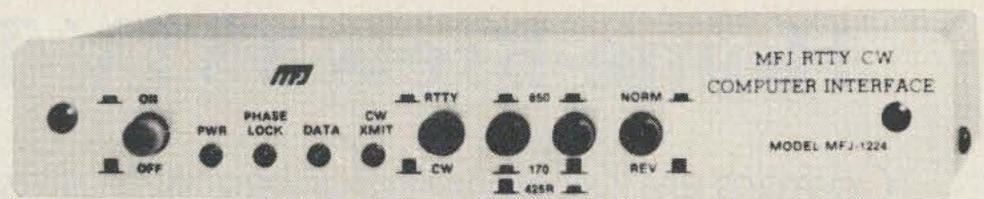Lets you send and receive computerized RTTY/ASCII/AMTOR/CW. Copies all shifts and all speeds. Copies on both mark and space. Sharp 8 pole active filter for 170 Hz shift and CW. Plugs between your rig and VIC-20, Apple, TRS-80C, Atari, TI-99, Commodore 64 or most other personal computers. Uses MFJ, Kantronics software and most other RTTY/CW software.



MFJ Software plus MFJ Interface for VIC-20/C-64

Software cartridge alone, \$49.95. Order MFJ-1250 for VIC-20, MFJ-1251 for Commodore 64. Includes cable to Interface MFJ-1224 to VIC-20 or C-64.

MFJ-1224

New MFJ-1224 RTTY/ASCII/AMTOR/CW Computer Interface lets you use your personal computer as a computerized full featured RTTY/ASCII/ AMTOR/CW station for sending and receiving. Plugs between rig and VIC-20, Apple, TRS-80C, Atari, TI-99, Commodore 64 and most others.

Use MFJ (see MFJ-1250/1251 below) software for VIC-20, Commodore 64 and Kantronics for Apple, TRS-80C, Atari, TI-99 and most other software for RTTY/ASCII/AMTOR/CW.

Easy, positive tuning with twin LED indicators. Copy any shift (170,425,850 Hz and all other shifts) and any speed (5-100 WPM RTTY/CW and up to 300 baud ASCII).

Copies on both mark and space, not mark only or space only, to improve copy under adverse conditions.

Sharp 8 pole 170 Hz shift/CW active filter gives good copy under crowded, fading and weak signal conditions. Automatic noise limiter suppress static crashes for better copy.

Normal/Reverse switch eliminates retuning. +250 VDC loop output drives RTTY machine. Speaker lack.

Automatic tracking copies drifting signal.

Exar 2206 sine generator gives phase continuous AFSK tones. Standard 2125 Hz mark and 2295/2975 Hz space. Microphone line: AFSK out, AFSK ground, PTT out and PTT ground.

FSK keying output. Plus and minus CW keying. CW transmit LED. External CW key jack.

Kantronics compatible socket.

Exclusive general purpose socket allows interfacing to nearly any personal computer with most appropriate software. Available TTL lines: RTTY demod out, CW demod out. CW-ID Input, +5 VDC, ground. All signal lines are buffered and can be inverted using an internal DIP switch.

Use Galfo software with Apple, RAK with VIC-20, Clay Abrams with TRS-80C, N4EU with TRS-80 III, IV. Some computers with some software may require some external components.

Metal cabinet. Brushed alum. front. 8x11/4x6 in. 12-15 VDC or 110 VAC with adapter, MFJ-1312, 19.95. MFJ-1223, \$29.95, RS-232 adapter for MFJ-1224.

CW INTERFACE CARTRIDGE FOR VIC-20/C-64 NEW



\$ 20 95

MFJ-1226

High performance CW Interface cartridge. Gives excellent performance under weak, crowded, noisy

conditions. Works for both VIC-20 and Commodore 64. Plugs into user's port.

4 pole 100 Hz bandwidth active filter. 800 Hz center frequency. 3 pole active lowpass post detection filter. Exclusive automatic tracking comparator.

Plus and minus CW keying. Audio in, speaker out jacks. Powered by computer.


Includes Basic listing of CW transmit/receive program. Available on cassette tape, MFJ-1253, \$4.95 and on software cartridge, MFJ-1254, \$19.95.

You can also use MFJ-1250 (VIC-20) or MFJ-1251 (C-64), \$49.95 each, RTTY/ASCII/CW software cartridge. Or use Kantronics, AEA and others.

Also copy RTTY with single tone detection.

UNIVERSAL SWL RECEIVE ONLY COMPUTER INTERFACE FOR RTTY/ASCII/AMTOR/CW

MFJ-1225 \$ **69** 95

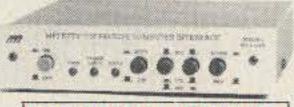

Use your personal computer

MFJ-1225 plus MFJ-1250 and communications | or MFJ-1251 \$99.95. receiver to receive commercial, military and amateur

RTTY/ASCII/AMTOR/CW traffic. Plugs between receiver and VIC-20, Apple, TRS-80C, Atari, Ti-99, Commodore 64 and most other

personal computers. Requires appropriate software. Use MFJ(see this ad), Kantronics, AEA and most other RTTY/ASCII/AMTOR/CW software.

Copies all shifts and all speeds. Twin LED indicators makes tuning easy, positive. Normal/Reverse switch eliminates tuning for Inverted RTTY. Speaker out jack. Includes cable to Interface MFJ-1224 to VIC-20 or Commodore 64. 41/2x11/4x41/4 Inches. 12-15 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO OBLIGATION, IF NOT DELIGHTED, RETURN WITH-IN 30 DAYS FOR PROMPT REFUND (LESS SHIPPING).

- One year unconditional guarantee
 Made in USA.
- · Add \$4.00 each shipping/handling · Call or write for free catalog, over 100 products.



MFJ ENTERPRISES, INC. Box 494, Mississippi State, MS 39762 TO ORDER OR FOR YOUR NEAREST DEALER, CALL TOLL-FREE 800-647-1800. Call 601-323-5869 in Mississippi and out-

side continental U.S.A. Telex 53-4590.



Peak Your Picture With Home-Brew SSTV Test Gear

Go from gray scale to color bars with these simple generators.

No monitor should be without them.

n my spare time I enjoy particular viewing slow-scan television on my home-brew ests in monitor and like to keep up descrito date with advances in ator hothis field. Also, I enjoy designing with all types of integrated circuits, CMOS in \$100.

particular. Thus, I have combined these two interests into the two projects described here. Each generator has nine ICs and few other components and both can be built for well under \$100.

The SSTV gray-scale generator is used as a standard to adjust brightness and contrast levels on commercial slow-scan monitors and to peak sync and bandpass filters on home-brew equipment. It also can be used to

check repairs or modifications on any monitor.

In addition to the abovementioned operations, the SSTV color-bar generator is useful when selecting red, green, and blue filters for color slow-scan photography. It provides a pattern with these colors plus mixtures of them into bluegreen, violet, yellow, and white.

Gray-Scale Generator

The MM5369 is a crystal-controlled oscillator providing a square wave at 3.58 MHz. This signal is divided by a factor of 10 through each of the 4017 dividers. A 35.8-kHz signal is present on pin 9 of the 4520 binary divider. A binary code is fed into the 4514 decoder.

Meanwhile, the 4069 clock provides a 240-Hz square wave to pin 1 of the other binary divider in the 4520 package. Here, the binary-coded output selects one of the 16 available input pins from the two 4051 digital selectors and passes reset information from the 4514 decoder through pin 3 of both 4051 ICs to the reset pin (pin 15) of the first binary divider.

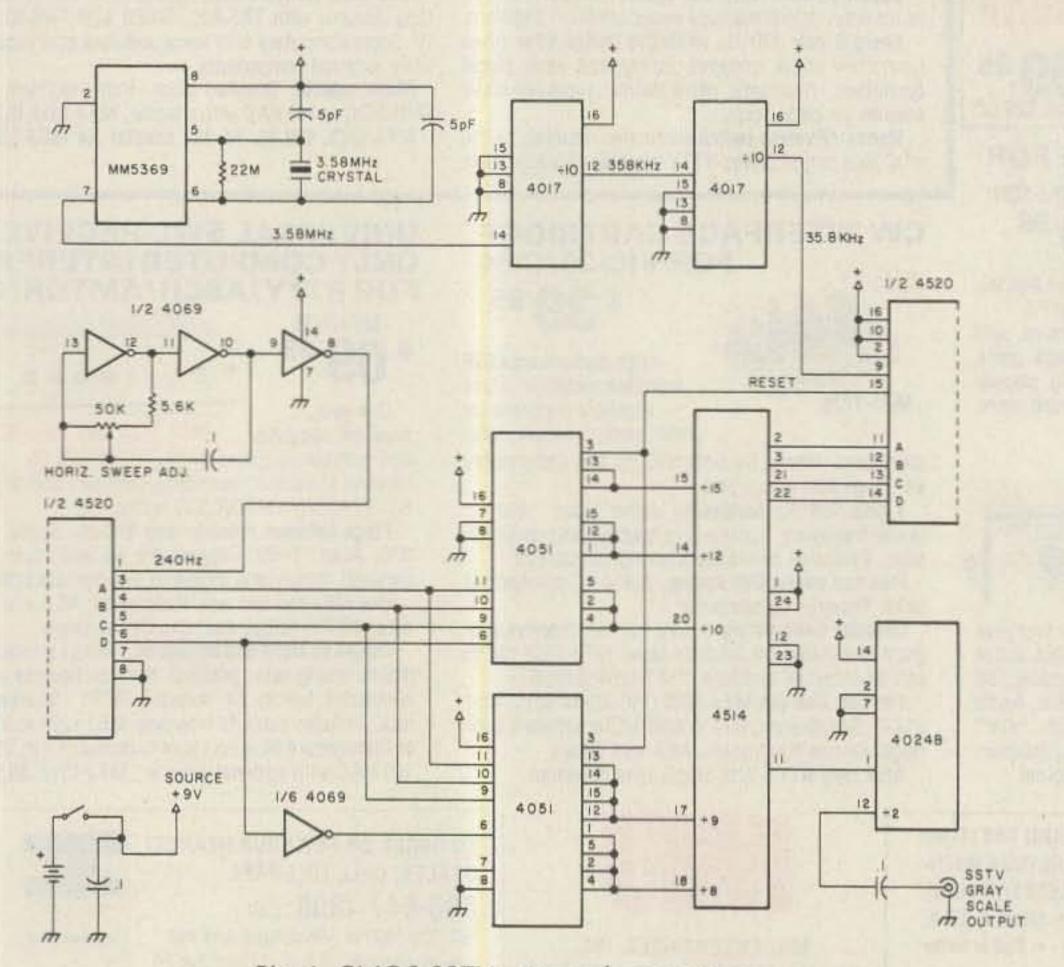


Fig. 1. CMOS SSTV gray-scale generator.

As the 16 input pins are swept through (top to bottom on the schematic), the 35.8-kHz frequency is divided by factors of 15, 12, 10, 9, and 8 respectively. This will constitute one scan line on the monitor. The 4024B takes frequencies from the "0" pin (pin 11) of the 4514 and divides all by a factor of two. The result is an SSTV gray scale with frequencies within one percent of 1200, 1500, 1800, 2000, and 2250 Hz. All are 50/50 duty-cycle square waves so gray-scale shades will result only from changes in frequency. The only adjustment necessary is horizontal sweep speed.

Color Bars for SSTV

The same general operation of the gray-scale generator can be redesigned to give us the three frame patterns necessary to produce, photographically, a slowscan color-bar frame.

We start again with a 3.58-MHz oscillator and divide by a factor of 100, this time in a single 4518. A 35.8kHz signal is fed to pin 9 of the 4520 and a binary-coded output is available at the address inputs of the 4514. Also, a clock frequency of 120 Hz is provided at pin 1 of the 4520 and a binary code is presented to a single 4051.

The action of the 4051 and the two sections of the 4053 can be described as switches in series. Binary data on address pins 9, 10, and 11 of the 4051 and control pins 9 and 10 of the 4053 will route data from the 4514 pins 15, 14, and 18 to pin 15 of the 4520. The timing of these connections will produce horizontal and vertical pulses as well as full cutoff and saturation (black and white) bars when viewed on the monitor. When looking at the three frame patterns, one can see a relationship forming between the width of the bars and the square-wave frequency at the RGB select switch.

A 555 timer is used as a 98/2 duty-cycle clock to


control pin 10 of the 4053. This clock and the bottom 4053 switch provide a vertical sync option for the generator. For about two scan lines worth of time, the generator will produce a 1200-Hz tone. The monitor will look at this tone as a vertical sync pulse.

The 4013 is a divide-bytwo stage that operates identically to the 4024B in the gray-scale generator. The output inverter is not necessary if one has a "B" series 4013 device.

Going Further

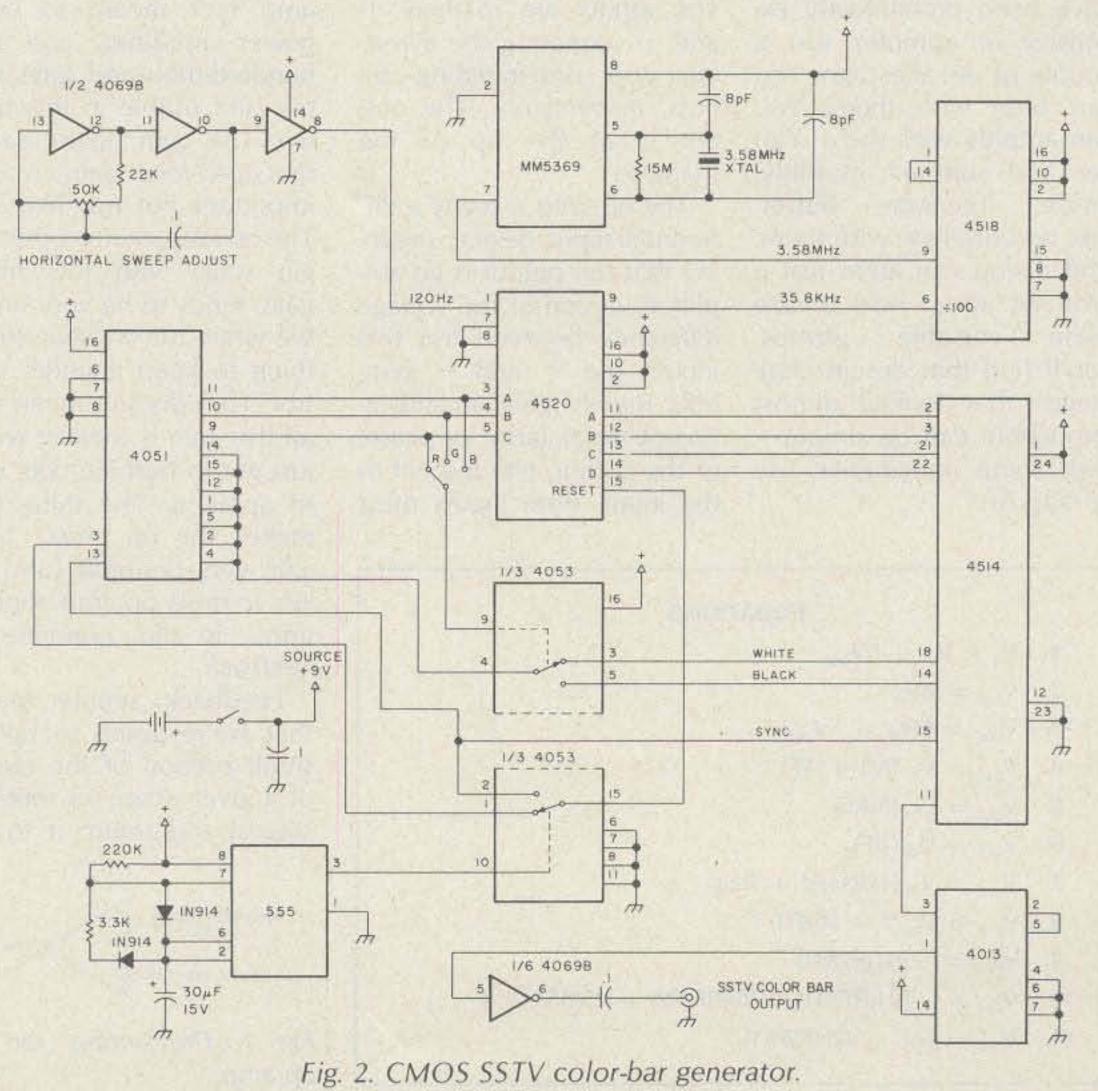The heart of these audiotone generators can be a good starting point for other projects. Add a memory (ROM) and send graphics or your call letters without a computer. Build a flying spot scanner, vidicon camera, or a totally solid-state SSTV camera with the new Reticon photodiode arrays (see Radio Electronics, March, 1982, page 75).





Op Art

Include the ubiquitous op amp in your next circuit. KCØEW tells how.

hen the Linear IC Hall of Fame is established, it's a pretty safe bet that among the first to be inducted will be the operational amplifier, or op amp. From the venerable 709 and 741 to the latest wideband wonders, this class of component has found its way into more circuits than practically any other chip.

The op-amp IC has made possible designs that would have been prohibitively expensive or complex just a couple of decades ago. You can filter with them. You can amplify with them. You can add, subtract, multiply, divide, integrate, buffer, mix, and oscillate with them. And if you can learn just a little bit about how to use versatile gizmos, these you'll find that design challenges that looked almost impossible can be simple with some imaginative use of "Op Art."

Simply put, an operational amplifier is just a very high gain voltage amp with high input impedance and practically no output impedance. A typical op amp will show a voltage gain of several hundred thousand, with an input impedance in the megohms.

On a schematic they're not much to look at-Fig. 1 shows the ubiquitous triangle symbol of the op amp. The inputs are marked + and -, denoting the inverting and non-inverting inputs, respectively. The output is at the tip of the triangle.

The op amp is really a differential-input device, meaning that the output is an amplified version of the voltage difference between the two inputs; the + and - symbols merely give an indication of the polarity, or phase, of the output with respect to the input. Both inputs must be used for the output to do anything meaningful.

So we've got a part which will amplify a voltage by a hundred thousand times or more. Seems like just the thing for a stage with lots of gain, right? Just think, we'll feed the input a few millivolts (maybe from that turntable over there) and drive our speakers directly from the output!

Well, not quite. The op amp isn't meant to be a power amplifier, and that hundred-thousand gain simply isn't usable in this fashion. This gain figure, called the open-loop gain, is very important but not like this. The op amp, or any other single stage with this much gain, tends to be very unstable when run without something to keep it under control. That doesn't mean that all this gain is useless; we've just got to find the right way to apply it. The thing that makes the op amp's huge gain very desirable (and the key to most op amp applications) is the principle of feedback.

Feedback simply means that we're going to take a small portion of the output of a given stage (or series of stages) and return it to the

input. Feedback can cause an otherwise stable circuit to suddenly go into violent oscillation—as anyone who's ever spent some time with PA systems knows! The squealing heard when a microphone is placed too close to the speaker it's driving is an example of positive feedback-the output signal is returned in-phase with the input, adding to it and driving the system farther and farther into oscillation. But if you return the output so that it is out of phase with the input, in negative feedback, you can actually improve the stability of the circuit. Here's how it works.

Consider the simple block diagram shown in Fig. 2. The triangle here is used to indicate some amplifier (not necessarily an op amp) with a voltage gain of A. This means that the output voltage is A times as big as the input voltage (Vin). Vin is applied to the amplifier so that it appears as the voltage difference between the two input leads, so we're still talking about a differential amplifier.

So far, no big deal, right? But suppose we add a block which returns a part of the output back to the input, as

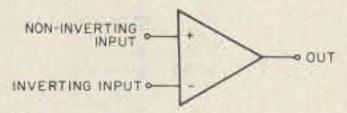


Fig. 1. The symbol for the op amp.

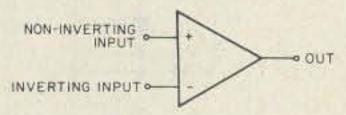


Fig. 2. An amplifier with a voltage gain of "A."

EQUATIONS

- 1. $V_a = V_{in} FV_{out}$
- 2. $V_{out} = AV_a$
- 3. $V_{out} = A(V_{in} FV_{out})$
- 4. $V_{out} = V_{in} (A/1 + AF)$
- 5. $V_{out} = V_{in} (A/AF)$
- 6. $V_{out} = V_{in} (1/F)$
- 7. $V_{out} = V_{in} [1/(R1/(R1 + R2))]$
- 8. $V_{out} = V_{in} (1 + R2/R1)$
- 9. $V_{out} = -V_{in} (R2/R1)$
- 10. $V_{out} = -[V1(RF/R1) + V2(RF/R2) + V3(RF/R3) + ...]$
- 11. $V_{out} = (V1 V2) (R2/R1)$

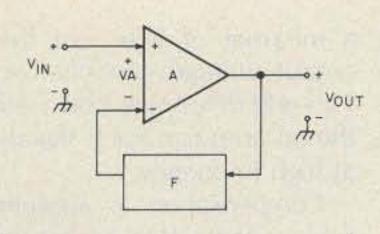


Fig. 3. An amplifier with feedback.

in Fig. 3. Here, the block marked F is doing just that. We'll use F as the gain of this block, saying that F times the output is fed back to the input. In Fig. 2, the output was just an amplified version (A times) of the input. But what's happening in this new arrangement?

Well, the output of the amplifier—the triangle stage—still has to be A times as big as the input. But the input to the amplifier is no longer just the input signal, V_{in}. The input to the amp—the voltage difference between the two input terminals—is now the difference between V_{in} and F times the output. If we call this signal V_a (for voltage at the amplifier), we can write Equation 1 (see box).

It is this combined signal that the amplifier block is working with, so the amplifier output (and the output of the whole thing, since they're the same) must be A times V_a (see Equation 2).

What we'd really like, though, is some relation between the original input signal (V_{in}) and the output. Well, Equation 1 gives us V_a in terms of both of these, so we can get rid of that pesky V_a just by plugging in the right side of 1 for V_a (see Equation 3).

This says that the output depends on both the input and itself. (Well, what did you expect with feedback?) A few more algebraic tricks: dividing both sides by Vout and rearranging gives us Equation 4.

This might not look all that impressive at first glance (heck, it might not look that impressive at second glance), but let's think a bit about what it means. Remember, A is the gain of

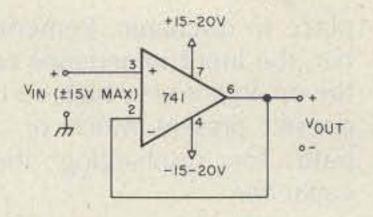


Fig. 4. A non-inverting buffer.

the triangle block in Fig. 3— the amplifier proper—and F is the gain of the feedback path around the amp. Since we know we're trying to find some use for a large gain amp, what happens if A in this equation becomes very large?

If A is a large number, then A times F must also be a large number, at least until F gets pretty small. And if A times F is large, then adding one to it shouldn't change it very much-I mean, 100,000 and 100,001 are pretty much the same, right? So in Equation 4, the $1 + (A \times F)$ might just as well be simply A × F-the added one isn't going to make much difference one way or another. Well, if we drop the one we get Equation 5 which then, dividing through by A, results in Equation 6.

Now, that's something we can use. What this has all boiled down to is the fact that if our assumption about $A \times F$ being large is true, then the output does not depend on the actual gain of the amplifier at all! As long as the gain of the amplifier (A) is large enough to make A × F much bigger than one, the output of this whole gadget will depend only on the input and the gain of the feedback path, F. The gain of that path might actually turn out to be a loss; if F is one-fifth, then Vout will be five times the amplitude of Vin regardless of the actual gain of the op amp we use to build it!

What's actually happening here is that we're comparing a part of the output to the input and getting a signal (V_a) which is a measure of how far off the output is from the desired signal. V_a is an "error volt-

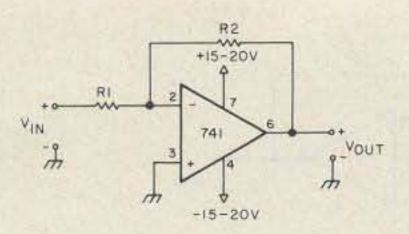


Fig. 5. An inverting amplifier.

age." If V_{out} were an exact copy of V_{in}, just five times bigger, and we compare V_{in} with one fifth of V_{out}, we would expect an error voltage of zero. This is how negative feedback controls the output of the stage.

As an example, look at Fig. 4. Here, F is one; all of the output is being fed back to the input. This says that the output will be an exact copy of the input. This circuit, called a non-inverting buffer, is useful for picking off a sample of a certain signal without loading down that signal's source-remember, the op amp has extremely high input impedance. If you'd rather get an inverted version of the signal, you can use the inverting amplifier circuit of Fig. 5, with R1 = R2. (Actually, Fig. 4 is a special case of the non-inverting amplifier shown in Fig. 6-it just has R2 = 0 and R1 infinite.)

Figs. 5 and 6 show how feedback is applied for the cases of inverting and non-inverting amps. Fig. 6, the non-inverting amp, is probably the easiest to understand: R2 and R1 form a voltage divider and the voltage across R1 is what is compared to the input. So, for this case, the F of our earlier equations is simply the voltage divider, and we can write Equation 7.

Equation 8, a rearranged Equation 7, is the usual way

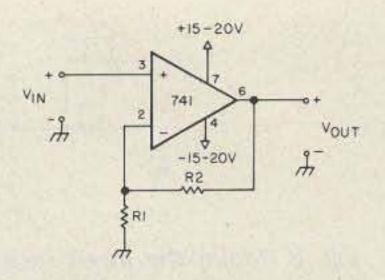


Fig. 6. A non-inverting amplifier.

of expressing the gain of this configuration. The inverting case is a bit more difficult to see since the feedback isn't in series with the input signal. But if you think of it in terms of current-the amount of current required through R2 to produce the same drop as a given amount through R1-then it looks like F will simply be the ratio of these resistances, and we get Equation 9. The minus sign shows up because this is an inverting amplifier-Vout is reversed from Vin. Notice that these circuits give us a quick and easy way to build voltage amplifiers with gains set simply by the proper selection of resistor values.

There are a couple of other things we can do with the inverting amp that you might be interested in. Since the gain is set by the ratio of the two resistors, we can use the circuit of Fig. 7 as a mixer. The output will be the sum of the input signals added in proportion to the ratio of their input resistor and the feedback resistor (see Equation 10). The input resistors might even be variable, as in Fig. 8, so that you can change the level of each signal simply by adjusting the proper potentiometer. This circuit could form the basis for an audio mixer for your home-brew PA system.

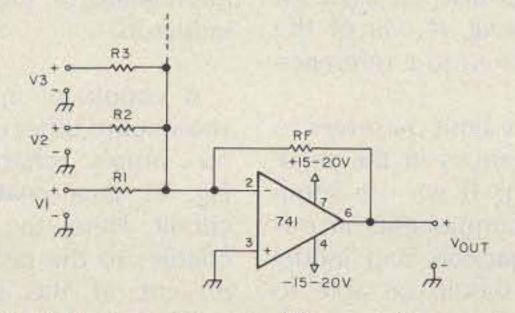


Fig. 7. An inverting amplifier used as a mixer.

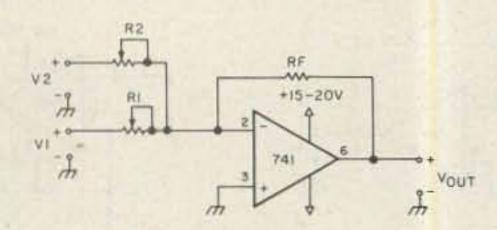


Fig. 8. Make the input resistors variable and you have the beginnings of an audio mixer.

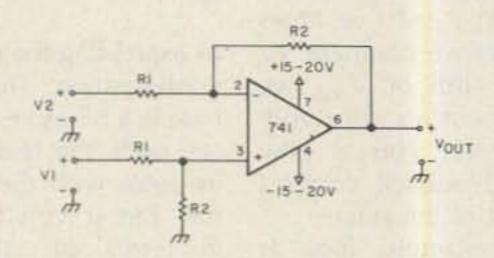


Fig. 9. A differential amplifier.

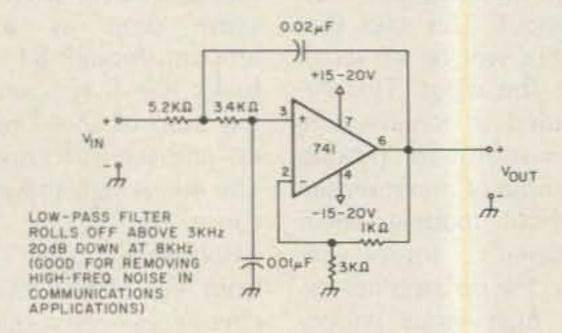


Fig. 10. A simple active filter.

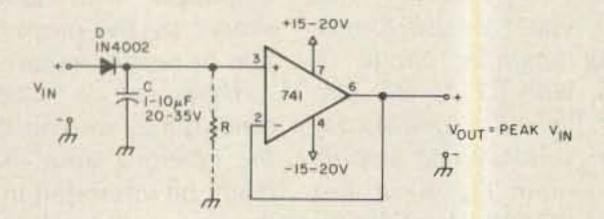


Fig. 11. A peak-detecting circuit.

Another interesting use for the op amp is the differential amplifier shown in Fig. 9. This circuit's output is related to the difference of the two input signals, V1 and V2. Note that the corresponding resistors on either side of the circuit are equal in value-R2A equals R2B, etc. The amplitude of the output is still set by the ratio of the resistances, and is expressed in equation II. This circuit can also be used for level shifting, if one of the inputs is fixed to a reference voltage.

But why limit ourselves to just resistances in the feedback loop? If we use some reactive components in this path (capacitors and inductors) we should be able to come up with a circuit whose output depends on the frequency of the input signal-in other words, a filter. Active filter design is a topic which can (and has) filled textbooks, but Fig. 10 shows a sample circuit to demonstrate the op amp's use in this area. Active filters turn out to be much simpler to design and build than their passive counterparts, due to the ease of isolating sections of the filter and the elimination of the need for inductors.

A couple of applications show some other uses of the op amp's characteristics. Fig. 11 is a peak-detecting circuit. Here, the capacitor charges to the peak voltage present at the input and stays there since it has no

place to discharge. Remember, the input impedance of the op amp is very high, so it doesn't present much of a path for discharging the capacitor.

You should recognize the way the op amp is connected here-it's just the buffer from Fig. 4. One might place a resistor across the capacitor so that the cap will eventually discharge. The bigger the resistor, of course, the longer the cap will take to discharge and the closer the output will remain to the peak value. This circuit can be useful in tailoring meter responses, such as slowing down the response of some of the new bar-graph displays so that you can follow them more easily.

This should give you some idea of how to use the op amp for various jobs, and maybe already you can think of some applications for the circuits I've shown. There are, though, a few practical considerations to keep in mind.

First, the op amp usually will require both positive negative supply voltages (though not alwayssee National Semiconductor's Linear Databook and Linear Applications Handbook). These supply voltages must not exceed the rating for the part you're using and will always limit the maximum amplitude allowed for the output. Make sure you're not asking for so much gain that you'd exceed this limit, or the output will clip at the maximum.

Also, while most modern op amps include some form of current limiting on the output, try not to use it. Keep your circuits running so that the op amp is running well within its maximum current-limit spec.

You should also be aware of the bandwidth and slew-rate limitations of the part you're using. Slew rate, usually expressed in something like volts per microsecond, is

a measure of how fast the output voltage can change. This will determine how well the op amp can track signals at high frequency.

Compensation is another subject that often comes up for discussions of op-amp circuits. Here, I'm going to have to refer you to the manufacturer's data sheet for the op amp you're using. Some parts are internally compensated, while others will require that some external components (usually a resistor and capacitor in series) be added for compensation. All compensation means is that the frequency response of the amplifier is being adjusted to ensure that it will operate properly over the desired frequency range. This can be tailored to suit the application, but for now you're safest sticking with the recommended compensation for the part you're using. The 709, for example, wants around 2000 pF and 1.5k Ohms in series across its compensation leads; the 741 is internally compensated and needs no external components.


As with most ICs, supply bypassing is always a good idea—and don't forget you've got two supplies to worry about. A ceramic capacitor from each supply lead to ground, say around 0.1 uF, should be about right. You might want to add more, maybe a 10- or 20-uF tantalum if you're a good distance from the filter caps in your power supply or if you run into noise or oscillation problems.

The applications for the operational amplifier are practically innumerable—so go right ahead and see what you can do with your own version of Op Art.

References

Linear Databook (1978) and Linear Applications Handbook (1978), National Semiconductor Corp.

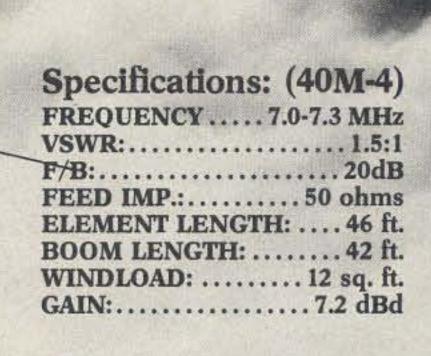Analysis and Design of Analog Integrated Circuits, Paul R. Gray and Robert G. Meyer, 1977, John Wiley and Sons, Inc.



Specifications: (15M-6)

BÂNDWIDTH: . . . 21.0-21.5 MHz

F/B: 30 dB

FEED IMP.:..... 50 ohms

ELEMENT LENGTH: 25 ft.

BOOM LENGTH: 36 ft.

WINDLOAD:......8.5 sq. ft. GAIN:..... 10.5 dBd

electronics, inc. Full Line Performance

The incredible performance of the World Class KLM 40M-4 is used by many DX'ers as a "Standard of Comparison" in Competitive Antenna Equipment.


Obviously, not everyone needs this type of Awesome performance, but its nice to know that the same performance proven design theory and quality construction have been carried over into our full line of quality antennas for all frequency ranges.



Specifications: (20M-6)
BANDWIDTH: 13.9-14.4 MHz
VSWR:1.5:1
F/B35 dB
FEED IMP.: 50 ohms
ELEMENT LENGTH: 37 ft.
BOOM LENGTH: 57 ft.
WINDLOAD: 12.8 sq. ft.
GAIN: 11 dBd

And there's more!

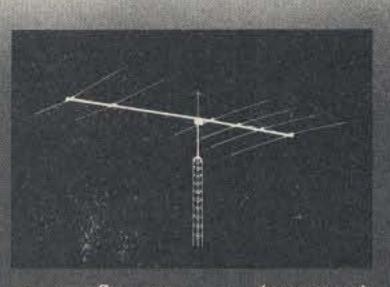See your local dealer or write to KLM, Electronics, P.O. Box 816, Morgan Hill, CA 95037.




Specifications: (30M-3)
BÂNDWIDTH: 10.1-10.150 MHz
VSWR:1.5:1
F/B20 dB
FEED IMP.: 50 ohms unbal.
ELEMENT LENGTH: 35'6"
BOOM LENGTH: 24'3"
WINDLOAD: 7 sq. ft.
GAIN: 7.0 dB



GAIN......3/7 dBd typical



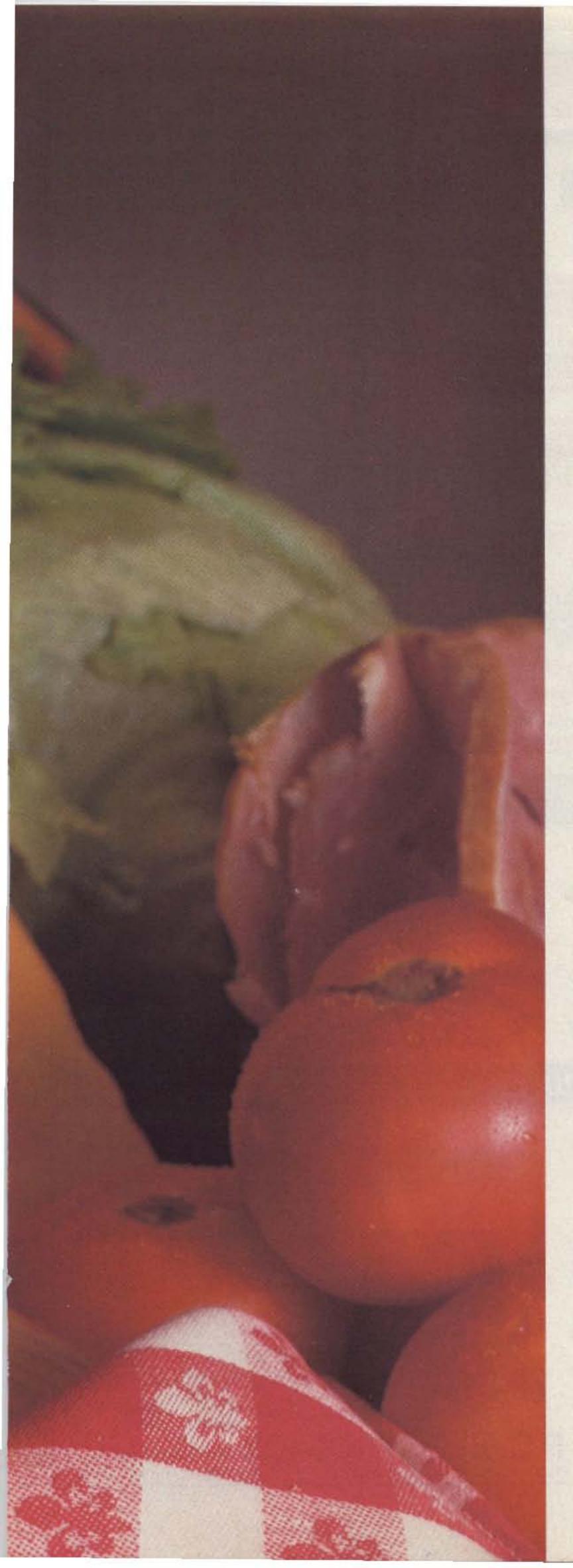

Food for thought.

Our new Universal Tone Encoder lends it's versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequency-just dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers repeaters; also, as a piece of test equipment to

or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.



- All tones in Group A and Group B are included.
- Output level flat to within 1.5db over entire range selected.
- · Separate level adjust pots and output connections for each tone Group.
- · Immune to RF
- · Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak.
- · Instant start-up.
- · Off position for no tone output.
- · Reverse polarity protection built-in.

Group A

	67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
1	71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
1	74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
1	77.0 XB	100.0 1Z	131.8 3B	173.8 6A
	79.7 SP	103.5 1A	136.5 4Z	179.9 6B
1	82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
1	85.4 YA	110.9 2Z	146.2 4B	192.8 7A
1	88.5 YB	114.8 2A	151.4 5Z	203.5 M1

- Frequency accuracy, ± .1 Hz maximum 40°C to + 85°C
- Frequencies to 250 Hz available on special order
- · Continuous tone

Group B


TEST-TONES:	TOUCH-TONES:		BURST TONES:			S:
600	697	1209	1600	1850	2150	2400
1000	770	1336	1650	1900	2200	2450
1500	852	1477	1700	1950	2250	2500
2175	941	1633	1750	2000	2300	2550
2805	21231		1800	2100	2350	

- Frequency accuracy, ± 1 Hz maximum 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Wired and tested: \$79.95





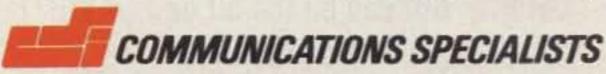

426 West Taft Avenue, Orange, California 92667 (800) 854-0547/ California: (714) 998-3021

REPEATER RC-850

of the Month



UPGRADE-ABILITY

The RC-850 Repeater Controller is unique - it's designed not to become obsolete. In a world of "planned obsolescence" a product designed for the future stands out. But designing high technology equipment to withstand the test of time requires foresight, experience, and commitment.

The '850 controller is designed to be upgraded through software and hardware. That means access to the latest technology and innovations, without getting left behind. The 850's original Version 1 software blew the socks off our competition. Version 2.0 blew the socks off our customers. Now our Version 3 software will have an unparalleled impact on your repeater.


The '850 represents years of experience in design of commercial microcomputer controlled repeaters. It's the first controller with remote programming. The first with synthesized speech. The first with scheduling, paging, mailbox, voice metering, and more. No one has as many features. Period.

At ACC, we're committed to preserving your investment in your repeater. And to bringing innovation, excitement, and fun to your group. With a full line of superior products. And support second to none.

We have set the standards for repeater control. Now we're raising them. The RC-850 Repeater Controller . . . leading the way.

MAKE YOUR REPEATER A WHOLE NEW ANIMAL WITH THE RC-850 REPEATER CONTROLLER

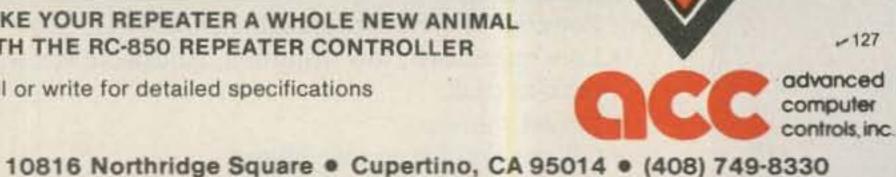
Call or write for detailed specifications





COMPLETE READY-TO-USE SYSTEMS

ATV TRANSMITTER/CONVERTER

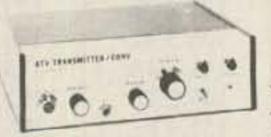


\$399

- High resolution and color video
- 10 watts output
- Broadcast standard sound
- TC-1 PLUS * Tunable downconverter and preamp

Connect to the antenna terminals of any TV set, add a good 450 MHz antenna, a camera and there you are . . . Show the shack, home movies, computer games, video tapes, etc.

ATV DOWNCONVERTER

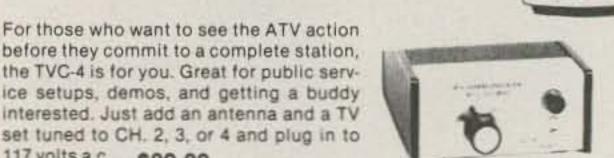

the TVC-4 is for you. Great for public service setups, demos, and getting a buddy interested. Just add an antenna and a TV set tuned to CH, 2, 3, or 4 and plug in to


For those who want to see the ATV action

117 volts a.c. \$89,00


TVC-4

TVC-4L extra low-noise version . . . \$99 delivered in USA

MODULES

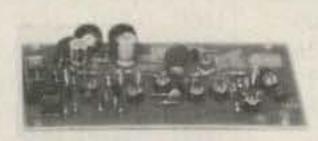

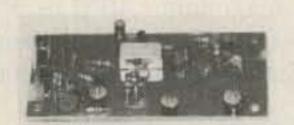TXA5-5 Exciter/Modulator \$89.00 ppd. Wired and tested module designed to drive PA5 10 watt linear amplifier. The 100 MHz crystal design keeps harmonics out of two meters for talk back. Video modulator is a full 8 MHz for computer graphics and color Requires 13 8 VDC reg @ 70 ma 80 mw output power Tuned with crystal on 439.25, 434 or 426.25 MHz Dual frequency model available Add \$15



TVC-2 ATV Downconverter \$49.00 ppd. Stripline MRF 901 preamp and double balanced mixer digs out the weak ones and resists intermed and overload. Connects between UHF antenna and TV set. Output channels 2 or 3. Varicap tuner 420 to 450 MHz Requires 12 to 18 VDC @ 20 ma

Extrasensitive TVC 2L with NE64535 preamp (.9 dB NF)\$59.00 ppd. Supersensitive TVC 2G with GaAs Fet preamp (.5 dB

Let P.C. put you on the air and SAVE! All four modules -Complete System price \$248.00 SAVE \$8.00 over price if purchased individually



FMA5 Audio Subcarrier Generator . \$29.00 ppd. Puts audio on your camera video just as broadcast does at 4.5 MHz. Puts out 1 V p-p to drive TXA5. Requires low Z mike, 150 to 600 Ω and 12 to 18 VDC @ 25 ma. Works with any transmitter with 5 MHz video band-



Tom W6ORG

PA5 10 Watt ATV Power Amplifier . \$89.00 ppd. The PA5 will put out 10 watts RMS power on sync tips when driven with 80 mw by the TXA5 exciter, 50 ohms in and out plus bandwidth for the whole band with good linearity for color and sound. Requires 13.8 VDC reg. @

Call or write for our complete catalog of specifications, station setup diagrams, and optional accessories which include: antennas, modulators, test generators, cameras and much, much more. See Ch. 14 1983 ARRL Handbook.

TERMS: VISA or MASTERCARD by telephone or mail, or check or money order by mail. All prices are delivered in USA. Charge orders normally shipped within 24 hours. Personal checks must clear first.

(818) 447-4565



P.C. ELECTRONICS 2522 Paxson Lane

Maryann WB6YSS

Arcadia, California 91006

Put the DX World on a Screen

Everything you need to know about a country can be at your fingertips. All you need is a VIC-20 and this program.

ow many times have you been sitting at your receiver listening to the DX come in when you suddenly heard a prefix that you couldn't identify at all? Well, if you own a VIC-20 with at least an 8K expansion cartridge or an Apple II Plus, your worries are over. With this program, all you have to do after loading it is enter the prefix at the keyboard and a variety of pieces of helpful information will appear on your screen.

Immediately available to you will be the name of the country, its latitude and longitude, prefix, antenna bearings, and distance in miles and kilometers. At the touch of another key, the computer will check for any other country listed by the same prefix. If you still are unsure of the location of the country, the computer can indicate which countries border the one in question.

In the Apple program, many of the major cities in the United States and around the world are included in the data so that you can determine exactly how far it is to New York, Denver, Colorado, or even Paris, France. In the program for the unexpanded VIC, only major US cities have been included in the data. A useful feature of this program is that the user can customize it for individual needs. If you are a VHF enthusiast, you can enter cities located within your listening radius.

Adaptability

The locator program can be adapted to almost any size of memory from the VIC-20's small 3.5K to the Apple II Plus with its 48K. I have found that in order to get all the prefixes in the world excepting the US, one needs at least 11773 bytes, or 12K of memory.

With this program, bearings and distances can be figured by the latitude and longitude on the keyboard. In this mode, the computer can perform a search and identify the countries located around your coordinates. Another feature of this program is that if you enter the name of a country or island on the keyboard, the com-

puter can tell you where the country is, its prefix, antenna bearing, and distance. At the touch of a key, the country's alternative prefix is provided, if it has one.

Program Run

After loading the program, type in the RUN command. At this time you will be presented with the following main menu with four selections: (1) Country or City, (2) Prefix, (3) Latitude and Longitude, and (4) Quit.

For our first example, let's take selection (1). Keystrokes: 1<RET>. Now you will be asked to enter the name of a country or city. Enter the name of the country in question. For our purpose, enter ITALY. Keystrokes: ITALY <RET>. The screen will clear. Then the flashing prompt SEARCH-ING DATA will appear. If the information is not found, the screen will clear, a prompt will say END OF DATA, and the program will return you to the main menu. If the data is found, the screen will clear and the information will appear.

First will be the name of the country. Next will be the latitude and longitude, followed by the prefix, antenna bearings, and the distance in miles or kilometers. At the bottom of your screen will be the prompt (F7)=SEARCH DATA OR HIT ANY KEY. If you press any key, you will return to the main menu. If you press the F7 key, the computer will search for any other listings for the country entered. If there are none, the program will return to the main menu. If there is another prefix, the alternative prefix and the country's data will be provided.

Now let's go back to the main menu again. Let's pick the second selection. Keystrokes: 2<RET>. You will now be asked for a prefix. For our example, let's use TT. Keystrokes: TT<RET>. Again the screen will go blank and the prompt SEARCHING DATA will appear. When the data is found, the prompt will stop flashing, the screen will clear, and the information for the Republic of Chad will appear. If you press the

F7 key, the computer will search for any other countries listed by the prefix TT. Finding none, the computer will return to the main menu.

For the third selection, 3<RET>. The keystroke screen will clear and then a prompt will appear asking for latitude. If it is a north latitude, enter the number as a positive number. If it is a south latitude, enter it as a negative number. For example, let's use negative 45 degrees. Keystrokes: -45 <RET>. If you enter a number larger than 90 or less than negative 90, you will get an error message and be asked for the information again. The program, as we say in computer language, will not crash.

After you have entered the latitude and pressed the Return key, another prompt will appear requesting the longitude. Enter east longitude as a positive number and west longitude as a negative number. For our example, enter a positive 120 degrees. Keystrokes: 120 < RET >. The computer will not accept any number larger than a positive 180 or less than a negative 180. A prompt will appear to ask you if your data is correct. Enter either a 1 for Yes or 2 for No. If you type a 2, the program will ask you for the correct latitude and longitude.

Our data is correct so you can press 1. The screen will display the latitude and longitude, the antenna bearings, and the distance in miles to the coordinates you have entered. At the bottom of the screen you will find the prompt (F7)=SEARCH DATA OR HIT ANY KEY. Any key will return you to the main menu. If you press the F7 key, this screen will first clear and this prompt will appear. I WILL SEARCH MY FILE FOR DATA ON LOCATION NEAR YOUR COORDINATES. HOW WIDE OF SEARCH IN DEGREES? You can enter any number between 1 and 360. Let's enter 20. Keystrokes: 20<RET>. The computer will go through its data file and locate any coordinates within 20 degrees of the search area. If the computer finds any country around the entered coordinates, it will stop the search and print the data on the screen. If you press the F7 key again, it will continue the data search for another country around your coordinates. When the program comes to the end of the data file, the screen will clear and the prompt END OF DATA will appear and return you to the main menu.

The last selection on our menu is number 4. I do not think this needs any explanation.

Now that we have been through the programs, let me point out a few things. First, when entering a city or country name, it must be spelled correctly. If the country in question is an island, it needs to be entered as such, e.g., CAICOS 15. Secondly, when entering south, north, east, or west, there should be no space between the abbreviation, the period, and the name, e.g., W.SAMOA. Whenever the word Saint is used, it should be abbreviated as ST, e.g., ST. VINCENT IS. This is done to conserve as much memory for data statements as possible.

I chose Basic for the program because of the language adaptability, and this makes it easy for the user to customize the program for special needs. A big gun DX-er may want prefixes from around the world while the net operator may want only cities across the nation.

The program design is as simple as I could make it to accommodate a lack of memory. Rewriting the program for the Sinclair, Atari, or the TRS computers should not be difficult. As you look through the listing, you will notice a few special characters. These generally concern the screen display. For a definition of some of the VIC special characters, refer to the sample run accompanying this article.

For a look at how the program works, start at line 10. Line 10 is where the main menu is printed. Line 24 is a very important line. This is where the user puts his information concerning his location. CLR will clear all variables. RESTORE returns the data pointer to the start of the data statements. The variable A is the latitude of the user's QTH. L1 is the variable for the user's longitude and SP\$ is the name of the user's city and state. Line 25 is the input line for your selection from the main menu and line 26 sends the program on its way.

Line 50 is the start of the routine for entering the name of the city or country. C\$ is the name of the country we are looking for. Line 55 is the gosub that sends the program to the read statement and a line of data is then read. After the data is read and the variables Z\$ prefix, L\$ name of the city or country, B latitude, and L2 longitude are filled in, then the program compares the L\$ and the C\$. If the L\$ and C\$ are the same, the program goes to subroutine 500 and then to line 200, the display routine. If the variables are different, the computer reads another line of data.

Line 57 checks to see if all data has been looked at. If it has, the program goes to line 250 and does an end-of-data routine. Lines 60 through 64 work the same as lines 50 through 58 except that the variables H\$ and Z\$ are compared for a match.

Lines 70 through 84 are the routine for entering the latitude and the longitude. Lines 85 through 110 are the area where I put the gosubs. Line 85 is the error message for whenever the user inputs data the computer cannot use. Line 100 is the flashing SEARCHING DATA prompt and the read statement. Line 110 is a delay loop.

Lines 200 through 227 contain the routine which displays the information

after it has been processed by the math subroutine located on lines 500 through 900. Line 200 prints the value of L\$, the name of the state or country. Line 201 prints the latitude, B. Line 202 prints the longitude, L2, and line 205 prints the prefix, Z\$. Line 210 prints antenna bearings, R2, derived from the math routine. Line 215 prints the name of the starting point, home QTH, and the distance in miles from SP\$. Line 220 prints the distance in kilometers from SP\$. Line 224 prints the prompt at the end of the display, (F7)=SEARCH DATA OR HIT ANY KEY.

At this prompt, the program waits for you to press a key. If you press the function key, F7, the program will go into the search routine depending on what selection you choose from the main menu. Lines 227 through 230 take care of this function. If you press any other key, the program will return to the main menu, line 232,

Lines 235 through 244 are the search routine used for main menu selection number 3, the latitude and longitude. Line 239 checks for the end of data. Lines 240 through 243 filter the value of the latitude and longitude read in the data statement. If all conditions are met, the value of the variables is filled from the math routine (lines 500 through 900) and forwarded to the display routine. Line 250 is the executed line whenever the data read statement reaches the end of the data (line 3000).

Math Routine

The math routine was derived from two sources, the ARRL Antenna Handbook and a math routine used in a program published in The Giant Book of Computer Software (1st Ed., pp. 264-265). I made a lot of changes in order to save memory, but basically it works the same. The math routine is

```
1 PRINT" INNINGRAL OCATOR PROGRAM (C)82" PRINT"BY E. MORGAN" GOSUB110
10 PRINT"3 **MAIN MENU**": PRINT" XXXHOW DO YOU WANT ME TO LOCATE DATA?"
15 PRINT"XXXI..COUNTRY OR CITY" PRINT"XX..PREFIX" PRINT"XX..LAT.& LONG. " PRINT"XX
...QUITO
24 CLR RESTORE A=41.14 L1=-111.58 SP#="DGDEN, UTAH"
25 PRINT"N" INPUTE
26 ONEGOTO50,60,70
31 IFE=4THENPRINT"," END
35 GOT025
50 PRINT"COMMENTER COUNTRY OR CITY." INPUTC$ IFC$="£"THEN10
55 GOSUB100
56 TFL ##C#THENGOSUB500 GOT0200
57 IFZ*="END"THEN250
58 GOTO55
60 PRINT" TENTER PREFIX" INPUTH$ IFH$="£"THEN10
61 GOSUB100
62 IFZ#=H#THENGOSUB500:GOTO200
63 IFZ$="END"THEN250
64 GOT061
70 PRINT" LATITUDE?" INPUTB IFB>900RB<-90THENGOSUBS5 GOTO70
77 PRINT M. ONGITUDE?" INPUTL2: IFL2>1800RL2<-180THENGOSUB85 GOTO77
78 PRINT"MIS YOUR INPUT CORRECT" PRINT"1=YES 2=NO" INPUTW
79 ONWGOTO84,70
84 PRINT"7" GOSUB500 GOTO201
85 PRINT" DERROR" GOSUBIIO RETURN
100 PRINT"INDUMUMUM SEARCHING DATA!" READZ$, L$, B, L2 RETURN
110 FORT=1T03000 NEXT RETURN
200 PRINT"DM"L#"=".
201 PRINT"MLATITUDE "B
202 PRINT"LONGITUDE "L2
205 PRINT"MPREFIX: "Z$
210 PRINT" XIBEARING: "R2
215 PRINT"MUDISTANCE FROM " PRINTSP$"M" PRINTD1" MILES"
220 PRINT"M"D2" KILOMETERS"
224 PRINT"MMM(F7)=SEARCH DATA OR
                                      HIT ANY KEY. "
226 GETS$ IFS$=""THEN226
227 PRINT"D" IFS#=CHR#(136)ANDE=3THEN235
228 IFS#=CHR#(136)ANDE=2THEN61
229 IFS$=CHR$(136)ANDE=1THEN55
230 IFS#=CHR#(136)ANDE=0THEN238
235 PRINT"IN WILL SEARCH MY FILE FOR DATA ON LOCATION NEAR YOUR CORDINATE."
236 PRINT WHOW WIDE OF SEARCH IN DEGREES?" INPUTOX
237 ZB=B:ZL=L2
238 GOSUB100
239 IFZ#="END"THEN250
240 IFB>ZB+0%THEN238
241 IFBCZB-QXTHEN238
242 IFL2>ZL+QXTHEN238
243 IFL2KZL-Q%THEN238
244 E=0:G0SUB500:G0T0200
250 PRINT"IM END OF DATA!" GOSUB110:GOTO10
500 A1=A*# /180 L=L2-L1 X=0
510 TFL <- 180THEN525
515 IFL>180THEN535
520 GOTO540
525 L=L+360 GOTO610
535 L×L-360
540 IFL COTHEN610
610 B1=B*#/180 L=L*#/180 P=COS(L)*COS(R1)*COS(B1)+SIN(R1)*SIN(B1)
625 P1=ATN(SQR(1-P*P)/P) P2=P1*180/m
635 IFP2<000T0645
640 GOTO650
645 P2=P2+180
650 D1=INT(P2*60*1.15152+.5):D2=INT(D1*1.6093+.5)
655 R=COS(B1)*SIN(L)/SIN(P1) R1=ATN(R/SQR(1-R*R)) R2=INT((R1*180/m)+.5)
670 IFABS(R)),999998THEN800
675 TEABS(R) (.00174THEN850
680 B2=(B+.1)*#/180 R3=COS(L)*COS(H1)*COS(B2)*SIN(B2)*SIN(H1)
690 R4=ATN(SQR(1-P3*R3)/P3) R6=CQS(B2)*SIN(L)/SIN(R4)
PRS IFX=1THEN740
710 IFABS(R6))ABS(R)THEN730
715 R2=360-ABS(R2) GOTO900
730 R2=180+ABS(R2) GOTO900
740 IFABS(R6) (ABS(R) THEN755
745 R2=180-ABS(R2) G0T0900
755 R2#AB8(R2) GGT0900
800 IFX=1THEN830
810 82=270 0010900
830 R2=90:50T0900
850 IFABS(L)>178THEN870
855 IFBCATHEN865
860 R2=0:GOT0900
865 R2=180 GOT0900
870 IFBOATHEN865
875 GOTO860
900 RETURN
1000 DATAAC4, SIKKIM. 32, 83, AP, PAKISTAN, 31, 88, AZ, BOTSNANA, -22, 24, ZS9, BOTSWANA, -22,
     DATAR35, TONGA, -21, -175, 84, DMAN, 20, 58, 85, BHUTAN, 27, 90, AC5, BHUTAN, 27, 90
1001
1892 DATAR6, UNITED ARAB EMIRATES: 24.54, 87, QATAR: 25,51, 89X, BAHRAIN: 26,50
1003 DATAR9X, BAHAIN, 26, 50, BV, TAIWAN, 23, 121, BY, CHINA, 35, 105, CE, CHILE, -30, -71
1884 DATACEGA, EASTER IS. 1-21:-177 CEBX, SAN FELIX IS. 1-26:-80
t005 DATACE0Z.JUAN FERANDEZ IS.,-33,-79,CM,CUBA.21,-80,CO,CUBA.21,-79
1006 DATACH, MOROCCO 32, -5, CP, BOLIVIA, -15, -65, CR3, GUINEA BISSAU, 12, -15
1887 DATAJ5, GUINEA BISSAU, 12.-15, CR5, PRINCIPE IS., 1, 7,89, PRINCIPE IS., 1,7
1008 DATACRS.SAO TOME [8. 12.6.59.SAO TOME IS., 12.6.CR8.TIMOR IS., -10.125
1010 DATACT3 MADEIRA IS. 32,-16.5 CX URUGUAY -33,-56 C2 NAURA IS. -. 3,166.5
1011 DATAVK9 NAURA IS. -. 3 166.5 C3 ANDORRA IS. 42 1 FX ANDORRA IS. 42 1
1012 DATACS GAMBIA: 13 .-15.ZD3.GAMBIA: 13.-15.C6.BAHAMA IS.:25:-75
1013 DATAVPZ, BAHAMA IS., 25, -75, C9, MOZAMBIQUE, -18, 35, CRZ, MOZAMBIQUE, -18, 35
1014 DATAD, W. GERMANY, 51, 9, DM. E. GERMANY, 52, 12, Y2-Y9, E. GERMANY, 52, 12
1015 DATADU PHILLIPPINES. 12, 125 DX. PHILLIPPINES. 12, 125, D2, ANGOLA, -12, 18
1016 DATAD3.ANGOLA:-12:18:D4.CAPE VERDE:16:-24:EA:SPAIN:40:-4
1018 DATAEA9, MELILLA, 35, -2, EI, IRELAND, 53, -8, EL, LIBERIA, 6, 9, EP, IRAN, 33, 55
1019 DATAET, ETHIOPIA, 9, 39, F, FRANCE, 46, 2, FBSN, CROZET IS. -46, 53, FBSX, KERGUELEN IS
 -49,69
1020 DATAFBSZ ST. PRUL & AMSTERDAM IS. -38.73 FC CORSIA.42,9 FG7 GUADELOUPE.16.-6
```

1021 DATAFH, MAYOTTE 18, -12.5, 45, 56, COMORO 18. -12, 44, FK8, NEW CALEDONIA, -21, 165

1024 DATAFPS ST. PIERRE 13. 46.5, -56, FP8, MIQUELON IS. 47, -56, FR, REUNION IS. -21, 55

1025 DATHER GLORIOSO IS. -9.51 FR JUAN DE NOVA IS. -17.42.5 FR TROMELIN IS. -15.

1826 DATAFS ST. MARTIN IS. 18,63 FB ST. MARTIN IS. 18,63 FW8 WALLIS & FUTUNA IS. >-

1028 DATAGI, N. IRELAND, 55, -8 GT, JERSEY IS. 49, -2 GC, JERSEY IS. 49, -2 GM, SCOTLAND,

1822 DATAFLS, DJIBOUTI, 11, 43, J2, DJIBOUTI, 11, 43, FMZ, MARTINGUE, 14, 4:-61

1027 DATAFY7 FRENCH GUIANA 4.-51.6 ENGLAND 52:-1.6D ISLE OF MAN 54.-4

1023 DATAFOS FRENCH POLYNESIA -18 -149, FOS CLIPPERTON IS. , 10 ,-109

performed only when there is a match between what is input by the operator (lines 50 and 60) and what is read in line 100 or when latitude and longitude are entered, main menu selection number 3 (lines 70 through 84).

Line 500 converts A to radians. Lines 510 through 545 determine the value of L and send the program to the correct place as determined by that value. The variable X is used to test the value of L. The first part of line 610 con-

18, -11, -61

3000 DATREND. 0.0.0

```
1032 DATAHH, HAITI-18,-72,5, HI, DOMINICAN REP. 19,-70, HK, COLOMBIA, 5,-75, HM, KOREA, 3
1033 DATAHKO, PROVIDENCIA IS., -9,51, HKO, MALPELO IS., 3.6, -81.4, HL, KOREA, 37, 127
1834 DATAHKO SERRANE BANK & RONCADOR CAY, 14, -80, KP3, SERRANE BANK & RONCADOR CAY,
1835 DATAKS4. SERPANE BANK & RONCADOR CAY 14 -80 HK0, SAN ANDRES IS. 13, -83
1036 DATAHP, PANAMA, 9, -80, HR. HONDURAS IS., 15, -86, HR, SWAN IS. /44, -68, 2, HS, THAILAND
1037 DATAHV. VATICAN CITY: 41.54.12.27.HZ. SAUDIA ARABIA: 25.45.72. SAUDIA ARABIA: 25.
1038 DATAI ITALY 42 12 IT STCILY 37,14 IS SARDINIA 40,9 IM SARDINIA 40,9 1039 DATAJA-JN JAPAN 35 139 JD OGASAWARA IS 28 142 KAI OGASAWARA IS 35,5 139.5
1848 DATAJD MINAMI-TORI-SHIMA IS. 24 154 KB1 MINAMI-TORI-SHIMA IS. 24, 154
1941 DATAJT MONGOLIA 46.100 JW SVALBARD IS. 78.5,16 LA SVALBARD IS. 78.5 16
1842 DATALP SVALBARD IS. 78.5 16 JX JAN MAYEN IS. 72 -9 LA JAN MAYEN IS. 72 -9
1043 DATALP JAN MAYEN IS. 72 -9 JY JORDON 31 36 KB BAKER IS. . . 1,178 KH1 BAKER IS
...1.178
1045 DATAKB HOW AND IS. 1 -178 KHI HOWLAND IS. 1 -178 KC4 NAVASSA IS. 19 -75
1846 DATAKPI NAVASSA IS. 19 -75 KC6 CAROLINE IS. 8 148 KG4 GUANTANAMO BAY 28.1.
1047 DATAKOS MARIANA IS. 15,145,KH0 MARIANA IS. 15,145,KG6,GUAM IS. 13,144.5
1048 DATAKH2.GUAM IS., 13.144.5.KH6.HAWAII IS., 20.-157.5.KH7.KURE IS., 27.-178
1049 DATAKJ6, JOHNSTON IS. 17, -169 KH3, JOHNSTON IS. 17, -169
1050 DATAKM6, MIDWAY IS. 28.-177, KH4. MIDWAY IS. 28.-177, KP4. PUERTO RICO, 18,-66.5
1051 DATAKP6 KINGMAN REEF 7 -163 KH5 KINGMAN REEF 7 -163 KP6 JARVIS IS. -. 4 -160
1852 DRTAKP6 PALMYRA IS. 6,-163 KS6 AMER. SAMOA, -14, -170.5 KH8 AMER. SAMOA, -14, -17
0.5
1053 THATAKV4 VIRGIN IS. 17.4 -65 KW6 WAKE IS. 19 166.4 LA NORWAY 62 10
1054 DATAKH9 WAKE IS. 19.166.4 KX6 MARSHALL IS. 10.170 LB NORWWAY, 62, 10
1055 DATALE NORMAY 62,10, LG NORMAY 62,10, LJ NORMAY 62,10, LU, ARGENTINA -40,-65
1056 DATALX, LUXEMBOURG, 49.5, 6, LZ, BULGARIA, 43, 25, M1, SAN MARIND, 43.6, 12.3
1057 DATACH, FINLAND, 64, 26, OF FINLAND, 64, 26, CHO, ALAND 15, ,60, 1, 20, CJØ, MARKET REEF
1858 DATROK CZECHOSLOVAKIA 50.19, ON BELGIUM 58, 4, 0X, GREENLAND 70 -40
1059 XP, GREENLAND, 70, -40,09, FREROES IS. 62, -7,02, BENMARK, 56,10, PA, NETHERLANDS, 52
1060 DATARD NETHERLANDS, 52, 5 PE NETHERLANDS, 52, 5 PI NETHERLANDS, 52, 5
1861 DATAPJ NETHERLANDS ANTILLES IS. 12.-69.PJ ST.EUSTATIUS, 12,-69.PJ SABA IS. 1
1062 DATAKP2.VIRGIN IS., 17.4, -65, PJ, ST, MAARTEN IS., 12, -69, PY, BRAZIL, -10, -50
1063 DATAPYO TRINDADE &MARTIM IS. -20.3.-29.PYO,ST.PETERS & ST.PAULS ROCK,2,29.5
1864 DATAPYR FERNANDO DE NORANHA IS. -3.5/32/PZ/SURINAM/5/-55/P2/NEW GUINEA/-7/1
1065 DATASK, SWEDEN, 62, 15, 9L, SWEDEN, 62, 15, SM, SWEDEN, 62, 15, SP, POLAND, 52, 19, 3Z, POLA
ND 52 19
1866 DATAST, SUDAN, 15.38.SU. ECYPT, 27.38, SV. GREECE, 39.22.SV. GRETE, 35.24.5
1867 DATASV, DODGECANESE IS., 36.6, 26.82, BANGLADESH, 24, 98, TA, TURKEY, 39, 35
1068 DATATE ICELAND 65.-18.TG GUATAMALA 15.-90.TI COSTA RICA 10.-85.TI9.COCOS IS
1969 DATATJ CAMEROON 6,12,TL CENTRAL AFRICAN REP. 7,21,TN CONGO -1,15,TR GABON -
1.11.5
1070 DATATT CHAD 15:19 TU IVORY COAST 8 -5 TY BENIN 9:2 TZ MALI 17:-4 UA U.S.S.R
...55 88
1071 DATAUK, U.S.S.R., 55,80, UT, U.S.S.R., 55,80, UB, U.S.S.R., 55,80, UY, U.S.S.R., 55,80
1072 DATAVE.CANADA.60.-95.VY.CANADA.60.-95.VK.AUSTRALIA.-25.130
1973 DATARK, AUSTRALIA, -25, 130, VK2, LORD HOWE IS., -31.3, 159, VK9, NORFOLK IS., -29, 16
1074 DRTAVK9 CHRISTMAS IS. -10.105.VK9.COCOS IS. -12.5.97.VK9.MELLISH REEF. -17.
1075 DATAVKO HEARD IS., -63,74,VKO MACQUARIE IS. -63,74,VKO MCDONALD IS., -54,74
1076 DATAVO1:NEW FOUNDLAND:52:-56:VO2.LABRADDR:54:-62:V3:BELISE:17:-88:J3:GRENAD
1077 DATAV2.ANTIGUA & BARBUDA.17.-61.5,VP2A.ANTIGUA 6 BARBUDA.17.-61.5
1078 DATAJ7.DOMINICA IS. 15.-61.VP2D.DOMINICA IS. 15.-61.VP2E.ANGUILLA IS.,18.-6
1079 DATAYP2K,ST.KITTS & NEVIS IS./17,-64.5,VP2L/ST.LUCIA IS./15.5/-61
1080 DATAJ6, ST. LUCIA IS. 15.5, -61, VP2M, MONTSERRAT IS., 16.5, -62.1, J8, ST. VINCENT I
1081 DATAVP2S.ST.VINCENT IS..13.-61.VP2V.BRITISH VIRGIN IS..18.-64.VP5.TRUK IS..
21.5 -71
1082 DATAVP5,CAICOS IS.,21.5,-71,VP8,FALKLAND IS.,-51,-60,LU,FALKLAND IS.,-51,-6
1083 DRTAVP8 S. GEORGIA IS. . +54. -36.5.LU-LZ.S. GEORGIA IS. . -54. -36.5
1884 DRTAVPS, S. DRKNEY IS. . -61, -45, LU-LZ, S. DRKNEY IS. . -61, -45
1985 DATAVP8 S.SANDWICH IS. -58.-38.LU-LZ.S.SANDWICH IS. -58.-38
1086 DATAMPS.S. SHETLAND IS. -65.-65.LU-LZ.S. SHETLAND IS. -65.-65.MP9.BERMUDA IS.
32, 464
1087 DATAVOS CHAGOS IS. -8.73.V09.SEYCHELLES IS. -4.55.S7.SEYCHELLES IS. -4.55
1988 DATAVRI, GILBERT & DOEN 15. .-. 5.169. T30. GILBERT & DOEAN IS. .-. 5.169
1989 DATAMPT PHOENTY IS: -4.-171.T31 PHOENIM IS: -4.-171.VR3.LINE IS: -5.-154
1090 DATAT32: LINE 19. -5.-154. VR4. SOLOMON IS. -8.159. H4. SOLOMON IS. -8.159
1891 THTEVRE PITCHTRN IS . -25 .- 130 VRS TUVALA IS . -8,178 VS5 BRUNEI . 4,114
1092 DATAVS6.HONG KONG.72.1.114.VS9.KAMARAN IS. 15.42.VU.INDIA 23.80
1893 DATAVU7. ANDAMAN KNICOBAR IS. 12,92, VU7. LACCADIVE 18, 10,73 XE, MEXICO, 23,-10
1094 NATAMERICO.23 -102,48 MEXICO,23 -102.6D MEXICO,23 -102
1895 DATAXE4 REVILLAGIGEDO IS. 19 -111.3 604 REVILLAGIGEDO IS. 19 -111.3
1096 DATANT, VOLTAIC REP. 12 -1 XU CAMBODIA 13 105 XV5 VIETNAM 16 108
1097 DATAXW8.LADS.18.105.XZ.BURMA.22.98.YA.AFGHANISTAN.33.65.YB.INDONESIA:-5.120
1098 DATAYS,EL SALVADOR,13.5,-88.5,YU,YUQOSLAVIA,44,19,YT,YUGOSLAVIA,44,19
1099 DATAYV, VENEZUELA 8 - 66.4M. VENEZUELA 8 - 66. YVO. AVES 13. 12 - 67.3 ZA ALBANIA
41,20
1100 DATAZB2.6189ALTAR.36 5.ZD7.ST. HELENA IS. 15.6.-5.4.ZD8.ASCENSION IS.,-5.6,-
tio: betazog.jp:steN be gunhe,-37,-12,ZD9,GOUGH IS.,-40,-9,ZE,ZIMBABWE,-20,30
1102 DATAZ2.ZIMBABWE.-20.30.ZF1 CAYMAN IS. 19.-80.ZK1.COOK IS. -20.-158
1183 DATAZK2, NIUE 18. -19. -169. 5. ZL, NEW ZEALAND -41. 174
1104 DATA2L CHATMAN IS. -44 -176 ZL AUCKLAND IS. -52 176 ZL CAMPBELL IS. -53 169
105 DATAZL.KERMADEC IS. -31.-178.5.ZM7.TOKELAU IS.,-8.-173.ZP.PARAGUAY.-23.-58
1186 DATAZS, S. AFRICA, -38 26 ZS2 PRINCE EDWARD 18. -47,38 ZS2 MARION 18. -47,38
1107 DATAZS3 NAMIBIA -22,17,18 SOVERIGN MILITARY ORDER OF MALTA 35.5,14.3
1108 DATAIS SPRATLY IS. 8.112.3A.MONACO.43.5.7.3B6.AGALEGA IS., -10.56.4
1109 DATA3B7.ST. BRANDON IS. -17.69.3B8.MAURITIUS IS. -20.57.3B9.RODRIGUEZ IS. -1
9 64
1118 DATASC EDUATORIAL BUINEA 2,18 EAR EQUATORIAL GUINEA 2,10,3D2 FIJI IS.,-18,1
1111 DATAVR2.F131 IS.,-18,175.3D6,SWAZILAND,-26,31,Z87,SWAZILAND,-26,31
1112 DRTAZD5 SWAZILAND.-26.31.3V8.TUNISIA.34.9.3X.REP.OF GUINEA.11.-10
1113 DATAZO REP OF GUINER 11 -18/39 BOUVET IS. -54/5 LA-LG BOUVET IS. -54/5
1114 DATA4S7 SRI LANKA 7.81.300 ANNOGON IS. -2.6.40/ITU NEW YORK 40.4 -74
1115 DATA4U1. ITU GENEVE 46.6.4W N. YEMAN 15,44,4% ISRAEL 31,35,4Z ISRAEL 31,35
1116 THTA5A.LIBVA.27.17.584 CYPPUS.35.33.ZC4 CYPRUS.35.33.5H3.TANZANIA.-6.35
1117 DATAMOS TANZANIA, -6.35.5NZ NIGERIA, 10.8 ZDZ NIGERIA, 10.8 5R8 MADAGASCAR, -19
1118 DATAFFS, MADAGASCAR, -19,46,5T, MADRITANIA, 20, -12,5U7, NIGER, 16,8,5V, T000,8,1
1119 DATASWI, W. SAMOR: -13, 5, -172, SX, UGANDA: 1, 32, VQ5, UGANDA: 1, 32, 5Z4, KENYA: 1, 38
1120 THTAYO4 KENYA 1.38 BU SOMALI 10.49 GWS SENEGAL 14 -14 6Y5 JAMAICA 18,-77
1121 DATAMPS, JAMAICA, 18, -77, 70, 5, YEMAN, 15, 48, VS9A, S, YEMAN, 15, 48, 7PS, LESOTHO, -29,
1122 DATAZSB.LESDTHO.-29.28.70.MALANI.-13.34.ZD6.MALANI.-13.34
1123 DATAZY ALGERIA 28.3 FA ALGERIA 28.3 BP BARBADOS IS. 13.-59. VP6 BARBADOS IS.
1124 DATASO MALTIVE IS, 3.73. VS9M MALDIVE IS, 3.73.8R GUYANA, 5, -59
1125 DATAVP3 GUYANA 5 -59 824 SAUDI ARABIA & IRAG NEUTRAL ZONE 30 43 9G1 GHANA 8
1126 DATAZDA, GHANA 8 -2 TAB MALTA 35,5 14,4 VQ2 ZAMBIA -15,30,9J,ZAMBIA,-15,30
    DATA9K2, KUWAIT, 29, 47, 5, 9L1, STERRA LEONE, 8, -11, 9M2, W. MALAYSIA, 5, 102
1:28 DATASM4, W. MAN AYSIA, 5, 102, 9M6, E. MALAYSIA, 5, 117, 9M8, SARAWAK, 4, 115, 9M1, NEPAL, 2
```

1029 DATAGLI GUERNSEY IS., 49, -2, GC, GUERNSEY IS., 49, -2, GW, WALES, 52, -3

7.9,4

1030 DATAHA, HUNGARY, 47, 20, HG, HUNGARY, 47, 20, HB, SWITZERLAND, 47, 8, HE, LIECHENSTEIN, 4

1031 DATAHBU LIECHENSTEIN 47.9.4 HC ECUADOR 0.-78 HCS GALAPAGOS IS.,-.3,-90.3

1129 DATA905, ZAIRE, -4.25, DQ5, ZAIRE, -4.25, 9U5, BURUNDI, -3.30, 9V1, SINGAPORE, 1.2.103

1 30 DATASK RUANDS -2.30 944 TRINIDAD & TOBAGO IS. 11 -61 VF4 TRINIDAD & TOBAGO

RUN Type: HOW DO YOU WANT ME Display: **MAIN MENU** -45<RET> TO LOCATE DATA? Type: Display: SEARCHING DATA HOW DO YOU WANT ME 1.. COUNTRY OR CITY Display: LATITUDE? ? -45 Display: AUSTRALIA TO LOCATE DATA? 2...PREFIX LONGITUDE? 1..COUNTRY OR CITY 3..LAT. & LONG. 2...PREFIX 4..QUIT 2<RET> 120<RET> 3..LAT. & LONG. Type: Type: Display: LATITUDE? 4..QUIT Display: ENTER PREFIX 1<RET> 2-45 Type: LONGITUDE? Display: ENTER COUNTRY OR CITY. TT<RET> Type: ? 120 Display: CHAD IS YOUR INPUT COR-ITALY<RET> LATITUDE 15 Type: RECT? Display: SEARCHING DATA **LONGITUDE 19** Display: ITALY 1 = YES 2 = NO BEARING: 50 LATITUDE 42 1<RET> DISTANCE FROM OGDEN, Type: Display: LATITUDE 45 Display: SEARCHING DATA LONGITUDE 12 UTAH **LONGITUDE 120** PREFIX: I 7437 MILES Display: AUSTRALIA PREFIX: BEARING: 39 11968 KILOMETERS DISTANCE FROM OGDEN, (F7) = SEARCH DATA OR BEARING: 246 DISTANCE FROM OGDEN, UTAH HIT ANY KEY 5699 MILES (Any key.) UTAH Type: 9864 MILES 9171 KILOMETERS Display: (Returns to the main 15874 KILOMETERS (F7) = SEARCH DATA OR menu.) Display: "MAIN MENU" (F7) = SEARCH DATA OR HIT ANY KEY (Function key F7 is located HOW DO YOU WANT ME HIT ANY KEY Type: on the lower right side of TO LOCATE DATA? Type: (Function key F7.) the VIC.) 1.. COUNTRY OR CITY Display: I WILL SEARCH MY FILE Display: SEARCHING DATA FOR DATA ON LOCATION 2...PREFIX Type: NEAR YOUR COOR-Display: SEARCHING DATA Display: END OF DATA 3..LAT. & LONG. DINATE. Display: (Returns to the main 4..QUIT Display: END OF DATA 3<RET> HOW WIDE OF SEARCH menu.) Type: Display: (Program returns to main Display: **MAIN MENU** Display: LATITUDE? IN DEGREES?

Sample run.

verts L and B to radians. The remainder of line 610 computes the distance angle, looks at its value, and checks to see if it is positive. If P2 is less than 0, 180 is added to its value (line 645).

After P2 is taken care of, the program moves to line 650. Line 650 computes the distance in miles and kilometers. Line 655 computes the bearing angle and converts bearings to degrees rounded to nearest tenth. Lines 670 and 675 determine which quadrant the bearing angle is in and adjust the degrees. Line 680 makes some adjustments to the value of B2. Line 690 makes adjustments to the value of R4. Lines 710 through 865 perform any necessary adjustments to the value of R2, the bearing angle, and send the program to line 900. This is the RETURN statement used to send the program back to the main program after performing the subroutine.

I have not gone into a great deal of explanation of the math routine as the purpose of this article is not to explain the geometry. If you would like a better explanation of this subroutine, I suggest you consult the ARRL Antenna Handbook or any other advanced math book.

Conclusion

I hope this program can be of help to some of you. I have used it a lot. I have needed to make some simple changes in the data statements, but I have attempted to keep the program simple enough so that changes can be made easily. I know that this program will have to be updated occasionally. I used the most current information available. Most of the locations are figured to the center of the country, give or take a degree. Most of the small island latitudes and longitudes have been taken to the tenth of a degree to make the data very accurate.

If you find that you do not have the time to type in the program, I will send it to you on tape for the VIC. The cost is \$5.00, and I need to know the amount of memory you have. I also have this program for the Apple II Plus and the VIC-20 on disk for \$9.00. (Checks should be made out to me at my address, above.) If you do take the time to type it in and run into trouble, write to me describing the problem you are experiencing and I will try to correct it. I know that no program is perfect.

20<RET>

LATITUDE -25

PREFIX: VK

8780 MILES

HIT ANY KEY

LATITUDE -25

PREFIX: AX

8780 MILES

HIT ANY KEY

(Function key F7.)

14130 KILOMETERS

(F7) = SEARCH DATA OR

UTAH

menu.)

BEARING: 268

LONGITUDE 130

(Function key F7.)

14130 KILOMETERS

UTAH

BEARING: 268

LONGITUDE 130

DISTANCE FROM OGDEN,

(F7) = SEARCH DATA OR

DISTANCE FROM OGDEN,

There are many things that can be done to spruce up the program, especially the Apple version. My main goal was to keep it as simple and efficient as possible, but you can have some fun trying to spruce it up a little. You can always add more data as you expand your memory configuration. Have fun and good luck!■

6 AMATEUR AND COMMERCIAL B COMMUNICATION SERVICES "*Technical assistance by F.C.C. licensed technicians using the finest repair, test, and alignment equipment to give you results you can count on. • REPAIRS •INSTALLATIONS TESTS MODIFICATIONS
 EVALUATIONS ALIGNMENTS **F.C.C. Licenses; *General Radiotelephone (ship radar endorsed) Second Class Radiotelegraph (ship radar and aircraft radiotelegraph endorsed) *Amateur Extra Class 6-10 P.M. Sun. thru Thurs. MasterCard. 13313 FOREST HILL RD. Geff N8CE VISA **GRAND LEDGE, MICHIGAN 48837** 517-626-6044



73 INTERNATIONAL

Each month, 73 brings you ham radio news from around the world. In this collection of reports from our foreign correspondents, we present the latest news in DX, contests, and events, as well as keep you abreast of the technical achievements of hams in other countries.

If you would like to contribute to your country's column, write to your country's correspondent or to 73: Amateur Radio's Technical Journal, Pine Street, Peterborough NH 03458, USA, Attn: Jack Burnett.



AUSTRALIA

Jim Joyce VK3YJ 44 Wren Street Altona 3018, Victoria Australia

THE AUSSIE YL

How often we have heard the pileups and QRM disappear when a rare DX station says those magic words "Please stand by-there's a YL calling." Even those persistent callers, jammers, and deliberate QRM merchants who have, unfortunately, become a sad fact of life on amateur radio these days seem to go QRT when the ladies are transmitting. Maybe it is chivalry, or perhaps a mark of respect to these adventurous young ladies who have involved themselves in what was predominantly a male hobby in the early days of amateur radio. Every so often, a YL operator is heard who is a fine example of why we OMs have that respect.

Austine VK3YL

Austine Henry VK3YL is such a young lady. As a life member of the Society of Wireless Pioneers and as a member of 54-years standing with the Wireless Institute of Australia, she has the distinction of having the longest YL membership record. In 1930, Austine was awarded a trophy from the WIA for the best piece of home-brew gear in the local WIA home-brew competition.

1930 was an active year for Austine, as she also became a member of the ARRL on April 14, 1930. She has 30 years of membership in the RSGB, plus she has been a member of NZART over the last few years. Austine has really kept her finger on the pulse of overseas amateur-radio activities. No wonder she has many tales to tell of the good old days in radio.

When she received her first crystal set as a child, she immediately pulled it to pieces to see how it worked, graduating to valve [tube] sets that she made herself, gaining enough expertise to pass her experimental license exam on May 13, 1930. Only the third woman to obtain an amateur license in Australia, Austine became VK3YL.

As there was no commercial gear available for amateurs in those days, Austine learned at an early stage how to get the best out of a home-brew 1-Watt-input transmitter. To get the crystals for her sets, she used to do a tour of the city opticians, getting their broken or rejected quartz lenses, and, if successful, would hurry home with them to grind her own crystals.

With this type of equipment, Austine had her first CW contact into Belgium on September 30, 1931, with Baron de la Rouche ON4HM. To commemorate this contact, the Baron sent her a bronze replica of the Sacred Guardian Monkey of Mons. She also had a successful contact with a South African amateur in the early 1930s, using a UV199 tube fed with dry batteries, with less than 1 Watt of input power, in a portable situation.

Being an adventurous young wisp of a girl, Austine was fond of horseback riding and driving a little sports car, plus riding motor bikes. It was only natural, therefore, to take up flying. On September 6, 1933, she became the first woman admitted to the Royal Australian Air Force Radio Reserve, the training for which included flying around in a Wapiti biplane. This plane, although old, was very solidly constructed and was used extensively to train both pilots and radio operators, with the pilot in the front cockpit and the radio instructor and pupil in the back cockpit. With these cramped conditions, the student virtually had to sit on the instructor's knee (lucky instructor!). The main requirement for flying in these conditions was to stand up when you landed. Otherwise, if the landing was bumpy and you were sitting down, you could crack your skull on all the gear.

Austine was most upset that they would not send her to the war zone as a radio operator in one of the planes, just because she was a woman, but despite other commitments during WWII, she spent a lot of her spare time at the WIA on a volunteer basis, instructing service personnel and others in the art of Morse code. It was not unusual for Austine to take them into her own home for free private tuition so that they could pass their exams.

After WWII, Austine maintained her interest in amateur radio, with a particular interest in DX. One of her most interesting contacts was in 1957 with Michael FO8AP/MM, on the ill-fated Tahiti Nui raft expedition between Tahiti and Chile. This expedition ended up 600 miles short of Chile when the raft broke apart after a week of storms. Michael was using a transceiver with 1 Watt of input power at that time. Can you imagine trying to send SOS, plus your position, on a raft of 20-inch logs that are breaking apart in the middle of the ocean with 30-foot waves pounding down on you? That would definitely take a steady hand on the key.

CW is a mode at which Austine has remained very proficient, proof of this being her entry to the DXCC Honor Roll as the first and only Australian YL to gain this achievement, but this is only one of Austine's many firsts in the field of amateur radio. Up until 25 years ago, Austine was using only a 40-meter Zepp antenna, graduating to a half-wave centerfed dipole, but in the last few years she has upgraded her antenna system to a triband beam. Her transmitters have graduated from home brew, to converted surplus WWII equip-



Austine Henry VK3YL.

ment, to these days, when she is using Drake equipment.

Austine is quite proud of some of her earlier award achievements, some of which are: the first to work WAC-YL, Certificate No. 22 for the YL-DXCC from Canada (hand-printed in gold), and from Heather Mitchell VK3AZU (the designer of the Alara award), a certificate for being the first VK YL to receive this award.

Those are only a few of the various awards Austine has to her credit. She is also a foundation member of Yasme, winning Certificate No. 7 in the prestigious Yasme award, one in front of the famous Don Wallace W6AM who got Certificate No. 8 in 1980.

What more can be said about a woman who, after 54 years of amateur-radio operating, is still heard in the pileups, keeping her operating techniques in CW and SSB sharp, just in case there comes on the air one of the four countries she still needs to have worked the lot.

88s, Austine!

CB RADIO


CB radio has been both a blessing and a curse to amateur radio in Australia. It started with the truckers in the Blue

Mountains of New South Wales (VK2), where it was put to good use as a safety device on the narrow, steep hills, but with the showing of the film Convoy, all of the rest of Australia became aware of what was to become a loss of 27 MHz to amateur radio in Australia and a headache for our Department of Communications, but a boom for amateur radio.


With the interest created by CB, it did not take long for people to realize that with ever-increasing chaos on 27 MHz, there had to be something better in the field of communications. It is here that both the Wireless Institute of Australia and the DOC, to their credit, got together with the result being a Novice class of amateur license.

To pass this, you had to answer a 50-question, multi-choice paper on relatively easy electrical laws, operating procedures, and basic radio theory. You also had a 30-question paper on rules and regulations (multi-choice). Your CW test was at 5 wpm, send and receive.

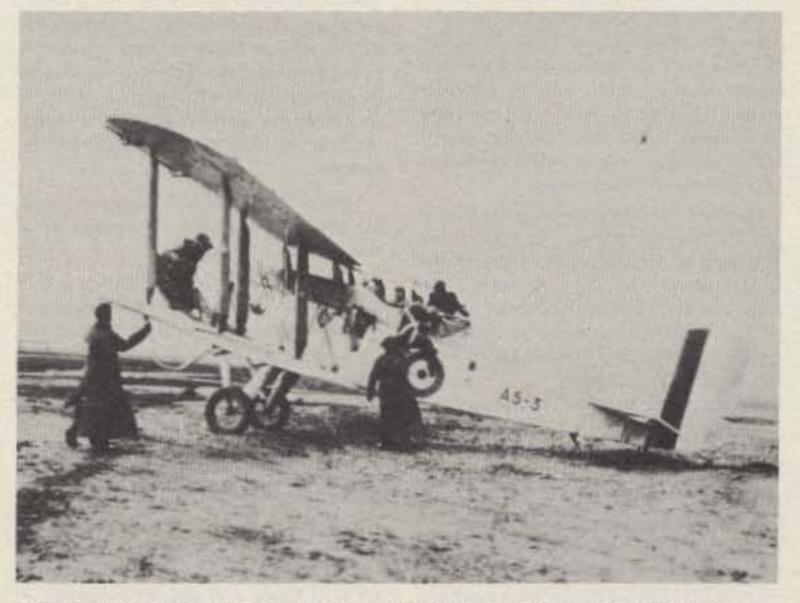If you passed this exam, you were allowed to operate both SSB and CW on a section of 10, 15, and 80 meters, with a maximum power output of 30 Watts PEP. A few countries have been thinking of also



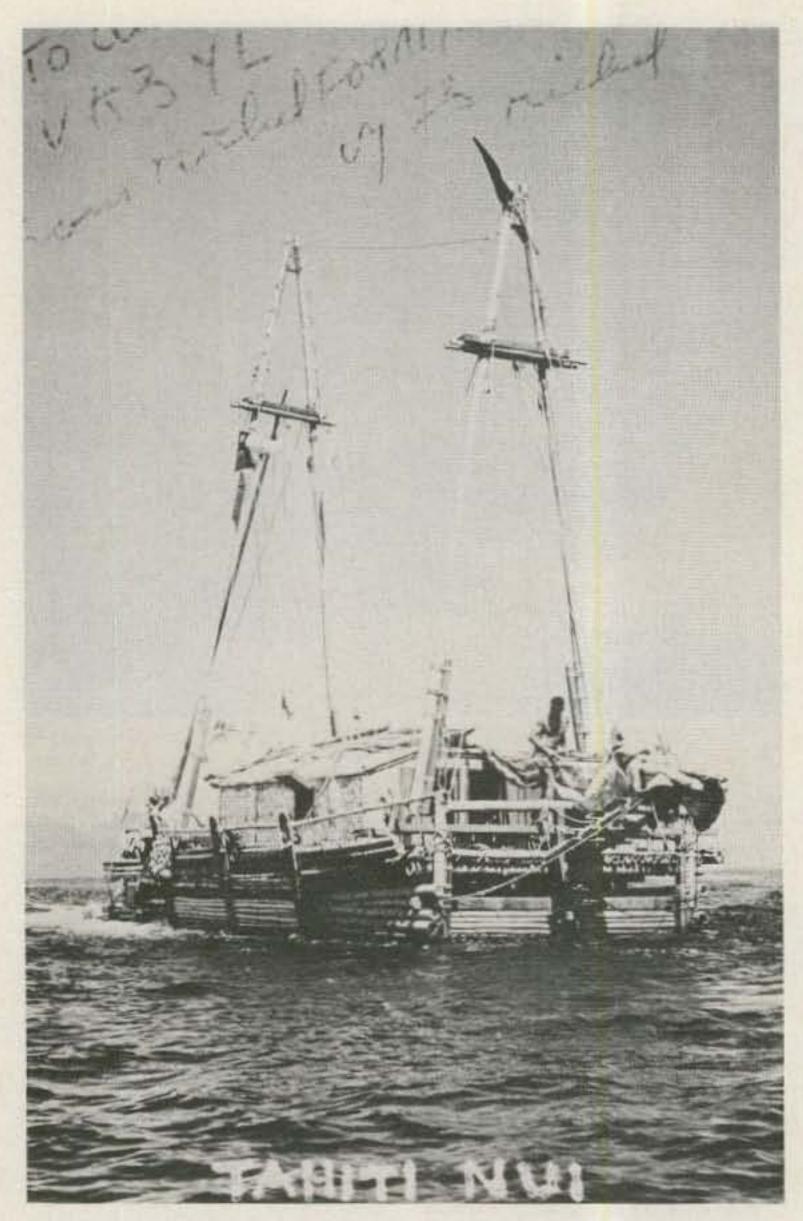Point Cook, 1933: The Wapiti in which Austine 3YL/3D6 made her flying debut. (Picture given to her by Jim 3NY/3B6.)



The card sent to Austine by Michael FO8AP/MM who, here in 1957, is looking over the rear of his raft.

introducing a similar Novice-class license and, going by the upsurge in amateur radio in Australia, it would be a good thing, as up until the advent of CB and the Novice-class license, the amateur-radio scene in Australia was virtually stagnant.

As an example, going by WIA membership (which has remained at approximately 60% of the total amateur population), from 1963, with 3,500 members, to 1973, there was an increase of 1,000 (28%), but by 1983, with the advent of CB and the Novice license, there was an unprecedented upsurge in new amateurs and membership was 8,500. That represented a 53% 10-year increase, nearly twice that of the previous 10-year period.

However, like everything else in life, you get nothing for nothing. The cost to the amateurs so far has been the loss of the 27-MHz band and, with retailers down here now quite blatantly advertising CBs with a frequency coverage of 26.965 to 28.805 MHz in 5-KHz steps, how long before we also lose 28 MHz?

"It will never happen," I hear the oldtimers saying into their 807s, but the CB fraternity in Australia now legally has 40 channels and no restrictions on antennas (six-element beams are quite common) plus freely-advertised linear amplifiers of up to 600 Watts output for 27 MHz. What happened to the legal limit of 12 Watts PEP for CB? The CB operators in Australia also enjoy a section of the UHF band quite legally, with access to repeaters and, believe it or not, freely-advertised linear amps for UHF.

I would not be surprised if in the near future, due to our archaic import and resale laws in Australia, 14-MHz sets appear for resale, as it is quite legal to import and retall any type of equipment providing it is not dangerous to health or does not interfere with emergency services. A CB operator can quite legally buy himself an FT-902DM with an FL2100Z linear, connect it to his 6-element monobander and, unless he causes interference (with a resulting visit from the overworked DOC investigator), can operate illegally to his heart's content.

That is the negative-but worth thinking about-side of the CB input to amateur radio In Australia.

The positive side has many pluses. It is not unusual to hear on the CW section of the Novice band a couple of Novices rattling away on CW at 20 wpm; some are even faster. These speed merchants on the key usually are ex-service signal personnel or postoffice telegraphists who, over the years, have forgotten all about radio but, with the advent of the Novice license, have found that with a little study on solid-state basics, they can get back into the communications field. As most of these gentlemen are now retired, they tend to study and get their full-call license. The result is that many ex-signal ops of the various services during WWII

now get on the air with their own net frequencies to chew the fat about old times.

Bureau PP1

PP2

PP5

PP6

PP7

PP8

PR7

PR8

PS7

PS8

PT2

PT7

PT8

PT9

PV8

PW8

PY1

PY2

PY3

PY4

PY5

PY6 PY7

PY8 PY9

We also have the lifetime SWL who could not pass the previous license test for the full call, but now, due to the Novice license, with a bit of study is able to transmit to stations he has logged as an SWL over many years.

In conclusion, due to the upsurge of CB radio we have had both gains and losses, and only time will tell if it has been good for amateur radio in Australia. I do personally feel, however, that with the advent of the latest toy, namely a cordless telephone with a 9-km range (together with other as-yet-untested frequency damaging devices being imported into this country), we may suffer an unprecedented interference problem on the amateur bands and commercial frequencies.

The extent of such interference could be such that the Department of Communications (DOC) may have some difficulty in controlling it, as in past instances with 27 MHz. There is some ray of hope, however, since at this very moment a new Act of Parliament (Radio Communications Bill) is in the final stages of debate and is expected to pass the Senate shortly. When this occurs, the Department of Communications will have little difficulty in obtaining a prosecution against illegal operations, since the mere possession of transmitting equipment without a license or just cause will be an indictable offense.



BRAZIL

Gerson Rissin PY1APS PO Box 12178, Copacabana 20000 Rio de Janeiro, RJ Brazil

Carlos Vianna Carneiro PY1CC Rua Afonso Pena 49, Apt. 701 20270 Rio de Janeiro, RJ Brazil

QSL BUREAU

The Brazilian amateurs who are members of the League (LABRE) may use the QSL Bureau to send and receive their QSL cards, free of charge. In this way, each

QSL Bureau handles thousands of cards monthly and it is easy for us to spread out our QSL cards around the world. Inside Brazil, the service is very good and fast. The QSL travels from one Bureau to another in only one day.

QSL BUREAUS IN BRAZIL

PO Box 692, 29000 Vitoria, ES

PO Box 676, 74000 Goiania, GO

PO Box 259, 49000 Aracaju, SE

PO Box 283, 69000 Manaus, AM

PO Box 372, 65000 Sao Luiz, MA

PO Box 251, 59000 Natal, RN

PO Box 137, 64000 Teresina, PI

PO Box 80, 57000 Maceio, AL

PO Box 224, 88000 Florianopolis, SC

PO Box 168, 58000 Joao Pessoa, PB

PO Box 07/0004, 70200 Brasilia, DF

PO Box 975, 60000 Fortaleza, CE

PO Box 149, 69900 Rio Branco, AC

PO Box 148, 69300 Boa Vista, RR

PO Box 84, 78900 Porto Velho, RO

PO Box 22, 01000 Sao Paulo, SP

PO Box 1455, 80000 Curitiba, PR PO Box 533, 40000 Salvador, BA

PO Box 1043, 50000 Recife, PE PO Box 71, 66000 Belem, PA

PO Box 560, 78000 Cuiaba, MT

PO Box 58, 20001 Rio de Janeiro, RJ

PO Box 2180, 90000 Porto Alegre, RS

PO Box 314, 30000 Belo Horizonte, MG

PO Box 008, 79100 Campo Grande, MS

Address

Working so well, it is not difficult to receive a Brazilian card via the Bureau after a short time. Foreign amateurs may also send their QSL cards to Brazil, addressing them to the QSL Bureau when they are not able to find out the right direction. The QSL Bureaus are located in all capital cities (see box). The main one is in Brasilia, the Federal District.

RESULTS OF THE **HUNTING LIONS ON THE AIR** CONTEST-1983

The principal objective of this contest is to create and foster a spirit of international understanding and cooperation among Lions and ham-radio operators through worldwide communications. The contest is held in tribute to the birthday of Melvin Jones, the founder of Lionism. It is sponsored by Lions and coordinated by the Rio de Janeiro (Arpoador) Lions Club.

About 13,000 contacts were made among stations located in 114 countries. In the Single-Operator Class-Phone, the winner was VK6NO, followed by K7OX, ZD8JD, ZL1SZ, and PY1BPE. In the Single-Operator Class-CW, the highest score was for the very well-known operator Tim Chen BV2A, followed by PY2ASV, OH6OC, K4EBT, and OH9SV. For the Club Station Class-Phone, the winner was GJ3DVC, the Jersey Amateur Radio Society, and in CW, CT1ARS, the Southern Radioamateur Association of Portugal.

MCG AWARD

Sponsored by the Morse Clube Gaucho (CW Group), the MCG Award is available to all licensed amateurs for confirmed contacts with 5 (five) different MCG members. Contacts must have been made after May 1, 1980, on any amateur band, only two-way CW mode. No QSLs. Send GCR list of stations worked (call, date, time, band, mode, and report) and 5 IRCs for mailing expenses to: MCG Bureau, PO Box 2180, 90000 Porto Alegre, RS, Brazil.

For SWLs, the same rules apply.

MCG members: PY3AVF, PY3AZL, PY3AKS. PY3AZ, PY3AO, PY3BC, PY3BYC, PY3BVI, PY3BOG, PY3BCD, PY3CMH, PY3CJI, PY3CFD, PY3CMZ, PY3CKI, PY3CNY, PY3COR, PY3CGJ, PY3CGW, PY3CEM, PY3FMC, PY3FJ, PY3FS, PY3HR, PY3HS, PY3JJ, PY3LIM, PY3MU, PY3OH, PY3OS, PY3PO, PY3PR, PY3SM, PY3TT, and PY3ZZ.

THREE STARS AWARD

Sponsored by the David Barros Scout Group, GREDB, the Three Stars Award is available to all licensed amateurs for confirmed contacts with 2 (two) GREDB members plus a contact with PY1EDB (the group station) and contacts with three different Brazilian prefixes. Contacts must have been made after January 1, 1982, on any amateur band and any mode. No QSLs. Send GCR list of stations worked (call, date, time, band, mode, and report), your personal QSL, and 10 IRCs for mailing expenses to: GREDB, PO Box 20033, 21022 Rio de Janeiro, RJ, Brazil.

GREDB members: PY1s ABK, AFA, AMG, ATR, AVV, AWA, AZF, BCZ, BON, BGI, BLG, BM, BPU, BUF, BV, BVB, CBG, CBW, CC, CCD, CCE, CCK, CCO, CDA, CGB, CKL, CKV, CKY, CLI, COA, CPC, CQV, CIP, DCO, DED, DIA, DWP, DMX, EEX, ELU, ENN, EHD, ER, FP, IP, IR, NE, RI, TBG, TBW, TCI, TFU, TFQ, TFW, THH, TNV, TOM, TPH, TPW, TTF, TTH, TUP, TUQ, UBX, UVP, USU, VBR, VIZ, VKK, VOP, VTU, VXO, WFR, WHO, WIO, WIR, WTA, XHK, XRI, XRX, XXP, YDQ, YJD, PY2BI, and PY4BCF.

JUBILEE OF LABRE

On February 2, 1984, the Brazilian Amateur Radio League (LABRE) will celebrate its 50th anniversary. The IV Brazilian Convention joining amateurs of the whole country will be held in Brasilia, the Federal District, for this purpose.

Besides the meetings and parties, etc., the convention will sponsor a lot of tourist happenings for those who haven't had the opportunity to know the capital city yet. In collaboration with LABRE, three excellent hotels will offer special prices for the amateurs.

Valmir J. Pereira PT2FA, President of LABRE, will do all he can to promote unforgettable events. For further information, please write to LABRE, PO Box 070004, 70000 Brasilia, DF, Brazil.

QSP-DX

To provide information for Brazilian DXers, Luc PT7WA with a group of PT7 friends established the QSP-DX Bulletin. In the bulletin, written in Portuguese, we can find details about DXpeditions, contests, rare countries on the air, QSL information, and everything interesting to the DXer, especially the newcomer.

The bulletin is bimonthly; after the second issue, about 150 amateurs had already subscribed. The subscription fee is only enough to pay the printing and mailing expenses. If you want to provide the bulletin with any DX information, please write to QSP-DX, Rua Ageu Romero 83, 60000 Fortaleza, CE, Brazil.

CWMG AWARD

Sponsored by the Minas Gerais CW Club (CW Group), the CWMG Award is available to all licensed amateurs for confirmed contacts with 5 (five) different CWMG members. Contacts must have been made after May 1, 1978, on any amateur band, only two-way CW mode. No QSLs. Send GCR list of stations worked (call, date, time, band, mode, and report) and 6 IRCs for mailing expenses to: CWMG Award, PO Box 314, 30000 Belo Horizonte, MG, Brazil.

members: PY4AAF, PY4ABI, CWMG PY4ADW, PY4AFP, PY4AD. PY4ACV. PY4AM. PY4AP, PY4APF, PY4AH. PY4AQM, PY4AUB, PY4AUN, PY4AQL, PY4BAT, PY4BCR, PY4BLR, PY4BMO, PY4BZS, PY4BW, PY4CMG, PY4CO, PY4DD, PY4DM, PY4DS, PY4DT, PY4HR, PY4IF, PY4IR, PY4IS, PY4JD, PY4KS, PY4LB, PY4LJ, PY4MA, PY4MG, PY4OA, PY40D, PY40P, PY4PR, PY4RA, PY4RL, PY4SM, PY4SS, PY4ST, PY4WG, PY4WAS, PY4XUP, PY4ZI, and PP2ZI.

GMPR AWARD

Sponsored by the GMPR Group of CW, the GMPR Award is available to all licensed amateurs for confirmed contacts with 6 (six) different GMPR members. Contacts must have been made after July 30, 1982, on any amateur band, only two-way CW mode. No QSLs. Send GCR list of stations worked (call, date, time, band, mode, and report), your personal QSL, and 10 IRCs for mailing expenses to: GMPR Award, PO Box 4143, 80000 Curitiba, PR, Brazil.

For SWLs, the same rules apply.

Endorsements: Besides the six GMPR members, confirmed contacts with 2, 3, 4, or 5 stations located in the State of Parana (PY5) earn an endorsement. It is not necessary that they be GMPR members.

GMPR members: PY5AFC, PY5AFD, PY5AGX, PY5AGZ, PY5AIO, PY5AIW, PY5AKX, PY5ALF, PY5AVR, PY5BYC, PY5CIG, PY5CIG, PY5CMS, PY5FI, PY5GI, PY5GJ, PY5HF, PY5IG, PY5IJ, PY5LA, PY5NGA, PY5OE, PY5PMR, PY5AJE, PY5RT, PY5VX, PY5XFR, PY5ZW, and PY1BVY.

de PY1APS

1983 WORLDWIDE SOUTH AMERICA CW CONTEST

Sponsored by the Brazilian magazine, Eletronica Popular, and supervised by the Argentina GACW group and the Brazilian PPC Picapau Carioca, the 1983 WWSA CW Contest was a hit, considering it's only in its second year.

Little by little, slow but sure, hams are coming to this contest, the only one gathering South American countries and spreading QSOs all over the world during 24 hours of operation, from 1500 UTC Saturday to 1500 UTC Sunday, the last weekend in June.

Not only the fun of the party, but also this FB opportunity of meeting bunches of still rare South American calls and special prefixes is raising DXers' interest for this unique WWSA CW Contest.

Argentina's, Uruguay's, and Brazil's groups and DXers are trying hard to bring more and more South American countries to the fun, thus aiming at increasing the interest of hams in other continents in the WWSA CW Contest.

We sure hope to meet many of you at the 1984 WWSA CW Contest, to take place from Saturday, June 9, 1500 UTC to Sunday, June 10, 1500 UTC.



CANADA

Cary Honeywell VE3ARS PO Box 2610, Station D Ottawa, Ontario K1P 5W7 Canada

The Department of Communications in Ottawa recently lifted the requirements for logging in Canada. For some amateurs, this

DX	STATIONS		27.77.770	nental Leaders	
3.5 MHz	YO3HP		Multiband/N	Multi-op	
7 MHz	LZ1GC	850	Europe	LZ1KDP	27,600
	YO3CD	600	South Am.	PY1EDB	650
	Y51XE	260			
14 MHz	JH3DPB	2,184	SOUTH	AMERICAN STA	TIONS
	W4VQ	1,276	3.5 MHz	CX8DT	1,296
	HB9BPP	864		PY2RNJ	84
21 MHz	OK2QX	2,728		PY2OHJ	8
	EI3DP	1,600	7 MHz	CX5AO	22,160
	Y32KE	1,122		PY3CFD	2,730
28 MHz	VE1BNN	1,254		PY5AAZ	280
Multiband	W3GM	27,710	14 MHz	YV5HUJ	60,588
	YU4YA	18,492		PY5MR	3,312
	LZ2DB	14,384		PY2DRP	2,604
Multi-op	LZ1KDP	27,600	21 MHz	PY1DFF	37,904
	SP9KTE	7,296		LU4FC	32,472
	OK3KEX	5,760		PY1BVY	31,044
			28 MHz	PY1HQ	15,984
				PY3XYZ/PP2	10,740
Conti	nental Wind	ners		PY1DPP	2,840
Asia	JA1BX	2,132	Multiband	CX7BY	266,304
Europe	YU4YA	18,492		LU9EIE	222,222
North Am.	W3GM	27,710		PT9EJ	87,720
South Am.	CX7BY	266,304	Multi-op	PY1EDB	650

1983 WWSA CW CONTEST

action means nothing, as I am sure better than half of the amateurs across Canada never logged their activities anyway. Rarely, if ever, was this requirement checked. It should be remembered, however, that logging is a form of self-defense in that you can always refer to your log should you be accused of an infraction of the regs.

The Canadian Amateur Radio Federation and the Canadian Division ARRL (CRRL) met at Cobourg, Ontario, during the summer to finalize a joint submission to the DOC regarding TRC24 (the requirements for examination for the amateur service). Between the two organizations, every area of importance was covered.

Each group submitted its own proposal and it seems that the DOC was open to these suggestions. The resultant redrafting of TRC24 should be common knowledge by this time. A great deal of credit for this work can be shared by many parties. Art Blick VE3AHU of Kingston, Ontario, the CARF General Manager, Ron Walsh VE3IDW, also of Kingston and one of CARF's Vice-Presidents, CRRL president Tom Atkins VE3CDM of Toronto, and ARRL Canadian Division Vice-Director Harry MacLean VE3GRO of London, Ontario, carried the amateur flame in a cooperative and constructive manner. The DOC was represented by G. Wintermeyer from the head office in Ottawa.


The 1983 CARF National Symposium was held in Halifax, Nova Scotia, during the middle of October this year. For those of you who don't know what this is: Amateurs from across Canada get together once a year (en masse) to provide direct input to the DOC on matters relating to the amateur service in Canada. The number of people attending these conferences is not usually great since most groups of amateurs provide only written submissions to be read and considered. This is far less expensive than sending a representative across the country for a one-day event. Full details will be provided in a future column.

A while back, a group of white caners in Toronto, Ontario, organized a reception to express appreciation for the work of an individual. Bill Choat VE3CO was stepping down as chief of the CNIB amateur-radio operation in Toronto, and some of his charges wanted him to be recognized for his efforts in the past. Bill has been in charge of this group for many years now, and through his efforts and the efforts of

others, many white caners were given the opportunity to experience the joys of amateur radio, despite their handicap. Nearly 100 blind and sighted amateurs participated and I think Bill went away with the feeling that all was right with the world.

Canada's national amateur-radio journal, TCA, has been plagued with postal problems for several years now. Recently, an Ontario amateur wrote the Minister responsible for Canada Post, complaining of the late delivery of his July/August copy. Some time later, I, as editor of TCA, received a call from a Canada Post employee who wanted to know when the magazine had been mailed. When the caller discovered that more than three weeks had passed between mailing and delivery, she became very defensive and tried to leave me with the impression that the system was not only better than it was, but would get better as time went by. She would not elaborate on what amount of time would pass before this event, but I got the distinct impression that it would coincide with the "second coming," or at least the blooming of century plants.

was mailed to every amateur in Canada as part of a membership drive on behalf of CARF. Canadian amateurs living in the USA did not receive a copy due to postal limitations and costs. If you would like to receive one, please write to the Canadian Amateur Radio Federation, PO Box 356 Station, Kingston, Ontario, Canada K1P 5W7. Depending on numbers remaining, we may be able to send you a copy. Enclose \$1.50 to cover postage and handling costs (mostly postage). You will notice that this is also the cover price, so it balances out.

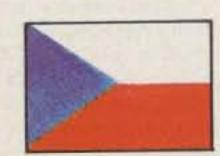

CZECHOSLOVAKIA

Rudy OK3KFO Februaroveho vit'azstva 955 01 Topol'cany Czechoslovakia

I have 25 years. I am a member of Radioclub OK3KFO in Topol'cany and have been an active amateur for 13 years. My call is OK3CMZ. I hope that you 73 magazine readers will enjoy the information I send. Please excuse that I am selftaught in the English language.

I should like to inform readers of 73 about radio-amateur life in Czechoslovakia. In Czechoslovakia, we have approximately four thousand licensed radio amateurs, not counting 1500 SWLs. The most activity is in DX work; there is less activity with contests.

Czechoslovakia is a little republic. One day a week-Thursday-OK3KAB in Bratislava (capital city of Slovakia) broadcasts about all radio-amateur activity. The program is popular because it sends quality information.

Approximately 10% of the people work 144 MHz and 433 MHz. Over the last 10 years, Czechoslovakian microwave stations have reached good places in international contests. Other OKs are working over satellites, and approximately 10 work EME. Tens of thousands are devoted to constructing various mechanisms.

I know my first column is not very interesting so I would like readers of 73 to ask for what they would like to know about activity in Czechoslovakia.



DOMINICAN REPUBLIC

M. F. (Tim) Pimentel HI8MFP PO Box 2191 Santo Domingo Dominican Republic

Some of you have probably worked Dominican (HI) stations in the 20- or 15-meter band but have been less fortunate in contacting the other bands and getting QSLs.

To contact and get QSLs from HI is not an easy task, and exotic bands such as 6 and 160 meters seem to be "Mission Impossible," but even so, there are possibilities.

To be successful, you first have to know which station you're looking for, at what time you should search for it, and last, be lucky enough to find it. Once you have made your contact, it will be easy for you to receive the QSL because there are few people who work on 6 and 160 and those who do confirm on time.

In the 6-meter band we have key people such as Waldo HI8WPC and Domingo HI8DAF. The same applies in the 160-meter band with Jose HI8JAG, Mike HI8MRF, and Virgilio HI8VMA. These stations generally work from 0000 GMT to 0800 GMT. Within these times, schedules could be arranged by sending the abovementioned stations a note to Box 1157, Radio Club Dominicano, Santo Domingo, Dominican Republic.

Another difficult HI contact is the one via satellite. The only representative there is Jorge HI8JAF, and he is on the radio as long as his business activities allow him. Jorge is one who loves that particular type of communication, and on the first DXpedition to Beata Island (HI1RCD) in 1979, he made some contacts there. If any of you are interested in this particular kind of communication with an HI, you could write for additional information to: Jorge Abbott HI8JAF, Rafael F. Bonely #8, Ens. Evaristo Morales, Santo Domingo, Domin-Ican Republic. I am sure he will fix a schedule and the QSL will get to you safely.

Another contact mode considered unobtainable in HI is CW. In the Dominican Republic, anybody who expects to get a ham-radio license is supposed to go through a CW exam. However, this is only in theory, because there are no effective mechanisms to guarantee that it will happen. For those 1500 that have already received their licenses, there's nothing to be done. The practice of CW is restricted to fewer than 1% of those listed in the Callbook; nevertheless, among them there are some excellent operators.

In CW, we have two young operators who are very good, Julito HI3JEI and Carlos HI8CPT, plus the hard-working veterans HI3PC, HI8LC, HI8OMB, HI8KW, HI8RPD, and HI8DAF.

The Dominican Radio Club frequently offers CW courses to its members and guests; thus it maintains a live spirit in this mode even though it has lost popularity in our country.

Can you get a contact with a YL in the Dominican Republic? For chatting there may be some, but for QSLs and DXs, there are very few. However, there are some surprises: Charo HI8RPD enjoys DX, works regularly, works with CW, and sends QSLs besides. You can also find Azilde HI7HHH or Maritza HI8MSS, and both will send their QSLs gladly.

Undoubtedly the language barrier limits many HI ham operators, so communication is made more difficult. On the other hand, the small active group in DX knows English well enough to obtain their contacts. Abed HI8IH and Victor HI8VAT look frequently for DX on 40 and 80 meters, and the same goes for an active group in the HI3 zone with Antonio HI3AMF leading them.

It is my hope that, with these hints, it will be easier to get HI stations and your QSLs, too. Also, for five years, the Dominican Radio Club has had a national campaign among ham-radio operators to stimulate the sending of QSLs, and the results have been positive. The annual average has increased more than 70%. The QSL Bureau is managed by the Dominican Radio Club and has worked efficiently for many years.

Before closing, I'd like to add that we know how important QSLs are and how much they mean, especially to DXers. We will be glad to help you find confirmation of a contact which was made during the past five years; we will help all we can.



ECUADOR

B. Patricio Recalde S. HC2PP PO Box 511 Guayaquil Ecuador

July 23 and 24 last year will be remembered by the technical department of the Guayaquil Radio Club as historical. They were a Saturday and Sunday. What did we do?

Well, a party of amateurs, HC2NW, HC2OL, HC2IH, HC2LU, HC2NS, and HC2KY, went up Chimborazo, the highest volcano in Ecuador (6,310 meters-18,930 feet), in order to install a 40-meter link in a 2-meter repeater. The idea became reality after a mere four weeks of planning. All Saturday they kept working until around 1700 hours, which is late for the altitude at the repeater (4,400-4,500 meters-13,500 feet). They did a lot of testing, and now it is giving the best results.

Now, from all the coast part of our country, it is possible to access the repeater from your car and get through to 40 meters. The frequency is 7080 kHz, and you'd better look for Ecuador so you can test the 40-meter/2-meter link.

Getting there was a lot of fun (troubles + adventures = fun). Saturday evening, HC2IH's car got stuck in mud and snow, and on the way out, the steel bar that keeps the front wheels aligned broke loose. Well, at that time and in that place, all that was left to do was sleep and wait until the next day. The hero (?) who slept in the car (with the engine running, the heater on) was HC2LU. The temperature was below freezing (0° C), so the car didn't even heat up.

Anyway, on Sunday was a tougher test: to try to reach the members of an expedition that was on the Irazu volcano, at 4,250 meters, in San Jose, Costa Rica (TI)! A lot of arrangements had been made through the goodwill and work of TI2KC and HC2EC. At those heights, the wind, the temperature, etc., were a challenge; the people at both places did a good job preparing for the contacts.

In San Jose, they were ready with 10,000 Watts FM, SSB, and HF. The link in 40 meters was not working due to the lack of a better antenna with the Chimborazo expedition, so HC2PP was the guy that linked them all together via 2 meters and 40 meters. While everybody was getting ready, many amateurs from all places were very helpful in clearing frequencies and giving good advice.


Exactly at 12:23 (HC)-1723 GMT-on July 24th—the Irazu expedition transmitted on 146.500 MHz with no results. After a few tries on FM and SSB on 2 meters, there were no positive contacts; the same was true with the Chimborazo expedition. Around 1800 GMT, we tried through a repeater situated where the Ecuadorian expedition was, and we heard three times that the repeater was activated. No modulation, but it gave us a nice feeling of something!

Anyway, after two hours, all the equipment and gear were diassembled. Our president, HC2KC, and the president of the Costa Rica Radio Club (TI2KC) interchanged greetings and thanks for all the efforts, and both confirmed that in the near future, with more testing, the link is going to work.

Well, they decided to try more testing in a new place, Cerro de la Meurte (Death Mountain), that is believed to be better. All amateurs who participated were not frustrated; we believe it is going to take some more coordinated efforts, and we are positive about out next results.

There is another project, and that is to try to put a repeater on a small island that belongs to Panama. Why? Because HC2NS, on old sailor, did access the repeater 146.895 (-) from that point, which is more than 200 nautical miles from the repeater, at 4,400-4,500 meters above sea level!

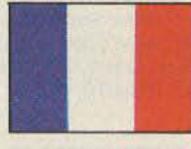I will keep you informed, and we are going to make it!



FRANCE

Claude Guee F1DGY 11 Rue Emile Labiche 28100 Dreux France

I would like to say some words about the first French association (REF-Reseau des Emetteurs Francais), founded in 1925. Some years ago, the situation was rather confused, but thanks to the work of a new and very good team, it is now completely reversed. We see that REF again has a fine future! Furthermore, dealings with the second association (URC-Union des Radio-

Clubs) are more hearty than formerly. At the beginning, the two were at daggers drawn, but now they cooperate in facing difficulties (new license examinations, UHF, regulations, etc.).

Some hams and SWLs are getting in trouble: They have bought general-coverage receivers, called "scanners," which unfortunately are illegal here. As a matter of fact, people are brought up for trial and convicted (with a fine and receiver confiscation). However, REF has lodged an appeal. The law amounts to saying that French hams have the right to listen only to the amateur allocations. No comment.

Once again, we have heard on the air that tickets for part of the 28-MHz band would be granted without a Morse-code test. Actually, this is utterly false. It is a CB rumor which till now officials have turned down, On the other hand, new regulations for 27 MHz are generous: 40 channels, 4 Watts SSB (peak), 4 Watts FM, 1 Watt AM, and the possibilities of 6-dB-gain antennas. It goes without saying that CBers are not yet satisfied. This band is so busy that some people escape to the 6-MHz band.

65-year-old hams without Morse-code knowledge can ask again for the full licenses (F6) without taking the 10-wpm test. Since the beginning of this year and the new license regulations, this gift had been forgotten.

A new ham magazine is born: Megahertz. Covering microcomputers, astronomy, private FM broadcast, and of course all ham activities, this third French ham magazine looks promising and means that amateur radio in France enjoys good health!



Jeff Maynard G4EJA 10 Churchfields Widnes WA8 9RP Cheshire England

One of my particular interests is RTTY (WAC and some 70 countries worked to date). The RTTY enthusiast over here is well looked after by BARTG, the British Amateur Radio Teletype Group, which promotes RTTY activities, contests, and awards, advises on RTTY matters, transmits a RTTY bulletin, and publishes the BARTG newsletter. (Readers interested in joining BARTG should write to the Membership Secretary, Mrs. T. Crane, Greta Woods, Bromley Road, Ardleigh, Colchester C07 7SF, England—dues are about US\$5 per year.)

A recent BARTG survey reveals that about 65% of its members still use traditional clanking teletypes for their RTTY with the Creed line (444, 54, 7, etc.) being by far the most popular. Even more surprising, to me at least, was the comment that a number of stations have 4 or 5 such machines in constant use. I am not sure that the floor of my shack (in the house loft) would stand the weight of even one such machine. I am sure though that the rest of the family would rebel at the noise from a traditional teletype.

Something like 34% of BARTG members use electronic RTTY systems or home computers (with 5% using AMTOR). Commercial units are best represented by the Microwave modules line although Hal has captured about 13% of the UK market.

With my own all-electronic RTTY station (Dovetron terminal unit, Extel VDU, and ma-

Continued on page 116

Convert the Oddball Hy-Gain Board

Some of these boards have two crystals and some have three. Now you can put them all on 10-meter FM.

ecently, the popularity of the Hy-Gain surplus boards has been tremendous. However, there are several types of these boards on the market today, and each type requires a different method of attack. The 3-crystal model with the PLL-02 phaselocked-loop chip has been well discussed in a previous article. The board I am going to discuss is the board with the part number PTBM051AOX, available from Surplus Electronics Corp.2

The major differences with this board compared with the other Hy-Gain boards is the 2-crystal approach. The third offset

crystal has been eliminated so that all frequencies are generated by the 10.24-MHz reference crystal. The other crystal, 10.695, is used to offset the synthesizer/ mixer output by the amount of the receiver first i-f.

This presents three problems. First, with this mixing process, the PLL programming is upside down. That is, if you increase the divide-by-N, the frequency goes down, and since a prerequisite of any of my 10-meter FM conversions is a direct frequency readout system, this makes it a bit difficult. The second problem is that you cannot decide what divide-by-N equals which frequency. This is decided for you. The


third problem is the odd 5-kHz output frequency. By that I mean that when this conversion is made, we want the operating frequency of the transceiver to be 29.600 MHz, not 29.595 or 29.605 MHz. So a change will have to be made there. All that is done here is to raise the reference frequency slightly, making each channel a few Hertz more than 10-kHz channel spacing.

Circuit Description


There will be three added circuits to the original board. Those are the FM detector/squelch board, the modulator board, and the frequency-selector board.

The FM detector/squelch board (see Fig. 1) consists of one IC and two transistors and is designed to interface the CB board easily. The 2111 IC is a common IC that is used in television receivers and scanners. This chip provides the i-f limiting and the quadrature detection necessary for FM detection. Transformer T01 is tuned to 455 kHz, and the transformer can be obtained from an old transistor radio. The primary winding is used.

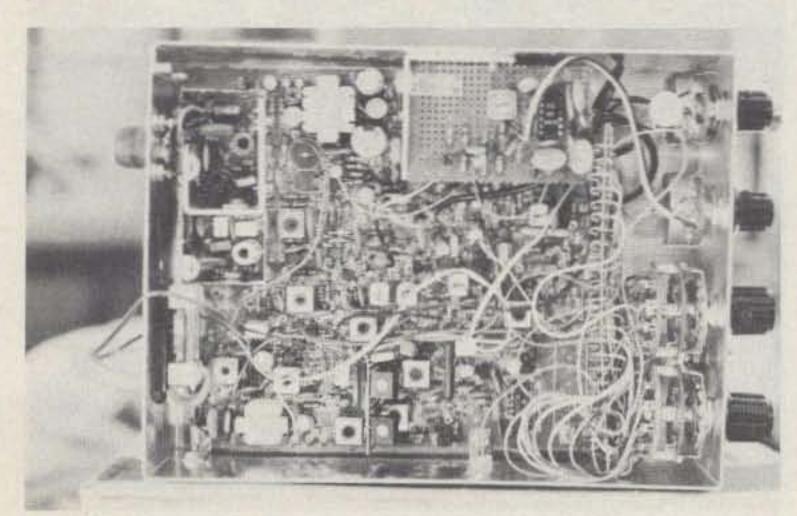The noise to operate the squelch is taken from pin 1 of the IC which is before the de-emphasis capacitor, C01. The noise is filtered and amplified by the two-



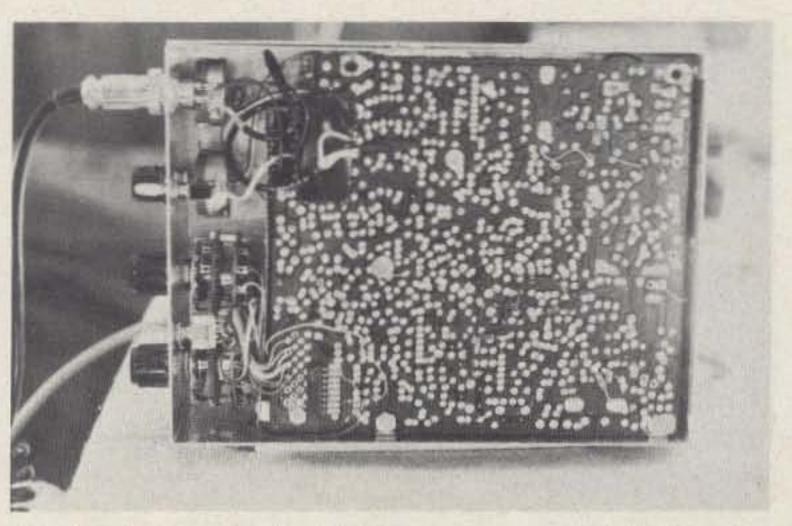A top view of the radio. Notice the mounting of the three added boards.



This is a bottom look with the cover removed. Next to the piece of electrical tape is the connection to the input of the FM detector/squelch board.

transistor circuit, and the output is applied to the base of the audio switch in the receiver (Q13). The input at C02 is taken from the secondary of the last i-f transformer through a short length of RG-174 coax. The volume and squelch pots are front-panel-mounted.

The easiest board to construct is the modulator board (see Fig. 2). The input is taken from the audio output chip in the receiver. On receive, this line is shorted to ground, causing the modulator to be disabled. The gain pot provides audio voltage to the diode clipper, which clips the audio peaks to approximately 1.2 volts p-p. The deviation pot selects which portion of this clipped audio is to be applied to the vco. This provides for direct FMing of the transmitter.

The third board is the frequency selector board. There are three controls on the front panel. There are two single-pole, 10-position switches, 29.50-29.59 and 29.60-29.60 MHz. There is also a three-position toggle switch (SPDT C-O), used so that either 29.50-29.59 MHz simplex, 29.60-29.69 MHz simplex, or 29.50-29.59 transmit and 29.60-29.69 MHz receive can be selected. The last combination is for repeater offsets.

A look at the frequency selector board circuit (see

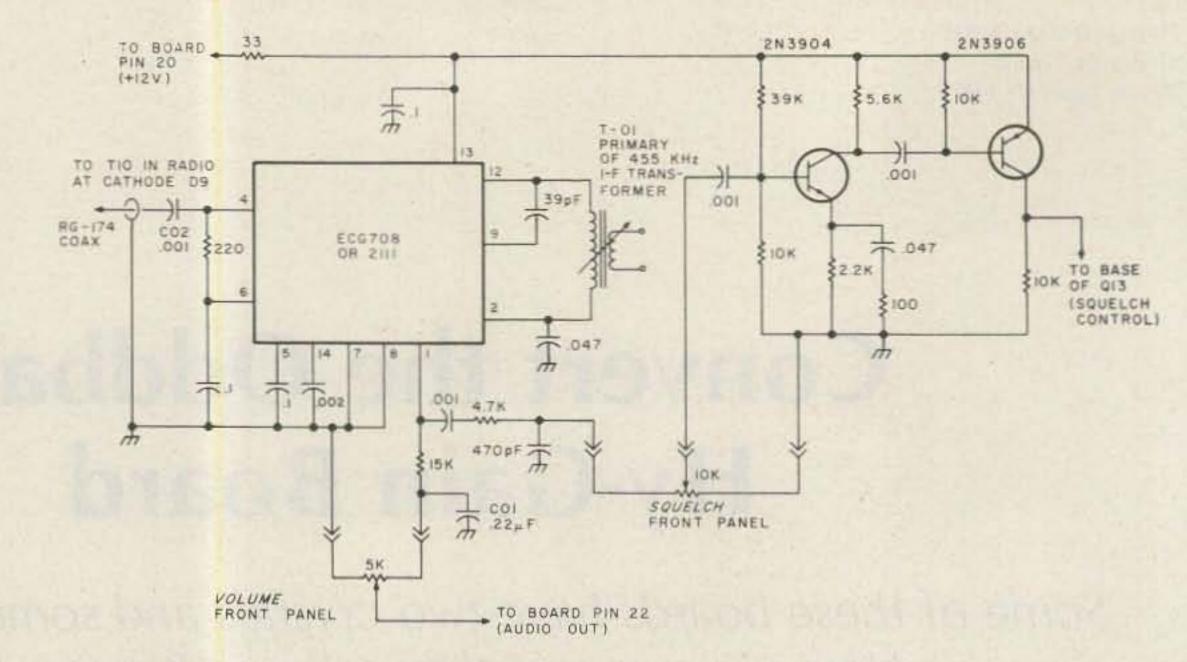


Fig. 1. FM detector/squelch board. Capacitors are in uF, 25 volts disc ceramic unless otherwise noted. Resistors are ¼ W.

Fig. 3) shows a diode matrix and a two-transistor circuit. The two transistors select which of the two single-pole, 10-position switches gets the 5 volts. The switch that gets the 5 volts is the switch that is active for frequency selection.

The steering for this circuit comes from board pin 12, which is operated by the PTT. This pin is high on receive and low on transmit. This is what happens: With the SPDT C-O switch in the center-off position, the 29.60-29.69 selector gets the 5 volts on receive and the 29.50-29.59 on transmit. By switching the SPDT C-O switch to one of the two other positions, the switching from pin 12 is dis-

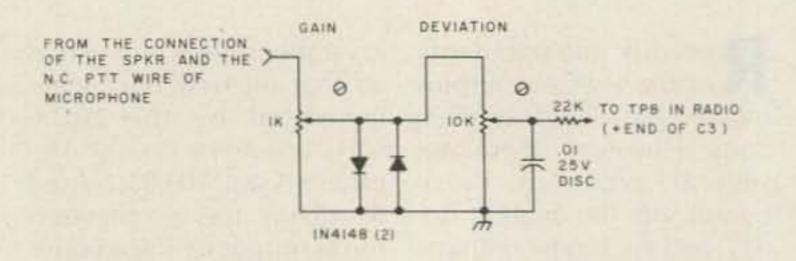


Fig. 2. FM modulator board.


abled and locks up to a certain 10-position switch in the switch positions are the transmit and receive. last two digits of the

The diode matrix programs the PLL-02 IC in the radio. On the right of the frequency selector circuit are the binary weight values for the PLL-02 IC, along with the pins to which the wires must be connected. Along the top are listed the total binary weighting values for the various


switch positions. Next to the switch positions are the last two digits of the operating frequency. The 5 volts to operate this circuit is brought from a 5-volt regulator which is part of the Hy-Gain board.

Construction

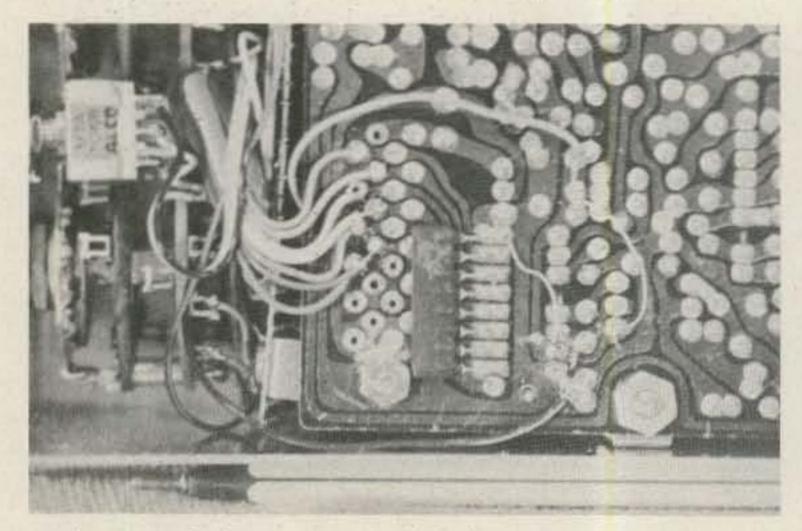First, a few modifications to the Hy-Gain board must be done. Connect board pins 38 and 39 together. Re-



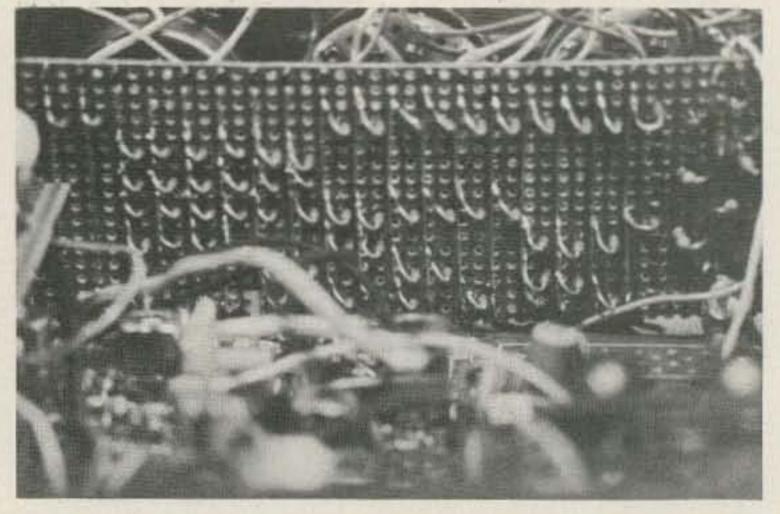A close-up of the PLL-02 IC. The thick wires go to the frequency selector board, and the thin wires are the circuit changes made to the PLL-02 circuit.



A close-up view of the frequency selector board, showing how the diodes are installed and the 20 bare wires that go to the selector switches.

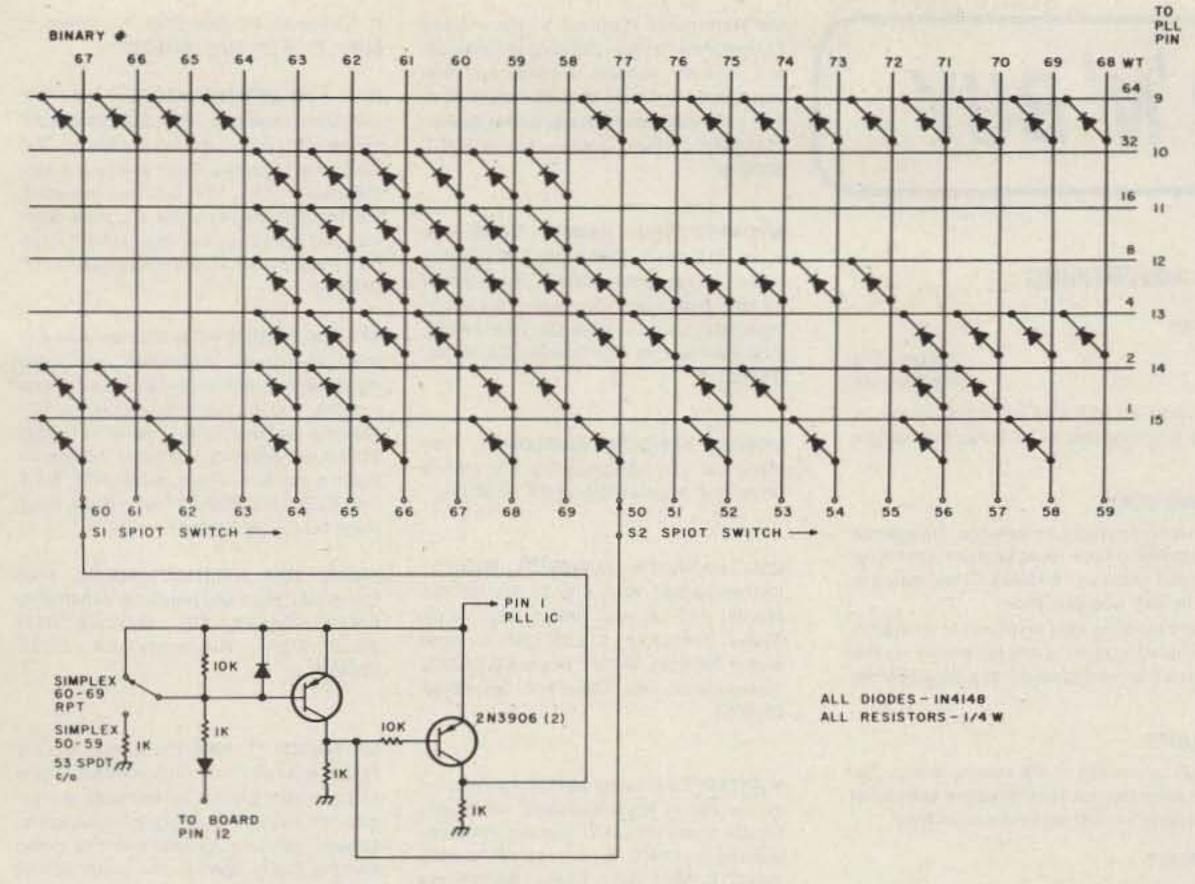


Fig. 3. Frequency selector board.

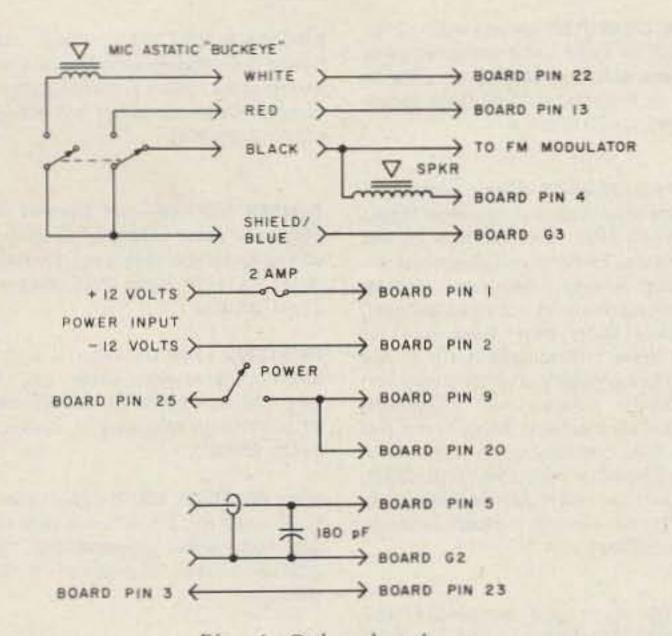


Fig. 4. Other hookups.

move R69, R71, D13, RV2, and C12. Connect a wire from board pin 20 to where the cathode of D13 was. To modify the PLL chip wiring, first isolate PLL IC pin 7 from the original wiring. Connect PLL IC pin 7 to PLL IC pin 8. Run a wire from PLL IC pin 1 to jumper J4. The other connections to the board are shown on the schematics. The three boards are made from .1"spacing perfboard.

To make the diode ma-

trix, on one side of the perfboard string 7 bare wires 4.5 inches (11.3 cm) across on one side. On the other side, string 20 bare wires perpendicular to those on the other side. Be sure to skip a row of holes between each string of wires. Then the diodes can be placed with one lead bent over in through the holes and soldered.

The FM detector can be mounted to the square hole above the BA521 IC with a

small angle bracket. The modulator perfboard can be glued against the side of vco coil L1, being sure that nothing interferes with the tuning of the coil. The frequency board can be mounted across the front of the CB board, standing up vertically.

Tuning

For tuning, you will need a dc voltmeter, an rf probe, a signal generator (or a weak signal from an amateur transceiver), a frequency counter, and a General Cement model 9440 tuning tool.3 A small hex head plastic tuning tool is also handy. Nothing ruins a powdered iron slug faster than trying to tune up with a regular screwdriver.

First, set the transceiver on 29.60 MHz simplex. Place a dc voltmeter on pin 6 of the PLL-02. Carefully tune vco coil L1 until 5 volts or so is reached. Move the voltmeter to pin 5 of the PLL-02. Carefully adjust vco coil L1 for 2.5 volts.

Next, attach a dummy load to the antenna jack.

Place the rf probe on the base of Q3 (rf predriver). Adjust T1, L2, T2, L5, and T3 for maximum rf. Then move the rf probe to the antenna jack and adjust L7, L11, and L12 for maximum. Place the frequency counter on the antenna jack, and the counter should read 29.600 MHz. If the reading is a few kHz off, adjust trimmer CT1. If the reading is unstable, check the vco tuning. Run through all channels and see how each frequency looks. If an error shows, check the matrix and associated wiring.

Now, on receive, place the dc voltmeter on board pin 39 and adjust T5, T6, L14, T7, T8, T9, and T10 for maximum. Be careful not to overload. Adjust the quadrature coil on the FM detector/squelch board, with no signal, for maximum noise. Later tune when listening to another FM signal for best sound.

As a building hint, the housing for this radio can be built from aluminum. The box size is 6" (15.24 cm) by 8.5" (21.6 cm) by 2.5" (6.25 cm). Two U-shaped pieces of metal make up the top and bottom covers which fit over the ring of metal which makes up the main chassis.

That's it. Just look at the way I constructed it. As they say in the old country, "Ein Bild sagt tausend Worte."4 I would like to thank Bob Russo WB2BMM for taking the photos shown here. If I can be of further help, please write, include an SASE, and I will try to help.

References

- 1. Knickerbocker K1DCS, Weise N1XN, Stielau W1WRO/N2XN, "CB on 10 FM - best conversion yet?", 73 Magazine, January, 1980, p. 117.
- 2. Surplus Electronics Corp., 7294 NW 54 St., Miami FL 33166. 3. General Cement Electronics, Rockford IL 61101, or from your electronics parts distributor.
- 4. "A picture is worth a thousand words."

BARTER'N' BUY

73 CLASSIFIED ADVERTISING

RATES

Individual (non-commercial)	 15¢ per word
Commercial	 50¢ per word

Prepayment by check or money order is required with your ad. No discounts or commissions are available. Please make your payment to 73. Rates for multiple insertions are available on request.

ADVERTISING COPY

Advertising must pertain to amateur radio products or services. No special layouts or positions are possible. All advertising copy must be submitted type-written (double-spaced) and must include full name and address. Copy limited to 100 words, maximum. Count only words in text. Address, free.

73 cannot verify advertising claims and cannot be held responsible for claims made by the advertiser. Liability will be limited to making any necessary correction in the next available issue. 73 reserves the right to reject any copy deemed unsuitable.

DEADLINES

Copy must be received in Peterborough by the 5th of the second month preceding the cover date. If copy is received after the deadline, it will be scheduled to run the following month, unless specifically prohibited by the advertiser.

MATERIALS

Send to Advertising Department, 73, Elm Street, Peterborough NH 03458.

DRESS UP YOUR CLUB! Jackets, teeshirts, hats, sportshirts, etc., with your logo or we'll custom design. Wavelength Productions, 20-22 120th St., College Point NY 11356. BNB048

FREE SAMPLE—send stamp. Buy/sell radio, computer equipment in "Electronic Exchange," Box 486E, Forest Lake MN 55025, BNB049

MENTS, microwave equipment, and components. Wanted: Late test equipment (H.P., Tek, G.R., Narda, etc.), waveguide/coax components. Immediate needs: H.P. K382A, R382A, S382C, 432A, 6522A, 415E, G.R. 874- and 900-series coax items, G.R. 1633, 1863, 1864. Request want list. Lectronics, 1423 Ferry Ave., Camden NJ 08104; (609)-541-4200. BNB050

HELP! Cleaning garage—test eqpt., 6m and 2m FM gear, tubes, 1000s of service manuals for all makes and models of commercial FM xceivers 1975 and older. Rea-

sonable prices. Send SASE for list. Tom McLaughlin WB4NEX, PO Box 411, Mango FL 33550; (813)-681-9709. BNB051

wanted—your unused TeletypeTM repair parts. High prices paid! Send SASE for list of Teletypewriter parts and supplies. TYPETRONICS, Box 8873, Fort Lauderdale FL 33310; (305)-583-1340 after 9:00 pm. N4TT. BNB052

WANTED: Old bugs for my telegraph and radiotelegraph key collection. I am trying to find each make and model of bug manufactured before 1950. Vibroplex, Martin, McElroy, Bunnell, Mecograph, MacDonald, D & K, Warner, etc. Also looking for Spark keys, Boston keys, cooties, sideswipers, and large or unusual radiotelegraph keys. 73 de Neal McEwen K5RW, 1128 Midway, Richardson TX 75081; 1-(214)-234-1653. BNB053

ON MARCH 11, 1984, the Morgan County Repeater Association Club will sponsor the Martinsville Hamfest at the Indiana Fairgrounds Pavilion Building in Indianapolis. Dealers, vendors, forums, and free paved parking. Doors open to the public at 8:00 am. Table reservations: Aileen Scales, 3142 Market Place, Bloomington IN 47401. BNB039

WYOMING-UTAH RANCH LAND. 10 acres, \$60 down, \$60/month. FREE information, maps, photographs. Trade equity for ham gear, home computer, test equipment, etc. Owner—Mike Gauthier K6ICS, 9550-B—Gallatin Rd., Downey CA 90240. BNB001

MOBILE IGNITION SHIELDING. Free literature. Estes Engineering, 930 Marine Drive, Port Angeles WA 98362. BNB006

QSL MANAGER ALBUMTM. Beautiful leather-grained vinyl ring binder for displaying 240 of your prized QSL cards. 30-day guarantee. \$18.95 ppd or send stamp for flyer. Walter Beaton WD8DVX, 3780 Cecilia Ave., Cleveland OH 44109. BNB009

WANTED: Early telegraph instruments for my collection. Keys, sounders, call boxes, registers, meters, and related items including pre-1910 paper. Larry Nutting WD6DTC, 5957 Yerba Buena, Santa Rosa CA 95405, BNB018

COLOR COMPUTER owners—call (212)-441-2807 for FREE color computer hardware and software catalog or write to Spectrum Projects, 93-15 86 Drive, Woodhaven NY 11421. BNB023

FOURTH ANNUAL Ohio State Convention and Flea Market: Join in the even bigger "Cincinnati ARRL '84," February 25 and 26. Activities for hams and electronics enthusiasts: forums, meetings, vendors, Wouff Hong, women's activities, banquet, hospitality suite, more. Sure cure for "cabin fever." Hospitality suite Friday and Saturday nights. The \$5 convention registration includes all convention awards. Flea market is \$4/space for two days-ham and electronics items, only. Write: Cincinnati ARRL '84, POB 11300, Cincinnati OH 45211 or telephone (513)-825-8234. Vendor and exhibitor inquiries invited, BNB024

WANTED: Cash paid for used SPEED RADAR EQUIPMENT. Write or call: Brian

R. Esterman, PO Box 8141, Northfield IL 60093; (312)-251-8901. BNB030

RTTY FDM DEMODULATORS. FDM RTTY exists on satellites, FM SCA broadcast subcarriers (e.g., Commodity News Service), and HF radio. Four solid-state synthesized models, NSA surplus, new-used, \$50 to \$350. Call/write for brochure. Electrovalue Industrial, Inc., Box 376-WF, Morris Plains NJ 07950; (201)-267-1117. BNB032

special Notice—Buy and sell your amateur equipment, computers, and video equipment on our national computer system that you access from your home, etc. Ads are updated daily. Low cost is only \$15.00 per year for unlimited access 24 hours a day. For details, send SASE, NAR-WID ELECTRONICS, 61 Bellot Road, Ringwood NJ 07456, BNB037

TRS-80 1/3/4 RTTY/ASCII/MORSE. Free specs. Software and hardware schematic, \$24.95 postpaid. KCQ Software, 6319 Boeuf Trace, Alexandria LA 71301. BNB038

ON MARCH 11, 1984, the Morgan County Repeater Association Club will sponsor the Martinsville Hamfest at the Indiana Fairgrounds Pavilion Building in Indianapolis. Dealers, vendors, forums, and free paved parking. Doors open to the public at 8:00 am. Table reservations: Aileen Scales, 3142 Market Place, Bloomington IN 47401. BNB040

FOR SALE OR TRADE: Swan 100MX 5-band solid-state transceiver and ac PS and Heathkit SB-201 amplifier, \$325 each. Wanted: CW transceiver. W7LHO, (505)-471-6377. BNB041

BUMPER STICKER—"My Favorite Radio Station Is (your callsign)." Display anywhere! Great gift idea. Only \$3. Arpress, Dept. ST, 1556 Hicks Pike, Walton KY 41094. BNB042

PRINTERS: LA36 Decwriter II with keyboard, variable-width paper, etc., \$325. CDI 1030 with keyboard, built-in modem, \$125. W9QH, 11209 Hwy. U, Wausau WI 54401. BNB043

WWV RECEIVER, \$35. Rf signal generator, 80 kc to 60 mc, \$35. Hickock tube tester, \$30. Audio signal generator, \$35. K6KZT, 2255 Alexander, Los Osos CA 93402. BNB044

MILITARY TECHNICAL MANUALS for old and obsolete equipment. 60-page catalog, \$3.00. Military Technical Manual Service, 2266 Senasac Ave., Long Beach CA 90815. BNB045

RUBBER STAMPS: Name, call, and address. \$3.75 postpaid, US. Floyd Durand W5YZC, PO Box 67, Westwego LA 70094. BNB046

on the air, comply with no-visible-antenna rules, from most indoor locations. Inexpensive, easy-to-build antenna couples directly to 50-Ohm coax; no antenna matcher required. Omnidirectional with vertical, bi-directional with horizontal polarization. Vswr typically 1.2:1 at resonance; useful bandwidth 3 to 5 percent of resonant frequency. Plans and instructions, \$12.50 postpaid. H. Stewart Designs, PO Box 643, Oregon City OR 97045. BNB047

VESTECH ELECTRONICS

ICOM	TEN-TEC	YAESU
IC2AT\$219	Corsair \$1,019	FT208R \$284
IC02AT\$319	Argosy II \$529	FT230R\$289
IC25A\$319	2591 2m HT \$289	FT726R \$729
IC25H\$349	Satellite Station \$419	FT290R \$359
IC27ACall	AZDEN	FT77\$539
IC730 \$599	PCS-300 \$279	NEW-FT757GX Call
IC745	PCS-4000/4800 \$289	FT102\$899
IC751 \$1,239	PCS-4300 \$349	FT980\$1,339
R70 \$599		FT-ONE

WESTECH ELECTRONICS is your dealer for Ten-Tec, ICOM, Yaesu, Azden, Astron, Hy-Gain, Cushcraft, Butternut, Bencher, Vibroplex, Nye-Viking, MFJ, Daiwa, Kantronics, Digimax, and more. Free shipping (UPS brown) on prepaid orders (Cashier's Check/M.O.). Prices and availability subject to change; please call for latest information.

RTE 286, PRESQUE ISLE PLAZA, PITTSBURGH, PA 15239 CALL (412) 733-1555 MT&W 10-6 Th&F 10-8 Sat 10-2

VISA

OWN THE WORLD WITH THE R3

NO RADIAL VERTICAL 10, 15, 20 METERS

The R3 half wavelength design eliminates the ground radial system required by other verticals. Optimum current distribution gives more efficiency and low angle radiation for DX communications.


R3 brings high performance antenna features to those living in apartments, condominiums or on small city lots. Even if you have plenty of space, R3's combination of neat appearance and DX capability make it ideal for your station. The R3 includes an integral turner to give a perfect match across 10, 15, and 20 meters. The remote tuning feature allows easy fingertip control as you operate your station.

R3 is a complete antenna system ready to install in virtually any location from ground level to roof top.


FEATURES


3 dB Gain, ref 1/4 Nwhip No Radials 360° Coverage Integral Tuner with Remote Control Console and Indicator 24 Volts To Tuner 110 or 220 Volt Operation 75 ft (22.9m) Control Cable Included Only 22ft (6.7m) High 1 sq ft (.09 sq m) Space Self Supporting Stainless Steel Hardware Mount: Sleeve Type Fits Pipe Up To 13/4 in (4.5cm) dia Can Be Easily Stored and Set Up For Portable or Temporary Operation

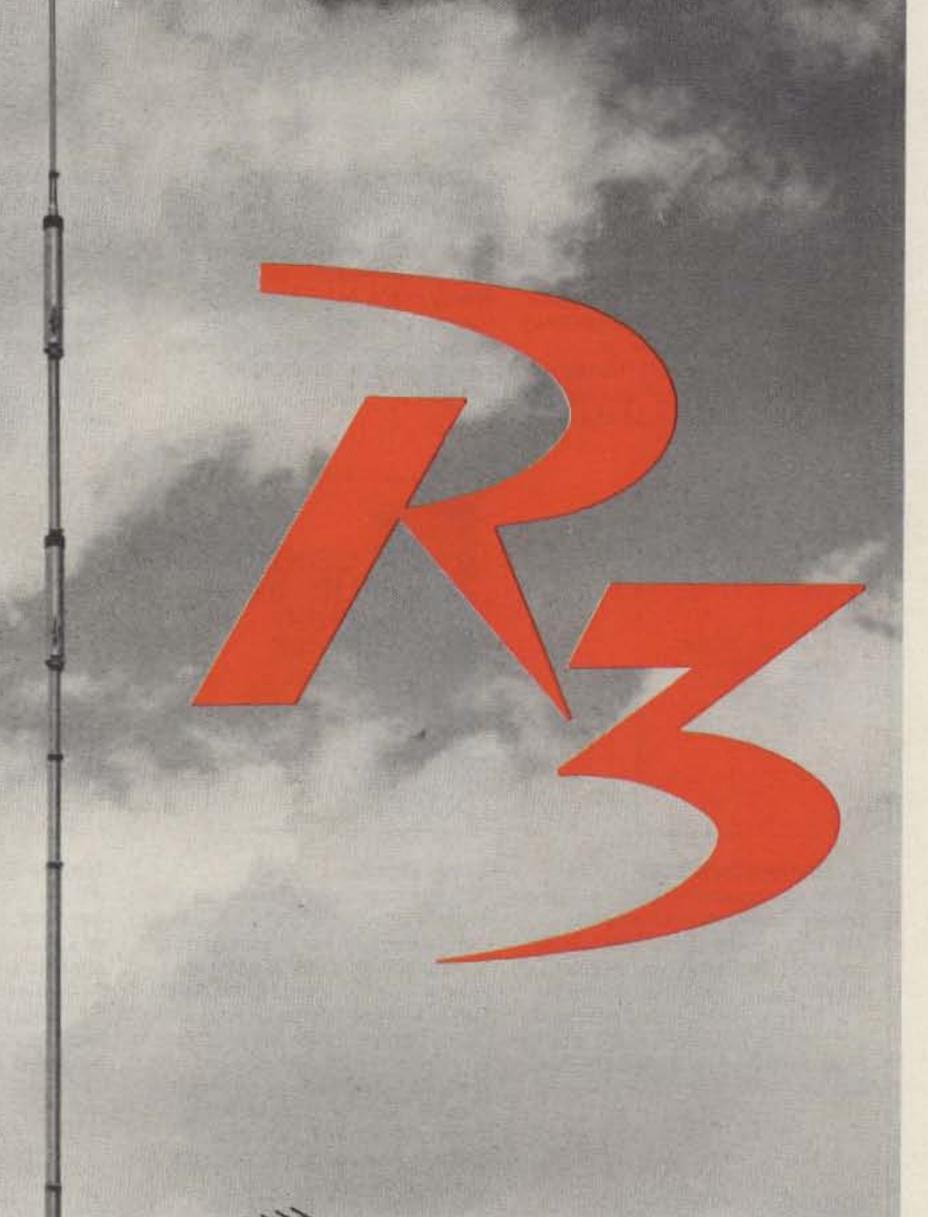Add up the features-you'll find that you can have ALL OF THIS PERFORMANCE without the need to buy tower, rotator and associated hardware. R3 IS ANOTHER PRODUCT CREATED FOR THE ENJOYMENT OF YOUR HOBBY BY THE WORLD RENOWNED CUSHCRAFT ENGINEERING DESIGN TEAM.



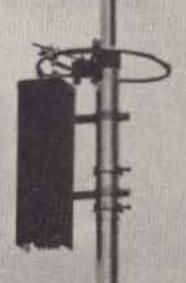THE ANTENNA COMPANY 48 Perimeter Road, P.O. Box 4680 Manchester, NH O3108 USA TELEPHONE 603-627-7877 TELEX 953-O50 CUSHSIG MAN AVAILABLE THROUGH DEALERS WORLDWIDE




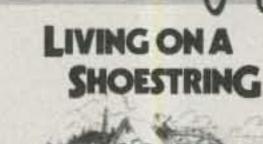




The New Weather Satellite Handbook

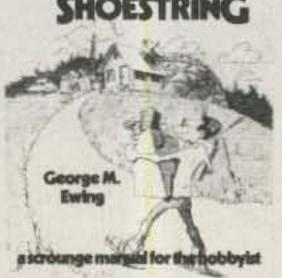All the information on the most modern spacecraft in orbit. This handbook includes material for newcomers and experienced satellite watchers. Included are hardware designs and instructions for building and operating a tracking station. One chapter covers tracking with a microcomputer. \$8.95 BK7383 131 pp.




Living on a Shoestring

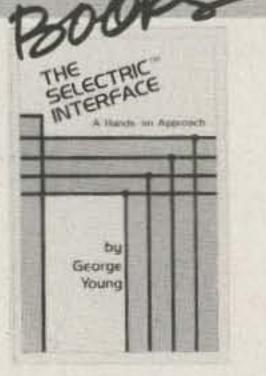Save money by scrounging surplus and putting it to use. This book shows you how—at home or in the ham shack. Projects include cutting energy costs, building a dome house, constructing ham gear, transportation, and more money-saving ideas. \$7.97 BK7393 125 pp.



The SelectricTM Interface

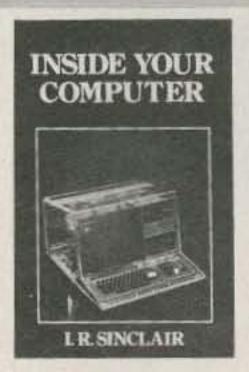
You can turn an IBM Selectric I/O writer into a letter-quality printer for your computer. The Selectric TM Interface gives you the programs and step-by-step instructions you need for Selectric models 2740, 2980, and Dura 1041. With slight modification, the instructions will work for various chips. \$12.97 BK7388 124 pp.



Inside Your Computer


Find out what goes on inside your machine. Inside Your Computer explains microcomputer circuits and how they work. Topics include chips, interpreters, circuits, machine language, binary numbers, algorithms, ASCII code, software, and what they all mean to the computer. Includes many photographs and schematics.

\$12.97 BK7390 108 pp.

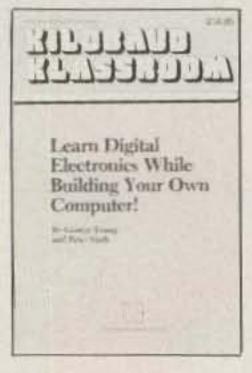

Kilobaud Klassroom

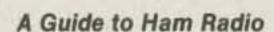Learn electronics with this hands-on course. This collection of electronics projects starts with simple concepts and takes you on to building your own small computer. You'll learn electronics theory and get the practice you need to master digital electronics. \$14.95 BK7386 393 pp.




Find out what it takes to communicate across the globe. This book answers your questions—from getting a license to setting up your station and broadcasting. You'll learn to use voice, Morse code, teletype, television, and satellites.

\$4.95 BK7321 48 pp.

The Propagation Wizard's Handbook

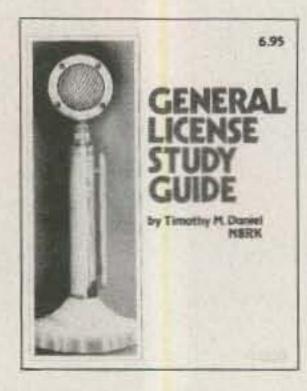This book by one of the best forecasters in America teaches the art of propagation forecasting. You'll read about magnetic storms, shortwave radio blackouts, long distance television, interference, and how they relate to the planets. \$6.95 BK7302 136 pp.



Study Guides

Join the hams who know what ham radio is all about. 73's study guides stress learning, not memorization, to help you study for the license exams. The General License Study Guide and the Novice License Study Guide provide all the information you need to earn a Novice or General ticket. Review questions included. Novice License Study Guide \$4.95 SG7357 General License Study Guide \$6.95 SG7358

The Magic of Ham Radio

Learn about the special hobby of ham radio in this account from a 60-year veteran. Jerry Swank has watched radio grow from the days of Model A spark coils to microprocessors and satellites. From his experiences and those of others, he has written this entertaining and moving account of ham radio history. \$4.95 BK7312 155 pp.

The Contest Cookbook

Discover the secrets of contest winners. This book covers domestic, DX, VHF, and 160-meter contests, with hints on everything from search and pounce to paperwork. You'll also learn to make 150 contacts in one hour. \$5.95 BK7308 170 pp.



Novice Study Tapes

It's easy to learn Novice theory from cassette. These tapes from the staff of 73 teach you what you need to know to breeze through the Novice written exam. Topics include theory, FCC regulations, operating skills, and setting up a station and getting on the air. \$15.95 CT 7300 Set of 3



Code Tapes

Mastering Morse code is easy with these code practice tapes. This series of tapes will help beginners and advanced hams get the practice they need. All cassettes are 60 minutes. Tapes are \$4.95 each. 5 wpm CT7305 6 + wpm CT7306 13 + wpm CT7313 20 + wpm CT7320 25 + wpm CT7325

Behind the Dial

You can have access to everything behind the dial, including government communications. This guide covers designing and using a receiving installation for the first 100 MHz of the radio spectrum. Included are electromagnetic spectrum, surveillance, station layout, antennas, and more. \$4.95 BK7307 57 pp.

SSB...The Misunderstood Mode

Discover the secrets of one of ham radio's least understood areas. This book presents several methods of sideband generation, which will let you construct a sideband generator. \$5.50 BK7351 96 pp.

VHF Antenna Handbook

A wealth of projects to show you how to build any kind of antenna. This book details theory, design, and construction of hundreds of VHF and UHF antennas. Included are dipoles, phased and parasitic arrays, polarized and nonresonant antennas, and more. \$5.95 BK7368 94 pp.

World Repeater Atlas

Special price on the 1980 edition.
You'll get repeater listings
throughout the world indexed by
location and frequency. Over 50
maps pinpoint 2000 repeaters
across the U.S. Foreign listings also
included. \$2.00 BK7315 274 pp.

-145

For credit card orders, call toll-free, 1-800-258-5473. Or send your order on a separate piece of paper to: Wayne Green Books, Retail Sales, Peterborough, NH 03458. Be sure to include the book title, order number, and price. Postage and handling is \$1.50 for the first book, \$1.00 for each additional book. Foreign air mail is \$10.00 per book. Check, money order, or complete credit card information must accompany your order. If you have questions about your order, write customer service at the above address.

SOCIAL EVENTS

Listings in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (if any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received by 73 Magazine by the first of the month, two months prior to the month in which the event takes place. Mail to Editorial Offices, 73 Magazine, Pine St., Peterborough NH 03458.

TRAVERSE CITY MI FEB 11

The Cherryland Amateur Radio Club will hold its 10th annual swap and shop on February 11, 1984, from 8:00 am to 1:00 pm, at the Immaculate Conception School Gym, 2 blocks south and 1 block west of the intersection of M-37 and M-22, Traverse City Ml. Registration will be at the door. Talk-in on 146.25/.85. For more information, call Jerry Cermak K8YVU at (616)-947-4848.

MANSFIELD OH FEB 12

The Mansfield Midwinter Hamfest/Auction will be held on Sunday, February 12, 1984, beginning at 8:00 am, at the Richland County Fairgrounds, Mansfield OH. Tickets are \$2.00 in advance and \$3.00 at the door. Tables are \$5.00 in advance and \$6.00 at the door. Half tables are available. Talk-in on 146.34/.94. For additional information or advance tickets and tables, send an SASE to Dean Wrasse KB8MG, 1094 Beal Road, Mansfield OH 44905, or phone (419)-589-2415.

MELVILLE NY FEB 19

The Long Island Mobile Amateur Radio Club will hold the LIMARC Indoor Hamfair '84 on February 19, 1984, from 0900 to 1600, at the Electrician's Hall, 41 Pinelawn Road, Melville NY. Admission is \$3.00 each for everyone. Table reservations are \$10.00 each, payable in advance to Bob Reed WB2DIN, 2970 Valentine Place, Wantagh NY 11793. Food and refreshments will be available. Talk-in on 146.25/146.85 (W2VL/R) or 146.52 simplex. For additional information, contact Al Flapan WA2FBQ at (516)-796-2965 or Hank Wener WB2ALW at (516)-484-4322.

LANCASTER PA FEB 19

SERCOM, Inc., and the Red Rose Repeater Association will sponsor the 1984 Lancaster Hamfest on Sunday, February 19, 1984, from 0800 to 1600, at the Guernsey Sales Pavilion, US Routes 30 and 896, Lancaster PA. General admission is \$3.00 for all hams and dealer personnel; tailgating is free with general admission, weather permitting. Commercial tables (main hall) are \$15.00 and noncommercial tables (rear annex) are \$6.00. Talk-in on 146.61 and 147.015. For reservations, send a check payable to SERCOM, Inc., to Hamfest Committee, PO Box 6082, Lancaster PA 17603.

ELKIN NC FEB 19

The seventh annual Elkin Winter Ham-

fest will be held on Sunday, February 19, 1984, at the Elkin National Guard Armory, located two miles off Interstate 77 at Exit 85 in Elkin NC. Doors will open to the public at 0830, and breakfast and lunch will be served at the hamfest by the Foothills ARC of Wilkesboro NC and the Briarpatch ARC of Galax VA. Talk-in on 144.77/145.37, 146.22/.82, and 147.69/.09. For table reservations (which are limited) or other information, contact either George Reeves WD4BMG, Route 6, Box 412, North Wilkesboro NC 28659, (919)-670-2803, or Tommy Lineberry WD4BTF, 308 Poplar Street, Galax VA 24333, (703)-236-8424.

GLASGOW KY FEB 25

The annual Glasgow Swapfest will be held on Saturday, February 25, 1984, beginning at 8:00 am Central time, at the Glasgow Flea Market Building, 2 miles south of Glasgow, just off highway 31E. Admission is \$2.00 per person. There is no additional charge for exhibitors. The first table per exhibitor will be free, and extra tables will be available for \$3.00 each. There will be a large heated building, free parking, free coffee, and a large flea market. Talk-in on 146.34/.94 or 147.63/.03. For further information, write Bernie Schwitzgebel WA4JZO, 121 Adairland Court, Glasgow KY 42141.

FRIDLEY MN FEB 25

The Robbinsdale Amateur Radio Club will hold its 3rd annual Midwinter Madness Hobby Electronics Show on Saturday, February 25, 1984, from 9:00 am to 3:00 pm, at Totino-Grace High School, 1350 Gardena Avenue NE, Fridley MN (a Minneapolis suburb). Admission is \$3.00 in advance and \$4.00 at the door. There will be manufacturers and dealers of ham, computer, satellite, and R/C gear, as well as seminars and a flea market. Talk-in on 146.52 simplex or the 147.60/.00 repeater (KOLTC). For more information, contact Robbinsdale ARC, PO Box 22613, Robbinsdale MN 55422, or call Bob at (612)-533-7354.

AKRON OH FEB 26

The Cuyahoga Falls ARC will hold its 30th annual electronic equipment auction and hamfest on Sunday, February 26, 1984, from 8:00 am to 4:00 pm, at North High School, Akron OH. There is easy access from the Tailmadge Avenue off-ramp of North Expressway (Rte. 8). Tickets are \$2.50 in advance and \$3.00 at the door. Some tables are available for \$2.00 or sellers may bring their own; advance reservations are advised. Talk-in on .871.27. For more details or reservations (please include an SASE), write CFARC, PO Box 6, Cuyahoga Falis OH 44222. Table reservations may also be made by calling Bill Sovinsky K8JSL at (216)-923-3830 and will be held until 9:00 am.

EGG HARBOR CITY NJ MAR 10

The Shore Points Amateur Radio Club, Inc., will hold the Springfest '84 on Saturday, March 10, 1984, from 9:00 am to 4:00 pm, at the Atlantic County 4-H Center, Egg Harbor City NJ (approximately 15 miles west of Atlantic City). Admission for buyers is \$2.50 in advance and \$3.00 at the door, sellers' space is \$5.00 (bring your own table). There will be 8,000 square feet of heated indoor selling space, and covered tailgating will be available, weather permitting. For more information, write SPARC, PO Box 142, Absecon NJ 08201.

INDIANAPOLIS IN MAR 11

The Morgan County Repeater Association Club will hold the Martinsville Hamfest on March 11, 1984, indoors at the Indiana State Fairgrounds Pavilion Building, Indianapolis IN. Admission is \$4.00 at the door. Premium tables are \$30.00 each, flea-market tables are \$8.00 each, and flea-market space without a table is \$1.00. All tables must be reserved in advance and setup will be Saturday, March 10, from 1:00 pm to 9:00 pm. Space setup will be Sunday, March 11, from 6:00 am to 8:00 am. There will be free paved parking. Talkin on 147.21 and 146.52 simplex. For more information or table reservations, send an SASE to Aileen Scales KC9YA, 3142 Market Place, Bloomington IN 47401 before March 1.

WINCHESTER IN MAR 11

The Randolph Amateur Radio Association will hold its 5th hamfest on Sunday, March 11, 1984, from 8:00 am to 5:00 pm, in the National Guard Armory, Winchester IN. Ticket donation is \$3.00 and children under 12 years old will be admitted free. Table space (by reservation only) is \$5.00 with a table and \$2.50 without. There will be a flea market, dealers, programs, food, and drink. Setups will be on Saturday from 6:00 pm to 8:00 pm and on Sunday from 6:00 am to 8:00 am. Talk-in on 147.90/.30, 224.90/223.30, and 146.50. For reservations and more information, contact RARA, Box 203, Winchester IN 47394, or phone Jake Life W9VJX at (317)-584-9361.

MIDLAND TX MAR 17-18

The Midland Amateur Radio Club will hold its annual St. Patrick's Swapfest on Saturday and Sunday, March 17-18, 1984, at the Midland County Exhibit Building, east of Midland TX on the north side of Highway 80. The hours on Saturday are from 10:00 am to 6:00 pm and on Sunday

from 8:00 am to 2:30 pm. Registration is \$5.00 in advance and \$6.00 at the door; tables are \$6.00 each. Refreshments will be available. Talk-in on .16/.76 and .33/.93. For further information and reservations, please contact Midland Amateur Radio Club, PO Box 4401, Midland TX 79704.

DAYTON OH APR 27-29

The 1984 Dayton Hamvention's International VHF/UHF Conference will be held concurrently with the Hamvention from Friday through Sunday, April 27-29, 1984, at the Hara Arena and Exhibition Center, Dayton OH. There will be technical forums by acknowledged experts; noise-figure, dynamic-range, and antenna-range measurement contests; and a hospitality suite with refreshments. Technical papers and presentations on VHF/UHF topics of interest are being solicited for consideration. Potential speakers should submit their reguests immediately. For further information, contact Jim Stitt WA8ONQ, VHF/UHF Conference Moderator, 4126 Crest Manor, Hamilton OH 45011.

DAYTON OH APR 27-29

The Dayton Amateur Radio Association, Inc., will sponsor the Dayton Hamvention on April 27-29, 1984, at the Hara Arena and Exhibition Center, Dayton OH. Admission, valid for all three days, is \$7.50 in advance and \$10.00 at the door. The Saturday evening Grand Banquet and Entertainment is \$14.00 in advance and \$16.00 at the door. Harry Dannals W2HD, past president of the ARRL, will be the featured speaker. Because seating is limited, early reservations are requested. There will be a giant flea market starting at noon on Friday and continuing all day Saturday and Sunday. Flea-market space is \$15.00 for all three days and will be sold in advance only. Entrance for setups will be available starting Wednesday and the special flea-market telephone is (513)-223-0923. Other features will include forums, awards, and exhibits. For special motel rates and reservations, write Hamvention Housing, Box 1288, Dayton OH 45402; no telephone reservations will be accepted. Address all other inquiries to Box 44, Dayton OH 45401, or phone (513)-433-7720. Please send advance registration checks to Dayton Hamvention, Box 2205, Dayton OH 45401.

FCC

Reprinted from the Federal Register

Changes in Procedures for Approval of Proposed Antenna Structures in the Amateur Radio Service; Announcement of Effective Date and Correction

AGENCY: Federal Communications Commission.

ACTION: Final Rule; announcement of effective date and correction.

SUMMARY: The effective date of rules amending this document sets Parts 17 and 97 to change procedures for approval of proposed antenna structures in the Amateur Radio Service (2-5-81; 48 FR 10915). The rule amendments were adopted by the Commission on January 8, 1981, but their effective date has been held in abeyance pending clearance of reporting requirements by the General

Accounting Office. The amendments are necessary to permit amateur radio operators to file a single form to obtain approval of proposed antenna structures, instead of the two forms (610 and 714) currently required. The effect of this action is a simplification of the antenna approval process for both amateur radio licensees and the Commission.

The antenna approval form number is 854.

DATE: The effective date of the rules changes is January 3, 1984.

In § 17.4(h), where there is a blank space following the word Form, insert the number 854. In § 97.45(a), where there is a blank space following the word Form, insert the number 854.

AWARDS

Bill Gosney KE7C Micro-80, Inc. 2665 North Busby Road Oak Harbor WA 98277

DX AWARDS FROM SWEDEN

The Bull Award

In order to make the province of Dalsland, Sweden, better known and to increase the activity of the amateurs in that region, the Melleruds Radio Club (SK6CM) decided to issue the Bull Award.

To qualify for this diploma, stations in Norway, Sweden, Finland, and Denmark must achieve 10 points, other European stations must achieve 5 points, and stations outside Europe must obtain 2 points credit. Every QSO with a radio amateur residing in Dalsland will give the applicant 1 point toward his or her goal. Should you have a QSO with SK6CM, 2 points will be credited to your total. All bands and modes will be allowed, but only one QSO with each station will count. All QSOs must be on or after January 1, 1979. Contacts via a repeater or satellite will not count.

Applications must list each callsign worked, date, time, GMT, band, mode, and the applicant's own name, call, and full mailing address. QSLs are not required. General certification rules apply. The award fee is 5 US dollars or 20 Swedish kroner. Send your application and award fee to Melleruds Radio Club, 464-00 Mellerud, Sweden.

As of April 25, 1979, the following amateurs would qualify for contacts to obtain this award: SK6CM, SM6s: AGW, ALJ, AMU, ASJ, AWZ, BER, BGG, BLE, BOT, BPX, CGI, CJK, CLX, CMK, CNC, COY, COZ, CQK, CUA, CWK, CYU, DKU, DXY, EOI, EPA, ESW, EUC, EUT, FCM, FFK, FLR, FNE, GAS, GDP, GMR, GQJ, HQZ, HRL, IHF, JJZ, JKB, JMA, JOD. JOG, JOM, JOO, JQA, JRB, JRY, JUJ, KFA, KFB, KFF, and ST.

The SWL Activity Club of Sweden and their award manager were very kind to send me complete award program information about the two major DX awards being offered by their organization.

Worked All Zone-14 Countries Award

This award is available to amateurs in three levels of achievement: Class A-work 27 countries in CQ Zone 14, Class B-work 22 countries in CQ Zone 14, and Class Cwork 15 countries in CQ Zone 14.

There are no band or mode limitations, nor are there any date restrictions known at this time. Applications for WAZ14CA are sent with US\$2.00 or 10 IRCs to SWL Club Activity, Fack 55, S-780, 40 Mockfjard, Sweden, GCR apply.

Countries in CQ Zone 14 are: CT1, CT2, C31, DA/DF/DJ/DK/DL, DM, EA, EA6, EI, F, G, GD, GI, GJ, GM, GU, GW, HB9, HB0, LA, LX, ON, OY, OZ, PA/PI, SL/SK/SM, ZB2, 3A, 4U (Geneva).

Worked ITU Zones 17/18 Award

This award is available to amateurs in three levels of operation: Class A-work all countries in ITU Zones 17/18, Class B-work 7 countries in ITU Zones 17/18, including TF (Iceland), and Class C-work 5 countries in ITU Zones 17/18.

Endorsements will be made available for single-band or -mode achievements. Applications must be sent to the SWL Club Activity with 10 IRCs or US\$2.00. Mailing address is Fack 55, S-780, 40 Mockfjard, Sweden.

Countries located in ITU Zones 17/18 are: ITU Zone 17-TF; ITU Zone 18-JW, JX, LA, OH, OHØ, OJØ/OHØM, OY, OZ, ZM.

Morokulien Award

Our good DX friend, Erland Belrup SM7COS, enlightened us with news about the charitable Morokulien (SJ9WL/ LG5LG) activity in the unique "state" on the Norwegian-Swedish border, east of Oslo, featuring radio calls LG5LG and SJ9WL and a lot more.

Recognizing the independency of this area, the Morokulien activities have been stimulated to benefit the handicapped radio amateurs in Norway and Sweden. Likewise, applicants for the Morokulien Award find their donated award fees going to aid these less fortunate people...a cause all of us can be proud to have assisted.

This unique DX award is available to licensed amateurs and SWLs. Only contacts after July, 1968, will count. Applicants are asked not to send QSL cards. GCR apply. Europeans must contact LG5LG and SJ9WL on two bands and on different days for a total of four days of operation.

All other applicants must work each of these two stations, each on a different day.

You may forward your application to the attention of Ulf Strandberg LA2ZN, Konglev. 3, N-2200 Kongsvinger, Norway. Please be sure to enclose an award fee of US\$3.00 or 8 IRCs. Additional contributions are most appreciated.

DX AWARD FROM ROMANIA

The Romanian Radio Amateur Federation takes pleasure in announcing the YO DX Club Award available to amateurs and SWL stations the world over.

YO DX Club Award

To qualify for the YODXC Award, applicants in Europe need to confirm contact with five YO DX Club members; stations outside Europe need confirm only two YO DX Club membership contacts. All QSOs must be made after August 23, 1949, and may be made on any mode or combination of modes and any band in the HF, VHF, or UHF segments.

To apply, have your list verified by at least two amateurs and send your list with US\$1.00 or 7 IRCs to: FRR (YODXC), PO Box 1395, R 76100 Bucuresti 5, Romania.

As of January 1, 1978, the following YO DX Club members count towards this award:

YO2s: ABW, AVP, BA, BB, BN, BS, BU, BV, CD, FP, GL, GZ, IS, KAB, KAC, KAR, QY, RA, VB, VF.

YO3s: AAJ, AAQ, AC, AVE, BAA, CR, DZ, FF, FU, JF, JU, JW, KAA, KBC, KSD, NN, QK, QO, RD, RF, RG, RK, RO, RX, VN, YZ. YO4s; ASG, CS, CT, HW, KAK, KBJ,

YO5s: AFJ, AMO, ATV, AUG, AVN, AY, BW, DS, KAD, KAU, KLA, LC, LD, LP, NB, NU, NZ, UW.

KCA, WO, WU, XF.

YO6s: ADM, AW, EX, KAF, KAL, KBA, KBM, LG, UX, XI.

YO7s: BI, DL, DO, KAJ, NA, NM, VS. YO8s: AGZ, CF, DD, FZ, GF, KAE, KAN, KGA, ME, MH, OK, OP, RL.

YO9s: APJ, ASS, BGV, CN, EM, GP, HH, HI, HT, IA, IF, KAG, KPD, VI, WL.

YOUS: ITU, YROA.

In YO-land, the suffix for the same licensed ham is the same for any prefix.

DX AWARDS FROM THE RADIO **CLUB OF PARAGUAYO**

The All Mediterranean Countries Award

The AMCA is given for confirmed contacts with Mediterranean countries in three levels of achievement: Class A-41 countries, Class B-30 countries, and Class C-20 countries. A ZP contact is obligatory in any class of award. The following prefixes qualify as valid contacts: A2, A5, AC3, C31, CP, HA, HB, HB0, HV, JT, LX, OE, OK, TL, TT, TZ, UC2, UD6, UG6, UH8, UI8, UL7, UM8, UO5, XT, XW8, YA, ZE, ZP, 3D6, 4U1, 5U7, 5X5, 7P8, 7Q7, M1(9A). 9J2, 9N1, 9U, 9X.

All Zone 11 Prefix Award

The AZ11PX Award is given for confirmed contacts with prefixes in CQ Zone 11 as follows: Class A-30 prefixes, Class B-19 prefixes, and Class C-12 prefixes.

ZP1 to ZP9, PY1 to PY0, and the special prefixes used for WPX contests are the only prefixes which qualify for this very difficult award.

The Tropics of Cancer and Capricorn Award

The TCCA Award is afforded to those applicants who confirm contacts with countries touched by the Tropics of Cancer and Capricorn boundaries. A ZP contact is obligatory for this award. For Class A, 28 country contacts are required from the list below. Class B requires 20 countries; Class C requires 12 countries. The following prefixes qualify as valid contacts:

Tropic of Cancer: S2/3, BV, BY, EA9, KH6, A4, A6, SU, TZ, C6, VU, XE, XZ, 5A, 5T5, 5U7, 7X, 7Z.

Tropic of Capricorn: A2, CE, C9, LY, PY, VK, ZP, ZS, ZS3, 5R8.

The Diploma Sud-America

The DSA Award is given for contacts with countries located in ITU Zones 12, 13, 14, 15, 16, and 73 as follows: Class A-33 DX countries and 6 ITU zones, Class B-25 DX countries and 6 ITU zones, and Class C-18 DX countries and 5 ITU zones.

Countries which are qualifying contacts are:

Zone 12-FY, HC, HC8, HK, HK0 (Malpelo), OA, PZ, 8R, YV, CP1/8/9.

Zone 13-PY6/7/8, PYØ (Fernando de Noronha), PYO (St. Peter, St. Paul).

CP2/3/4/5/6/7, ZP, CX, LU-A/U/Y. Zone 15-PY1/2/3/4/5/9, PYØ (Trinidad

Zone 14-CE1/2/3/4/5, CE0X, CE0Z,

Island). Zone 16-CE6/7/8, VP8 (Falkland), LU-

V/W/X.

Zone 73-KC4USP, LU-Z, CE9AA/AM, VP8 (Graham Land), VP8 (Georgia), VP8 (So. Orkney), VP8 (So. Sandwich), VP8 (So. Shetland).

Diploma Paraguay

The DP Award is given for confirmed contacts with five different ZP stations. Stations in South America are required to contact 15 ZP operators.

Worked All ZP

The WAZP Award is being offered to amateurs making at least one confirmed contact with ZP stations in each of the ZP call districts, ZP1-ZP9.

Diploma Departmentos Del Paraguay

The DDP is given for confirmed contacts with the nation's capital and different departments into which Paraguay is divided. Class A requires 20 contacts; Class B requires 16 contacts; Class C requires 12 contacts.

Departments by prefix are: ZP1-Boqueron, Chaco, Nueva, Asuncion; ZP2-Altos, Pte. Hayes; ZP3-Amambay, Concepcion; ZP4-Canendiyu, San Pedro; ZP5-Asuncion (nation's capital); ZP6 -Central, Cordillera, Paraguari; ZP7-Caaguazu, Caazapa, Guaira; ZP8-Misiones, Neembucu; ZP9-Alto Parana, Itapua:

Contacts must be made on or after May 15, 1952, to qualify for any of the awards sponsored by the Radio Club of Paraguay. A certified list of contacts with a fee of 5 IRCs for each award should be sent to: Elio Donna ZP5CE, Award Manager, RC Paraguayo, PL Box 512, Asuncion, Paraguay.

3905 CENTURY CLUB **AWARDS**

Representing the 3905 Century Club, Bill Herbert WA2ZYM writes to share with us the various awards available to amateurs who frequent their net operation.

The 3905 Century Club is basically a WAS (Worked All States) net which grew out of the old Bicentennial Net on 80 meters back in 1976. The net now operates daily on 40 and 80 meters, 0100 -0500Z on 7.233 MHz and 0500-0800Z on 3.905.

Naturally, as time went on, it became apparent that an awards program of some kind was in the offing. As amateurs work each other on the band, they gather a point per contact. Once 100 points are earned, you become a full-fledged member of the club and are issued a certificate to illustrate your affiliation.

As members continue their contacts on the net, several levels of achievement are recognized, with the ultimate being the 1,000-Point Award, which is certainly no overnight venture.

Among the certificates afforded net participants is the 3905 Century Club State Capitals Awards, which requires the applicant to contact at least 35 state capital cities. Endorsements are given for 40, 45, and the maximum of 50 state capitals worked on the sponsor net.

HAROAA AWARDS

We believe the many long hours of dedicated operation should not go unnoticed, nor should the high degree of enthusiasm of amateur-radio operators go neglected in their pursuit of self-set goals. That is why we have an awards column in this magazine and why I introduce to you the awards and certificates made available by HAROAA.

As we review each one individually, we find that all their awards are of high quality and will make a very impressive addition to any radio shack.

GCR apply in making application for HAROAA Awards. Each award is two dollars or 5 IRCs. At your request, special endorsements will be added for CW, SSB, RTTY, SSTV, FM, QRP, All YL, or single band. There is no date restriction on contacts made and satellite contacts are permitted.

HAROAA DX Award

For this, the most popular of all HAROAA achievement awards, the applicant is awarded recognition for contacting 10 DX stations. Endorsements are also given for 25, 50, 75, 100, 200, and 500 DX contacts. Keep in mind we are not speaking of DX countries, but instead, DX "contacts," which makes this award unique.

Great Lakes Award

This award requires one contact from each state bordering the Great Lakes: New York, Pennsylvania, Ohio, Michigan, Indiana, Illinois, Wisconsin, and Minnesota.

Insomnia Award

This award is earned for communicating with a single amateur station anywhere in the world for a minimum of one hour between the hours of 1:00 and 5:00 am. Truly a super conversation piece for any ham shack.

Super Certificate Hunters Award

This award is designed for the serious certificate hunter. To earn this award, you must have a minimum of ten amateurradio awards in your possession. Simply list these awards on your application and note the certificate number of each. Special endorsements are given for your collection of 25, 50, 75, 100, and 100 plus.

Official Traffic Handler Award

This award is a self-issued achievement, allowing you to display the fact that you are indeed an official handler of radio traffic.

HAROAA Super Operator Award

This certificate is rendered for those providing a service on behalf of amateur radio, such as weather observer, public service, emergency, helping a new ham, providing communications for a community function, etc. The requirements are for the applicant to briefly describe the event of service. The officials at HAROAA will determine whether it deserves this special recognition.

For your personal copy of HAROAA award program rules or to apply for any awards presented here, write: HAROAA Award Program, PO Box 341, Hinckley OH 44233.

NORAC WINTER CARNIVAL

The North Okanagan Radio Amateur Club will have a special station set up dur-

HAM HELP

I need schematics and manuals for the Hallicrafters S77 communications receiver, Heathkit HR-10 receiver, and Johnson Viking II transmitter. Thank you.

> Shawn Jerin 4-710 West Leila Ave. Tampa FL 33616

Has anyone had any trouble building the "Down-Under Depth Sounder" (July, 1983)? Mine won't work.

> C. G. Wortham N9AKD 28 W. 559 Rogers Ave. Warrenville IL 60555

I wonder if anyone has a parts catalog so that us old-timers can find radio and ham gear such as transformers, coils, chokes, and hard-to-find tubes.

> Clarence L. Frady 1207-A Old 70 West Black Mountain NC 28711

Needed: schematic for a DSI counter, Model 5600A. Happy to pay reproduction costs.

> John E. Greve 4211 7th Ave. Rock Island IL 61201

CORRECTIONS

Two errors crept into recent issues. In November (page 103), we inadvertently listed DA1TN as the third-place DX multiop finisher in the 1983 40m World SSB Championship. The correct callsign is DA1US.

Also, in "Idiot Buzzer for the 1978 Honda Civic" ("Circuits," December, page 99), the bottom three diodes are reversed.

CONNECTORS

TYPE 'N'

Jack Burnett Executive Editor

THE ONE STOP SOURCE SINCE 1959!!

UHF

PL-259 57¢ ea.

PL-258 79¢

UG-175/U OR 176/U .16e

UG-21/BU(MALE) \$2.35

COAXIAL CABLE RG-8/U (95% BRAID-FOAM)\$235/M" MICRO 8/U (95% BRAID-FOAM)115/M' RG-213/U (96% BRAID-POLY)270/M' RG-214/U (2-96% BRAIDS-POLY)495/M1

ROTOR CABLE 8/C HAMLINE (2-18/6-22)\$150/M' 8/C HAMLINE HD (2-16/6-18)340/M'

CALL COLLECT CALL FOR LARGE QUANTITY DISCOUNT



UG-27/CU(RIGHT ANGLE) \$4.45

UG-57/BU(DOUBLE MALE) \$3.15

UG-29/BU(DOUBLE FEMALE) \$3.15

(914) 947-1554-1555

Garnerville, New York 10923

ing its Winter Carnival (western Canada's largest). This is a free award but we would sure appreciate \$1.00 or 2 IRCs to cover the postage. The award is available to all amateurs worldwide who contact 3 Vernon area stations or QSO once with our club station VE7NOR; any mode or band is permissible. Our special station will be operating daily from February 1 until February 12, 1984. Times will be from 2100Z to 2430Z. Look for us in the General portion of each band, about 50 kHz up, calling "CQ Winter Carnival Award."

SCHOLARSHIP HONORS SENATOR GOLDWATER

In Washington DC on November 9, Senator Barry Goldwater (R-Arizona) announced to his fellow ham-radio operators around the world that the American Radio Relay League had established an annual \$5,000 scholarship award in his honor.

The League will award the scholarship to a licensed radio amateur enrolled in college-level study of electronics, communications engineering, or a related field. The program will be administered by the ARRL Foundation, Inc., the League's tax-exempt research and educational organization.

Goldwater, known to thousands of radio amateurs as K7UGA, made the announcement from his "ham shack" on Capitol Hill. Within seconds after the ceremonial transmission, Goldwater began receiving congratulatory messages from ham operators throughout the US and several foreign countries.

The late Vic Clark, League president, explained that Goldwater was selected as

honoree for the organization's new scholarship because his "selflessness and dedication to purpose as a government servant is widely recognized and deeply appreciated by both his fellow citizens and the radio amateurs of our country."

"Through his amateur-radio involvement, Senator Goldwater has brought joy to thousands of members of our armed services," Clark said, recalling that the Arizona senator opened his radio facilities for around-the-clock operations during the Vietnam War to provide a communications link between US military personnel in Southeast Asia and their families.

Goldwater, whose interest in amateur radio dates back to his teenage years, said the value of ham operators has been demonstrated repeatedly in times of local or national emergency.

The recent Grenada mission is a case in point. Practically no normal communications were available to the public. Hamradio operators quickly opened links with the Caribbean island, particularly handling messages relating to the safety of several hundred American students at St. George's College. It was through these amateur channels that the press and public received most of their information during the early days of the mission.

For a brief while, Americans were once again reminded of the important role played by radio amateurs. More often, though, the crucial contribution made by ham-radio operators has become "so commonplace that it often goes unnoticed and uncredited," Goldwater said.

Information about the scholarship program can be obtained from the ARRL Foundation, 225 Main St., Newington CT 06111.

SLEP SPECIALS

• -------

ROCKWELL/COLLINS

KWM-380 transceiver 9 band plus general coverage receiver, 5-30 MHz with WARC/MARS coverage, latest model with s/n above 2,200. All production bulletins thru #18, built-in AC/DC power supply LIST \$6,600.00, SALE \$5,475.00

KWM-380 OPTIONS

į	AC-3801 noise blanker	LIST	5	360.00, SALE \$	320.00
	AC-3802 speech processor				
	AC 3803 control interface	LIST	5	208.00, SALE \$	185.00
,	AC-3805A Keypad, ready to plug in control interface, as seen				
	in Collins ads,		5	175.00, SALE \$	135.00
,	AC-3810 CW filter, 360Hz,	LIST	5	180.00, SALE \$	160.00
	AC-3811 CW filter, 140 Hz,				
	AC-3812 RTTY filter, 1.7 KHz.				
	AC-3821 emergency DC stand-by cable,				
i	MM-280 hand held microphone,	LIST	5	64.00, SALE \$	56.00 .
	SM-280 desk microphone,	LIST	5	144.00, SALE \$	128.00 •
i	KWM-380 service manual			5	40.00 4

HENRY LINEAR TUBE AMPLIFIERS

1KD5, 1200 W PEP desk type, 3-500Z	LIST	\$ 695.00, SALE \$ 625.00
2KD Classic, 2KW PEP, desk type, pair 3-500Z	LIST	\$1,080.00, SALE \$ 969.00
2K Classic, 2KW PEP, console type, pair 3-500Z	LIST	\$1,395.00, SALE \$1,249.00
AK Classic X, 2KW PEP, console type, pair 3-500Z,	LIST	\$1,695.00, SALE \$1,525.00
3K Classic, 2KW PEP, console type, 8877 tube	LIST	\$2,695.00, SALE \$2,450.00

GO VHF/UHF DX WITH A HENRY SSB/CW AMPLIFIER

1002 A 146 MHz, 1 KW PEP input, rack mount, 8874 tube	\$ 895.00 .
1002 A-220, 220 MHz, 1 KW PEP input, rack mount, 8874 tube	\$ 995.00
1004A 430 to 450 MHz, 1 KW PEP input, rack mount, 8874 tube	. \$ 995.00
2002A 146 MHz, 2 KW PEP input, console, 3CX 800A7 tube	\$1,295.00
2002A-220 220 MHz, 2 KW PEP input, console, 3CX800A7 tube	
2004A 430 to 450 MHz, 2 KW PEP input, console, 3CX800A7 tube	

Shipping charges additional. We accept VISA/MC or TAKE ADDED BONUS OF 2% DIS-COUNT off purchase price by cashiers check or money order.

For personal service, write or phone Bill Slep 704-524-7519.



Slep Electronics Company

P.O. BOX 100, HWY. 441 OTTO, NORTH CAROLINA 28763

NEW PRODUCTS

TC-1 PLUS ATV TRANSMITTER/ DOWNCONVERTER

P. C. Electronics has upgraded their TC-1 all-in-one-box 420-450-MHz full-color ATV unit with some new features. The new unit is called the TC-1 Plus. With more and more amateurs using computers and VCRs on ATV, separate video and audio inputs were added to the existing camera and mike inputs. This allows front-panel switching back and forth between the camera and computer, or transmitting the VCR audio along with voice-over commenting using a microphone. It has made learning Basic computer language over the air and retransmitting the Space Shuttle video and audio easy.

Capability for external 13.8 V dc has been added to the built-in ac supply for those who want to go mobile or portable on battery power during Field Day, emergency services, CAP searches, parades, marathons, or other public-service events.

A video monitor output is now provided to enable seeing your own picture exactly as it is transmitted in order to better set modulation levels, lighting, etc. This is accomplished by the built-in diode detector on the transmitter rf power output stripline which then connects to the composite video-monitor line-driver circuit.

The TC-1 Plus has the new TXA5-5 exciter/modulator which features two-frequency plug-in crystal switching with just the addition of an SPST switch. Also, the bulletin sync stretcher and hi/lo power switch capability enable superior stable color video if a higher-power linear amplifier, such as the Mirage 100-Watt D1010N, is added later or run barefoot at its greater than 10 Watt PEP rf output.

The 420-450-MHz tunable downconverter has the low noise NE64535 preamp stage to dig out the weak signals. It acts like a super hot UHF TV tuner but covers only the 70cm ham band when connected to your TV set antenna input and set for channel 3 or 4. Both color video and sound live action ATV are available on your TV set just as the broadcast stations provide. The standards are the same.

With the TC-1 Plus, the only other items necessary to get on ATV are a good 70cm antenna and low-loss coax, your TV set, and any device with a standard low-voltage p-p composite video output commonly found on black and white CCTV cameras, home video color cameras and VCRs, computers, RTTY/video converters, etc. A Technician class or higher amateurradio license is required for operation and purchase from P. C. Electronics.

For more information and a complete catalog of ATV equipment, antennas, cameras, modules, and accessories, call or write P. C. Electronics, 2522 Paxson Lane, Arcadia CA 91006; (818)-447-4565.

SOFTWARE PROTECTION SYSTEM

Software Protection Devices, Inc., a division of Wayne Green Enterprises, has introduced Copyrighter, a hardware-based protection system using encryption technology. The Copyrighter system has been proven by beta testing to provide pirateproof software protection.

Software to be protected by Copyrighter is first encoded using a Data Encryption Standard (DES) algorithm which scrambles the machine code of the program. The customer, on the first use of the protected program, calls an 800 number and obtains a code which will unlock the program. The user types in this enabling number to decode the DES encryption and prepare it for use with the Copyrighter CPU (C-CPU).

The C-CPU is a standard CPU with a different decoder built into each unit. It is installed by a dealer on owned equipment or at the factory on new computers.

One C-CPU can be used to decode any number of protected programs, yet it will run unprotected software with no interference. This system does not slow down the CPU, even on protected programs. A protected program may be freely backed-up by the user on any medium and will run only on the user's computer.

Copyrighter software protection boundaries are flexible to allow the publisher to leave certain portions of their software, such as I/O routines, unprotected and modifiable by the user. All unprotected portions may be written in any programming language.

For more information, contact Ken Witham at Wayne Green Enterprises, Inc., 80 Pine St., Peterborough, NH 03458; (603)-924-9471. Reader Service number 480.



The System 70X satellite receiver from Lowrance Electronics.

SATELLITE RECEIVER

Lowrance Electronics of Tulsa, Oklahoma, has introduced a new satellite receiver for 1984. The new receiver unit, called the System 70, follows the firm's system 7 and will be manufactured at the company's headquarters in Tulsa. The receiver will be marketed through a worldwide distributor network.

The System 70 receivers feature detent tuning, polarity control, a signal-strength meter, built-in modulator, scan tuning, and wide and narrow audio filters. The receivers are available as the standard model 70X or the stereo version, 70S, which decodes both matrix and discrete stereo sound and features simplified stereo tuning. Both models carry a full one-year warranty.

For additional information, contact Lowrance Electronics, Inc., 12000 E. Skelly Drive, Tulsa OK 74128. Reader Service number 479.

NEW TRIBAND BEAMS

Palomar Engineers has announced the availability of two triband beams. Model DX-33 has three elements on 10, 15, and 20 meters. Model DX-43 has four elements.

These antennas have long been used by European DXers and are being made available in the US for the first time.

Designed for use with solid-state transceivers, the antennas feature low swr and wide bandwidth. Gain and front-to-back ratio are particularly good. Each trap is individually sweep tested at the factory for uniform performance. Stainless-steel U-bolts are used throughout.

For more information, contact Palomar

Engineers, 1924-F West Mission Road, Escondido CA 92025; (619)-747-3343.

NEW SOFTWARE FOR THE TRS-80

Woodall Software has announced a TRS-80 program for transmission and reception of RTTY that does not require a TV or interface for operation. The SOFTTY program will work as well or better than software/hardware packages requiring a PLL decoder. Only the much more expensive TUs may give consistently better results.

Gary Woodall has devised an algorithm for this program that samples the incoming audio signal to measure the tone frequency and shift using the cassette READ port. This method is very effective and makes the system immune to most noise. The only thing that may be a problem is other signals which are almost exactly on your operating frequency.


The program was written entirely in Z-80 machine language to obtain the processing speed necessary for the algorithm and associated functions. Timing is very critical and necessitated close attention to T states and M cycles during programming (down to micro-seconds).

The tone-generating section of SOFTTY simulates the two RTTY tones by producing an alternating time-controlled voltage and outputting via the cassette WRITE port. The output from the AUX plug is then fed into the microphone input circuit of the transmitter. Most mike input circuits will smooth the simulated sine-wave signal, making it sound like a true sine wave when transmitted.


SOFTTY Version 1.0 has split-screen



P. C. Electronics' ATV unit.

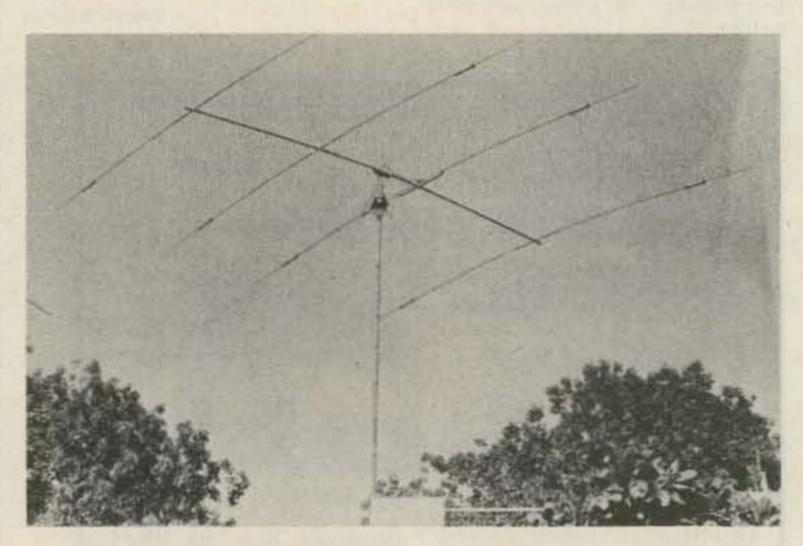

Triband beams from Palomar Engineers.

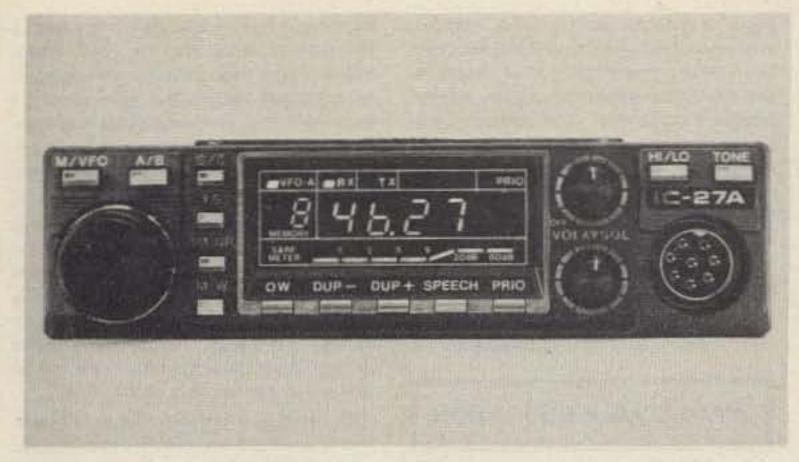

The IC-27A mobile unit from Icom.

operation so that the main buffer may be filled while decoding and displaying the received signal. A choice of high and low toners is keyboard selectable, as well as normal and inverted (mark/space or space /mark) tone detection.

SOFTTY 1.0 is set for a 170-Hz tone shift used by amateur-radio operators. Other versions are available for different shifts used by news and weather services. A visual tuning indicator makes setup easy to accomplish.

There are five programmable buffers available, each of which can hold up to 255 characters. They can be filled from the keyboard and saved to magnetic tape for later retrieval.

For more information, contact Bill Gouge or Gary Woodall at Woodall and Associates, PO Box 284, 11 Glenda Drive, Plainfield IN 46168; (317)-271-2565. Reader Service number 481.

NEW FROM ICOM

of amateur equipment: the IC-27A twometer 25-Watt mobile unit, the IC-04A and IC-04AT 440-MHz hand-held transceivers, and the IC-271H 100-Watt two-meter basestation transceiver.

IC-27A

The IC-27A is an important breakthrough in two-meter mobile communications. Measuring 1-1/2 inches high by 5-1/2 inches wide, the IC-27A contains an internal speaker making it easy to mount. Although the IC-27A is compact, it has not sacrificed any features. Standard features include 25 Watts of output power, 32 PLTM frequencies, ten full-function tunable memories, scanning of memories and the band, priority scan, and a microphone which includes a 16-button touchtone TM pad for access to a repeater or dialing through to an autopatch. An optional speech synthesizer also is available to verbally announce the receiver frequency of the transceiver through the push of a button.

The IC-25A, measuring 2 inches wide by 5-1/2 inches high, will continue to be available for those individuals preferring a 25-Watt two-meter mobile unit with larger operating knobs.

IC-04A and IC-04AT

Icom has announced their latest in 440-MHz hand-held transceivers: the IC-04A and IC-04AT. These multi-function, multi-feature hand-helds for 440-449.995 MHz feature frequency entry, control functions, and 32 PL tones which are controlled by the 16-button pad on the face of the radio. Also included are priority scanning (both of memories and programmable band scan) and DTMF (04AT only).

For scanning, 5-kHz increments are front-panel selectable. Ten memories with internal lithium battery backup afford flexibility for channelizing operation for easy access to most-used channels. The custom LCD readout with S-meter is unique.



The Icom IC-271H transceiver.

The IC-04A and IC-04AT have the same styling, control features, and functions as the IC-02A(T) and utilize the existing accessory line available for the IC-2A and IC-2AT plus new accessories such as long-life and high-power battery packs.

IC-271H

For two-meter communications, Icom also has developed the IC-271H, a transceiver with a high dynamic range receiver and a 100-Watt transmitter. Operating from the IC-PS30, IC-PS15, or the internal IC-PS35 (optional), the IC-271H integrates all the functions of the latest CPU-controlled radios.

Standard features include 100 Watts of power, 32 built-in subaudible tones, 32 full-function tunable memories, 10-Hz PLL locking, easy-to-read fluorescent display, scanning, and mode scan. It is 11-1/4 inches wide by 4-3/8 inches high.

To facilitate the operation of the IC-271H, Icom has incorporated a duplex touch switch, all-mode squelch, receive audio tone control, S-meter, center meter, seven-year lithium battery memory back-up, 24-pin accessory connector, and microphone. Optional features include a switchable preamplfier, CTCSS encoder/decoder (encoder is standard), computer interface, and voice synthesizer.

For more information, contact Icom America, Inc., 2112 116th Ave. N.E., Bellevue WA 98004; (206)-454-8155.



The IC-04A 440-MHz hand-held from Icom.

LETTERS

LOG PROGRAM AVAILABLE

The response to my article "Foolproof Logging" on page 58 of the November, 1983, issue of 73 was overwhelming. I had noted in the article that if enough persons were interested, I would make the program available.

The program is now available for the TRS-80 Model III under TRSDOS 1.3 and for the IBM-PC under PC-DOS 1.1 or 2.0. The cost is \$35.00 each including the diskette and user's manual. Postage is included in the cost. A version written in dBASE-II source code will be available by January 1, 1984, for several computers.

John E. Fall KL7GRF Long Beach CA

NO SNOBS IN SANTA FE

In response to the letter from Mr. Fearon printed in the October issue, please be advised that the snobbery he felt in Albuquerque has not reached the higher elevations and arrived in Santa Fe. Being 60 miles apart, there is a world of difference in all attitudes and amateur radio especially.

The Northern New Mexico Amateur Radio Club in Sante Fe will be more than happy to assist Mr. Fearon in directing him to hams who have the time and energy to be an Elmer. When I made up my mind to go for a ticket, I started going to the Saturday morning breakfasts the club holds each week at The Pantry restaurant. There I met the most helpful and supportive crowd of guys and gals and before you knew it, I had my ticket.

The NNMARC holds regular classes both for the Novice and for upgrading to other classes. All are at no charge.

The hams who helped me on the way to a license were most eager to do so and extended every courtesy to the point of going out of their way several times, especially when it came time for the Novice exam and code test.

So, not all Southwest hams are snobs, and I hope Mr. Fearon has by now found that to be true.

Michael Langford KA5SAT Santa Fe NM

ALBATROSS

The editorial in the October issue of 73 revealed some interesting things. I have found 73 to be a very enjoyable magazine. The editorial touched on one area I am in agreement with. QST and the League are getting to be a useless albatross to ama-

teur radio. The magazine has fewer and fewer technical articles and more and more pages of contest results and pat-emon-the-back data.

I am of the old school of home brew: If you want a transformer, wind it. I've even made my own tubes out of light bulbs. Now I run my computer on what the filament used to draw.

I am an amateur more interested in construction than in operating, so the "incentive" of the League left me cold. Similarly, there is a trend to buy everything from Japan, yet we developed the technology they copied or stole.

This country still has creative engineers, people who are amateurs. I call it poor-boy research, amateur because of low funds, not lack of skill. This country is becoming a high-technology and farm export country, though our government and corporations are too stupid to foster education or family farms.

I like 73's view of trying to stay ahead of the pack. The concept of developing a colledge (no, I didn't misspell college) can provide an "edge" to a student not fulfilled by some of our prestigious structured schools, provided it teaches creativity. Creativity is a rare commodity at best, yet it is the very thing that once made this country great.

Escalating the college via cable is a good limited short-term idea. But cable TV is dead, only still quivering because of greed and failure to make it duplex. The time will soon come when fiber optics will replace it, allowing duplex operation. There is your future.

In the meantime, the proliferation of satellite dishes (7-10') will fill the void of cable. Direct satellite broadcast (2' dishes) will bankrupt the cable companies.

The concept of interactive teaching is an area not touched. Suppose the main program (class) was on laser disk, supported and controlled by a magnetic diskette for your microcomputer. Q&A would be on the disk and your terminal CRT. Further support could be by packet transmitted to the satellite or local data line.

At present, I spend about \$1000 (plus) four times a year to go to schools: \$500 travel, \$500-\$800 class and lodging. Wouldn't it be more profitable if I could take an interactive class here for \$750 a year total?

The University of Wisconsin at Madison and Milwaukee has superb extension programs. George Washington University,

Georgia Tech, and UCLA have extension work in engineering. These people have skilled people come in from all over the country to teach a class, yet the school only organizes the class. I have made friends all over the country this way and gotten credits as a bonus.

Phil Jedlicka WD@EED Norman OK

CALL FOR PAPERS

The American Radio Relay League will hold its Third Amateur Radio Computer Networking Conference on April 15, 1984, in Trenton, New Jersey. The conference will be in cooperation with the 9th Trenton Computer Festival (TCF84) being held April 14–15 at Trenton State College.

The deadline for camera-ready papers is March 1, 1984. All papers should be mailed to Paul L. Rinaldo W4RI, American Radio Relay League, 225 Main Street, Newington CT 06111. If you plan to present a paper, please request an author's guide and identify the title of your paper immediately. Proceedings will be sold at the conference and by mail from ARRL Headquarters.

Technical papers are invited on all as-

pects of amateur packet radio, AMTOR, computer-based message systems, digital speech, presentation-level graphics, and related amateur-radio digital communications via terrestrial, ionospheric, meteor-scatter, and satellite media including AMSAT-OSCAR 10 and PACSAT. Topics may include network and system architecture, proposed standards, hardware, software, protocols, modulation and encoding schemes, applications, and practical experience.

Paul Rinaldo W4RI Newington CT

MARKETABLE EDUCATION

I enjoyed the editorial in the October issue of 73. However, I would go a little bit
further. I think that education is a big issue now and, if handled correctly, will
bring huge profits for the first businesses
to take full advantage of it. I think that the
attention focused on education by the
presidential commission and the media
has helped to make the time ripe for business to enter. I speak with some experience, since I now teach mathematics and
computer science at the college level. The
emphasis placed on computers and high

technology has created an anxiety among the general public to the point where those people unacquainted with computers either fear them or feel guilty about it. I have several friends who have made decent amounts of money by conducting private classes in Basic and in the operation of specific home computers.

I think that video disks—the interactive kind—would be fantastic educational media. There is now out an arcade game using interactive video disks and the kids line up ten deep waiting to use it at the arcades. Compared to standard video games, the graphics (or effective memory) of these things is really astounding.

On a slightly different subject, I think that if a simple and reliable packet node controller could be developed to the point where it was a black box whose use was transparent to the user, it would revolutionize both the ham-radio and the home-computer communities. With the popularity of computer networks such as Compuserve and The Source and with drastic rises in local telephone rates imminent, the time will very soon be ripe for both a digital (no-code) license and PACSAT-type satellites.

Warren Ziegler KI1E/2 Staten Island NY

DR. DIGITAL

Robert Swirsky AF2M PO Box 122 Cedarhurst NY 11516

ON LANGUAGE

At a recent meeting of the WA2DCS computer club, John KI2U asked me if I was working on any interesting computer projects. John always expresses interest in my programming endeavors; perhaps it's because I tend to write unusual programs. I have been known to spend months doing some of the weirdest things ever done with a computer (at least by means of a program).

One of my favorite projects that I finished this past year was an adventure game called "Time Warp." This program needs three interconnected computers to run, not to mention a sound system. The game is based on the movie, The Rocky Horror Picture Show, and the objects are to save Dr. Frank N. Furter from death and to lead some other characters to safety. I'm not so sure if my results were worth the effort, but at least I gained some insight on how to interconnect computers to handle a distributed processing task.

Another of my favorite programs was an absolutely silly piece of PL/I code to play the game "dots." (I'm sure you know how to play dots-two players take turns connecting dots in a grid. The player who can make the most boxes wins.) This program was written on punch cards for an IBM 370 computer. As I had no interactive terminal at my disposal, I had to look at the output to see what move the program made and then punch my move on a card and resubmit the program deck to the computer operator. A complete game took about 4 hours to play. It played a pretty good game, and as far as I know, nobody else has ever analyzed this game before. Maybe I'll start something. (First Pacman, then Q-bert, and now, dots!)

My latest major project on a computer

was an implementation of the programming language SNOBOL for microcomputers. After I informed John of this, he asked this thought-provoking question: "Why can't you develop a special hammadio computer language?" He gave me some thoughts on what such a language might contain—Morse, Baudot, or ASCII I/O statements, as well as interrupt handling, I/O buffering, math functions for metric conversion, and "great circle" functions.

I didn't feel that ham-radio applications warranted their own language. After all, the things that John suggested could be handled with a subprogram library. Nevertheless, the suggestion started a lively discussion among our club members. So let's hear what you think about the matter. If anyone has suggestions on what a ham-radio computer language might include and what the structure might be, drop me a line. It would be interesting to see if there is a need for such a thing.

The issue of computer languages is, in itself, a hot topic. I am frequently asked what the best language is or what the easiest language is. Unfortunately, there are no answers to these questions, but because this subject generates such interest, I will devote some space to matters regarding languages and compatiblity among computers.

Everything-

—you've always wanted to know about assembly language and... A number of people have written me asking about assembly language. The question I have been hearing most is how one should go about getting started with it. "It just seems so darn complicated" is the common cry of distress. As I tend to use many assembly-language programming examples, some people have commented that they felt lost while reading through a listing.

My reason for using assembly language is simply that there is no other way of doing certain things with a computer. When one uses a so-called "high-level" language such as Basic or FORTRAN, one finds oneself shielded from the machine. You are, so to speak, a few levels removed from the hardware of the machine. Unfortunately, this lack of intimacy between user and machine prevents the user from establishing complete control. One must be happy with how the interpreter or compiler chooses to do certain things. (Please pardon my anthropomorphism; it simply makes the sentences less cumbersome.) Like most others, I like to take the easy solution to a problem. In many instances, assembly language is that easy solution.

My own first experience with assembly language came from a course I took at Hofstra University: CS 110. The course assumed some prior PL/I programming knowledge and made the student realize that computers worked on a much simpler level than PL/I. Of course, everyone realized that the mechanism for the computer's understanding of PL/I was a program called a "compiler," but not too much thought was given to that fact. The compiler was simply regarded as a "black box." Nobody cared how it performed its black magic; the only thing people concerned themselves with was what went in and what came out.

The point of this diversion is that assembly language is simpler than any other programming language. That's rightsimpler! The instructions are very primitive: Move a byte of data, add two binary numbers, compare a number to zero. In fact, while microcomputers usually have at least fifty different instructions, only a few are needed. The late computer scientist, Alan Turing, proved that only a few very primitive operations on binary data would suffice to compute any problem that a better equipped (i.e., a larger instruction set) machine could handle. In particular, all a computer needed were the basic logical operators and a branch statement.

With all this historical information aside, it is time for us to consider the matter of a painless approach to learning assembly language. First, get it out of your mind that this is a complicated matter. It is, in fact, a simple one—so simple that people tend to make it much more difficult. Let's start at the beginning.

In the beginning, there was machine language. Programmers would program by punching holes or flipping switches corresponding directly to memory locations in the computer. This was a tedious affair, but engineering and math types were content with this method for a number of years.

The instructions that a computer program consists of are represented as numbers in the computer's memory, and the same memory is used for both data and instructions. That means that the contents of a byte containing the binary number 10101010 could be anything from a computer instruction to a data item. One cannot tell the exact meaning of an isolated byte of memory—it must be looked at in context.

Needless to say, this business of binary numbers soon got confusing. It was extremely difficult to debug a program consisting solely of spots on a storage tube, or perhaps binary numbers represented in base 16 or base 32. Because of this, assembly language was developed.

Assembly language and machine language are very closely related. There is a one-to-one correspondence between statements written in the two languages. It is best to think of assembly language as a tool for writing machine-language programs. Much of the tedious memorizing and mathematical calculating that a programmer must take care of when programming in machine language are dutifully performed by the assembler.

The primary function of the assembler is to provide a set of mnemonic codes for the binary instructions of the computer. It is much easier to remember that BNE means "branch if not equal to zero" than that 01001100 means jump to the memory location specified by the next two bytes.

Assembly language also allows the user to work with decimal or hexadecimal numbers; conversion from one radix to another is another function handled by most assemblers. Finally, an assembler allows a person to create a program to run in various parts of memory. A machine-language program generally cannot be relocated to another portion of memory. An

assembly-language program can be placed into another portion of memory by reassembly of the program.

Each microprocessor has its own machine language and, therefore, its own assembly language. For example, the Atari computer and the Apple computer both use a microprocessor chip in the 6502 family. Because of this, they both have the capability of "understanding" the same assembly language. The obvious conclusion a person could make is that those two machines would be software compatible, at least at the machine-language level. Unfortunately, this conclusion is erroneous.

There is another factor to consider when dealing with software compatibility: differences in hardware. Let's continue with the Apple vs. Atari comparison and look at some of the hardware differences. Consider the simple matter of the clock speeds of the computers. The Atari's internal clock, which controls the speed of the microprocessor, runs at about 1.8 MHz as compared with the 1.024 of the Apple.

Does this mean that the same machinelanguage program will run 56% faster on an Atari? No! The Atari will be about the same speed, if not slower, because of Atari's special display processor chip. This chip takes control of the computer's bus every so often in order to fetch display data from memory. In order to do this "direct memory access" (DMA) of data, the 6502 microprocessor must be "halted" during the DMA cycle.

Another thing that slows down the computer's performance is Atari's use of interrupts. Every 60th of a second, and sometimes more often, the microprocessor is interrupted from the program that it is executing and runs a system-maintenance routine. All this interrupt and DMA business simply means that the amount of time the Atari computer takes to execute a program cannot be calculated by simply knowing the clock speed, nor can the speed of the computer be compared to another computer's just by looking at the clock frequency.

The reason that we have to consider

hardware when dealing with assembly language is that one cannot separate the two. It is necessary to have some hardware knowledge in order to program effectively in assembly language. This is especially true when doing I/O-related tasks. After all, how can you get data into or out of a computer without knowing the hardware configuration?

Just keep in mind that assembly language is simpler than any other language. Think small. Each statement can do only very little. If you approach the matter with this attitude, you will find learning assembly language to be equally simple.

High-Level Languages

High-level languages remove the user from the computer's hardware. Many things that an assembly language must worry about are "shielded" by the language processor. It is this shielding that makes some things impossible to do in a high-level language; sometimes complete control is needed. However, most of the time a high-level language (such as Basic) is the better choice. The easiest solution is often the high-level language.

A wide variety of high-level languages is now available for microcomputers. In addition to Basic, implementations of C, PL/I, Algol, Pascal, FORTRAN, LISP, Ada, COBOL, PL/M, Forth, and Logo are commonly available. I will devote some time to these and comment on their suitability for amateur radio applications in future months.

Graphics

I still need more feedback on the development of a graphics standard for amateur radio. As I mentioned in past columns, I would like to establish some standards to allow users of different computers to exchange graphics data. Possible techniques could include "unit square" graphics (where coordinates are given relative to a 1 by 1 screen thereby making the center point 0.5,0.5) or standard graphics character sets. Any comments along these lines would be appreciated. Don't forget: Include an SASE to ensure a reply!

FUN!

John Edwards KI2U PO Box 73 Middle Village NY 11379

BASIC ELECTRONICS

I've just finished looking through the FCC's new list of suggested questions for Novice-class exams. Most of the material looks pretty good. Still, it comes off looking kind of dull-row upon row of gray boilerplate. I can't help but think that the FCC could have done better by coming to me. Boy, would I have put together a test for them-you know, crossword puzzles, matching, acrostics, and so on. Don't laugh. Is it any sillier to make prospective hams memorize a binary code system? ASCII code yes, Morse code no. At least my puzzles would have a relevance to current technology, which is more than you can say for those silly dits and dahs.

Taking things a step further, imagine the new look in study guides. Page after page of puzzle solutions. Can't you just see Dick Bash at the Dayton Hamvention hawking his Final Exam Crossword Dictionary?

Hey, FCC! I can still help you with the General, Advance, and Extra-class tests lists. Drop me a line.

ELEMENT 1 MULTIPLE CHOICE

- An electrical generator's magnets are:
 - 1) small
- 2) non-polarized
- oppositely-polarized
- 4) similarly-polarized
- What is the current value in the circuit of an 8-Watt lamp running at 200 volts?
- 1) 0.04 Amps
- 2) 40 Amps
- 3) 400 Amps
- 4) .4 Amps 3) The henry is the unit of:
- 1) work
- 2) voltage
- 3) capacitance
- 4) inductance 4) Impedance is:
- the total opposition offered by a

- circuit to the flow of alternating current
- the total opposition offered by a circuit to the flow of direct current
- 3) the complete resistance offered by a circuit to ac or dc
- 4) determined by dividing voltage by resistance
- The two most common semiconductor materials are:
 - 1) germanium and curium
 - silicon and argon
 - 3) Iron and lead
 - 4) germanium and silicon
- 6) Transistors can:
 - 1) amplify voltage
- 2) amplify current and voltage
- 3) amplify current
- 4) none of the above
- 7) The banded end of a diode indicates the:
 - 1) anode
 - 2) cathode
 - 3) emitter filament
- 8) A multivibrator is a type of:
 - Hartley oscillator
- 2) Armstrong oscillator
- 3) Colpitts oscillator
- resistance-capacitance oscillator
- A disconnected capacitor:
 - is harmless
 - does not contain energy
 - can be used as a transistor
- 4) can kill you
- 10) D'Arsonval:
 - was the inventor of the transistor
 - is a type of analog meter
 - is a type of digital meter
 - 4) refers to D'Arsonval's Law

ELEMENT 2 MATCHING

Match the term to its definition. Column B

Column A

- 1) Acorn
- 2) Klystron
- Nuvistor
- 4) Dyne
- C) Squat UHF tube

- D) Miniature metal/ceramic
 - tube

A) Diode rectifier

B) Unit of work

- E) Microwave tube-has a 5) Newton bunch cavity
- 6) Magnetron 7) Phototube
- 8) Mercuryvapor tube
- 9) Thyratron
- H) Miniature tube with pins extending from its ends and sides
- I) Gas triode or tetrode 10) Doorknob J) Converts light energy to
 - electrical energy K) Unit of force

F) Air-filled VLF tube

G) Microwave diode

ELEMENT 3 TRUE-FALSE

True False The daraf is the unit. of elastance. Doubling a number and adding one is called "dibbling." 3) One handy oscilloscope use is the measurement of capacitors. 4) The coulomb is the unit of quality.

sites repel while likes attract. 6) A "zig-zag" is a type

5) In magnetism, oppo-

- of rectifier circuit. 7) A "zener" can be used as a voltage
- regulator. 8) There are two individual rectifiers in a bridge rectifier.
- 9) Batteries generate voltage through photosynthesis.
- 10) A logic probe is used to test 5-volt dc circuits.

ELEMENT 4 FILL IN THE BLANK

_is a precisely dimensioned, hollow metal pipe through which microwave energy is sent.

2) The instrument that presents visual representations of an electrical quantity is

3) The soft form of carbon used in most resistors is called 4) The main control electrode in a vacuum

tube is the 5) In a bipolar transistor, emitted current

travels toward the

THE ANSWERS

Element 1:

1-3, 2-1, 3-4, 4-1, 5-4, 6-2, 7-2, 8-4, 9-4, 10-2.

Element 2:

1-H, 1-E, 2-D, 4-B, 5-K, 6-B, 7-J, 8-A, 9-I, 10-C.

Element 3:

- 1-True It measures the opposition of the capacitor to be charged. Incidentally, "daraf" is farad spelled backwards.
- 2-True Not to be confused with "dribbling," which is a
- basketball term. 3-False By studying its waveform, I guess.
- 4-False Quantity.
- It's the other way around. 5—False
- 6-True A variation on the threephase, half-wave star theme.
- 7—True Zener diode.
- 8-False Four.
- 9-False Plants use photosynthesis, batteries generate voltage
- with chemicals.

10-True Computer circuits.

- Element 4:
- 1-waveguide
- 2-oscilloscope 3-graphite
- 4-grid
- 5-collector

SCORING

Element 1:

Two and one-half points for each correct answer.

Element 2: Two and one-half points for each correct

match. Element 3:

Two and one-half points for each correct

answer.

Element 4: Five points for each word correctly filled

Are you up on your basics?

1-20 points—Your Bash is showing.

21-40 points-Good thing the FCC doesn't re-test.

41-60 points—Qualified for your

license class.

61-80 points-Time to upgrade? 81-100 points-Obviously, you hold an MSEE degree.

REVIEW

THE YAESU FT-980 TRANSCEIVER


As transceivers became completely solid state, size and weight were reduced dramatically, so I was particularly surprised at the FT-980, the latest descendant of the Yaesu FT-line. This nowfamous line began with the FT-400 and became perhaps most popular with the FT-100 series. But the FT-980 HF Transceiver CAT System (for, I suppose, computer-aided transceiver) is lightweight and it's packed full of features aimed at providing the serious radio amateur with the best communications tool available. For this review, along with the FT-980 I had the optional SP-980 speaker system and the MD-981 stand microphone. More about these accessories later. General specifications for the transceiver are shown in Table 1.

Packed in with the set was a pretty good installation and operation manual that explains the rig's capabilities. The manual included a couple of loose sheets that detail connections for an alternate means of keying a linear amp if it requires more than 200 mA of switching and updated filter installation instructions. Because this FT-980 had all the optional AM and CW filters already installed and I was trying to key a linear with current requirements less than 200 mA, these provided no extra trouble-and I doubt they would anyway.

The manual is reasonably well written and doesn't contain many misspellings and odd sentence structures typical with some imported equipment. Separate from the manual are 22 pages of schematics and 7 pages of block diagrams! If you have the "right stuff" to tear into the FT-980, at least you'll have a fighting chance with this documentation. Also in the manual is a thorough description of accessory interconnection along with pinouts for each plug and connector. An added bonus in the package is a nice fourcolor map of Japan for award use; it's in Japanese, though.

So much for the documentation—let's get this unit on the bench and start operating. "Oof," says I. "This thing weighs a ton." Actually, it weighs close to 40 pounds with all the options installed. In the shipping box I found a bag of all kinds of plugs and connectors, tilt feet, fuses, three-wire line cord, and two AA-cells for the power-off memory retention. The AAcells were the first of several oddities. Memory backup is provided solely through these cells-no nicads, lithium cell, or anything else. Yaesu says to replace them every six months or "adios" to the FT-980's memory.

As with several other available "competition-grade" transceivers, the FT-980 covers all the amateur bands, including WARC, and acts as a separate 150-kHz-to-29.9999-MHz general-coverage

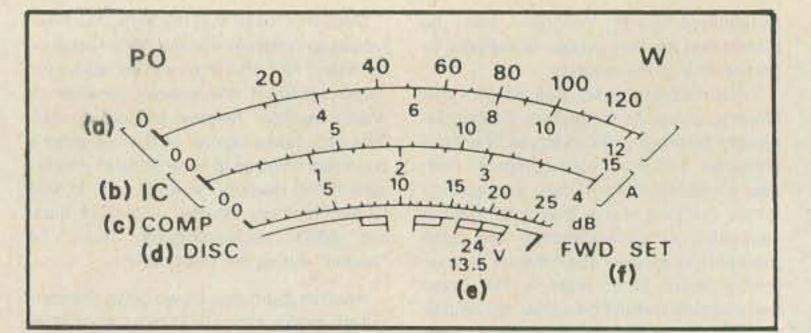

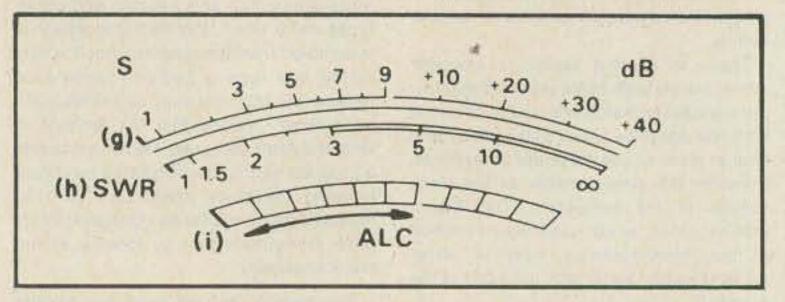


Fig. 1. Details of the FT-980's two multifunction meters: a) power output in Watts (output of 10-Watt low-power version of FT-980 is read on bottom of this scale); b) output-transistor transmit current (all modes); c) SSB speech processor compression; d) center-scale tuning for FM reception; e) Vcc safe zone; f) swr forward set mark; g) S-meter; h) swr scale; i) safe alc zone for SSB.

receiver. With the memory backup energized, upon power-up the FT-980 greets you exactly as you last left it. Should you elect not to use the memory back-up or should the AA-cells fail, the 980 defaults to 7.000 MHz, general coverage.

Rocking the power switch on illuminates the two large analog meters and the blue digital frequency/mode displays. The meters provide quite a monitoring capability as shown in Fig. 1. The upper digital display includes frequency readout to 10 Hz as well as USB, LSB, CWN (narrow), CWW (wide), AMN, AMW, FSW, and FM, to match the position of the Mode switch.

Receive Features

To operate, first select Ham or Gen (eral) coverage by depressing the appropriate push-button. Band selection is made through three momentary-contact push-buttons: Up, Down, and Repeat. These as well as most other functions are selected via momentary-contact pushbuttons that function either as toggles (push-on/push-off) or as simple entry switches. A soft beep verifies that switch contact has been made and the beep can be turned off.

Operating frequency can be selected five ways: 1) main tuning knob, 2) 10-kHz/step push-button, 3) Up/Down 5-kHz push-buttons, 4) a keypad, and 5) up to 12 memory frequencies selected by a rotary switch. Yaesu's optional stand and hand-held microphones afford frequency selection via push-buttons, although without as many options.

Upon power-up, I was impressed with

TRANSMITTER

Frequency	Range
Band	Frequency (MHz)
160	1.5-1.99999
80	3.5-3.99999
40	7.0-1.49999
30	10.0-10.49999
20	14.0-14.49999
17	18.0-18.49999
15	21.0-21,49999
12	24.5-24.99999
10	28.0-29.99999
160 80 40 30 20 17 15 12	1.5-1.9999 3.5-3.9999 7.0-1.4999 10.0-10.4999 14.0-14.4999 18.0-18.4999 21.0-21.4999 24.5-24.9999

Emission Types

LSB,USB (A3J/J3E) CW (A1/A1A) AM (A3/A3E) AFSK (F1/J1B) FM (F3/F3E)

Power Output (Watts, all bands) SSB, CW 100 (PEP) AM 25 FM, FSK 50

Maximum FM Deviation +5 kHz

AFSK Shift 170, 425, 850 Hz

Output Impedance 50 Ohms, unbalanced

Frequency Accuracy Better than +3 ppm

RECEIVER

Frequency Range 150 kHz to 29.99999 MHz, continuous

Triple-conversion superheterodyne

Circuit Type

Image and I-f Rejection Better than 70 dB

Dynamic Range Better than 95 dB with 300-Hz CW filter

Audio Peak Filter Range 350-1400 Hz

I-f Notch Filter Range (demodulated) 500-2700 Hz

Selectivity

(Adjusted for maximum i-f width)

	-6 dB	- 60 dB
Mode	(wie	dth in kHz)
SSB,CW (W/N),		
FSK	2.5	4.2
CW (narrow)	0.3	0.6
CW (wide)	0.6	1.2
AM (no filters)	6.0	17.0
AM (wide)	5.0	12.0
AM (narrow)	3.0	9.0
FM	12.0	24.0

POWER REQUIREMENTS

Voltage

Ac: 100 to 120 volts or 200 to 234 volts 50-60 Hz


Power Consumption Receive: 72 VA

Transmit: (100 Watts out): 530 VA

Physical Characteristics Overall Dimensions: 15 inches wide 6-1/2 inches high

18-1/2 inches deep Weight:

Approximately 38 pounds

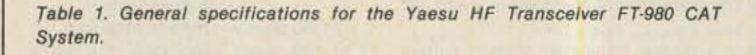

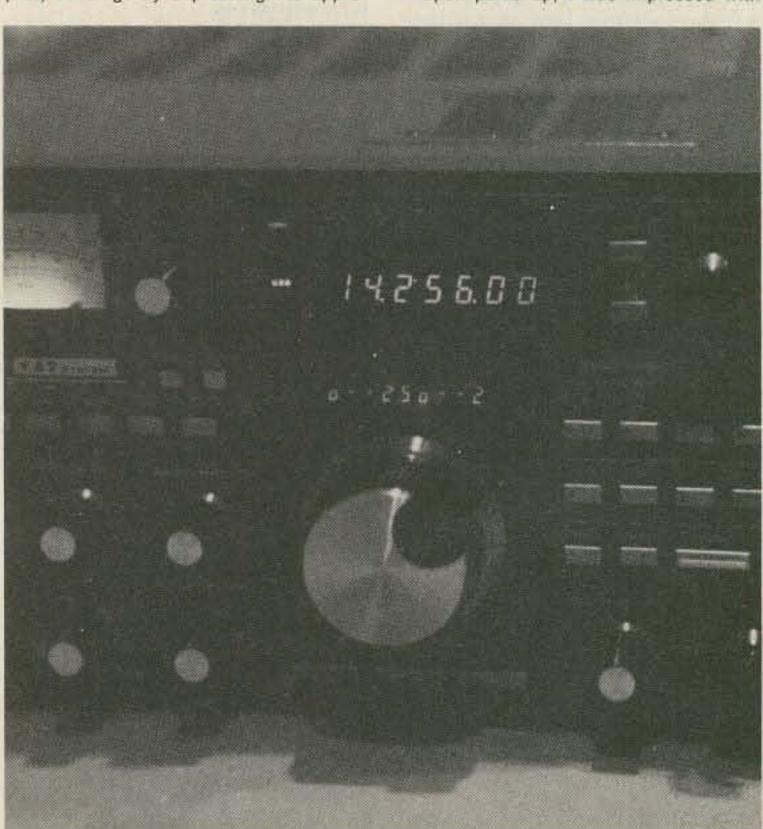


Fig. 2. Comparison of the digital (top) and analog (bottom) "sub-display" arrangements. The digital display is straightforward; the analog one is inscrutable.



The Yaesu FT-980 with companion mike and speaker.

the audio quality of the receiver. It has an excellent built-in speaker. When the accessory speaker or headphones are plugged in, the internal speaker is disconnected.

On receive, you have AF gain, RF gain, Noise Blanker, Tone, Squelch (FM only), i-f Width and Shift, wide and narrow filters (if installed), a calibrated 0-30-dB rf attenuator (in 10-dB steps), a Mode switch, and Notch and APF (audio peak filter-CW only) controls to play with. You can do some pretty fine knob-twiddling and slice away at the pileups and heterodynes. The narrow filters are very sharp and a dial-lock push-button holds the frequency in case you accidentally bump the main tuning knob while tweaking all the other controis.

The frequency displays require some special mention. Beneath the upper digital frequency and mode display is another window, a sub-display that Yaesu calls a "...synthesized analog display [that] provides a relative frequency indication which scrolls when the frequency of the selected vfo is changed." What it amounts to is a digital simulation of an analog dial display of frequency. See Fig. 2. It's confusing; I couldn't find a single reason for its being there. Because a digital frequency display accurate to 10 Hz is right above it and this pseudo-analog display is accurate only to 1 kHz, I'm curious as to Yaesu's intentions. And while speaking of displays, a Dim push-button reduces meter and display brightness by about half for low-light or nighttime operating.

transmit and receive clarifiers that actual-

tle strange if you are used to a separate clarifier knob. Also included are push-buttons for selecting which vfo (ham or general coverage) will be used for transmit (ham only) or receive (either) or which memory channels will do the frequency controlling. Split-frequency operation is possible, along with push-buttons to give you the difference between vfo and memory channel frequencies. It's relatively easy to store and retrieve a memory frequency, but it's too complex to describe here all the possible interactions, shifting, and operating options available. This transceiver does not have a built-in scan capability, but you can store, retrieve, and exchange memory and vfo frequencies handily. In place of a bfo control, there's a rear-panel CW pitch slide switch that selects 500, 600, or 700 Hz as the CW receive tone.

One thing that I really did miss was a WWV calibration control. Yaesu must figure that the synthesizer is right on because there is no way that I could find to adjust zero-beat with WWV. The specs say frequency accuracy is better than 3 ppm for 0-40 degrees C (32-104 degrees F). That means WWV should only be about 30 Hz off at 10 MHz!

Transmit Features

Satisfied that I wouldn't do any damage, I next tried loading the FT-980-no problem. Power output is adjustable with a Drive control. I was, however, a little suspicious of the built-in swr metering circuitry when it indicated an absolutely flat 1-MHz bandwidth on the 10-meter eletoring circuitry will protect the finals, though, reducing power out to about 75



Rear panel of the FT-980 has almost as many switches as the front panel. The projecting module holds the power amplifier (left) and the power supply (right).



Operating side of the FT-980. The curious pseudo-analog display is right above the main tuning control (more on this in the text and Fig. 2).

percent of available output power at ideal (1:1) conditions when a 3:1 swr is encountered. An on-demand fan cooling system is employed to control output transistor temperature.

This rig also had the Curtis 8044-chipbased keyer option installed and the whole system is set up for full break-in operation. I was a little disappointed at the speed control of the keyer, though. It seemed to have a very narrow realistic speed range but would go phenomenally high.

The FT-980 has a nice control and metering setup for speech compression. You can read dB of compression and use the Monitor control and a pair of headphones to adjust the processor for maximum punch and minimum distortion while listening to yourself. And an Automatic Mike Gain control enables you to set a modulation threshold to help eliminate background noise. Although a little tricky to adjust, these controls can give you tremendous audio capabilities.

Recalling memory frequencies and returning to your original frequency, using the transmit and receive clarifiers, and figuring out just what split frequencies you are on is a little confusing at first. The yellow LEDs next to some of the switches help, but because the radio can do so much, it's a little overwhelming. You eventually feel comfortable after getting to experiment for a while. Three Tab push-buttons can be employed on transmit and receive to limit the frequency excursion between a high and low limit you select. As the manual states, possible uses for this feature include limiting operation to legal bands or subbands of an operator's license class.

An FSK Shift slide switch on the rear panel selects shifts of 170, 425, or 850 Hz while the mark tone stays at 2125 Hz. Power output is limited to 50 Watts for FSK as well as FM, 25 Watts on AM.


SP-980 Remote Speaker

This outboard speaker not only complements the FT-980, it also adds some more knobs to twiddle during receive.

Built-in passive L-C circuits are switched in and out of the circuit via front-panel selector switches. Response curves on the front panel show the bandpasses produced as the Low and High filter switches are clicked through their ranges. An Input switch enables you to select from two separate audio inputs, and there's also a Phones jack. Combined with the Tone switch on the transceiver, the filters provide an extra dimension in receive capability. All in all, a nice addition to the station.

MD-1 Microphone

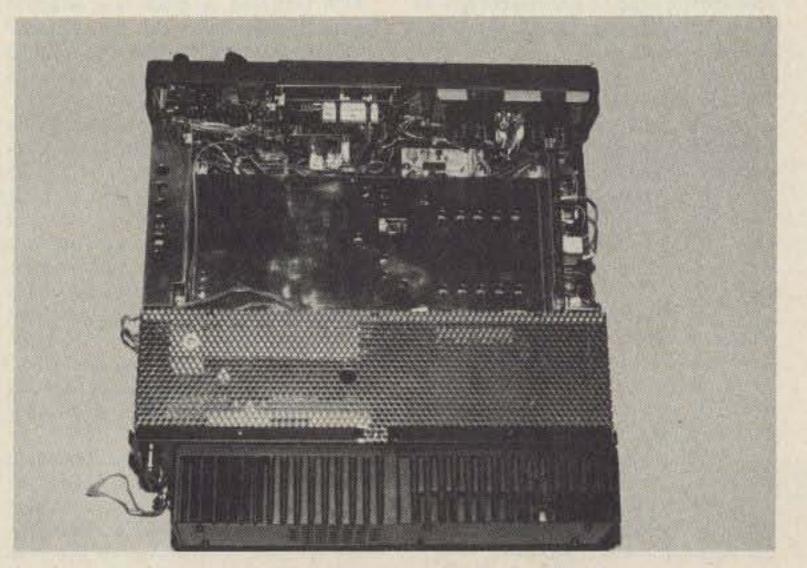Yaesu's penchant for buttons and switches carries over into their "stand" microphone. In addition to a standby/ transmit switch located on the mike itself, the rig's Up/Down/Fast frequency-select



Top view of the FT-980. The optional keyer module is the small rectangular PC board located at about the one-o'clock position. The vco, PLL, and vfo subassemblies are under the metal covers. Power supply and control circuitry are under the screened-in section at the rear.

buttons are duplicated on the mike stand, just in case you're comfortably settled into your easy chair and can't quite reach the tuning buttons on the rig. There's also push-to-talk and lock switches, a high (50k-Ohm)/low (600-Ohm) mike impedance switch, and a three-position tone switch. The mike can be easily removed from its cradle stand but the short cord limits your mobility. An optional MH-1 hand-held mike also is available that includes Up/Down/Fast push-buttons and a twoposition tone switch.

Conclusion

I really liked the FT-980. While it's designed with the serious amateur in mind, it also can help simplify the operating position because it can include a keyer, swr monitor, FM circuitry for transverter drive, full break-in QSK switching circuitry, a separate receive-only antenna switch, and a full array of interface connectors. It also has rear-panel jacks that access its internal microprocessor and a serial interface that allows external control via an outboard microcomputer. Unfortunately, details other than plug pinouts and some cryptic signal names are not provided. So you'll just have to experiment (carefully).

The current crop of amateur transcelvers offers tremendous flexibility, along with capabilities unheard of a few years ago. The penalty for this is increasing cost and initial bewilderment when confronted with the maze of controls and switches. But get your hands on an FT-980 and spend some time getting used to it. I think you'll find this is one nice piece of equipment.

For more information, contact Yaesu Electronics Corp., 6851 Walthall Way, Paramount CA 90723, (213)-633-4007. Reader Service number 476.

> Gene Smarte WB6TOV Hancock NH

DX HIDDEN ASSET LOOP ANTENNA


H. Stewart Designs has just introduced a new antenna design called the DX Hidden Asset Loop Antenna. What you get for \$12.50 are the plans to build the antenna and a complete description of the antenna itself, including history, performance, configuration, construction, and installation. It is called the DX Hidden Asset Loop because it is capable of working DX, it can be installed indoors and is thus "hidden," it is undeniably a loop, and it is an asset to your station. Read on and find out how we proved to our satisfaction that this antenna is well-named.

73 received a prototype antenna that had been made up by H. Stewart Designs to illustrate the construction materials and method of assembly. They even included a wooden mounting support!


Jim Gray W1XU asked me if I would be interested in reviewing the DX Hidden Asset Loop Antenna for 73. I readily agreed. Not knowing what to expect, I went to work.

After opening the package, I discovered that I had a support board with vertical antenna sections aiready attached, two antenna loops, each consisting of three pieces of small-diameter aluminum tubing, connectors, clamps, four corner pieces with clamps, and one set of plans and instructions.

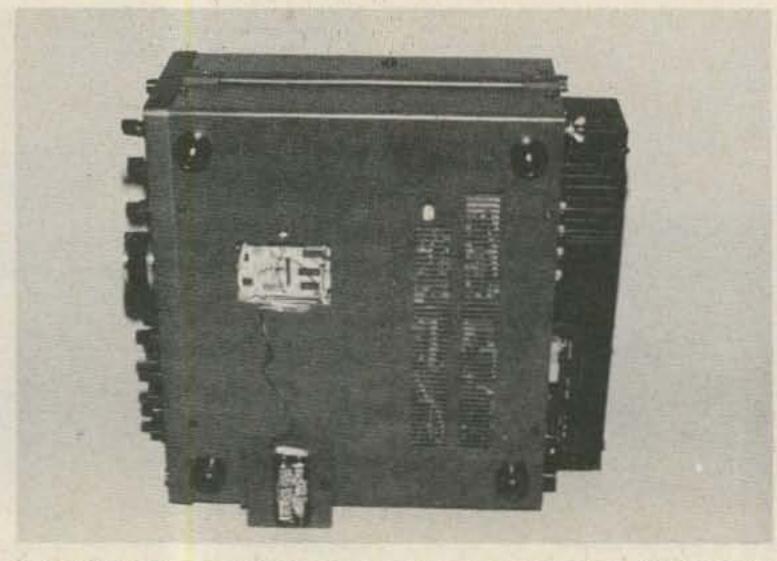With the vertical elements already attached to the support board (which had all the necessary holes pre-drilled), it was easy to insert the four corner pieces (tubing elbows) through the holes provided and slide them over the ends of the vertical elements. The required distance be-



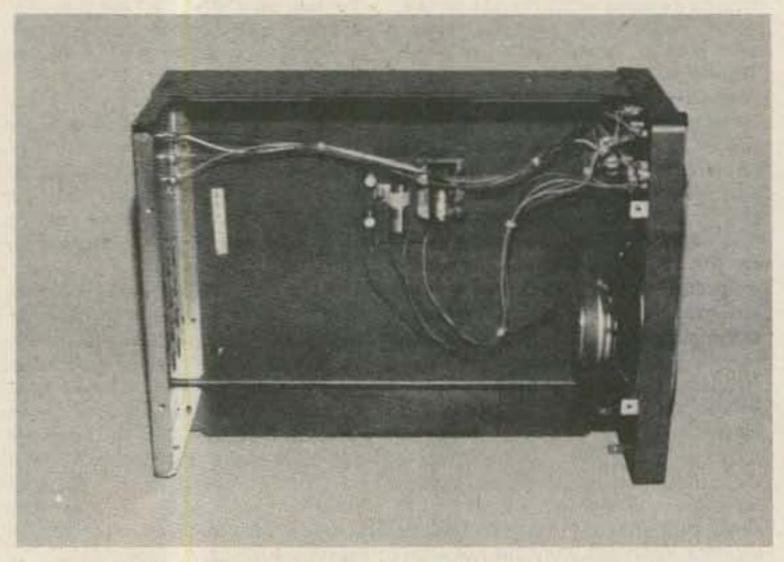Bottom view. The small door to which the memory backup-supply AA-cells mount dangles free. The circuitry on this side is the i-f (left) and the rf (right). Most of the rig is fairly accessible.



Inside the SP-980 speaker. If you've ideas for station accessories, you have plenty of room here.

tween the two loops (39.5") was already pre-marked on the support board, so the next step was to clamp these pieces in place with the hose clamps.

Next, I assembled the loops themselves by butting the three pieces of tubing in the connectors and clamping them with the hose clamps. Then, I inserted the ends of each loop into the four elbow pieces to a depth indicated by black tape wrapped about 9" from each end and clamped them in place for a first trial. This resulted in an assembly that looked like two large basketball hoops, one above the other, attached to the board and connected to each other by a pair of vertical elements spaced a few inches apart, forming a loop at each end of the board. The instructions said that the antenna should resonate at 28.5 MHz if the dimensions were followed exactly during assembly. However, depending upon the environment in which the antenna is erected, it is possible that the resonant frequency will be slightly different due to house wiring, plumbing, proximity to power lines, etc. (In my case, with the antenna in the attic, no changes had to be made.)

I attached the vertical support board to a horizontal two-by-four that I nailed to the attic rafters. Now it was time to connect the coax to the parallel vertical elements. One of these is separated by about an inch in the middle, forming a gap across which the coax is fastened. The shield braid of the coax goes to one side (lower) of the element, and the center conductor goes to the other (upper) side. Soldering is easily and quickly accomplished. The coax was then led away from the antenna at right angles for about ten feet (instructions say for at least a half-wave-16 feet-for best results) and then downward through a plastic conduit to my shack in the basement.

After that, I was ready to get on the air, but I felt that a test of swr should be made first, so W1XU brought over his bridge. Applying power at 28.1 MHz (the lower end of the 10-meter Novice band), the swr came out at less than 1.5:1, so I decided not to change anything. Now for the on-the-air test!

Within an hour's time, I worked two Texas stations on 10 meters. The band had just opened, yet one station gave me a 579, and the other (a few minutes later) gave me a 599! This was with about 70 Watts output from my FT-707.

Just for fun, we switched to 40 meters to see if we could receive anything there. Signals were jumping! So, what the heck, it couldn't hurt to see if the antenna loaded on 40, could it? Believe it or not, it did, even though the swr was high. The FT-707 has a shut-down circuit in the final to protect it from overload, but I found that the output was still about 50 Watts...so I went ahead and called CQ. I worked one ham in Maine and another in New York, with a 559 and a 589, respectively! I was hooked on the DX Hidden Asset Loop Antenna. Even on 80 meters, the reception I

get is remarkable, but I haven't had the nerve to try transmitting on 80.

I feel that the antenna is highly suited for emergency and Field Day communications and is ideal for the ham who lives in an apartment or condominium or otherwise must put up with limited space. The DX Hidden Asset Loop Antenna occupies a space only about six feet square and four feet high, so I can highly recommend it for any ham who has a space problem. Not only that, it works out like gangbusters on ten, so you will really have a DX antenna-I'm sure.

General Description

In essence, the DX Hidden Asset Loop Antenna is a single quad loop turned in upon itself. It retains the quad's characteristics of quiet reception, low cost, and ease of assembly. However, its configuration is such that it can be installed in a roughly cubical space that is approximately equal to one-sixth wavelength on a side at the operating frequency. The only other requirement is that the selected installation site permit the coax to be brought away from the antenna at right angles for at least one-half of an electrical wavelength.

One of the features of the DX Hidden Asset Loop Antenna is direct feed with 50-Ohm coaxial cable without an antenna coupler or matcher required. (We think that its performance would certainly not be hurt in the least by the unbalanced feed recommended, but, if desired, a balun could be installed at the feedpoint to ensure balanced feed of this balanced antenna.) The antenna is very broad-banded; you can expect a useful bandwidth of about 3 to 5 percent of the resonant frequency, meaning that on ten meters, it will cover between 500 kHz and 1 MHz from the resonant frequency. By sliding the adjustable-length pieces in and out, you can set the resonant frequency anywhere you want it in the band. Typically, the swr at resonance will be 1.5:1 or less, and it is probable that you will be able to get it below 1.2:1 with careful tuning. However, if the antenna is mounted close to conductors like house wiring or copper plumbing, you may have trouble getting the swr as low as otherwise possible. One good feature is that H. Stewart Designs covers these contingencies in the plans and instructions and tells you how to make the necessary adjustments to compensate.

The only comment that might be considered a negative aspect is that the DX Hidden Asset Loop Antenna is not yet available in kit form! You will have to make up your own kit from the instructions and plans...which won't be at all difficult to do. We hope that H. Stewart Designs will consider offering this unique and practical antenna in kit form later on, because we think they have a winner. I'm sure you will think so, too, after you build yours. Plans and instructions are \$12.50 from H. Stewart Designs, PO Box 643, Oregon City OR 97045, Reader Service number 478.

> Ross Kenyon KA1GAV 73 Staff

BENCHER KEYER PADDLE


One of the great delights of CW is the beautiful "music" that can be generated by a good operator using good equipment. Today's CW operator has the advantage of a variety of keys and keyers to choose from, most of which have full lambic capabillty. As you know, iambic-mode keying allows certain characters to be formed more easily and quickly. For example, letters like F, L, Q, Y, and so forth require fewer paddle movements when keyed in the lambic mode.

Many operators have discovered the Bencher full-iambic keyer paddle, suitable for use with all of the electronic keyers and well known for its functional beauty. In fact, I have been using a Bencher paddle since 1979 and find that I like it better and better each year. It seems to be settling in...or perhaps I am the one that's settling in! Unfortunately, I never learned lambic keying, and I use the key in the ordinary bug fashion. Just the other day I was talking with Bob Locher W9KNI, who -with Jerry Benedict- is a partner in Bencher, Inc. (Benedict plus Locher = Bencher.) I lamented the fact that I had never learned iambic keying and therefore wasn't making full use of my paddle. Bob laughed and said, "You're not alone, but we have just developed something for hams like you and for hams who are used to a bug-a non-iambic paddle for use with either full-lambic or non-lambic keyers."

We chatted a while longer about keys, keyers, and paddles, and, after a bit of adroit arm-twisting on my part, Bob finally knuckled under and promised to send me one of the new paddles, realizing perhaps that I was one of the last old-fashioned holdouts who could never learn iambic CW. Maybe he just took pity on me.

Whatever the reason, I soon received a large box full of plastic worms. Buried within the plastic protection was a smaller box enclosing the key. Inside that box I found a cardboard partition or separator that holds the very heavy paddle base in place and prevents the relatively delicate paddle mechanism from being dislodged and damaged during shipment. The entire package is neat, strong, and extremely well designed...a hint about the contents, too!

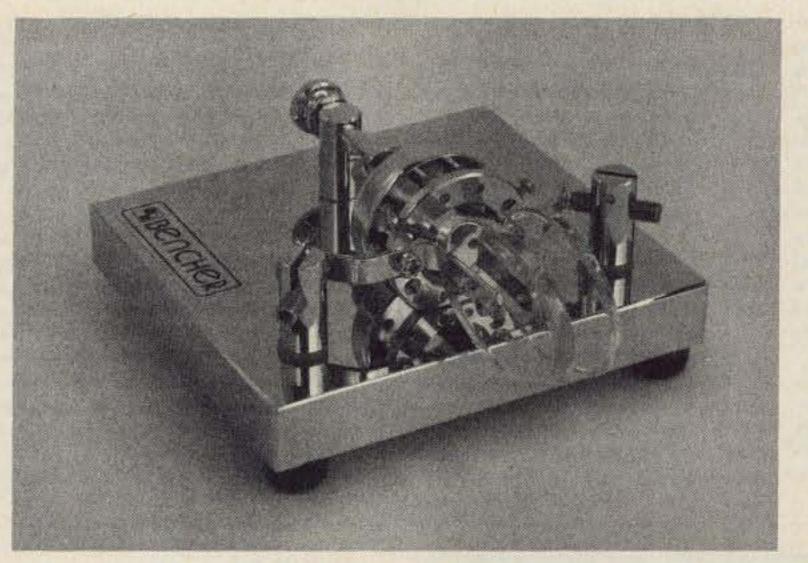The key itself looked much like the original—only better, if that is possible. It has



Model ST-2 Bencher paddle.

a heavy chrome-plated base with rubber feet that keep the key solidly in place on your bench or desk and inhibit its walking around when energetically operated. The paddles and their unique gimballed actuating mechanism are supported on sturdy pillars screwed into the base. The finger pads are clear plastic ovals (as opposed to triangles on the original Bencher paddles) with chamfered, or bevelled, edges that invite your fingers to slip over

them while keying...providing a very nice feel.

The tension spring is very easy to adjust on this model because the spring loop is captured by an adjustable screw with a knurled knob at the center post. The contact space adjustment between paddles and slide posts is made as before, with Allen screws and lock screws set into the posts. Bencher has thoughtfully supplied the Allen wrench for you, attached to the

underneath side of the base, where it can't get lost. Perfect spacing adjustment and tension, suited to your own specifications, can be obtained quickly and easily the first time you try.

The two sides of the key, that is, the paddle electrical contacts, are brought through the base by insulated bushings to solder lugs attached by 10-32 Phillipshead screws. The ground side of the key is a solder lug firmly screwed to the base itself. There is also a plastic retainer that firmly holds the lead wire from your paddle to your electronic keyer. The wire is not provided, of course, but the one you use now will be satisfactory. I use a vinylcovered, double conductor, shielded cable...similar in size and appearance to a microphone cable, or a piece of coax. After the electrical attachments are made to the solder lugs, the cable is clamped down so that the connections can't pull loose.

You'll find the Bencher paddle easy and pleasant to use...it seems to invite your fingers to use it easily and correctly. In my own case, I was extremely pleased to find that I stopped making keying errors through misuse of the iambic feature. My CW improved perceptibly, if not dramatically. I think you'll like your new Bencher paddle, especially if (like me) you don't know iambic keying, yet you want a key that will enable you to get the most out of your electronic keyer and make beautiful "music."

The Bencher paddle, Model ST-1 (black-finished base), is available at \$46.95 amateur net. Model ST-2 (chrome-finished base) is priced at \$59.95, and Model ST-3 (gold-plated base, available on special order) costs \$150.00. Write to Bencher, Inc., 333 West Lake Street, Chicago IL 60606. Reader Service number 477.

Jim Gray W1XU 73 Staff

WHAT DO YOU THINK?

Have you recently purchased a new product that has been reviewed in 73? If you have, write and tell us what you think about it. 73 will publish your comments so you can share them with other hams, as part of our continuing effort to bring you the best in new product information and reviews. Send your thoughts to Review Editor, 73: Amateur Radio's Technical Journal, Peterborough NH 03458.

RTTY LOOP

Marc I. Leavey, M.D. WA3AJR 6 Jenny Lane Pikesville MD 21208

It's February, and, not to offend the followers of your friendly neighborhood groundhog, I'd like to celebrate Valentine's Day this year. A Valentine to all of you readers, who send me the most interesting mail.

I would like to lead off with a note from Peter Martinez G3PLX of AMTOR fame. In part, Peter writes, "I am glad to see that interest is picking up over there after such a long time. It seemed for many years that AMTOR was strictly a European system.

"It is true that in the early days of AMTOR, I was offering a program that would run AMTOR on a 6800-based computer, but this was written in source code only and was incomplete in that it required all the interfacing to the computer hardware to be written. There were very few people able enough to use the program in this form.

"So this program is no longer available, and I turned my attention at that time to designing a small PCB, with on-board CPU, ROM, etc., which would enable people to get on the air much easier than tackling the difficult software task. The Mk2 version of this kit is still available from

ICS Electronics Ltd, PO Box 2, Arundel, West Sussex, England, either in kit form or as a ready-made board. It requires a single 5-volt supply, and will interface at TTL serial Baudot code to any existing RTTY system.

"I think you will see that the initial approach to AMTOR in its early days 5 years or so ago has fallen by the wayside and given way to others. There are not, as then, very many experienced machine-code programmers amongst the amateur-radio fraternity, and most users now and in the future will prefer to buy ready-made hardware or software. There will be no shortage of either before very long."

I do appreciate these comments, excerpted from a much longer letter written by this pioneer of AMTOR.

Bill Emerson WA1EVD, D.M.D., passes along his comments that he would like to see a compilation of RTTY Loop columns and also that, "I hear more AMTOR now, but 60-wpm Baudot is still the common mode. Lingua Franca?" I suspect that Murray, or Baudot, will remain such for quite a while, Bill. With the number of machines out there, I doubt if the "sixty standard" will soon roll over and die.

Nonetheless, several of you are expressing various forms of interest in computerized RTTY. Lester L. Johnson AH6AA of Sandpoint, Idaho, relates having built a demodulator from an article in an old issue of 73. He couples that with a commercial AFSK oscillator and a TRS-80(R) computer, model unspecified. Lester would like a way to interface his computer to the terminal unit and such. He notes that the I/O structure of the Model I TRS-80 is different than the Model III; but does not say which he has. I do not have any ready information to accomplish this, Lester, but I am sure that a number of our readers have. Let me hear from you out there, and I will publish the best schemes for all to benefit.

Lester also notes that he would like to run his rig, a Kenwood TS-120, on RTTY, with the power cut back to about ten Watts. I would say, off the top of my head, that this should be okay. Normally, cutting the power back to that extent should be sufficient to protect the finals from overheating. I have run my 100-Watt transmitter at about 50 or 60 Watts for prolonged periods without damage, but I like to take chances!

Another computer user is Anson R. Hyde K4EK, M.D. Dr. Anson, who lives in Alexandria, Virginia, just over the river from Washington DC, has used his IBM-PC on two-meter ASCII RTTY using a telephone modem to output tones. He would like to know if there are any programs around to run Murray on this machine. Well, that is one machine that I have seen nothing for RTTY printed on. I don't know if IBM-PC users are not the "hamming" type (I suspect that they are not) or if the average ham is looking for a more modestly priced machine (so that that is where

the manufacturers concentrate their marketing), but RTTY for the IBM-PC? Zip! I would encourage anyone who has put together such a program to write it up and send it to me here for inclusion in a future column, or make it a full-scale article and send it to our fair editor. We're waiting, we're waiting!

Greetings to Dean E. Strand KA®KKZ of Davenport, Iowa. Dean passes along a string of thoughts, a few of which I shall share with you all. Dean notes that he is using a Robot 800 keyboard, and when using it on CW in the Novice bands, he likes to set it to send characters at ten words per minute, with five-word-per-minute spacing. He feels that this makes the code more copyable and helps the newcomer improve his code speed. I agree, Dean, and this has even been the way the best code tapes are made.

Dean writes he has difficulty tuning in stations using a dedicated scope display on his terminal unit. Well, in an edition of this column several years ago, I covered how to hook up a general-purpose oscilloscope to act as a tuning device for RTTY. All you need are mark and space signals out of your demodulator. Feed them to the vertical and horizontal input of any old scope and tune the "+" pattern to maximum. Cheap scopes can be picked up at most hamfests and can be used for other things when not tuning in a RTTY signal.

Like all of us, Dean is looking to computerize his station. He notes that "there are at least two ways to go, one to get a good general-purpose computer (when I say good, I mean DEC Rainbow, IBM-PC, or HP Professional class, not VIC or Atari stuff) and use and interface...that includes AMTOR. The other way would be to get a...top-of-the-line unit...with all the whistles and bells." Now hold on, Dean. I think you might find that the top-of-the-line computers you mentioned might just be overkill for a ham shack. Don't knock the cheap stuff. I just got another small computer in here, a TRS-80C (also known as the CoCo), and am amazed at what can be done. The 6809 is a fantastic chip that can run rings around many other systems. If you want a big computer for business use or such, fine, but don't sell the little stuff short. It ain't so little anymore.

Leonard Laurel WA6FBL of Fort Bragg, California, is one of those with what might be considered a small system. He is looking to hook up his TI-99/4A on RTTY. Well, Len, as I write this column, the newspaper is filled with the news of Texas Instruments' decision to stop production of the 99/4A, so I don't know what the future holds. As with the IBM-PC, I have seen next to nothing in print about using the 99/4A on RTTY. I only hope that someone out there is doing it and sending the information in to be passed along. Good luck.

From the "left hand don't know what the right hand is doing" department comes a note from Karl Thurber W8FX from Millbrook, Alabama. Karl asks, "Have you run into anyone who has successfully interfaced a Commodore VIC-1525 printer to a Hal CT-2100 Communications Terminal? The Commodore printer (which is the standard one used commonly with the VIC-20 and C-64 computers) has a so-called 'Commodore serial

ASCII' bus, while the CT-2100 has provisions for an 'ASCII printer' and 'RS-232C' output, neither of which appears to be suitable for connection to the 1525 printer without some sort of interface. A letter to Hal brought a 'we know nothing about that printer' response, so I'm stymied at this point."

The first thing which occurs to me is to check that both devices are operating at the same baud rate. It is possible that one may be set at, say, 110 baud—like for a Teletype KSR-33—where the other may be at 300 or1200 baud, such as most serial printers are. Also, check to see if the Ready To Send (RTS) and Clear To Send (CTS) lines are used to inhibit and enable print, and, if so, that they are hooked up correctly. Without some sort of documentation, those are my first suggestions.

Perhaps others have done this hookup and will let us know. I have confidence in you all out there!

Several of you in your letters suggested. that a book compilation of the first several years of this column would be helpful. I agree with you, but it will take more than your notes to me and my intentions to make such a book a reality. Drop a line to the editor of 73, and to me as well, and let us know that there are enough of you out there interested to make a go of it. In the meantime, keep up with all the new developments yet to come. With the arrival of the CoCo here in the shack, I hope to be able to take a look at some of the 6809 software that has been floating around beyond my reach for a while. As soon as I see it, I'll tell you about it-right here, in RTTY Loop.

CONTESTS

Robert Baker WB2GFE 15 Windsor Dr. Atco NJ 08004

ARIZONA QSO PARTY Starts: 1800 GMT February 4 Ends: 0600 GMT February 5

Sponsored by the Southern Arizona DX Association. Single-operator and club entries; all bands and modes but no repeater contacts allowed. Each station may be worked only once per band per mode.

EXCHANGE:

RS(T) and state, province, DXCC country, or Arizona county. Novices and Technicians also sign /N or /T respectively.

FREQUENCIES:

Phone—3895, 7230, 14280, 21365, 28560.

CW-60 kHz up from lower band edge. Novice-25 kHz up from lower band edge.

SCORING:

Count 1 point per phone QSO, 2 points for each CW or other mode QSO, and 4 points per QSO with Novice or Technician in the Novice bands. Arizona stations multiply QSO points by number of states, provinces, and DXCC countries. Others multiply QSO points by number of Arizona counties (15 max.). The club station W7NQ also counts as 1 multiplier for non-Arizona stations. Non-Arizona stations working all Arizona counties and W7NQ may double the multiplier.

AWARDS

Certificates for the highest-scoring station in each category: Arizona, non-Arizona, and Novice/Technician. In addition, certificates for highest score in any Arizona county, state, province, or DXCC country in which there are entries.

Other certificates for Arizona and non-Arizona clubs whose members' scores combine for the highest score. Club entries must consist of at least 5 individual entries to be eligible. Club residency is determined by mailing address.

ENTRIES:

Individual entries should show each station worked, exchange plus time, frequency, and mode of each QSO. Include a summary sheet of your scoring and dupe sheets for bands with more than 50 QSOs. Entries may designate one club with which they are participating. Deadline for individual entries to be received is March 4.

Club entries should be submitted by a club officer with a summary of callsigns and claimed scores. To be counted toward the club total, the individual entries must also designate the club. Deadline for club summaries is April 4.

Include a large SASE for results. Entries should be addressed to: Southern Arizona DX Association, c/o Philip M. Stickney N7BUP, 1890 West Paseo Cuenca, Tucson AZ 85704.

ZERO DISTRICT QSO PARTY 1900 GMT February 4 to 0100 GMT February 5 and 1500 GMT February 5 to 2400 GMT February 5

Sponsored by the Davenport Radio Amateur Club. Stations outside of Zero district will work Zero stations only, Zeros may work any station. The same station may be worked once on each band (80, 40, 20, 15, and 10 meters only) and each mode (CW and phone). However, mobile stations may be worked each time they change counties.

EXCHANGE:

RS(T) and ARRL section. Zero-District stations also must send county.

FREQUENCIES:

3560, 7060, 14060, 21060, 28060, 3900, 7270, 14300, 21370, 28570, 3725, 7125, 21125, and 28125.

SCORING:

Each phone QSO is worth one point; CW QSOs are worth two points. Non-Zero-District stations multiply by the number of Zero-District counties. Zeros multiply QSO points by the total ARRL sections, Zero-District counties, and DXCC countries worked.

ENTRIES & AWARDS:

A plaque will be awarded to the high scorer in the Zero District and high scorer from outside Zero Land. Certificates will be awarded for high scores in each ARRL section, DXCC country, Novice/Technician class, and mobile categories. Results and a participation certificate will be issued to all entrants who include an SASE. Mail logs by March 10 to W@BXR, 2131 Myrtle, Davenport IA 52804.

SOUTH CAROLINA QSO PARTY Starts: 1800 GMT February 4 Ends: 2359 GMT February 5

The QSO party is again sponsored by the Colleton County Contestors. The same station may be worked on each band and mode, simplex only. South Carolina mobile stations that change counties are considered new stations. Novice and Technician stations please sign /N or /T.

EXCHANGE:

RS(T) and state, province, country, or South Carolina county.

SCORING:

Phone contacts are worth 2 QSO points; CW contacts are worth 3 points. The multiplier for South Carolina stations is the number of states, provinces, and DX countries worked. Others multiply QSO points by the number of South Carolina counties worked (46 max.).

FREQUENCIES:

Phone—3895, 7230, 14280, 21365, 28560.

CW-3560, 7060, 14060, 21060, 28060. Novice-3725, 7125, 21125, 28125.

AWARDS:

Certificates to top-scoring station in each South Carolina county, state, province, and DX country. Novices and Technicians compete only with other Novices and Technicians.

ENTRIES:

Include a summary sheet with your entry showing scoring and other information. Indicate each new multiplier in your log as it is worked. Novices and Technicians must indicate class on entry. Include a large SASE for results. Send entry by March 5 to: Colleton County Contestors, c/o Elliott Farrell, Jr. KE4VP, Rt. 3 Box 658, Walterboro SC 29488.

VERMONT QSO PARTY 2100 GMT February 4 to 0700 GMT February 5 and 1100 to 2400 GMT February 5

Sponsored by the Central Vermont Amateur Radio Club (W1BD). Each station may be contacted once on each band and mode (CW, phone, RTTY). CW and RTTY contacts must be in the CW and RTTY subbands.

CALENDAR

Feb 4-5	South Carolina QSO Party
Feb 4-5	Arizona QSO Party
Feb 4-5	Vermont QSO Party
Feb 4-5	Zero District QSO Party
Feb 4-6	New Hampshire QSO Party
Feb 11-12	Dutch PACC Contest
Feb 18-19	YL-ISSB Commo System QSO Party-Phone
Feb 18-19	ARRL DX Contest—CW
Feb 18-20	America Radio Club International DX Contest
Feb 24-26	CQ Worldwide 160-Meter DX Contest—SSB
Feb 25	RTTY World Championship Contest
Mar 3-4	ARRL DX Contest—Phone
Mar 17-18	YL-ISSB Commo System QSO Party—CW
Mar 17-18	Bermuda Contest
Mar 17-18	Spring QRP CW Activity Weekend
Jul 13-15	A5 International SSTV-DX Contest
Aug 11-12	New Jersey QSO Party
Aug 24-27	A5 North American UHF FSTV-DX Contest
Sep 22-23	Late Summer QRP CW Activity Weekend

RESULTS

1983 ARIZONA QSO PARTY CERTIFICATE WINNERS

ARIZONA STATIONS

K6LL Yuma County
KB7KZ Pima County

Pima County 16,965

Score

75,468

NON-ARIZONA STATIONS
W5PWG Texas 200

EXCHANGE:

QSO number and state, province, country, or two-letter designator for Vermont county (AD, BE, CA, CH, ES, FR, GI, LA, OE, OS, RU, WA, WM, WR). Do not send RS(T).

FREQUENCIES:

Phone-3910, 7230, 14260, 14320, 21360, 28570, 50.110, 144.2.

CW-3530, 3730, 7030, 7130, 14060, 21060, 21160, 28060.

RTTY-3620 and **090 other RTTY subbands.

SCORING:

Score one point per phone contact, 2 points per CW or RTTY. Vermont stations multiply QSO points by number of states plus Canadian provinces plus ARRL countries (exclude US/Canada). Others multiply QSO points by the number of Vermont counties (14 max.).

AWARDS:

For non-Vermont stations, certificate to highest-scoring station in each state, province, and country. Certificates will be given each Vermont station submitting a log; annual plaque to highest-scoring Vermont station. W/VT Award given to stations working 13 of Vermont's 14 counties.

ENTRIES:

Send an SASE for official log and score sheets. Send logs/facsimiles, name, class of license, and address not later than March 1 to: D. Nevin KK1U, W. Hill, Northfield VT 05663. Include an SASE for a copy of the results.

NEW HAMPSHIRE QSO PARTY 1900 GMT February 4 to 0700 GMT February 5 and 1400 GMT February 5 to 0200 GMT February 6

Sponsored by the New Hampshire Amateur Radio Association. Stations may be worked once per band per mode. New Hampshire stations may work each other.

EXCHANGE:

Send RS(T) and country, ARRL section, or New Hampshire county, as appropriate.

FREQUENCIES:

Phone-3935, 3975, 7235, 14280, 21380, 38575, 50.115, 145.015.

CW-1810, 3555, 7055, 14055, 21055, 28055.

Novice-3730, 7130, 21130, 28130. RTTY-3625, 7085, 14085, 21085, 28085.

SCORING:

New Hampshire stations score 1 point per QSO, multiplied by the number of ARRL sections plus countries plus New Hampshire counties. Others score 5 points per New Hampshire QSO times the number of New Hampshire counties worked.

ENTRIES:

Send your entry no later than March 15 to Pete Cantara K1IM, 19 Haverhill St., Hudson NH 03051. Include a large SASE for results.

DUTCH PACC CONTEST Starts: 1400 GMT February 11 Ends: 1700 GMT February 12

Use all bands, 160 through 10 meters on CW and SSB. No crossmode operations allowed. Each station may be worked only once per band regardless of mode. Oper-



NEWSLETTER OF THE MONTH

We think that the Beacon is one of the best newsletters we've ever seen. Basically, it is packed with information: news notes, hamfest and club calendars, bylaw excerpts, net skeds, reports from members and other media, contest and DX info, League news, a membership application, and more. You name it and it's in the Beacon-and it's presented in a very neat, easy-to-read format. Congratulations to Editor Mike Head WB9ZQE and the Indianapolis Repeater Association. The Beacon is a real winner.

To enter your newsletter in 73's Newsletter of the Month Contest, send it to 73, Pine Street, Peterborough NH 03458, Attn: Newsletter of the Month.

ating categories include single operator, multi-operator, and SWL.

EXCHANGE:

RS(T) plus sequential QSO serial number starting with 001. Dutch stations will send their two-letter province abbreviation instead of a QSO number: GR, FR, DR, OV, GD, UT, YP, NH, ZH, ZL, NB, and LB.

SCORING:

Each QSO with PA, PB, or PI counts one point. Multiply QSO points by the number of provinces worked on each band (72 max.).

SWLS count one point per Dutch station heard and multiply by provinces heard on each band (72 max.).

ENTRIES:

As usual, a score calculation is required. Please use a multiplier column and insert multipliers only if new. A log must be signed for observations of the contest rules. SWL logs must contain condegroups given by the Dutch station and the foreign station worked with. Send logs no later than March 31 to: F. Th. Oosthoek PAØINA, PO Box 499, 4600 AL Bergen op Zoom, Netherlands.

A certificate will be awarded to each country winner in each category along with the second- and third-place stations provided that there are sufficient participants in that country. Certificates will also go to winners in each call district of JA, LU, PY, UA9/0, VE/VO, VK, W, ZL, and

AMERICA RADIO CLUB INTERNATIONAL

Starts: 0500 GMT February 18 Ends: 0500 GMT February 20

DX CONTEST

Any amateur station making two con-

RESULTS

1983 DUTCH PACC CONTEST

LISA WINNERS BY CALL AREA

	QSOs	Mult.	Score
K1KI	129	46	5934
WA2UDT	31	18	558
W3ARK	63	30	1890
W4VQ	106	37	3922
KN60	8	5	40
N6ZX/7	11	7	70
WD8MGQ	28	20	560
W9OA	47	19	893
WØKZV	22	13	286

tacts with America Radio Club DX member operators during the two-day contest will be eligible to apply for the Special Silver QSL Award. Stations making three contacts will be eligible for the Special Gold QSL Award. Contacts must be made during the two-day period listed above. Suggested frequencies include all authorized frequencies in the 10-, 15-, 20-, and 40-meter phone and CW bands. Exchange RS(T) and QTH. SWL stations may also apply for this award on a heard basis. For special awards, send QSL and \$2.00 in US funds or 6 IRCs to: America Radio Club QSO Contest, PO Box 3576, Hialeah FL 33013.

YL-ISSB COMMO SYSTEM **QSO PARTIES** Phone

Starts: 0001 GMT February 18 Ends: 2359 GMT February 19 CW

Starts: 0001 GMT March 17 Ends: 2359 GMT March 18

Use the General portion of all bands. Deadline for all logs, summary sheets, and comments is June 1. Entries should be addressed to: Rick and Minnie Connolly, Star Route 1, Crocker MO 65452. Individuals needing extra application and instruction forms send a 4 x 9 SASE to the same address.

CQ WORLDWIDE 160-METER CONTEST - SSB

Starts: 2200 GMT February 24 Ends: 1600 GMT February 26

Operating classes include both single and multi-operator (maximum of 5 ops per station).

EXCHANGE:

RS plus QTH, state for USA, and prov-Ince for Canada.

RESULTS

1983 A5 NORTH AMERICAN **UHF-FSTV CONTEST**

1 K6YGX/W6VCF	26,530
2 WB0ZJP	9,420
3 WB9MCF	5,440
4 W2WHK	4,520
5 KAØBVT	4,360
6 W2RPO	3,755
7 N2BJ	3,350
8 WA2CXW	2,815
9 WB2KGM	1,695

SCORING

Contacts with stations within own country are 2 points, other countries but same continent are 5 points, other continents are 10 points. KH6 and KL7 are considered countries.

Multipliers are each US state, VE province, and DX country. USA and Canada are not country multipliers. However, there are three VE1 provinces: New Brunswick, Nova Scotia, and Prince Edward Island. Final score is total QSO points times the sum of the multipliers. Maritime mobile scoring will be determined by the location.

AWARDS:

Certificates to the top scorers in each class in each US state, VE province, and DX country. Special plaques are also being awarded for top USA, Europe, and world scores.

PENALTIES:

Three additional contacts will be deleted from the score for each duplicate, faise, or unverifiable contact removed from the log. A second multiplier also will removed for each one lost by this action.

Violation of the rules and regulations pertaining to amateur radio in the country of the contestant or the rule of the contest, or unsportsmanlike conduct, or taking credit for excessive duplicate contacts or multipliers will be deemed sufficient cause for disqualification. Disqualified stations or operators may be barred from competing in CQ contests for a period of up to three years.

ENTRIES:

Sample log and summary sheets may be obtained from CQ by sending a large SASE with sufficient postge to cover your request, it is not necessary to use the official form, you can use your own. Logs should have 40 contacts per page and show time in GMT, numbers sent and received, and separate columns for QSO points and multipliers. Indicate the multiplier only the first time it is worked.

Include a summary sheet with your entry showing the scoring and other essential information, and a signed declaration that all rules and regulations have been observed. Mailing deadline for SSB entries is March 31. Logs can be sent directly to the 160 Contest Director, Don Mc-Clenon N4IN, 3075 Florida Avenue, Melbourne FL 32901 USA. Alternatively, they can be sent to CQ 160-Meter Contest. 76 North Broadway, Hicksville NY 11801 USA. Please indicate "SSB" on the envelope!

3RD ANNUAL RTTY WORLD CHAMPIONSHIP 0000Z to 2400Z February 25, 1984

SPONSORED BY:

73: Amateur Radio's Technical Journal and The RTTY Journal

OPERATOR CLASSES

(A) Single operator, single transmitter. (B) Multi-operator, single transmitter.

ENTRY CATEGORIES:

(A) Single band. (B) Allband. 10-80 meters.

MISCELLANEOUS RULES

The same station may be worked once on each band. Crossmode contacts do not count. Single-operator stations may work 16 hours maximum, while multi-operator stations may operate the entire 24-hour period.

Off times are no less than 30 minutes each and must be noted in your log(s).

EXCHANGE

Stations within the 48 continental United States and Canada must transmit RST and state or province/territory. All others must transmit RST and consecutive contact number.

QSO POINTS

5 QSO points for contacts with W/VE stations located within the continental United States and Canada. 10 QSO points for all other contacts.

MULTIPLIER POINTS:

1 multiplier point is awarded for each of the 48 continental United States (a District of Columbia contact may be substituted for a Maryland multiplier). Canadian provinces/ter ritories, and DX countries worked on each band (excluding US and Canada).

FINAL POINTS

Total QSO points times total multipliers equals claimed score.

CONTEST ENTRIES

Entries must include a separate log for each band, a dupe sheet, a summary sheet, a multiplier checklist, and a list of equipment used. Contestants are asked to send an SASE to the contest address for official forms.

ENTRY DEADLINE

All entries must be postmarked no later than April 15, 1984.

DISQUALIFICATIONS

Omission of the required entry forms, operating in excess of legal power, manipulating scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate dis-

qualification. Decisions of the contest committee are final.

AWARDS.

Contest awards will be issued in each entry category and operator class in each of the US call districts and Canadian provinces/territories, as well as in each DX country represented. Other awards may be issued at the discretion of the awards committee. A minimum of 25 QSOs must be worked to be eligible for awards.

CONTEST ADDRESS.

RTTY World Championship, c/o The RTTY Journal, PO Box RY, Cardiff CA 92007.

DX

Chod Harris VP2ML Box 4881 Santa Rosa CA 95402

QATAR

One of several tiny countries around the Persian Gulf, Qatar's chief claim to fame is its black, gooey, crude oil under a barren landscape. Actually, Qatar is a peninsula sticking into the Persian Gulf from Arabia, not far from the island country of Bahrain. Most of Qatar's 4000 square miles are barren sand and low hills; annual rainfall is about 5 inches. Most of the country's 170,000 inhabitants live in the capital city of Dona.

As are most Middle Eastern countries, Qatar is antagonistic toward strangers. These countries are highly suspicious of foreigners and not only discourage but actually prohibit most visitors. (Consider Iran's feelings toward Americans, for example.) DXpeditions and amateur operations by foreigners living in these countries are seldom permitted, and few of the native amateur operators spend much time handing out DX contacts or QSL cards. So the report of an American with a well-equipped station active from Qatar is good news indeed.

Mike Smedal A71AD (Photo A) is the first foreigner to receive an amateur-radio license since the country became independent 14 years ago. To qualify for the license, Mike had to show that he worked and lived in Qatar, and he had to pass a security clearance. That done and the \$250 license fee paid, A71AD was on the air.

Mike's station includes a Yaesu FT-1 transceiver feeding a Yaesu FL-2100Z amp. When conditions get a little rough, Mike runs the output of the Yaesu amp into an export version of Alpha's 77SX amplifier! The antenna farm is also first class (Photo B): a Hy-Gain TH7DDX above a Hy-Gain 402BA two-element 40-meter beam. An inverted V provides 80-meter coverage. Mike says that the TH7 handles the high-power levels without difficulty. Mike runs RTTY on his Radio Shack TRS-80 Model I and is active on OSCAR, too.

The best times to look for Mike (and other Middle Eastern amateurs) are Thursday evening and Friday. The work week is six days long in Qatar, with Friday (the Arab holy day) as the day off. So their equivalent to our weekend is Thursday night and Friday.

On the subject of QSL cards, Mike writes, "Please tell everyone that we do not have a radio club in Qatar. Therefore,

we do not have a QSL bureau. If [DXers] want a QSL card, please QSL direct to PO Box 4747, Doha, State of Qatar, Middle East."

SAUDI ARABIA

An exception to the no-visitor policy of the Middle Eastern countries was made for the recent visit of Lloyd and Iris Colvin, W6KG and W6QL, of Yasme DXpedition fame. The Colvins managed not only to visit most of the countries in the region, but also actually obtained permission to operate in many of them.

Iris faced special problems in Saudi Arabia. Women occupy a very special role in the Arab world, quite different from that in the more liberal Western nations. Women are seldom seen out in public, and then only heavily veiled. Those few women who do venture out of doors find themselves escorted to the head of the line and receive other special attentions. On the other hand, an unveiled woman in Saudi Arabia faces a nasty surprise from the local authorities.

Saudi policemen carry two items on their belts: a can of black spray paint and an ice pick. Upon seeing a woman with bare face or arms, the policeman will, very politely, spray black paint over the exposed skin! (The ice pick sees similar service in the Saudi's swift, uncomplicated justice system. Illegally parked automobiles are not ticketed or towed. The policeman simply stabs all four tires with the ice pick!) And petty theft is unknown; the Saudis still cut off the hand of an offender.

In the amateur-radio field, most of the local hams are big wheels in the government or are in the Saudi family, which is the same thing. With the billions of dollars flowing into the country as the oil flows out, Saudi hams can afford good equipment. One local ham employs a graduate electronics engineer just to maintain his amateur-radio station!

However, the Saudi princes aren't likely to spend much time running stateside hams in pileups. One of your best bets to work Saudi Arabia is HZ1AB, the amateur-radio club at the American compound on the Persian Gulf, which is home in Saudi Arabia for about 50,000 foreigners. HZ1AB is another first-class station, with Collins S-lines, amplifiers, and a substantial antenna farm. The latter includes a rhombic, rotatable KLM tribander and a 2-element beam on 40 meters. The Colvins operated the ARRL CW DX Test from HZ1AB, but could work the States for only about 7 hours a day.

Among the regular operators of HZ1AB are Dave Ernest W7SE and N6OL. QSL the station through K8PYD, except for the February 19–20, 1983, operation by the Colvins, which is confirmed via Yasme, Box 2025, Castro Valley CA 94546.



Photo A. Mike Smedal A71AD in his well-organized and well-equipped shack in Doha, Qatar.

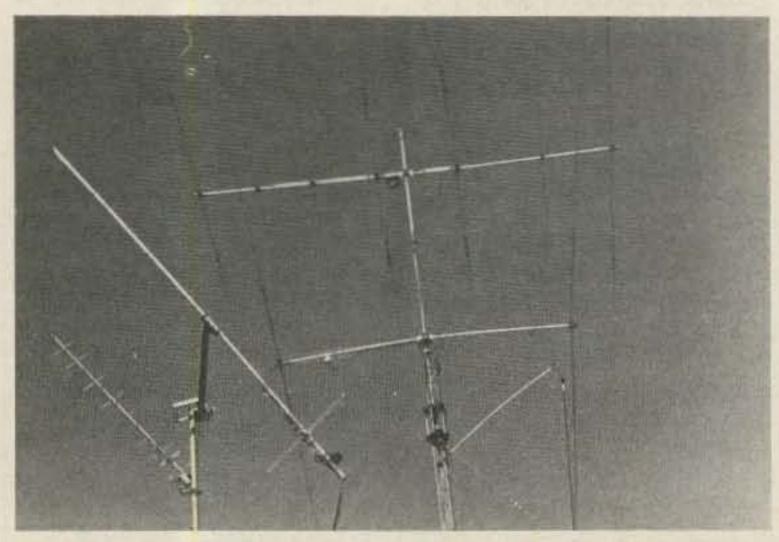


Photo B. The antenna farm at A71AD, including a TH7 and 2 elements on 40 meters. In the foreground are the Oscar 10 antennas.

QRO-EXCESSIVE POWER

Lloyd and Iris Colvin stopped by Houston between DXpeditions this past fall. At the International DX Seminar, held in conjunction with the ARRL National Convention, the Colvins joined several other prominent DXers and contesters on the panel discussion of excessive power in amateur radio. The problem of excessive power drew a large and interested crowd to hear the DXers discuss alternative solutions.

The seminar opened with a discussion of what we mean by "excessive power." Under the old FCC regulations, any amplifier was restricted to a maximum of about 800 Watts output. However, many of the "standard" off-the-shelf amplifiers openly sold in the amateur community were capable of significantly greater power levels, often 50% more. Active contesters and DXers owned amplifiers capable of running power levels above the FCC maximum because of the greater dependability and longer lifetime of an "over-rated" amp. A 1000-Watt amplifier running 1000 Watts all the time won't hold up as well as a 2000-Watt amp coasting along at half power.

However, there was always a strong temptation, particularly in DX pileups and contests, to run the amp flat out. "Tuning



Photo C. Gene Zimmerman W3ZZ (standing) makes a point at the Excessive Power seminar of the First International DX Symposium, in Houston. Al Slater G3FXB (left) and Bob Ehrhardt YS9RVE listen intently.

for maximum smoke" is the usual practice, and many amateurs have run "excessive power" for years. Under the new FCC power regulations, most of these amplifiers have been "grandfathered" into legality.

But there is a greater problem in excessive power than squeaking out a couple extra Watts over the legal limit. While some amateurs are still saving their bucks for a better antenna, some hams have quietly been installing real high-power amplifiers, amps that require 500-1000 Watts of drive.

The Houston seminar turned to the problem of what to do about that small number of amateurs who run super-power. Frequent contester (and occasional DXpeditioner) Gene Zimmerman K3ZZ (Photo C) suggested that the current rules about power during contests be changed. Gene recommended that inspectors stop by the shacks of hams seriously involved in the contest and look at the amplifiers. If any amp had final plate dissipation (or the transistor equivalent) of more than 1600 Watts, the contestant would be disqualified. He reasoned that if you don't have an amp capable of running excessive power, you won't run it! The same idea holds for DXers, of course, with the offending amateur losing the right to participate in DXCC, for example.

Al Slater G2FXB (Photo C) talked about a similar program used by the Radio Society of Great Britain for their Field Day, which is even more popular there than the same activity on this side of the Atlantic. The RSGB requires each Field Day team to register before the contest and include their operating locations. During the contest, a volunteer RSGB inspector stops by and checks that the group is meeting their strict rules of 30 Watts maximum input power!

This 30-Watt limit poses special problems for British amateurs; most standard transceivers have little or no output at the 30-Watt input level. So the G hams build special final amplifiers designed for maximum output with 30 Watts of input power. These simple amps often are fed with a 100-Watt output transceiver and are run so close to the limit that some groups change final tubes every hour of the contest!

The question of high power is of special interest to Al, who spends much of his time on 160 meters, where the British hams face a 10-Watt power limit. Al said the government licensing authorities no longer worry about power and have suspended their station inspections. Most

hams run a full 200 Watts on 160 meters, and 2000-Watt amplifiers are not unknown.

In other comments on the high-power question, panelist Ellen White W1YL felt that the contest rules already permit disqualification of anyone running illegal power. On the other hand, Ellen felt that the idea of inspectors coordinated from League headquarters would be unworkable. Ellen favored handling excessivepower users at the local level, by drumming them out of the local DX club, for example.

Both Iris and Lloyd Colvin recommended increasing the existing power limits as a means to eliminate the "excessive-power" problem. Lloyd particularly suggested higher power limits on the lower frequencies, including .160. Iris noted the advantages of high power on DXpeditions, when the power helps to control the pileup. If the stateside stations calling can't hear the DX station very well, the rate of contacts drops and fewer hams get a chance to work the DX station.

Several members of the audience took exception to the idea of ever-increasing power limits. Tod Olsen K@TO disagreed with the concept of letting the manufacturers of amateur equipment decide what the legal or moral limits to excessive power should be. "Just because it is openly sold to hams doesn't mean that the power level is acceptable." Dick Norton N6AA felt that in the contest field the power level doesn't really matter as long as the final contest results are not affected. But if someone wins the contest or moves ahead of a legal power station by running excessive power, he should be disqual-

I have my own definition of "excessive power." The FCC amateur regulations state that amateurs should always use the minimum power necessary for the communications. So two hams talking across town on 20 meters don't need the amplifiers, much less the excessive-power amps. And frankly, even a few thousand Watts of power cannot compensate for bad operating techniques or inadaquate antennas.

How much power is really needed for amateur communications? Listen any time to 14100. A series of beacons all over the world ticks down every ten minutes with ever-lower power levels. See how far down into the mud you can copy the beacons' signals. We'll be talking more about this beacon network and other propagation aids and suggestions in future issues. Stay tuned. Meanwhile, keep an ear out for some of these coming attractions.

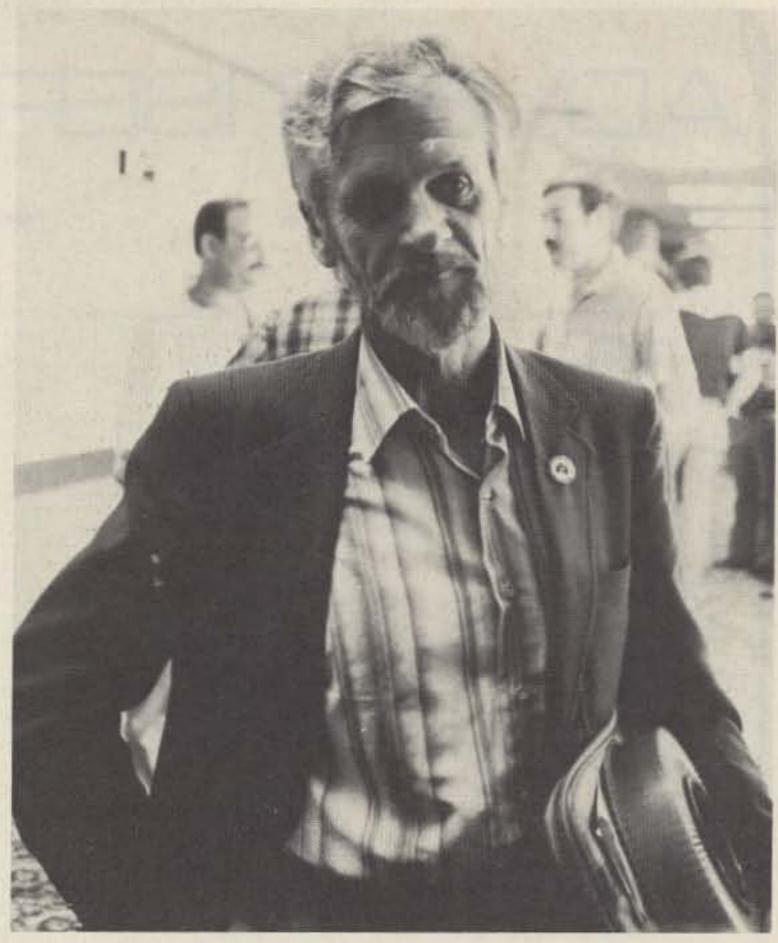


Photo D. Jim Smith VKONS is aiming for Kermadec Islands this season, after his eventfilled DXpedition to Heard Island last year.

COMING ATTRACTIONS

The DXpedition circuit continues to hum in February, with two major expeditions scheduled for the month. Jim Smith VKONS (Photo D) is spearheading an amateur and scientific DXpedition to the Kermadec Islands, a small, sparsely-inhabited group of volcanic islands about halfway between New Zealand and Tonga. Under the control of New Zealand, they have no special amateur call prefix.

The Kermadec Islands have been slowly moving up in the Most-Wanted-Countries list and now rank 17th, up with Spratly, Laos, and Clipperton. This DXpedition should satisfy a good chunk of that demand, with several operators and plenty of time on the island.

Jim Smith organized the Heard Island DX Association trip to Heard Island last winter and hopes for fewer problems on this year's DXpedition. Jim is also looking for donations for the trip and memberships in his Heard Island DX Association. Contact Jim via PO Box 90, Norfolk Island, South Pacific 2899.

Also scheduled for this month is a DXpedition to Aves Island, halfway around the world in the Caribbean. Isla de Aves

(The Island of Birds) is a tiny part of a submerged reef about 150 miles west of the Windward Islands. The Island is under the control of Venezuela, and the Venezuelan military restricts access most of the time.

The island itself is only about 1500 feet long and about 400 feet wide at the largest. Its maximum ten-foot elevation means it really is a large rock out in the middle of the ocean. Whenever the waves or tides are high in the Caribbean, landing on Aves is impossible. Only during a short period in mid-winter do calm conditions permit amateur operations.

Because of the restrictions and landing problems, DXpeditions to Aves are few and far between. Any station on the island is easy to work from the States, thanks to the excellent propagation from that part of the world. (Why do you think I lived there?) But you won't want to miss this DXpedition, as the next one might be years down the DX road. And Aves is already in the top 30 most wanted.

The DXpedition is sponsored by the Radio Club Venezolano, which is celebrating its 50th anniversary this year. The callsign on Aves will be YVØAA, with QSLs handled by YV5DFI, PO Box 50332, Caracas, Venezuela 1050-A, South America.

TMULTI-BAND SLOPERS

160, 80, and 40 meters

Outstanding DX performance of slopers is well known. Now you can enjoy 2 or 3 band BIG-SIGNAL reports! Automatic bandswitching . Very low SWR . Coax feed . 2kw power . Compact . Ground or tower feed · Hang from any support 25 ft. high or higher · Easy to install · Very low profile . Complete instructions . Immediate shipment - Check ok

3 BAND SLOPER: 160, 80, & 40 Meters: 60 ft. long \$ 43 00 frt ppd 2 BAND SLOPER: 80 & 40 Meters - 41 ft, long \$ 30.00 frt ppd. \$ 66.00 frt ppd. 3-BAND NO TRAP DIPOLE, 160, 80, & 40M - 11311, long 2-BAND NO TRAP DIPOLE. \$ 49.00 frt.ppd. 80.& 40M + 84ft. long

FOR ADDN'L INFO on these and other unique antennas:

send SASE


W9INN ANTENNAS BOX 393-S MT. PROSPECT, IL 60056

ADVERTISERS

*Please contact these advertisers directly.

To receive full information from our advertisers please complete the postage-paid card.

R.S	. No. Page	R. S. No.	Page R.	S. No. Page	R.S	No. Page
	AEA/Advanced Electronic	25 Control Products,	Unlimited99 *	Kantronics		Simplex
	Applications	141 Cushcraft Corp	81 *	Kenwood Cov. IV, 7	154	Slep Electronics Company85
127	Advanced Computer Controls	106 Cushcraft Corp.	45 *	KLM Electronics, Inc 65	68	Spectrum Communications13
		* DGM Electronics,	Inc 50 47	9 Lowrance Satellite	436	Spectrum International, Inc 34
*	Amateur Communications, Etc.	346 Data Service	102 82	MCM Communications		Spider Antenna
	45	 Dayton Hamventi 	on16 9	MFJ Enterprises	224	Teltone
*	Amateur Electronic Supply 35	425 Doppler Systems	47 48	MHz Electronics 104-113		The Computer Journal103
243	Amateur-Wholesale Electronics	153 DX Tours		Madison Electronics57		The Ham Shack
	68	120 Electra Company		Micro Control Specialties 115	205	The Metheny Corp 4
334	Amidon Associates45	18 Electronic Specia	lists, Inc 61 51	Microlog Corporation	104	Trionyx Industries 49
71	Applied Invention52	135 Encomm, Inc	117 *	Mirage Communications 16	136	Tucson Amateur Packet Radio
	BMG Engineering	29 Esoteric Engineer	ing 103 25	8 Missouri Radio Center12		32
11	Barker & Williamson, Inc 49	99 Faxscan		Moler Antenna, Inc102	149	Unique Communications
305	Barry Electronics	23 Flesher Corporati	on20 13	8 Nampa Satellite Systems25		Corporation103
152	Bencher, Inc	139 Fox-Tango Corpo	ration57 25	4 National Comm. Group Co 32	*	University Microfilms 103
477	Bencher, Inc	151 Fox-Tango Corpo	ration53 41	2 Nemal Electronics100		Van Gorden Engineering47
*	Bill Ashby & Son	95 Fox-Tango Corpo	ration47 13	7 Nuts & Volts102	311	Vanguard Labs102
*	Blacksburg Group50	178 Galaxy Electronic	s103 *	Orbit Magazine		W9INN Antennas
*	Break Comm. Systems, Inc 99	143 GLB Electronics .		P. C. Electronics	135	WELZ117
	Butternut Electronics57	352 Grove Enterprises	,Inc41 *	Palomar Engineers	79	Wacom Products, Inc 47
12	CZ Labs85	478 H. Stewart Design	s92 4	Parsec Communications 72	480	WGE Copyrighter
462	CES, Inc	31 Hal-Tronix	56 14	8 Public Domain, Inc53	145	Wayne Green Books 82
111	Ceco Communications, Inc50	101 Ham Masters Tap	es	Radio Amateur Callbook, Inc 4		Wayne Green Shelf Boxes56
13	Coin International102	* Ham Radio Outlet		4 Radiokit		Westcom
14	Communications Concepts, Inc.	33 Hamtronics, NY	126, 127 62	Ramsey Electronics 125, 128		Westech Electronics, Inc 80
		59 Heil, Ltd		3 Rivendell Associates72		Western Radio Electronics 103
15	Communications Specialists, Inc.	123 Hustler, Inc		0 Royal		Wheeler Applied Research Lab
		* ICOM	Cov. II, 87 *	RUN Magazine51		102
	Computer Trader102	36 International Crys	tal 50	0 73	481	
(40)	Connect Systems, Inc		,Inc 52	Dealer Ad	83	Yaesu Electronics Cov. III
37	Contemporary Technology, Inc.	122 John J. Meshna, Jr	The state of the s	Moving101		Yaesu Electronics90
				Subscriptions		

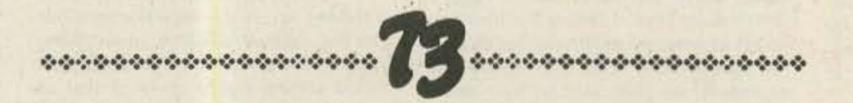

BOOKS, ETC.

To order, complete the postage-paid card, or itemize your order including detailed credit card information or check and mail to: 73 Magazine/Mail Order Dept./Peterborough NH 03458.

Catal	og# Item	Price	Catalo	g#	* Item	Price	Catalog	# Item	Price	Catalog#	Item	Price
		-	BK7309	CHALLEN	IGE OF 160	\$ 4.95	BK7310	OWNER REPAIR OF RADIO E	QUIPMENT	SG7358	STUDY GUIDE - GENERAL CLAS	S \$ 69
			BK1011	CMOS CO	ооквоок	\$10.50			\$ 7.95	BK1190	THE TEN METER FM HANDBOO	K \$ 49
73300	7) BACK ISSUE - BEFORE JULY	1980	C17305	CODE TA	PE-5 WPM	\$ 495	BK1185	THE PRACTICAL HANDBOOK	K OF FM	1.87360	TEST EQUIP LIB V2-AUDIO TES	STERS
			C17306	CODE TA	PE-6+ WPM	\$ 495		REPEATERS	512.95			5 49
73350	73 BACK ISSUE - JULY 1980 TH	RU	C17313	CODE TA	PE-13+ WPM	\$ 4.95	BK7302	PROPAGATION WIZARD S H.	ANDBOOK	LB7361	TEST EQUIP LIB V3 - RADIO FOL	
	OCT 1981		C17320	CODE TA	PE-20+ WPM	\$ 4.95			\$ 6.95	LB7362	TEST EQUIP LIB V4-IC TEST EQ	5 49
73350P	7) BACK ISSUE - NOV 1981 TO	PRESENT	C17325	CODE TA	PE-25+ WPM	\$ 4.95	QW0250	QSL CARDS-STYLE W-250	0 \$ 8.95	BK7387	TEXTEDIT - WORD PROCESSING	
		\$ 350	C17394	CODE TA	PES JANY FOUR A	BOVE: \$15.95	QW0500	QSL CARDS-STYLE W-50		1000000	CINCIL DEFECTION	\$9.9
73005	73 BACK ISSUE -5 YOUR CHOK	CE	BX1241	THE COM	PLETE SHORTWA	VE		OSL CARDS-STYLE X-250		D57387	TEXTEDIT - DISK	\$19.9
		\$10.75		LISTENER	RS HANDBOOK	\$ 9.95		QSL CARDS-STYLE X-500		BK7348	TOOLS & TECHNIQUES	\$ 49
	Add \$1.00 per magazine for shippin	10	BK7366	THE CON	TEST COOKBOOK			QSL CARDS STYLE Y 250		BK1063	TTLCOOKBOOK	\$ 95
73010	73 BACK ISSUE - 10 YOUR CHO	ICE	BK7381	40 COMP	UTER GAMES	\$ 7.95	QY0500	QSL CARDS-STYLE Y-500		BK1064	TVT COOKBOOK	\$ 99
		\$16.00	BK1244	EVERYTH	HING YOU ALWAYS	WANTED TO	BK1199	THE RADIO AMATEUR ANTE		BK7382	UNDERSTANDING A PROGRAM	
73025	73 BACK ISSUE -25 YOUR CHO	ICE		KNOW AS	BOUT AMATEUR T	v \$ 9.95		HANDBOOK	\$ 6.95		MICROCOMPUTERS	\$10.9
		\$27.00	BK7321	A GUIDE	OIDAR MAH OT	\$ 4.95		RE & DIGITAL TEST EQUIPMI		BK7368	VHF ANTENNA HANDBOOK	\$ 59
73125	73 BACK ISSUE -25 OUR CHOIC	30	8K7322	HOBBY C	OMPUTERS ARE	HERE \$ 2.47	0.0750	73 DIPOLE & LONG WIRE AN		BK1198	VHF HANDBOOK FOR RADIO A	
		\$14.00	BK 1201	HOW TO	DEFEND YOURSE	LF AGAINST			\$ 550		THE THIRD BOOK TO THE BOOK	\$ 6.9
: A	Add \$7.50 per order for shipping	-0000		RADAR		\$ 6.95	8X1000	SHELF BOX-1	\$ 2.00	BK1202	WORLD PRESS SERVICE FREQU	
			BK1028	IC OF AM	PCOOKBOOK	\$14.95	BX1001	SHELF BOXES-2-7	\$1.50 each	3417.555	Manies West Services Const	\$ 7.9
			BK1230	INTERFE	RENCE HANDBOO		BX1002	SHELF BOXES B AND UP	\$1.25 each	BK1184	WORLD RADIO TV HANDBOOK	\$16.5
iK1196	ALL ABOUT CUBICAL QUAD ANT	ENNAS	BK7386	KILOBAU	D KLASSBOOM	\$14.95	BK 1200	SIMPLE LOW COST WIRE AT		BK7315	WORLD REPEATER ATLAS	\$ 20
		\$ 5.95	BK7312	MAGIC D	F HAM RADIO	\$ 495		FOR RADIO AMATEURS	\$ 6.95		TO THE PARTY OF TH	
K7384	ANNOTATED BASIC VOL 1	\$10.95	BK7340		HOBBY COMPUT			SOME OF THE BEST FROM P				
3K7385	ANNOTATED BASIC VOL 2	\$10.95	BK7383	THE NEW	WEATHER SATEL				\$10.95	SHIPPING	AND HANDLING CHARGES: \$1	50: for th
BK1197	BEAM ANTENNA HANDBOOK	\$ 5.95		HANDBO		\$ 8.95	BK7351	SSB THE MISUNDERSTOOD			\$1 for each additional book for U	1
BK7307	BEHIND THE DIAL	\$ 4.95	CT7300		HEORY TAPES	\$15.95	120000000000000000000000000000000000000	STUDY GUIDE - NOVICE CLA			n surface. \$10 per book for foreig	
						2.0.00		2.00 2020 101105 050	9 - 20		and the same of the same of the said	-

HAM HELP

We are happy to provide Ham Help listings free, on a space-available basis. We are not happy when we have to take time from other duties to decipher cryptic notes scrawled illegibly on dog-eared postcards and odd-sized scraps of paper. Please type or print your request (neatly!), double spaced, on an 81/2" x 11" sheet of paper and use upper- and lowercase letters where appropriate. Also, please make a "1" look like a "1," not an "l," which could be an "el" or an "eye." and so on. Hard as it may be to believe, we are not familiar with every piece of equipment manufactured on Earth for the last 50 years! Thanks for your cooperation.

I'm looking for a schematic for a Lavoie oscilloscope, model no. LA265A. I will pay for copying and mailing costs.

> L. C. Hocutt WE40 4257 Via Alta Dr. Mobile AL 36609

I am interested in obtaining the vox relay that plugs into the back of the Swan 700 transceiver. I would appreciate hearing from someone who may have one of these lying around that they don't have any future use for.

> Augustus B. Wells PO Box 50 Tunica LA 70782

I am looking for a copy of the instruction booklet for the Knight KG6/0 H/C tester made by Allied Radio. I will pay the costs for copying and mailing or for the original manual.

> Lionel Roach KD5VO 3033 Teakwood Garland TX 75042

Wanted: Collins 70E-7A PTO (permeability-tuned oscillator) for a Collins 75A1 receiver. This PTO covers 2-3 MHz and is used to tune the receiver.

> Harold Smith W2GKE 26 Linden St. Bayonne NJ 07002 (201)-436-1405

I am using the VIC-20 as a RTTY terminal with Kantronics interface and software. Can anyone help me with information on building an adapter which would let me use Atari cartridges on the VIC-20?

> Robert F. Cann W4GBB 1606 Lochwood Dr. Richmond VA 23233

I would appreciate receiving a copy of the schematic for an NCX-3 SSB/CW transceiver by National. I have the owner's manual already. I will gladly reimburse for costs.

> Jeffry M. Blackmon W2YI 2107 Turnbull Road Beavercreek OH 45431

I need the schematic for the Model TV-7D/U tube tester.

> Stan LaDage W2EZM 431 Oakland Ave. Maple Shade NJ 08052

I want to replace the tubes in my Collins R-392 receiver with solid-state devices. Any information on replacement parts would be greatly appreciated. I also need information on the R-392 Club and sources for 2-kHz filters for the Collins R-390A.

> J. P. Barnes G8AHN 2 Mappins Rd. Catcliffe, Rotherham South Yorkshire S60 5TH England



The Spider Antenna

WE HAVE NO DEALERS - ORDER DIRECT

NOW! A State-of-the-Art Antenna for State-of-the-Art Transceivers-Why Settle for Anything Else!

At last there is a mobile antenna that is truly a fit companion for today's solid state, no-tune transceivers.

Once the SpiderTM 4-Band Antenna is tuned for 10, 15, 20 and 40 meters, all you have to do is turn the band switch on the transceiver-the antenna follows by itself.

Write or call now for full information on this, the top of the line in mobile antennas.

MULTI-BAND ANT

7131 OWENSMOUTH AVENUE, SUITE 463C CANOGA PARK, CALIF, 91303 TELEPHONE: (818) 341-5460

NICAD MEMORY ERASE — WHAT??

- Complete automatic operation
- Erases + Charges + Checks
- Rapid charges in 35 min. (typically)
- Automatically repairs shorted cells
- No dangerous heat build up
- Front panel selects up to 3 different packs
- Unlimited battery combinations with program modules (user programable)
- LED status indicators
- Supplied with universal EZ hook wire leads

Specify Voltage of Battery Pack(s) with order. One program module included - optional modules \$2.25 each.

\$89.00 plus \$4.00 Shipping

(PA Residents add 6% sales tax)

Now Available—A commercial version of the GMS 401. Designed to charge up to and including the commercial 15 volt Nicad packs, \$139.00 plus same shipping and module cost as the GMS 401.



The GMS 401 is a complete automatic NICAD conditioner and rapid charger. Never before has this been offered anywhere at any price and it's so good it's being patented. NICAD memory characteristics must be dealt with otherwise your battery pack is not delivering all it could. The GMS 401 will automatically erase and rapid charge any type NICAD pack from 1 to 10 cells.

CONTROL PRODUCTS UNLIMITED, INC.

P.O. Box 10, Downingtown, PA 19335 215-383-6395



4 console displayed

Break Communications Systems, Inc.

MICA COMMUNICATIONS CONSOLES

4'-6'-8' Wide - 1 to 8 wide optional "L" & "U" & Circular set up's – with optional corner table Replaceable Front Panel – for station changes Precisely cut panel holes – by computerized wood cutter High station density – because no shelves are used! Hidden accessory shelf - for power supplies dummy load Puppets of all your equipment – for easy station layout

OPTIONAL ITEMS:

Drawer Bookshelf combination – hangs under desk 1000 Mica's to select from – to match your decor Desk recessed for keyboard – optimum 26 typing height Desk top extensions: into panel – for apple computer or storage Matching dolly for floor amp's – with concealed casters Shelf under desk, quick access – for headphones, Key Mic. Exhaust cooling fan system – thermostatically controlled Wire duct, wire labels, etc...

5817 S.W. 21st Street, Dept. 73 • Hollywood, Florida 33023 Phone (305) 989-2371

W2NSD/1 NEVER SAY DIE

editorial by Wayne Green

from page 6

lem was not unique, that indeed the problem was universal
and probably at the root of the
general dislike of cocktail parties. I have a problem there.
While I may hate meeting people and being expected to be
entertaining on demand, I can't
stay away from the food. I think
I'd take a plane to the Shetland
Islands if they promised me an
interesting meal.

Much of my life has been an extended diet interspersed with fantastic meals which make the dieting even more imperative. About ten years ago I got fed up, if you'll pardon the expression, and went on a diet for about nine months. I lost 85 pounds, going from 250 bloated pounds down to 165. What an un-orgy that was! These days I hang around 175, not looking too fat, but feeling ten pounds overweight and guilty when gorging on ice cream, cake, and such.

Getting back to my ego: I wonder if my hopes to inspire you to greater things come across as ego? I delight in getting letters from people who have several basic drives: One is to educate and another is to share my enthusiasms. You may have noticed that all of my magazines are both educational and fun—expressions of my drives.

I don't believe that you can make all of the money you want, I know it. I hate it when I get letters complaining that, gee, I can't afford your magazine, a new rig, or something. What rot! There are so many ways to make money these days that just about anybody who wants to can do it...from kids right up to the retired.

No, if you are going to pursue a life goal of swilling several thousands of gallons of beer and seeing every Monday-night football game, you're a loser. You don't get rich very often without working hard at it. But

you have to work with some goals in mind. A lot of people work their butts off and never get anywhere. The brutal fact is that, though not by any conscious design, this is the normal pattern. You do have to outwork the average person to make it big.

Why am I getting ready to invest several million dollars in a college? Here we are at a time when colleges are going out of business all around the country and I want to start a college! Dumb or shrewd? Well, I think I have a plan which will teach kids to become entrepreneurs and to beat the system. The end result will be a bonanza for our country and a few thousand more millionaires. Everyone will win.

There's Wayne's ego again? Well, perhaps—yet I've gone over my idea with the presidents of ten colleges now and haven't yet found one who doesn't think it will work. I'm getting quite a bit of support.

The average 73 reader is way above the average person in this country. It isn't easy to get a ham ticket, even with the Bash method, so that's a filter. And beyond that, the average 73 reader is another step ahead of the average ham just by virtue of his interest in keeping up with technology. The ham who does not read 73 has far less of

an opportunity to be a success just because he doesn't take advantage of this remarkable resource.

From that aspect, I really feel sorry for the foreign hams who can't afford 73 or who are prohibited from subscribing because their money can't be sent away.

Most of my time is spent these days looking for people to help me with my projects. I really need help—enthusiastic, non-smoking help. My editorial a few months ago discussed this and resulted in a couple hundred letters. Some of those people are already here in Peterborough helping me get new projects started.

One enterprise, a franchise chain of software stores, is getting started. I have a whole new approach to the business which should make it possible for several thousand people to make an awful lot of money. It's an ingenious concept that no one else has thought of yet, so we have a very good chance, despite the recent proliferation of software stores.

Software Production Devices, Inc., is also moving along on schedule. This isn't my idea, but when I saw what two chaps from Bangkok had come up with and realized how desperately the computer industry needs the product, it seemed like a good investment. Indeed, I know of no other practical appoach to software protection, and I think I know 'em all.

I have several new magazines in mind which are needed, each to help a new industry to grow just as Byte and Kilobaud helped the microcomputer industry to flower. Magazines can't be started unless I have editors, writers, ad sales, circulation, administration, typesetting, production, photography, accounting, data processing, promotion, and so on. It takes about 25 people (minimum) to make a magazine work, and between the seven magazines we have now, the two of McGraw-Hill, and a half dozen others in the area, we've just about cleaned out southern New Hampshire of available talent. Interested?

A surprising number of the people we've been hiring of late are hams, fliers, and computer-ists—quite a combination for success, I suspect.

And speaking about proj-



ects, a chap who used to work for me started his own computer mail-order business here in town and is already doing well over a million in sales per year. He started out with a small ad in inCider, my Apple magazine, and went over the million mark in sales the first month. I talk with him often...on the street, at the Folkway for lunch, or when he stops by my office.

He's a success because he did his homework and then had the guts to give it a try. The failures are those who spend their time watching TV, gossiping on

the air, and wasting their lives. What a pity! Thousands of hams have used the hobby to get the technical smarts to develop new products and go into business with them. It only takes one good idea to make it.

That's one of my problems. I spend a good deal of my time staying abreast of the technology in communications and computers, with the result that I have a bright idea a day for a business...and a terrific idea a week. I lack only the people to help me make these ideas bear fruit.

A chap from Texas visited a

few days ago. A ham, of course, a flier, and a computer nut. He was fascinated to see the high energy here, the people all working hard and obviously having one hell of a time. Sure, it's like a rabbit warren, but it's fun and very productive. People come here, often with little background, and they learn fast. Yes, he signed on and is moving here.

He found just what he wanted in a house in a couple of hours and is busy moving up here to help me start a new magazine. He's going to need a bunch of people to work with him...what

are you doing? We're going crazy for people to help set type, paste up pages, shoot the pages into negatives, handle the circulation, and so on.

One of the new magazines I want to start will have as a goal the generation of several thousand new hams a year-maybe as many as 50,000 or even double that. No, I don't know of any way to let you work from homeyou really have to be here.

Well, if you are all set with what you are doing, at least say hello on the air. I get a couple hours a week on 20m and my ego will be looking for you.

SATELLITES

PROJECT OSCAR

Project OSCAR, Inc., has prepared a new set of orbital predictions for the period covering the calendar year 1984. The predictions provide the UTC times and longitude for all south-tonorth equatorial crossings of the 4 Russian satellites carrying Mode A transponders (RS5, RS6, RS7, and RS8). In addition, the UTC time and sub-satellite latitude and longitude are given for the apogee of each orbit of AMSAT OSCAR 10 (AO-10). This document, when used with the appropriate plotter, allows the user to determine the access times to all the presently available amateur-radio satellites carrying communication transponders.

The large expense incurred in producing and disseminating a calendar of this magnitude necessitates a request for a minimum donation of \$10 for mailings to the US, Canada, and Mexico (\$12 for all overseas mailings). To receive your copy of this set of orbital predictions, send a completed mailing label along with a check or money order payable to Project OSCAR, Inc., POB 1136, Los Altos CA 94022. The donation covers the cost of first-class mailing within the US, Canada, and Mexico, and airmail printed matter to overseas destinations.

Amateur Satellite Reference Orbits

	OSCAR B	RS-5	RS-6	RS-7	RS-8	
Date.	UTC EQX	UTC EQX	UTC EQX	UTC EQX	UTC EQX 14	Dote
****		*******	*******	*******	*******	****
Feb 1	0045 103	0114 292	0119 300	0058 291	0155 300	
2	0049 104	0109 293	0104 298	0048 290	0153 301	2
3	0054 105	0103 293	0049 296	0039 289	0150 301	3
4	0058 106	0058 293	0033 294	0029 288	0147 302	4
5	0102 107	0053 293	0018 291	0.019 287	0144 303	5
6	0107 108	0047 293	0002 289	0010 286	0141 304	6
7	0111 110	0042 293	0146 316	0000 285	0138 305	7
8	0115 111	0037 294	0130 314	0150 314	0136 305	8
9	0120 112	0031 294	0115 312	0140 313	0133 306	.9
10	0124 113	0026 294	0059 309	0130 313	0130 307	10
11	0128 114	0021 294	0044 307	0121 312	0127 308	11
12	0133 115	0015 294	0029 305	0111 311	0124 309	12
13	0137 116	0010 295	0013 302	0101 310	0121 310	13
14	0141 117	0005 295	0156 330	0052 309	0119 310	14
1.5	0002 93	0159 325	0141 327	0042 308	0116 311	15
16	0007 94	0154 325	0126 325	0032 307	0113 312	16
17	0011 95	0148 325	0110 323	0023 306	0110 313	17
18	0015 96	0143 326	0055 321	0013 305	0107 314	18
19	0020 97	0137 326	0039 318	0003 305	0104 314	1.9
20	0024 98	0132 326	0024 316	0153 334	0102 315	20
21	0028 99	0127 326	0009 314	0143 333	0059 316	21
22	0033 100	0121 326	0152 341	0134 332	0056 317	22
23	0037 102	0116 327	0137 339	0124 331	0053 318	23
24	0041 103	0111 327	0121 336	0114 330	0050 319	24
25	0046 104	0105 327	0106 334	0105 329	0047 319	25
26	0050 105	0100 327	0050 332	0055 328	0045 320	26
27	0054 106	0055 327	0035 329	0045 327	0042 321	27
28	0059 107	0049 327	0019 327	0036 326	0039 322	28
29	0103 108	0044 328	0004 325	0026 326	0036 323	29
Mar 1	0107 109	0039 328	0147 352	0016 325	0033 323	1
	0112 111	0033 328	0132 350	0007 324	0030 324	2
- 3	0116 112	0028 328	0117 347	0156 353	0028 325	3 4
3 4	0120 113	0023 328	0101 345	0147 352	0025 326	4
5	0125 114	0017 329	0046 343	0137 351	0022 327	5
6	0129 115	0012 329	0030 341	0127 350	0019 328	6
6 7	0133 116	0007 329	0015 338	0118 349	0016 328	7
8	0138 117	0001 329	0000 336	0108 348	0013 329	5 6 7 8 9
9	0142 118	0156 359	0143 3	0058 348	0011 330	
10	0003 94	0150 360	0127 1	0049 347	0008 331	10
11	0008 95	0145 360	0112 359	0039 346	0005 332	11
12	0012 96	0140 360	0057 356	0029 345	0002 332	12
13:-	0016 97	0134 0	0041 354	0020 344	0159 3	13
14	0021 98	0129 0	0026 352	0010 343	0156 4	14
15	0025 99	0123 1	0010 349	0000 342	0153 5	15
16	0029 100	0118 I	0154 17	0150 11	0150 6	16

CONTACT-80 MARK-II TRS-80 MOD. III-IV

"RTTY your TRS-80 with CONTACT-80!"

SOFTWARE FEATURES, DISK & CASSETTE VERSIONS: BAUDOT-ASCII-MORSE . Morse AUTOSYNC, FIST-FIXER . TRI-SPLIT screen . "Unlimited" STORED MSG sizes . AUTO BUFFER ALLOCATION . HARD-COPY . AUTO-ID'ing . TIME/DATED X-missions. NAME-LINE . AUTO DIDDLE • Scrn COUNTERS-CLOCK-OSCILLOSCOPE • CLOCK KEYING • K/B ROLLOVER-REPEATING KEYS . Fast flexible I/O . Full EDITING using "word processing techniques".

ADDITIONAL DISK VERSION FEATURES:

SAVE-LOAD-KILL-DIR . AUTO-MONITOR . File REVIEW 2-way MSG SELCALL, a "PERSONAL MSO" . AUTO-LOAD.

With CONTACT-80 INTERFACE (1-KHz CW Tone DECODER, mates with any

With MFJ-1224 RTTY/CW COMPUTER INTERFACE, P/S and Royal MFJ ADAPTER. A COMPLETE FULL FEATURE SYSTEM!. \$239 Guaranteed • Include Amateur CALLSIGN • POST PAID

ROYAL, 407 Conkle Rd., Hampton, GA 30228 150

Tel. (404) 946-9314

Let us know 8 weeks in advance so that you won't miss a single issue of 73.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly. Write to:

Subscription Department P.O. Box 931 Farmingdale NY 11737

Extend my subscription	one	additional	year	for	only	\$17.97
Payment enclosed		☐ Bill me				

Canada & Mexico \$20.97/1 year only US Funds drawn on US bank. Foreign Surface \$25.00/1 year only US Funds drawn on US bank. Foreign Airmail, please inquire.

If you have no lubel hundy, print OLD address here.

Name		
Address	E Sevil Swai	
City	State	Zip_
p	int NEW address	here:
Name		
Address		
City	State	Zip

N8BKR Introduces the... E Field Displacement Antenna



- . Out performs any 60 ft. 1/4 wave vertical on transmit and receive
- Covers 3.5 to 4.0 MHZ with better than 1.5 to 1 SWR
- No tuner needed
- Money back guarantee

Send S.A.S.E. for more information to:

MOLER ANTENNA CORP. 2623 Morris Lane . Girard, OH 44420 (216) 530-2059

IT'S INCREDIBLE!

Master code or upgrade in a matter of days. Code Quick is a unique breakthrough which simplifies learning Morse Code. Instead of a confusing maze of dits and dahs, each letter will magically begin to call out its own name! Stop torturing yourself! Your amazing kit containing 5 powerpacked cassettes, visual breakthrough cards and original manual is only \$39.95! Send check or money order today to WHEELER APPLIED RESEARCH LAB, P.O. Box 3261, City of Industry, CA 91744. Ask for Code Quick #103, California residents add 6% sales tax.

One User Comments:

"First new idea in code study and the darn thing works! So much fun you don't realize how much you're learning.

M.S. Greneda, Miss.

Hundreds of satisfied customers! You can't lose! Follow each simple step. You must succeed or return the kit for a total immediate refund!



MICROWAVE PREAMPLIFIERS

Ampire 1690N:

- 1.6 to 1.8 GHz
- 25 dB gain
- · 3.0 dB noise figure
- · N connectors standard
- Use on GOES & METEOSAT systems

Ampire 2001:


- 2.0 to 2.6 GHz
- 20 dB gain
- 3.5 dB noise figure
- BNC connectors standard
- DC & RF cables included
- Use with microwave TV converters


Ampire 1690N \$139°5 Ampire 2001129°5 Ampire 2001N14905 Shipping: USA ... \$200 Foreign ... \$1000

Data Service Company

3110 Evelyn Street -346 Roseville, MN 55113


612-636-9469

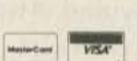

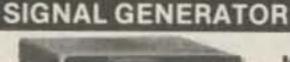

SYNTHESIZED

MADEIN USA

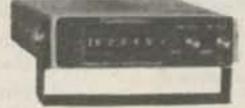

MODEL SG100D \$349.95 plus shipping

. Covers 100 to 185 MHz in 1 kHz steps with thumbwheel dial . Accuracy 1 part per 10 million at all frequencies . Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate . Spurs and noise at least 60 dB below carrier . RF output adjustable from 5-500 mV at 50 ohms . Operates on 12 Vdc @ 1/2 Amp . Available for immediate delivery . \$349.95 plus shipping · Add-on Accessories available to extend freq. range, add infinite resolution, voice and sub-audible tones, AM, precision 120 dB calibrated attenuator . Call for details . Dealers wanted worldwide

> **VANGUARD LABS** 196-23 Jamaica Ave., Hollis, NY 11423 Phone: (212) 468-2720



scription of the problem, enclosing your most recent label (or print correct address) and send to:

Subscription Dept. P.O. Box 931

Farmingdale, NY

Thank you and enjoy your subscription.



New CMOS DTMF Chip Kit

Teltone's TRK-957 Kit makes it easier and less expensive to breadboard a low-power, central office quality DTMF detection system. All you need is a power source from 5 to 12 VDC. The sensitivity, wide dynamic range, noise immunity, and low-power consumption make the TRK-957 ideal for telephone switching, computer, and remote control applications. The TRK-957 DTMF Kit is only \$24.75. To order call:

(800) 227-3800, ext. 1130.

TELTONE'

-224


YOU EARNED YOUR CALL!

NOW DISPLAY IT PROUDLY IN A TOP QUALITY LACOSTE-TYPE KNIT SHIRT.

ONLY \$14.00 With your call in rich embroidery.

\$1.50 extra for first name. Choose from 10 great colors: rust, cream, brown, green, yellow, navy, It. blue, aqua, white, and

black.

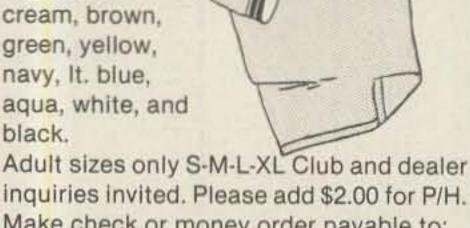

Y KNAYAS

inquiries invited. Please add \$2.00 for P/H. Make check or money order payable to:

Coin Int'l Inc. 7861 SW 53rd Ave. Miami, FL 33143 (305) 662-6900



Allow 4 weeks for delivery Fl. residents add sales tax

THE BEST PLACE To Look For New & Used Equipment Buy-Sell-Trade Our 4th Year



NUTS & VOLTS MAGAZINE

PO BOX IIII-G . PLACENTIA, CA 92670 (714) 632-7721

JOIN THOUSANDS OF READERS NATIONWIDE, EVERY MONTH

U.S.A. SUBSCRIPTIONS \$ 7.00 - I YR. 3RD CLASS MAIL \$12.50 - I YR. IST CLASS MAIL

\$25.00 - LIFETIME - 3RD CLASS With Free Classified Ad



MULTI-CHANNEL

Complete Antenna Systems from \$6995

Full 800 Mhz Range Tune 1.9-2.7 Ghz Includes all **ITFS Channels**

DEALERS WANTED

COD's and Credit Card Orders call TOLL FREE

1-800-247-1151



Glendale, AZ 85301



RADIO DIRECTION FINDER

The SuperDF

Inexpensive kit and assembled units for use with Hand-Held, Mobile, or Base Station. 100 to 260 MHz or 200 to 550 MHz with one antenna. Non-ambiguous. No overloading. Use with unmodified HT, scanner, or transceiver. No attenuator or "S" meter needed. Can DF signals below the noise. Averages out local reflections while mobile-in-motion. Used by FCC, US Army, State of California, Coast Guard Aux. Prices start at \$125. For details send SASE to: BMG Engineering, 9935 East Garibaldi, Temple City, Cal, 91780.



COMPUTER APPLICATIONS

Are you interested in:


- ·Hardware construction?
- Software development?
- Interfacing computers to external devices?
- Low cost robotics?
- Dedicated microprocessor devices?

The Computer Journal

is a magazine for those who interface, build, and apply micros. Subscription price \$24/year in the U.S. (12 issues).

PO Box 1697H Kalispell, MT 59903

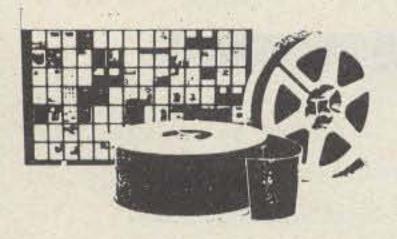this publication is available in microform



University Microfilms International

300 North Zeeb Road Dept. P.R. Ann Arbor, MI 48106 U.S.A.

18 Bedford Row Dept. P.R. London, WC1R 4EJ England

WORK THE WORLD ON AN HT!

The RB-1 easily interties 2 transceivers. A 220 or 450 rig can intertie to control a fixed station. By utilizing the squelch of the new TS 430 or IC-740, the HF bands can even be worked from the HT. UHF to VHF — VHF to HF.

- Simple to connect all connectors supplied.
- · Can be used as simple RPTR control.

REMOTE BASE INTERTIE

+ \$3.00 shipping

RB-1



HEIL, LTD Marissa, IL 62257 618-295-3000

ALL BAND TRAP

FULL 1/4th WAVE - All Bands! Automatic Selection with proven Hi-Q Traps. 3 Models-ALL self supporting Ground or roof mount. HEAVY Double wall seamless Aluminum lower section - HI STRENGTH FIBER-GLASS TUBING OVER -ALL. NO WOBBLY, LU-MPY TRAPS - NO UNSIGHTLY CLAMPS needed Same size all the way up 1 1/4" Traps hidden inside. You can use it in a 1 ft. sq. Backyardi Neighbors will never know this is a Hi-Power ALL Direction DX Antenna. FOR APARTMENTS, ROW HOUSES, MOBILE HOMES - CONDOS etc. where minimum space and next appearance is MANDATORY! Instant "Drive In ground mount (Included). Use with or without radials (Included) (All angle roof mount - Extra) COMPLETELY PRETUNED - NO ADJUSTMENTS NEEDED EVER! NO TUNER NEEDED Over All Bands (except 80 meter - 400 KC) SWR 1-1 to 2-1 at Band edges, Stnd, SO239 connecter - 50 ohm for any length RG58U -RG8U feedline. Matches ALL MAKES TRANSCIEV-ERS. 2000 Watt PEP, input power. Shipped - PRE-PAID IN USA. Assembles in 10 min. using only screwdriver. WEATHERPROOF!


No.-AVT80-10 — 5 Band — 25'6" — \$179.95 No.- AVT40-10 — 4 Band — 18'9" — \$129.95 No.- AVT20-10 — 3 Band — 11'4" — \$99.95.

SEND FULL PRICE FOR PP DEL IN USA (Canada is \$10.00 extra for postage, cierical, Customs etc.) or order using VISA, MASTER CARD or AMERICAN EXPRESS. Give Number and Ex. date. Ph 1-308-236-5333 9AM-6PM weekdays. We ship in 2-3 days. Prices will increase, so order NOW AND SAVE. All Antennas Guaranteed for 1 year - 10 day money back trial, if returned in new condi-Free Inf.

68847

WESTERN ELECTRONICS Dept. A7-2 Kearney

Engineering Incorporated

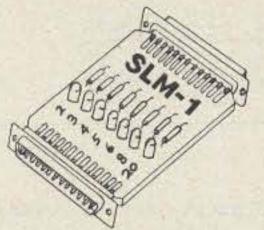

RS-232 SERIAL LINE MONITOR

- Quick and easy operation
- Red/Green LEDs show polarity of 7 most used signals
- Comprehensive users manual
- Line powered, NO battery \$29.95 plus \$2 for P/H

Esoteric Engineering Incorporated Post Office Box 33602 San Diego, CA 92103

(619) 569-7060

DX TOUR

VK-ZL-3D2-KH6-VK-ZL-3D2-KH6-VK-ZL-3D2-KH6-VK-ZL

- Australia
- New Zealand
- · Fiji

KH6

3D2

KH6

ZL 3D2

KH6

VK

ZL 3D2

KH6 VK

ZL 3D2

ZL

3D2

VK

ZL 3D2

KH6

VK

ZL

3D2

KH6

Hawaii

THREE WEEKS OCTOBER 11 thru 31, 1984

Departs from Los Angeles

For Hams. Spouses and Friends Meet and greet your ham friends in their own countries. Welcoming events by local hams and clubs

Tour directors: Jean (WA6AKP) and Bill (W6UFS) Thompson

Write for brochure:

DX TOURS

81 Fashion Island Newport Beach, CA 92663

Call Jean (714) 640-0821

SPACE LIMITED — RESERVE EARLY

VK-ZL-3D2-KH6-VK-ZL-3D2-KH6-VK-ZL-3D2-KH6-VK-ZL

Telephones & Accessories

AT LOWEST PRICES

- Memory Phones
- Answerers
- Dialers
- Hardware
- Speaker Phones
- Call Diverters
- Feature Phones

Send \$2.00 for Complete Catalog



UNIQUE COMMUNICATIONS, INC. 181 E. Longview, P.O. Box 5234 Mansfield, Ohio 44901 (419) 526-6996

KH6

KH6

ZL

3D2

KH6

VK

ZL

3D2

KH6

VK

ZL

3D2

KH6

VK

ZL


3D2

KH6



EIMAC 4CX10,000D/8171 with SK300 and SK1306 SK300 and SK1306 Only.

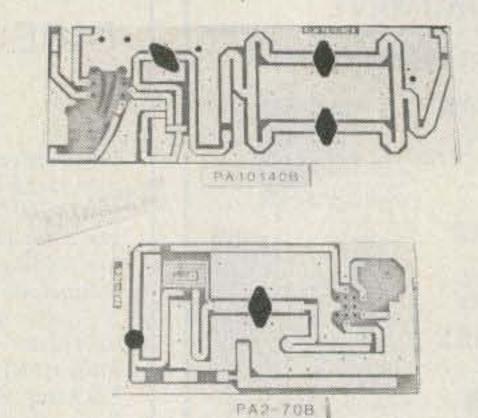(These are all new not used.) Limited Supply.



KLM ELECTRONICS, INC. VHF AMPLIFIER PC BOARDS AND RF TRANSISTOR KITS. Model PA2-70B RF power input 2watts at 144 to 148MHz output 70watts 13.5vdc at 10amps. \$49.99 with data PC Board Only \$14,99

MODEL PA10140B RF power input 10watts at 144 to 148MHz output 140watts 13.5vdc at 18amps. \$89.99 with data PC Board Only \$19.99

GENEVA CALCULATOR WATCH

This attractive watch has the following modes: Normal Time Setting, Calendar Setting, Daily Alarm Time Setting, Weekly Alarm Time Setting, Chronograph, Calculator.

Featured in Black Plastic

\$18.99

\$1200.00

\$ 350,00

Featured in Stainless Steel

\$29.99

SILICON DIO	DES			
MR751	100vdc	6Amps	10/\$5.00	100/\$38.00
MR510	1000vdc	3Amps	10/\$3.75	100/\$24.00
HEP170	1000vdc	2Amps	20/\$2.00	100/\$15.00
1N3209	100vdc	15Amps	\$2.00	10/ \$15.00
BYX21/200	200vdc	25Amps	\$2.00	10/ \$15.00
1N2138A	600vdc	60Amps	\$5.00	10/ \$40.00
DS85-04C	400vdc	80Amps	\$10.00	10/ \$80.00
1N3269	600vdc	160Amps	\$15.00	10/\$120.00
275Z41	300vdc	250Amps	\$20.00	10/\$175.00
7-5754	300vdc	400Amps	\$30.00	10/\$250.00
RCD-15	15KVDC	20ma.	\$3.00	10/ \$20.00
SMFR20K	20KVDC	20ma.	\$4.00	10/ \$30.00
1N4148	signal		30/\$1.00	100/ \$3.00

FAIRCHILD 4116 16K DYNAMIC RAMS 200ns. Part # 16K75

25 For \$25.00 or 100 For \$90.00 or 1000 For \$750.00

FEED THRU SOLDER RF CAPACTORS

470pf +-20%

5/\$1.00 or 100/\$15.00 or 1000/\$100.00

1000pf/.001uf +-10%

4/\$1.00 or 100/\$20.00 or 1000/\$150.00

E PROMS

27L32/25L32

\$2.00 each 2708 1024x1 2716 2048x8 \$4.00 each

\$10.00 each

HEWLETT PACKARD MICROWAVE DIODES

1N5711	(5082-2800)	Schottky	Barrier	Diode	s	\$1.00	or	10	for	\$ 8.50
IN5712	(5082-2810)	11	11:	11		\$1.50	or	10	for	\$10.00
1N6263	(HSCH-1001)	Maria Maria	31	2116		\$.75	or	10	for	\$ 5.00
5082-2835		H.	11	11		\$1.50	or	10	for	\$10.00
5082-2805	Quad Matched	"	"	"	per set	\$5.00	or	10	for	\$40.00

For information call: (602) 242-3037

Toll Free Number 800-528-0180 (For orders only)

MH z electronics

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

"MIXERS"

WATKINS JOHNSON WJ-M6 Double Balanced Mixer

LO and RF 0.2 to 300MHz

Conversion Loss (SSB) 6.5dB Max. 1 to 50MHz

Noise Figure (SSB)

Conversion Compression

IF DC to 300MHz

8.5dB Max. .2 to 300MHz WITH DATA SHEET

same as above

8.5dB Max. 50 to 300MHz

.3dB Typ.

\$21.00

NEC (NIPPON ELECTRIC CO. LTD. NE57835/2SC2150 Microwave Transistor

NF Min F=2GHz dB 2.4 Typ.

F=3GHz dB 3.4 Typ. F=4GHz dB 4.3 Typ.

MAG F=2GHz dB 12 Typ.

\$5.30

ea

ea

ea

F=3GHz dB 9 Typ.

F=4GHz dB 6.5 Typ.

Ft Gain Bandwidth Product at Vce=8v, Ic=10ma. GHz 4 Min. 6 Typ. 25v Vceo 11v Vebo 3v Ic 50ma. Pt. Vcbo

UNELCO RF Power and Linear Amplifier Capacitors

These are the famous capacitors used by all the RF Power and Linear Amplifier manufacturers, and described in the RF Data Book.

5pf	10pf	18pf	30pf	43pf	100pf	200pf 1 to	10pcs.	\$1.00
5pf 5.lpf	12pf	22pf	32pf	51pf	110pf	220pf 11 to	50pcs.	\$.90
6.8pf	13pf	25pf	33pf	60pf	120pf	470pf 51 up	pcs.	\$.80
	14pf	27pf	34pf	80pf	130pf	500pf		
7pf 8.2pf	15pf	27.5pf	40pf	82pf	140pf	1000pf		

NIPPON ELECTRIC COMPANY TUNNEL DIODES

Peak Pt. Current ma. Ip Valley Pt. Current ma. IV Peak Pt. Voltage mv. Vp Projected Peak Pt. Voltage mv. Vpp Vf=Ip Series Res. Ohms rs

Terminal Cap. pf. Valley Pt. Voltage mv.

MODEL 1S2199 9min. 10Typ. 11max. 1.2Typ. 1.5max.

95Typ. 120max. 480min. 550Typ. 630max.

2.5Typ. 4max. 1.7Typ. 2max. 370Typ.

\$7.50

1S2200 9min. 10Typ. 11max. 1.2Typ. 1.5max.

75Typ. 90max.

440min. 520Typ. 600max.

2Typ. 3max. 5Typ. 8max. 350Typ.

FAIRCHILD / DUMONT Oscilloscope Probes Model 4290B

Ct

VV

Input Impedance 10 meg., Input Capacity 6.5 to 12pf., Division Ratio (Volts/Div Factor) 10:1, Cable Length 4Ft., Frequency Range Over 100MHz.

These Probes will work on all Tektronix, Hewlett Packard, and other Oscilloscopes.

PRICE \$45.00

MOTOROLA RF DATA BOOK

Listsall Motorola RF Transistors / RF Power Amplifiers, Varactor Diodes and much much more.

PRICE \$7.50

For information call: (602) 242-3037

MH z electronics **Toll Free Number** 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

RF TRANSISTORS, MICROWAVE DIODES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2N1561	\$ 25.00	2901678 \$	2.00	M1134	\$ 16.90	MSC1821-3	\$125.00
2N1562	25.00	2SC1729	20.00	M9579	7.95	MSC1821-10	225.00
2N1692	25.00	2SC1760	1.50	M9588	7.50	MSC2001 MSC2223-10	40.00 200.00
2N2957 2N2857JANTX	1.55	2SC1909 2SC1946	4.00	M9622 M9623	7.95 9.95	MSC3000	50.00
2NZ857JANTXV	4.10 4.10	2SC1946A	40.00	M9624	11.95	MSC3001	50.00
2N2876	13.50	28C1970	2.50	M9625	17.95	MSC73001	50.00
2N2947	18.35	2SC1974	4.00	M9630	18.00	MSC82001	40.00
2N2948	13.00	2SC2166	5.50	M9740	29.90	MSC82014	40.00
2N2949	15.50	2SC2237 2SC2695	32.00 47.00	M9741 M9755	29.90 19.50	MSC82020 MSC82030	40.00
2N3375 2N3553	17.10	A50-12	25.00	M9848	37.00	MSC83001	50.00
2N3632	15.50	A209	10.00	M9850	16.90	MSC83005	100.00
2N3733	11.00	A283	5.00	M9851	20.00	MT4150	14.40
2N3818	5.00	A283B	6.00	M9887	5.25	MT5126	POR
2N3866	1.30	AF102	2.50	MEL80091 MM1550	25.00 10.00	MT5596/2N5596 MT5768/2N5768	99.00 95.00
2N3866JAN 2N3924	2.20	AFY12 BF272A	2.50	MM1552	50.00	MT8762	POR
2N3927	17.25	BFR21	2.50	MM1553	50.00	NEO2136	2.50
2N3950	25.00	BFR90	1.00	MM1614	10.00	NE13783	POR
2N4012	11.00	BFR91	1.65	MM1943/2N4072	1.80	NE21889	POR
2N4041	14.00	BFR99	2.50	MM2608	5.00	NE57835	5.70
204072	1.80	BFT12 BFW16A	2.50	MM3375A MM4429	17.10	NE73436 TRW	2.50
2N4080 2N4127	4.53 21.00	BFW17	2.50	MM8000	1.15	PRT8637	POR
2N4427	1.30	BFW92	1.50	MM8006	2.30	PT3190	POR
2N4428	1.85	BFX44	2.50	MM8011	25,00	PT3194	POR
2N4430	11.80	BFX48	2.50	MPF102	.45	PT3195	POR
2N4957	3.45	HFX65	2.50	MPSU31	1.01	PT3537	7.80
2N4959	2.30	BFX84	2.50	MRA2023-1.5	42.50	PT4166E	POR
2N5090	13.80	BFX85 BFX86	2.50	MRF208 MRF212	16.10 16.10	PT4176D PT4186B	POR POR
2N5108 2N5109	3.45 1.70	BFX89	1.00	MRF223	13.25	PT4209	POR
2N5160	3.45	BFY11	2.50	MRF224	15.50	PT4209C/5645	POR
2N5177	21.62	BFY18	2.50	MRF231	10.92	PT4556	24.60
2N5179	1.04	BFY19	2.50	MRF232	12.07	PT4570	7.50
2N5216	56.00	BFY39	2.50	MRF233	12.65	PT4577	POR
2N5583	3.45	BFY90	1.00	MRF237	3.15	PT4590	POR
2N5589 2N5590	9.77 10.92	BLX67 BLX68C3	15.24 15.24	MRF238 MRF239	13.80 17.25	PT4612 PT4628	POR
2N5591	13.80	BLX93C3	22.21	MRF245	35.65	PT4640	POR
2N5637	15.50	BLY87A	8.94	MRF247	35.65	PT4642	POR
2N5641	12.42	BLY88C3	13.08	MRF304	43.45	PT5632	4.70
2N5642	14.03	BLY94C	21.30	MRF309	33.81	PT5749	POR
2N5643	15.50	HLY351	10.00	MRF314	28.52	PT6629	POR POR
2N5645 2N5646	13.80 20.70	BLY568C/CF C458-617	30.00	MRF315 MRF316	28.86 POR	PT6709 PT6720	POR
2N5651	11.05	C4005	20.00	MRF317	63.94	PT8510	POR
2N5691	18.00	CD1899	20.00	MRF420	20.00	PT8524	POR
2N5764	27.00	CD2188	18.00	MRF421	36.80	PT8609	POR
2N5836	3.45	CD2545	25.00	MRF422A	41.40	PT8633	POR
2N5842/MM1607	8.45	CTC3005	100.00	MRF427	17.25	PT8639	POR
2N5849	20.00	Dexcel GaAs FET DXL3501A-P100F	49.30	MRF428 MRF433	46.00 12.07	PT8659 PT8679	POR POR
2N5913 2N5916	3.25 36,00	Fujitsu GaAs FET	40+50	MRF449/A	12.65	PT8708	POR
2N5922	10.00	FSX52WF	58.00	MRF450/A	14.37	PT8709	POR
2N5923	25.00	GM0290A	2.50	MRF453/A	18.40	PT8727	29.00
2N5941	23.00	HEP76	4,95	MRF454/A	20.12	PT8731	POR
2N5942	40.00	HEPS3002	11.40	MRF455/A	16.00	PT8742	19.10
2N5944	10.35	HEPS3003 HEPS3005	30.00	MRF458 MRF463	20.70 25.00	PT8787 PT9783	POR 16.50
2N5945 2N5946	11.50 14.40	HEPS3006	19.90	MRF472	1.00	PT9784	32.70
2N6080	10.35	HEPS3007	25.00	MRF475	3,10	PT9790	56.00
2N6081	12.07	HEPS3010	11.34	MRF476	2.00	PT31962	POR
2N6082	12.65	Hewlett Packard	***	MRF477	14.95	PT31963	POR
2N6083	13.25	HFET2204 35821E	112.00 38.00	MRF492 MRF502	23.00	PT31083	POR POR
2N6084 2N6094	15.00 11.00	35826B	32.00	MRF503	6.00	PTX6680 RCA	14.00
2N6095	12.00	35826E	32.00	MRF504	7.00	40081	5.00
2N6096	16.10	35831E-H31	30.00	MRF509	5.00	40279	10.00
2N6097	20.70	35831E	30.00	MRF511	10.69	40280	4.62
2N6105	21.00	35832E	50.00	MRF515	2.00	40281	10.00
2N6136	21.85	35833E 35853E	50.00	MRF517 MRF559	2.00	40282 40290	20.00
2N6166 2N6201	40.24 50.00	35854E	75.00	MRFG05	20.00	40292	2.80 13.05
2N6304	1.50	35866E	44.00	MRF618	25.00	40294	2.50
2N6459	18.00	HXTR3101	7,00	MRF628	8.65	40341	21.00
2N6567	10.06	HXTR3102	8.75	MRF629	3.45	40608	2.48
2N6680	80.00	HXTR5104	30.00	MRF644	27.60	40894	1.00
2SC703	3.00	HXTR6104	68.00	MRF646	29.90	40977	10.00
2SC756A	7.50	HXTR6105 HXTR6106	31.00	MRF816 MRF823	15.00 20.00	62800A RE3754	60.00 25.00
2SC781 2SC1018	2.80 1.00	J310	.70	MRF901 (3) Lead		RE3789	25.00
2SC1042	12.00	TRW	2317.20	MRF901 (4) Lead		RF110	25.00
2SC1070	2.50	J02000	10.00	MRF904	2.30	S50-12	25.00
25C1239	2.50	J02001	25.00	MRF911	3.00	S3006	5.00
2SC1251	12.00	JO1015	25.00	MRP961	2.30	S3031	5.00
2901306	2.90	Motorola Comm. M1131	8.50	MRF8004 MS261F	2.10 POR	SCA3522 SCA3523	5.00
2SC1307 2SC1424	5.50 2.80	M1132	11.95	MSC1720-12	225.00	PRICE ON REQU	
			- 10				ERS SEE

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: (602) 242-3037



GaAs, TUNNEL DIODES, ETC.

			* R F TRANSIS	TORS *			
TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE 1	PRICE
THOMSON CSF	0 = 00	601110	P T 00	CD1070 E	610 00	SD1453-1 \$	48.00
SD345	\$ 5.00	SD1119	\$ 5.00	SD1278-5	\$18.00	SD1454-1	48.00
SD445	5.00	SD1124	50,00	SD1281-2	8,00	SD1477	48.00
SD1004	15,00	SD1127	3.50	SD1283	10,00	SD1478	21.00
SD1009	15.00	SD1133	14.00	SD1289-1	15.00	SD1480 (60.00
SD1009-2	15.00	SD1133-1	14.00	SD1290-4	15,00	SD1484	1.50
SD1012	9.90	SD1134-1	3.00	SD1290-7	15.00	SD1484-5	1.50
SD1012-3	9,90	SD1135	8,00	SD1300	3.00	SD1484-6	1.50
SD1012-5	9.90	SD1136	15.00	SD1301-7	3.00	SD1484-7	1.50
SD1013-3	13,50	SD1136-2	15.00	SD1305	3,00	SD1488	39.00
SD1013-7	13.50	SD1143-1	12.00	SD1307	3.00	SD1488-1	28.00
SD1014	11.00	SD1143-3	17,00	SD1308	3,00	SD1488-7	27.00
SD1014-6	11,00	SD1144-1	3.00	SD1311	1.00		28,00
SD1016	15.00	SD1146	15,00	SD1317	10.00	SD1499-1	39,00
SD1016-5	15.00	SD1147	15,00	SD1335	3.00		18.00
SD1018-4	15.00	SD1188	10.00	SD1345-6	5,00		33.00
SD1018-6	15.00	SD1189	24.00	SD1365-1	2.50		24.00
SD1018-7	15,00	SD1200	1.50	SD1365-5	2.50		34.00
SD1018-15	15.00	SD1201-2	10.00	SD1375	7,50		38.00
SD1020-5	10,00	SD1202	10.00	SD1375-6	7,50		41.00
SD1028	15.00	SD1212-11	4.00	SD1379	15.00	Marie Control of the	34.00
SD1030-2	12.00	SD1212-12	4.00	SD1380-1	1.00	- 1700 (1700)	79.00
SD1043	12.00	SD1212-16	4.00	SD1380-3	1,00	The state of the s	25.00
SD1043-1	10.00	SD1214-7	5,00	SD1380-7	1.00	SK3048 RCA	5.00
SD1045	3.75	SD1214-11	5.00	SD1405	40,00		15.00
SD1049-1	2.00	SD1216	12.00	SD1409	18,00	SMS7714 Mot.	2,50
SD1053	4.00	SD1219-4	15.00	SD1410	22.00		36.00
SD1065	4.75	SD1219-5	15.00	SD1410-3	21.00	SRF1018 Mot.	5.00
SD1068	15.00	SD1219-8	15,00	SD1413-1	18.00		22.00
SD1074-2	18,00	SD1220	8.00	SD1416	50.00		38.00
SD1074-4	28.00	SD1220-9	8.00	SD1422-2	24.00		16.00
SD1074-5	28,00	SD1222-8	16,00	SD1428	33,00		40.00
SD1076	20.00	SD1222-11	7.50	SD1429-2	15,00	A DOMEST CONTROL MAN AND A DOMEST OF THE PARTY OF THE PAR	25.00
SD1077-4	4.00	SD1224-10	18.00	SD1429-3	15.00		20.00
SD1077-6	4.00	SD1225	18,00	SD1429-5	15,00		15.00
SD1078-6	24.00	SD1228-8	POR	SD1430	12,00	TIS189/MRF966	3.55
SD1080-8	6.00	SD1229-7	13.00	SD1430-2	18.00	TP312	2.50
SD1080-9	3.00	SD1229-16	13.00	SD1434-5	30.00	TP1014 TRW	5.00
SD1084	8.00	SD1232	4.00	SD1434-9	30.00	CONTRACTOR OF CO	15.00
SD1087	15.00	SD1240-8	15,00	SD1438	26.00	01-80703T04/	10.00
SD1089-5	15.00	SD1244-1	14,00	SD1441	91.00	458-949 Mot.Comm. (65 00
SD1095	15.00	SD1262	12,00	SD1442	15.00		50.00
SD1100	5.00	SD1263	15.00	SD1444	6.00		00.00
SD1109	18,00	SD1263-1	15.00	SD1444-8	6.00		80.00
SD1115-2	8.00	SD1272	13,00	SD1450-1	28.00		75.00
SD1115-3	8.00	SD1272-2	15.00	SD1451	18,00		50.00
SD1115-7	2.50	SD1272-4	15.00	SD1451-2	18.00	The Property of the Control of the C	18.00
SD1116	5,00	SD1278	20,00	SD1452	20.00	MRF479	8.05
SD1118	22.00	SD1278-1	18.00	SD1452-2	20.00	MIM I I O	6,00


We Can Cross Reference Most RF Transistors, Diodes, Hybrid Modules And Any Other Type Of Semiconductor.

1N21	\$ 3.40	1N21B	\$ 3.40	1N21BR	\$ 3.40	1N21C	\$ 3.4
1N21D	4.00	1N21DR	4.00	1N21FR	6.00	1N21RF	5.0
IN21WE	5.80	1N21WG	5.80	1N22	5.00	1N23A	10.0
1N23B	3,40	1N23C	3.40	1N23CR	3.40	1N23D	4.9
1N23DR	4.00	1N23WE	5.00	1N25	7.50	1N25AR	18.0
1N28WE	10.00	1N29	10.00	1N32	20.00	1N53A	55.5
1N76	26.00	1N76R	28.00	1N78	26.00	1N78A	20.0
1N78B	26.00	1N78D	28.00	1N78DR	28.00	1N78R	28.0
1N149	6.00	1N15OMR	18.00	1N415	4.00	1N415C	4.0
1N415G	15.00	1N416D	5.00	1N416E	6.00	1N446	10.0
1N831	10.00	1N833	10.00	1N950	4.00	1N1084	2.0
1N2930	15.00	1N2932	15.00	1N3540	15.00	1N3712	11.0
1N3713	18.00	1N3714	11.00	1N3715	16.00	1N3716	10.0
1N3717	14.00	1N3718	10.00	1N3721	14.00	1N3733	10.0
1N3747	21.00	1N4386	20,00	1N4396	15.00	1N4785	11.0
1N4812B	9,00	1N5139A/B	4.25	1N5140A/B	4.25	1N5141A/B	4.2
1N5142A/B	4.25	1N5143A/B	4.25	1N5144A/B	4.25	1N5145A/B	4.2
1N5146A/B	4.25	1N5147A/B	4.25	1N5148A/B	4,25	1N5167	5.5
1N5453	3.75	1N5465	7.65	1N5711	1.00	1N5711 JAN	2.0
IN5713	5.00	1N5767	2.00	1N6263	1.00	1S2199	15.0
1S2200	15.00	182208/9	1.00	8B1087/48R869558	THOSE CHIEF	8D3020	65.0
A2X116M Aertech	50.00	BB105B	1.00	BB105G	1.00	BD4/4JFBD4 G.E.	
BL161 Bomac	5.00	CMD514AB C.M.	POR	D4060 Alpha	POR	D4159 Alpha	POR
04233B Alpha	POR	D4900 Alpha	POR	D4959 Alpha	POR	D4987M Alpha	POR
06047C Alpha	POR	D5147D Alpa	POR	D5503 Alpha	POR	D5506 Alpha	POR
CCB6158-98 Alpha	POR	DMD6022 Alpha	POR	DMD6460A Alpha	POR	DP20054 Crown	POR
C1691-89 GHZ	31.35	GC1602-89 GHZ	31.35	GC1607-40 GHZ	31.35	GC2531-88 GHZ	37.4
3C2542-46 GHZ	37.40	GC3208-40 GHZ	37.40	GC17044 GHZ	50.00	HP33644A-HO1	125.0
HP5082-0112	14.20	HP5082-0241	75.60	HP5082-0253	105.00	HP5082-0320	58.0
₽5082-0112 ₽5082-0375	POR	HP5082-0386	POR	HP5082-0401	POR	HP5082-0438	POR
	POR	HP5082-1332	POR	HP5082-2254	POR	HP5082-2302	10.7
IP5082-1028		HP5082-2696	POR	HP5082-2711	23.15	HP5082-2727	POR
IP5082-2303	5.20	HP5082-2805	4.45	HP5082-2835	1.00	HP5082-2884	POR
IP5082-2800	1.00	HP5082-3040	36.00	HP5082-3080	2.00	HP5082-3188	1.0
IP5082-3039	6.70	HP5082-6459	POR	HP5082-6462	POR	HP5082-6888	POR
HP5082-3379	1.50					MA450A	POR
HP5082-8016	POR	HP5082-8323	POR	K3A Kemtron MA41487	7.00 POR	MA41765	POR
MA475	POR	MA40008		MA43589	POR	MA43622	POR
MA41766	POR	MA43004	48.00		POR	MA47051	25.5
1A43636	POR	MA45104	27.00	MA47044	POR	MA47838*	POR
MA47100 MA47852	3.05 POR	MA47202 MA49106	30,80 37,95	MA47771 MA49558	POR	MA86731	125.0

For information call: (602) 242-3037

Toll Free Number 800-528-0180 (For orders only)

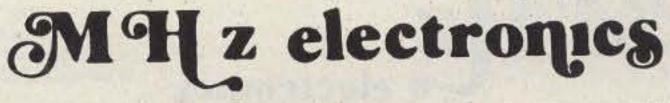"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."



COAXIAL RELAY SWITCHES SPDT

Electronic Specialty Co./Raven Electronics Part # 25N28 Part # SU-01 26Vdc Type N Connector, DC to 1 GHz.

FSN 5985-556-9683

NC

\$49.00

NO



Ampheno1 Part # 316-10102-8 115Vac Type BNC DC to 3 GHz.

FXR Part # 300-11182 120Vac Type BNC DC to 4 GHz. FSN 5985-543-1225

Part # 300-11173 120Vac Type BNC Same FSN 5985-543-1850

\$39.99


FXR


COM

SWITCH, COARIAL FEN SPES 556 9683


MER RAVEN ELECTRONICS 20176 PN SU-101

SPEC NAS 7231 A US SER NO

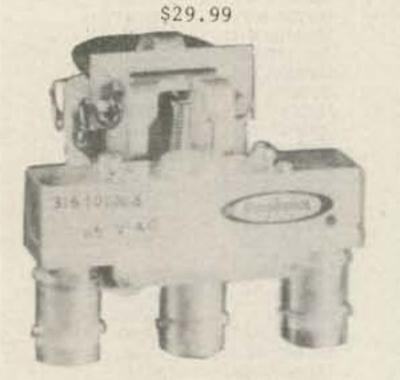

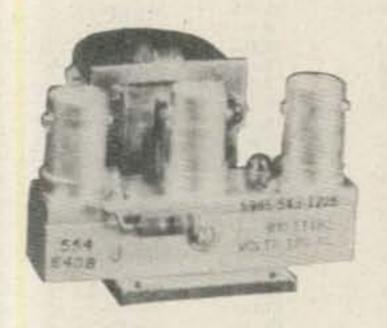


\$39.99

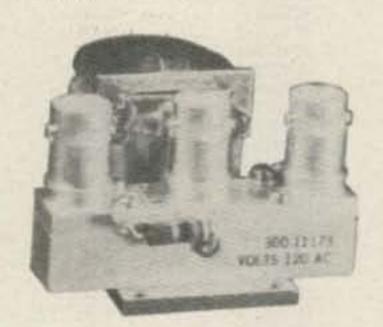


BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

\$7.99 or 2 For \$13.99 or 10 For \$50.00

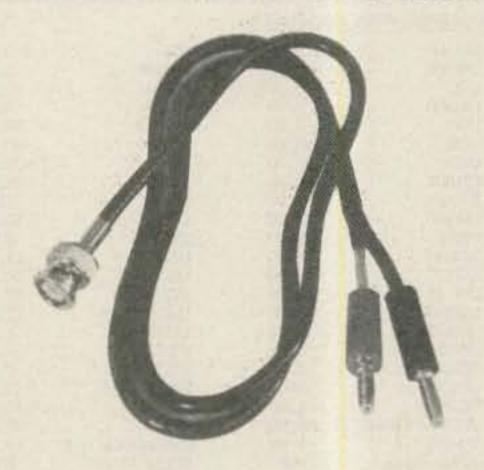\$8.99 or 2 For \$15.99 or 10 For \$60.00



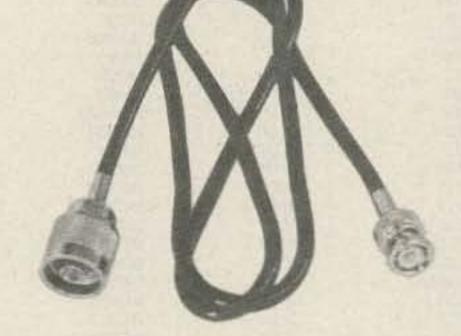

SOLID STATE RELAYS

P&B Model ECTIDB72 PRICE EACH \$5.00

PRICE EACH \$7.50

5vdc turn on

120vac contact at 7amps or 20amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

Digisig, Inc. Model ECS-215 5vdc turn on

240vac contact 14amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

Grigsby/Barton Model GB7400 5vdc turn on

240vac contact at 15amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

PRICE EACH \$7.50

NOTE: *** Items may be substituted with other brands or equivalent model numbers. ***



"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

Toll Free Number 800-528-0180 (For orders only)

For information call: (602) 242-3037

RECALL PHONE MEMORY TELEPHONE WITH 24 NUMBER AUTO DIALER

The Recall Phone Telephone employs the latest state of art communications technology. It is a combination telephone and automatic dialer that uses premium-quality, solid-state circuitry to assure high-reliability performance in personal or business applications. \$49.99




ARON ALPHA RAPID BONDING GLUE

Super Glue #CE-486 high strength rapid bonding adhesive.Alpha Cyanoacrylate.Set-Time 20 to 40 sec.,0.7fl.oz.(20gm.) \$2.00




TOUCH TONE PAD

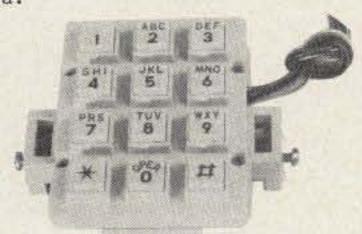This pad contains all the electronics to produce standard touch-tone tones. New with data.



MITSUMI UHF/VHF VARACTOR TUNER MODEL UVE1A

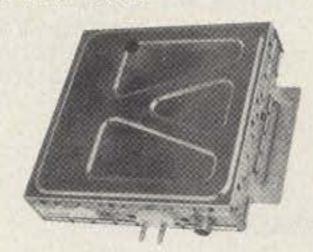Perfect for those unscrambler projects. New with data.



\$9.99 or 10/\$89.99

\$19.99 or 10/\$149.99

INTEGRATED	CIRCUIT.	1 to 10	11up
MC1372P	Color TV Video Modulator Circuit.	\$ 4.42	\$2.95
MC1358P	IF Amp., Limiter, FM Detector, Audio Driver, Electronic Attenuator.	5.00	4.00
MC1350P	IF Amplifier	1.50	1.25
MC1330A1P	Low Level Video Detector	1.50	1.15
MC1310P	FM Stereo Demodulator	4.29	3.30
MC1496P	Balanced Modulator/Demodulator	1.50	1.25
LM565N	Phase Locked Loop	2.50	2.00
LM380N14	2Watt Audio Power Amplifier	1.56	1.25
LM1889N	TV Video Modulator	5.00	4.00
NE564N	Phase Locked Loop	10.00	8.00
NE561N	Phase Locked Loop	10.00	8.00

FERRANTI ELECTRONICS AM RADIO RECEIVER MODEL ZN414 INTEGRATED CIRCUIT. Features:

1.2 to 1.6 volt operating range., Less than 0.5ma current consumption. 150KHz to 3MHz Frequency range., Easy to assemble, no alignment necessary. Effective and variable AGC action., Will drive an earphone direct. Excellent audio quality., Typical power gain of 72dB., TO-18 package. With data. \$2.99 or 10 For \$24.99

NI CAD RECHARGEABLE BATTERIES

AA Battery Pack of 6 These are Factory New. \$5.00


SUB C Pack of 10 2.5Amp/Hr. \$10.00

Gates Rechargeable Battery Packs

12vdc at 2.5Amp/Hr. \$11.99 12vdc at 5Amp/Hr. \$15.99 MOTOROLA MRF559 RF TRANSISTOR

hfe 30min 90typ 200max.
ft 3000mhz
gain 8db min 9.5typ at 870mhz
13db typ at 512mhz
output power .5watts at 12.5vdc
at 870mhz.

\$2.05 or 10/\$15.00

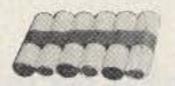

MHz electronics

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item." For information call: (602) 242-3037

Toll Free Number
800-528-0180
(For orders only)
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"SOCKETS AND CHIMNEYS"

EIMAC TUBE SOCKETS AND CHIMNEYS

SK110	Socket	SPOR
SK300A	Socket For 4CX5000A,R,J, 4CX10,000D, 4CX15,000A,J	\$520.00
SK400	Socket For 4-125A, 250A, 400A, 400C, 4PR125A, 400A, 4-500A, 5-500A	260.00
SK406	Chimney For 4-250A, 400A, 400C, 4PR400A	74.00
SK416	Chimney For 3-400Z	36.00
SK500	Socket For 4-1000A/4PR1000A/B	390.00
SK600	Socket For 4CX250B, BC, FG, R, 4CX350A, F, FJ	51.00
SK602	Socket For 4CX250B, BC, FG, R, 4CX350A, F, FJ	73.00
SK606	Chimney For 4CX250B, BC, FG, R, 4CX350A, F, FJ	11.00
SK607	Socket For 4CX600J, JA	60.00
SK610	Socket For 4CX600J, JA	60.00
SK620	Socket For 4CX600J,JA	66.00
SK626	Chimney For 4CX600J, JA	10.00
SK630	Socket For 4CX600J, JA	66.00
SK636B	Chimney For 4CX600J, JA	34.00
SK640	Socket For 4CX600J,JA	36.00
SK646	Chimney For 4CX600J,JA	71.00
SK700	Socket For 4CX300A,Y,4CX125C,F	225.00
SK711A	Socket For 4CX300A, Y, 4CX125C, F	225.00
SK740	Socket For 4CX300A,Y,4CX125C,F	86.00
SK770	Socket For 4CX300A,Y,4CX125C,F	86.00
SK800A	Socket For 4CX1000A,4CX1500B	225.00
SK806	Chimney For 4CX1000A,4CX1500B	40.00
SK810	Socket For 4CX1000A,4CX1500B	225.00
SK900	Socket For 4X500A	300.00
SK906	Chimney For 4X500A	57.00
SK1420	Socket For 5CX3000A	650.00
SK1490	Socket For 4CV8000A	585.00
JOHNSON TUB	E SOCKETS AND CHIMNEYS	

124-111/SK606	Chimney For 4CX250B, BC, FG, R, 4CX350A, F, FJ	\$ 10.00
122-0275-001	Socket For 3-500Z, 4-125A, 250A, 400A, 4-500A, 5-500A	(pair)15.00
124-0113-00	Capacitor Ring	15.00
124-116/SK630A	Socket For 4CX250B, BC, FG, R, /4CX350A, F, FJ	55.00
124-115-2/SK620A	Socket For 4CX250B, BC, FG, R, /4CX350A, F, FJ	55.00
	813 Tube Socket	20.00

				TUBE CAPS (Plate)	
CHIP CAPACITORS				HR1, 4	\$11.00
.8pf	10pf	100pf*	430pf	HR2,3,6 & 7	13.00
lpf	12pf	110pf	470pf	HR5, 8	14.00
1.1pf	15pf	120pf	510pf	HR9	17.00
1.4pf	18µf	130pf	560pf	HR10	20,00
1.5pf	20pf	150pf	620pf		
Rnf	22nf	160nf	680nf		

16UPT TQUOD 2.2pf 24pf 180pf 820pf 2.7pf 27pf 200pf 1000pf/.001uf* 3.3pf 220pf* 1800pf/.0018uf 33pf 2700pf/.0027uf 3.6pf 39pf 240pf 3.9pf 47pf 270pf 10,000pf/.01uf 4.7pf 51pf 300pf 12,000pf/.012uf 5.6pf 56pf 15,000pf/.015uf 330pf 68pf 6.8pf 18,000pf/.018uf 360pf 8.2pf 82pf 390pf

PRICES: 1 to 10 - .99¢ 101 to 1000 .60¢ * IS A SPECIAL PRICE: 10 for \$7.50 11 to 50 - .90¢ 1001 & UP .35¢ 1000 for \$65.00 51 to 100 - .80¢

WATKINS JOHNSON WJ-V907: Voltage Controlled Microwave Oscillator \$110.00

Frequency range 3.6 to 4.2GHz, Power ouput, Min. 10dBm typical, 8dBm Guaranteed. Spurious output suppression Harmonic (nfo), min. 20dB typical, In-Band Non-Harmonic, min. 60dB typical, Residual FM, pk to pk, Max. 5KHz, pushing factor, Max. 8KHz/V, Pulling figure (1.5:1 VSWR), Max. 60MHz, Tuning voltage range +1 to +15volts, Tuning current, Max. -0.1mA, modulation sensitivity range, Max. 120 to 30MHz/V, Input capacitance, Max. 100pf, Oscillator Bias +15 +-0.05 volts @ 55mA, Max.

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."



For information call: (602) 242-3037

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2039/7289	\$ 34.00	1182/4600A	\$500.00	ML7815AL	\$ 60.00
2E26	7.95	4600A	500.00	7843	107.00
2K28	200.00	4624	310.00	7854	130.00
3-500Z	102.00	4657	84.00	ML7855KAL	125.00
	G16000 10000			7984	14.95
3-1000Z/8164	400.00	4662	100.00		
3B28/866A	9.50	4665	500.00	8072	84.00
3CX400U7/8961	255.00	4687	P.O.R.	8106	5.00
3CX1000A7/8283	526.00	5675	42.00	8117A	225.00
3CX3000F1/8239	567.00	5721	250.00	8121	110.00
3CW30000H7	1700.00	5768	125.00	8122	110.00
3X2500A3	473.00	5819	119.00	8134	470.00
3X3000F1	567.00	5836	232.50	8156	12.00
4-65A/8165	69.00	5837	232.50	8233	60.00
4-125A/4D21	79.00	5861	140.00	8236	35.00
4-250A/5D22	98.00	5867A	185.00	8295/PL172	500.00
4-400A/8438	98.00	5868/AX9902	270.00	8458	35.00
4-400B/7527	110.00	5876/A	42.00	8462	130.00
4-400C/6775	110.00	5881/6L6	8.00	8505A	95.00
4-1000A/8166	444.00	5893	60.00	8533W	136.00
4CX250B/7203	54.00	5894/A	54.00	8560/A	75.00
4CX250FG/8621	75.00	5894B/8737	54.00	8560AS	100.00
4CX250K/8245	125.00	5946	395.00	8608	38.00
4CX250R/7580W	90.00	6083/AZ9909	95.00	8624	100.00
4CX300A/8167	170.00	6146/6146A	8.50	8637	70.00
4CX350A/8321	110.00	61468/8298	10.50	8643	83.00
4CX350F/8322	115.00	6146W/7212	17.95	8647	168.00
4CX350FJ/8904	140.00	6156	110.00	8683	95.00
4CX600J/8809	835.00	6159	13.85	8877	465.00
4CX1000A/8168	242.50*	6159B	23.50	8908	13.00
4CX1000A/8168	485.00	6161	325.00	8950	13.00
4CX1500B/8660	555.00	6280	42.50	8930	137.00
4CX5000A/8170	1100.00	6291	180.00	6L6 Metal	25.00
4CX10000D/8171	1255.00	6293	24.00	6L6GC	5.03
4CX15000A/8281	1500.00	6326	P.O.R.	6CA7/EL34	5.38
4CW800F	710.00	6360/A	5.75	6CL6	3.50
4D32	240.00	6399	540.00	6DJ8	2.50
4E27A/5-125B	240.00	6550A	10.00	6DQ5	6.58
4PR60A	200.00	6883B/8032A/8552	10.00	6GF5	5.85
4PR60B	345.00	6897	160.00	6GJ5A	6.20
4PR65A/8187	175.00	6907	79.00	6GK6	6.00
4PR1000A/8189	590.00	6922/6DJ8	5.00	6HB5	6.00
4X150A/7034	60.00		22.00	6HF5	8.73
		6939			
4X150D/7609	95.00	7094	250.00	6JG6A	6.28
4X250B	45.00	7117	38.50	6JM6	6.00
4X250F	45.00	7203	P.O.R.	6JN6	6.00
4X500A	412.00	7211	100.00	6JS6C	7.25
5CX1500A	660.00	7213	300.00*	6KN6	5.05
KT88	27.50	7214	300.00*	6KD6	8.25
4168	45.00	7271	135.00	6LF6	7.00
416C	62.50		34.00	6LQ6 G.E.	7.00
572B/T160L	49.95	7325	P.O.R.	6LQ6/6MJ6 Sylvania	
592/3-200A3	211.00	7360	13.50	6ME 6	8.90
807	8.50	7377	85.00	12AT7	3.50
811A	15.00	7408	2.50	12AX7	3.00
812A	29.00	7609	95.00	12BY7	5.00
813	50.00	7735	36.00	12JB6A	6.50


"ALL PARTS MAY BE NEW, USED, OR SURPLUS. PARTS MAY BE SUBSTITUTED WITH COMPARABLE PARTS IF WE ARE OUT OF STOCK OF AN ITEM.

NOTICE: ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE.

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

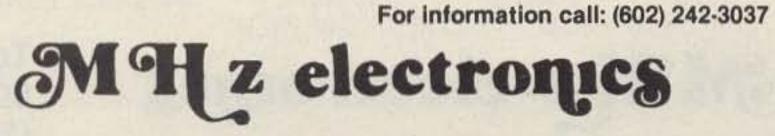NOTE * = USED TUBE NOTE P.O.R. = PRICE ON REQUEST



PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"FILTERS"

COLLING Machaniani	Filtor	#EOC 0704 010	MODEL	FLEETZOF
COLLINS Mechanical	FILTER	#7/0-4//4-1111	CHILL	F477/3/F
COLLING HOCHAILT COL	1 4 4 5 0 1	11-200 21 21 010	IIVELL	1 1 2 2 6 2 6 1

455KHZ at 3.2KHz wide. May be other models but equivalent. May be used or new, \$15,99 ATLAS Crystal Filters 5.595-2.7/8/LSB, 5.595-2.7/LSB 8 pole 2.7KHz wide Upper sideband. Impedence 800ohms 15pf In/800ohms 0pf out. 19,99 5.595-2.7/8/U, 5.595-2.7/USB 8 pole 2.7Khz wide Upper sideband. Impedence 800ohms 15pf In/800ohms 0pf out. 19.99 5.595-.500/4, 5.595-.500/4/CW 4 pole 500 cycles wide CW. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99 9. OUSB/CW 6 pole 2.7KHz wide at 6dB. Impedance 680ohms 7pf In/300ohms 8pf out. CW-1599Hz 19.99 KOKUSAI ELECTRIC CO, Mechanical Filter #MF-455-ZL/ZU-21H 455KHz at Center Frequency of 453.5KC. Carrier Frequency of 455KHz 2.36KC Bandwidth. Upper sideband. (ZU) 19,99 Lower sideband. (ZL) 19.99 CRYSTAL FILTERS 7.8MHz \$10.00 FX-07800C NIKKO 10.00 FEC-103-2 10.6935MHz TEW SCH-113A 10.00 11.2735MHz SDK 19.99 CF 3179.3KHz TAMA TF-31H250 TYCO/CD 001019880 10.7MHz 2pole 15KHz bandwidth 5.00 4884863B01 11.7MHz 2pole 15KHz bandwidth 5.00 MOTOROLA 12MHz 2pole 15KHz bandwidth 5.00 PTI 5350C 5426C 21.4MHz 2pole 15KHz bandwidth 5.00 PTI 10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB PTI 1479 20.00 6.00 45MHz 2pole 15KHz bandwidth COMTECH A10300 ERXF-15700 20.6MHz 36KHz wide 10.00 FRC 2131 10.00 FILTECH CF 7.825MHz CERAMIC FILTERS 12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 11.8-13.4KHz AXEL 10.00 4F449 CLEVITE TO-01A 5.00 455KHz+2KHz bandwidth 4-7% at 3dB 455KHz+1KHz bandwidth 6dB min 12KHz, 60dB max 36KHz 10.00 TCF4-12D36A 2.50 BFB455B MURATA 455KHz 3.50 455KHz BFB455L 6.65 455KHz +-5.5KHz at 3dB , +-8KHz at 6dB , +-16KHz at 50dB CFM455E 455KHz +-7KHz at 3dB , +-10KHz at 6dB , +-20KHz at 50dB 6.65 CFM455D 455KHz +-5.5KHz at 3dB , +-8KHz at 6dB , +-16KHz at 60dB 8.00 CFR455E 455KHz +-2KHz bandwidth +-15KHz at 6dB, +-30KHz at 40dB 2.90 CFU455B CFU455C 455KHz +-2KHz bandwidth +-12.5KHz at 6dB , +-24KHz at 40dB 2.90 455KHz +-1KHz bandwidth +-4.5KHz at 6dB , +-10KHz at 40dB CFU455G 2.90 CFU455H 455KHz +-1KHz bandwidth +-3KHz at 6dB , +-9KHz at 40dB 2.90 2.90 CFU455I 455KHz +-1KHz bandwidth +-2KHz at 6dB , +-6KHz at 40dB 2.90 CFW455D 455KHz +10KHz at 6dB , +20KHz at 40dB 455KHz +-3KHz at 6dB , +-9KHz at 40dB 2.90 CFW455H 2.50 SFB455D 455KHz 455KHz +-2KHz , 3dB bandwidth 4.5KHz +-1KHz 5.00 SFD455D SFE10.7MA 2,50 10.7MHz 280KHz +-50KHz at 3dB , 650KHz at 20dB SFE10.7MS 10,7MHz 230KHz +-50KHz at 3dB , 570KHz at 20dB 2.50 10.7MHz 10.00 SFG10.7MA 2.90 NIPPON LF-B4/CFU455I 455KHz +-1KHz 2.90 LF-B6/CFU455H 455KHz +-1KHz 2.90 LF-B8 455KHz 10.00 IF-C18 455KHz 5.00 CF455A/BFU455K 455KHz +-2KHz TOKIN 7.00 MATSUSHIRA EFC-L455K 455KHz SPECTRA PHYSICS INC. Model 088 HeNe LASER TUBES POWER OUTPUT 1.6MW. BEAM DIA. .75MM BEAM DIR. 2.7MR 8KV STARTING VOLTAGE DC 1000VDC +-100VDC 68K OHM LWATT BALLAST \$59.99 At 3.7MA ROTRON MUFFIN FANS Model MARK4/MU2A1 14WATTS 50/60CPS IMPEDENCE PROTECTED-F 88CFM at 50CPS 115 VAC \$ 7.99 THESE ARE NEW 105CFM at 60CPS

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Toll Free Number 800-528-0180 (For orders only) "All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: (602) 242-3037

HEWLETT PACKARD SIGNAL GENERATORS


606A	50KHz to 65MHz in 6 bands +-1%, Output level adjustable 0.1u to 3V into 50 ohms. Built-in crystal calibrator, 400 -1000Hz	iV	616B	Same as above but later model.	\$ 600.00
cocn	modulation.	\$ 650.00	618B	3.8 to 7.6GHz range, with calibrated output and selection a pulse-FM or square wave modulation.	f \$ 600.00
606B	Same as above but has frequency control feature to allow operation with HP 8708A Synchronizer.	\$1100.00	618C	Same as above but later model.	\$2200.00
608C	10MHz to 480MHz,0-1uV-1V Into 50 ohms,AM,CW,or pulse mod- ulation, calibrated attenuator.	\$ 500.00	620A	7 to 11GHz range, with calibrated output and selection of pulse-FM or square wave modulation.	\$ 750.00
608D/ TS510	10MHz to 420MHz, 0.1uV-0.5V into 50 ohms,+-0.5% accuracy, built-in crystal calibrator, AM-CW or pulse output.	\$ 375.00	620B	Same as above but later model,	\$2200,00
608E	Improved version of popular 608C.Up to IV output.Improved stability.low residual FM.		626A	10 to 15GHz,10mw output power with calibrated output and pulse-square wave or FM modulation.	\$4200.00
608F 612A	10MHz to 455MHz in 5 bands +-1% frequency accuracy with built-in crystal calibrator.Can be used with HP 8708A Synchronizer, Output continuously adjustable from .luV to .5V into 50 ohms. 450-1230MHz .o.luV-0.5V into 50 ohms.calibrated output.	\$1450.00 \$1100.00 \$ 750.00	8708A	Synchronizer used with 606B,608F. The synchronizer is a phase-lock frequency stabilizer which provides crystal-oscillator frequency stability to 430MHz in the 608F signal generator. Phase locking eliminates microphonics and drift resulting in excellent frequency stability. The 8708A include a vernier which can tune the reference oscillator over a resulting frequency settability to 2 parts in to the seventh. Provides a very stable signal that satisfie	des ange
614A	900-2100MHz with many features including calibrated output and all modulation characteristics.	\$ 500.00		many critical applications. (With HP 606B or 608F) (Without)	\$ 350,00 \$ 450.00
616A/ TS403	Direct reading and direct control from 1.8 to 4.2GHz. The H.P.616A features +-1.5dB calibrated output accuracy from -3127dBm to -dBm. The output is directly calibrated in micro volts and dBm with continuous monitoring. Simple operation frequency diad accuracy is +-1% and stability exceeds 0.005		EMC-10	ELECTROMETRICS EMC-10 RFI/EMI RECEIVER Low frequency analyzer covering 20Hz to 50KHz frequency range.Extendable to 500 KHz in wideband mode.	\$2500.00
	within +-1.5dB over entire output band, 50 ohm impedance un has internal pulse modulation with rep rate variable from 4 Hz to 4KHz, variable pulsewidth(1 to 10usec) and variable pul	it 0 se	NF-105F	Empire Devices Field Intensity Meter. Has NF-105/TA,NF-105/TX,NF-105/T1,NF-105/T2,NF-105/T3. Covers 14KHz to 1000MHz.	\$2100,00
	delay(3 to 300usec).External modulating inputs increas ver- satility.	\$ 375.00		ALL EQUIPMENT CARRY A 30 DAY GUARANTEE.	
				EQUIPMENT IS NOT CALIBRATED.	

UNEX LABORATORIES THS-2 FLEXICOM HEADSET.

these headsets come with data to hook up to a ICDM radios and many other equipment.

Perfect for Airplanes , Helicopters , Mobile Radios , or Just the Telephone.

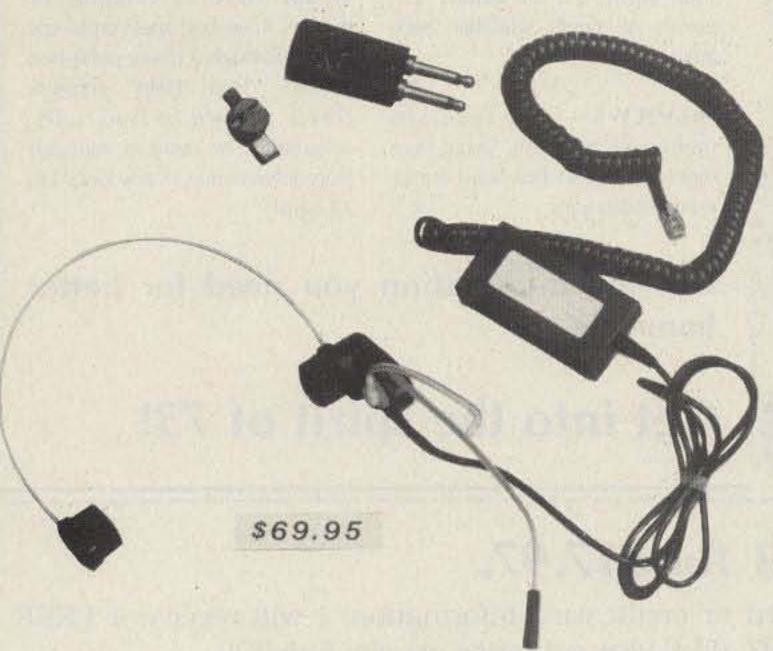These Are Factory New In Sealed Boxes, Limited Supply Only



ORDERING INSTRUCTIONS

DEFECTIVE MATERIAL: All claims for defective material must be made within sixty (60) days after receipt of parcel. All claims must include the defective material (for testing purposes), our invoice number, and the date of purchase. All returns must be packed properly or it will void all warranties:

DELIVERY: Orders are normally shipped within 48 hours after receipt of customer's order. If a part has to be backgrdered the customer is notified. Our normal shipping method is via First Class Mail or UPS depending on size and weight of the package. On test equipment it is by Air only, FOB shipping point

FOREIGN ORDERS: All foreign orders must be prepaid with cashier's check or money order made out in U.S. Funds. We are sorry but C.O.D. is not available to foreign countries and Letters of Credit are not an acceptable form of payment either. Further information is available on request.

HOURS: Monday thru Saturday: 8:30 a.m. to 5:00 p.m.

INSURANCE: Please include 25¢ for each additional \$100.00 over \$100.00. United Parcel only.

ORDER FORMS: New order forms are included with each order for your convenience. Additional forms are available on request.

POSTAGE: Minimum shipping and handling in the US, Canada, and Mexico is \$2.50 all other countries is \$5.00. On foreign orders include 20% shipping and handling.

PREPAID ORDERS: Order must be accompanied by a check.

PRICES: Prices are subject to change without notice.

RESTOCK CHARGE: If parts are returned to MHZ Electronics due to customer error, customer will be held responsible for all extra fees, will be charged a 15% restocking fee, with the remainder in credit only. All returns

SALES TAX: Arizona must add 5% sales tax, unless a signed Arizona resale tax card is currently on file with MHZ Electronics. All orders placed by persons outside of Arizona, but delivered to persons in Arizona are sub-

SHORTAGE OR DAMAGE: All claims for shortages or damages must be made within 5 days after receipt of parcel. Claims must include our invoice number and the date of purchase. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

> OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY NO INFORMATION WILL BE GIVEN. 1-800-528-0180

TERMS: DOMESTIC: Prepaid, C.O.D. or Credit Card

FOREIGN. Prepaid only, U.S. Funds-money order or cashier's check only.

C.O.D.: Acceptable by telephone or mail. Payment from customer will be by cash, money order or cashier's check. We are sorry but we cannot accept personal checks for C.O.D.'s.

CONFIRMING ORDERS: We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy necessitates a confirming order, please mark "CONFIRMING" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, customers will be held responsible for any charges incurred, plus a 15% restock charge on returned parts.

CREDIT CARDS: WE ACCEPT MASTERCARD VISA AND AMERICAN EXPRESS.

DATA SHEETS: When we have data sheets in stock on devices we do supply them with the order.




DOWNER

For information call: (602) 242-3037

2111 W. CAMELBACK ROAD PHOENIX, ARIZONA 85015

Toll Free Number 800-528-0180 (For orders only)

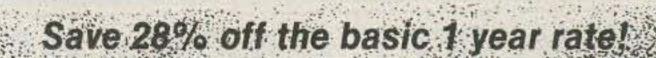"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."



A year of 73

\$17.97

Amateur Radio's Technical Journal

A Wayne Green Publication

73 keeps you up to date on what's happening in the ham world. For only \$17.97, 73 gives you a year of:

•CONSTRUCTION PROJECTS— 73 publishes more easy-to-build projects than any other ham magazine.

 73 INTERNATIONAL—Get reports from 73 correspondents around the globe. Amateur radio is a worldwide pastime and 73 is your source for international news.

•NEWPRODUCTS - 73 gives you reports on state-of-the-art amateur-radio equipment. In 1982 alone, 73 introduced 137 pieces of newly-available ham gear!

•REVIEWS - From keyers to transceivers to tuners, you'll save money with 73's first-hand equipment evaluations.

•DXING-Get the best DX column there is. 73 columnist Chod Harris VP2ML provides tips for newcomers, profiles of the hams behind those famous callsigns, and constant DXpedition updates. Don't miss it!

 NEVER SAY DIE—W2NSD's controversial editorials have livened up the ham scene for more than 22 years. Is he right or wrong? "Never Say Die" let's you be the judge.

•HAM HELP-Thousands of readers have had their problems solved through a query published in 73's "Ham Help" column. Need a hard-to-find part, schematic, or owner's manual? Ham information of any kind? Let 73 help!

Get the information you need for better hamming.

Get into the spirit of 73!



Stay in Step

Technical Journal

with Amateur Radio's

I would like a year of 73 for \$17.97.

I understand that with payment enclosed or credit card information, I will receive a FREE issue making a total of 13 issues for \$17.97. (Full year sub-price usually \$25.00!)

☐ Check/M.O. ☐ MC

Address

□ VISA

□ AE

☐ Bill Me \$17.97 for 12 issues.

Card#

Signature____

Exp. Date

Name____

State Zip____

City_ Canada & Mexico, \$20.97 1 year only, US funds drawn on US bank. Foreign Surface, \$25.00, 1 year only, US funds

342F6

drawn on US bank. Foreign Airmail please inquire. Please allow 6-8 weeks for delivery.

73: Amateur Radio's Technical Journal • Box 931 • Farmingdale, NY 11737

here is the next generation Repeater

MARK 4CR

In 1978 we created the first microprocessor based repeater and here is its successor the incomparable MARK 4CR. Of course it has autodial and tail messages, after all, we invented those features. Sure it has autopatch, reverse patch and built-in ID. But hold on -- it also has Message Master™ real speech and receiver voting. Its all new receiver puts 7 large helical resonators up front for extremely high dynamic range. Yes, MARK 4CR is the next generation!

- Unlimited vocabulary speech messages in your own voice
- Hundreds of tone access functions, many with time-of-day setting
- All vital parameters can be set remotely by tone access
- Two phone lines and dozens of input/output control lines
- 4 channel receiver voting plus full linking capability
- Bus structured design for easy hardware/software expansion
- "Overload proof" receiver with 7 large helical resonators
- Our famous MCS squelch, often called the best in the business, is now even better with automatic fast/slow switching





MICRO CONTROL SPECIALTIES

23 Elm Park, Groveland, MA 01834 (617) 372-3442

Dealer Selling 73 will make money for you. Consider the facts: Fact 1: Selling 73 increases store traffic-our dealers tell us that 73 is one of the hottestselling amateur radio magazines on the

Fact 2: There is a direct correlation between store traffic and sales-increase the number of people coming through your door and you'll increase sales.

newsstands.

Fact 3: Fact 1 + Fact 2 = INCREASED \$ALE\$, which means more money for you. And that's a fact.

For information on selling 73, call 800-343-0728 (in New Hampshire call 1-924-9471) and speak with Ginnie Boudrieau, our bulk sales manager. Or write to her at 73, 80 Pine St., Peterborough, NH 03458.

Amateur Radio's Technical Journal

80 Pine Street Peterborough, NH 03458 800-343-0728









ORBIT is the Official Journal for the Radio Amateur Satellite Corporation.

For a SAMPLE COPY please send \$2 to:

(AMSAT), P.O. Box 27, Washington, DC 20047.

73 INTERNATIONAL

from page 76

trix printer), I am obviously not a fan of mechanical systems. I was surprised, therefore, to note that 60% of traditionalists plan to keep their mechanized RTTY.

As more and more computers come into amateur-radio shacks, so the desire for higher transmission speeds takes on a more urgent note. After years of watching news agency reports print at 50 baud, the thought of 300 (or even 1200) baud is indeed enticing. A problem with the existing de facto amateur data-transmission standard (CUTS or Kansas City) is that it uses harmonically-related tones which will give very poor results in conditions of low signal-tonoise ratio.

BARTG has therefore proposed (for consideration at the IARU region conference in 1984) that existing RTTY standards be used as follows-300 baud, 170-Hz shift; 1200 baud, 850-Hz shift. FSK transmissions will have space on the lower radio frequency and AFSK will use 1275 Hz for space and 1445 Hz (170-Hz shift) or 2125 Hz (850-Hz shift) for mark for 300 baud or 1200 baud, respectively.

Further BARTG proposals for the conference include:

- The adoption of a 10-bit ASCII code using even or indeterminate parity (plus 1 start, 7 data, and 1 stop). (Author's note: Many commercial systems use 11 bits for asynchronous ASCII by adding a second stop bit.)
- The adoption of CCIR 476-1 at 100 baud (the basis of AMTOR) as the international amateur standard for an error-correcting code.
- Standard amateur RTTY speeds of 50, 75, and 100 baud (note the dropping of 45.45).
- · Dropping the requirement that amateur RTTY stations regularly transmit voice or CW identifications when using CCITT alphabet no. 2 (Baudot).
- The adoption for amateur mailbox operations of the protocols used for Viewdata (Videotex).

I find the last proposal rather odd and think it is almost a backward step! Viewdata does not use error-correction and is asymmetric (uses different speeds in the forward/return directions).



INDIA

R. Subha Post Box No. 725 3 Thiru-VI-Ka Road Madras 600 006 India

A VISITING HAM'S **GUIDE TO INDIA**

The time is gone when the mention of India conjures up visions of snake charmers, elephants, and maharajas. All these are there, but there is much more of interest to the visitor-ham radio, for instance.

Those who believe that India is a backward country are in for a jolt. Your first exposure to India will, of course, be the airport (or the seaport, if you are the M/M type). Modern communications and facilities at these entry points convince the visitor that

he has come to yet another advanced country. What, then, is this talk about underdeveloped and developing countries? That is for consumption by the World Bank and other UN organizations. Yes, we do have a lower per capita income, but everything is cheap in the same proportion. In brief, you can live in India on as many rupees as you would need dollars living in the US for a comparable standard of living, India builds its own nuclear power plants and launches its own satellites on its own rockets-a littie late, but with the technological advantages of the state of the art. Soon, Indian hams will be using a satellite built by them and launched for them by the Indian Space Research Organization. It will probably be called the Indamsat-such an appropriate acronym!

So, you probably landed in Bombay on a Pan Am flight. Bombay has over 200 callsigns and most of them are members of a club called the Radio and Electronics Society of India. One of the dream shacks is that of Capt. D. Dasan VU2AID, a senior manager in Air India who also holds the Australian call VK6IK. Most shacks in Bombay have Icom or Kenwood equipment, thanks to VU2RX (who represents these two companies). Quite a few of them sport quads or tribander beams. Activity is mostly on the 14-, 21-, and 28-MHz bands, 2 meters is just getting started, but it will take a repeater to really turn this band on. It won't be long before one is installed. The calling frequencies are 145.0 and 145.5 MHz all over the country.

There are more than 50 callsigns in Delhi,

but quite a few are inactive. The active calls were Bernd VU2LQA from the German embassy, Aoki VU2JPN from the Japanese embassy (both of whom have left India), and brothers Rakesh VU2RAK and Rahul VU2YK, who are still in Delhi. Brad VU2USE from the American embassy was active, but he has now been posted to some other country.

Madras has its share of active hams, including Chauhan VU2MV, President of the Federation of Amateur Radio Societies of India (FARSI), who uses a Ten-Tec Delta. Equipment in the Madras shacks is mostly Heath, Ten-Tec, and Yaesu. In this city of 4 million, you will find the pace of life brisk but not breakneck. Hams here will find time for a friendly chat with you, even if you arrive unannounced. Avoid morning visits if you can, except on holidays. Life begins early-around 5:00 in the morning-and most hams are at work (known in India as morning QTH) by 8:30. Most of them can receive visitors at their place of work and in any case can be got at on the telephone. The 2-meter net meets on 145.5 at 0800 and 2000 hours daily.

Bangalore, promoted as the Garden City of India, is about the same as Madras, except that work for many begins at 7:00 in the morning. The Bangalore boys are back home by 5 in the evening even after commuting tens of miles. Many of these are not available by telephone, but put your 2-meter rig on scan and you may meet many of them.

If you are planning a short visit of a few weeks to India, you will probably not have enough time to obtain a reciprocal license. You can, however, operate from an Indian shack with the permission of the OM, and you can save the trouble of bringing along your shack. However, the path towards W opens up at an inconvenient time for working hams (around 1100Z), so unless you plan to operate from a pensioner's shack, it is likely that you will get to everywhere except your homeland!

In the event that you are planning to have a home in India for a few months, you can apply for a license about the same time that you apply for a visa. Your application should be addressed to the Wireless Adviser to the Government of India, Dept. of Communications, WPC Wing, Sardar Patel Bhavan, Sardar Sq., Parliament Street, New Delhi 110 001. The application form can be obtained from that office or more promptly by writing The Federation of Amateur Radio Societies of India, 3 Thiru-VI-Ka Road, Post Box No. 725, Madras 600 006, India (include 3 IRCs to cover postage). A self-addressed envelope will further speed up action; the forms will be posted the same day as your letter is received in India. Send 10 more IRCs if you want a copy of the Indian Callbook (which also contains telephone numbers).

You need not send money with your application, but do send a copy to the Federation. When you get your visa, write a letter to The Wireless Adviser to the Government of India, confirming that you got it. Send a copy to the Federation. You will normally get the license by the time you arrive in India, although much depends upon the workload in the licensing department at the time of your application.

The power allowed in India is 150 Watts rf output to antenna, which covers any barefoot transceiver other than the KWM2. Unless you are holding a Novice license, you will be allowed the use of the following bands: 7.000-7.100 MHz; 14.000-14.350 MHz; 21.000-21.450 MHz; 28.000-29.700 MHz; and 144-146 MHz.

The Indian government is extremely friendly towards amateur radio and foreign amateurs. If there is a delay in response to your application, interpret it generously as resulting from excessive workload. Once in a while the government may turn down your application. The reason will probably be the same as when the US embassy turns down an Indian application for a visa to visit the US. You cannot fight Capitol Hill, so resign yourself to operating from an Indian shack if your visa is not also refused. In the latter event, the problem neatly solves itself!

Now that you have a fairly good idea of what to do, plan your next vacation in India. Air India is a good airline and will be pleased to be of service if you choose to fly with them. You might even run into Capt. D. Dasan VU2AID, their operations manager, Vice-President of FARSI, on one of the jumbos or at one of the airports.

NEW OPERATING FREQUENCIES FOR HAMS

The government of India has authorized the following operating frequencies for VU2 hams. Certain frequencies as indicated (*) are shared with other services: 3500-3540* kHz; 3890-3900 kHz: kHz: 7000-7100 1400-14350 kHz: 18068-18168* kHz; 21000-21450 kHz; 24890-24990* kHz; 28000-29700 kHz; and 144-146 MHz.

The type of emission allowed to grade II operators in the band up to 24.900 MHz is A1 only with 50 W maximum dc input power. On 28-29.7 MHz, A1, A3, A3A, A3J, and A3H are permitted. On 144-146 MHz, A3, A3A, A3J, and F3 are permitted with a power limit of 10 W.

For grade I license holders, A1, A3, F3, A3A, A3J, A3H, F1, F2, F3, and A5 are permitted on the HF band; A2 is permitted, in addition to the above, for the VHF band. Power is limited to 150 W in the HF band and 25 W in the VHF band for terrestrial and satellite work.

For the advanced amateur telegraph



N. L. Krishnan of Bharat Electronics.



SP-600

SP-600

Select 1 of 3 sensors by soft touch switch. Three wide bandwidth sensors cover 1.6-500MHz. \$159.00

RS-1: 1.6-60MHz 0-2kW

0-200W

RS-2: 1.6-150MHz RS-3: 130-500MHz 0-200W

SP-200

Two position antenna switch and indicators. Three power ranges to 1kW, 1.8-160MHz. \$107.00

SP-400

Three band sensors (2m, 220, 450MHz), 10 percent accuracy, 0-150W CW, LED power range indicators. \$109.00

Distributed by

Encomm, Inc.

2000 Avenue G, Suite 800, Plano, Texas 75074 Phone (214) 423-0024 TLX 79-4783 ENCOMM DAL

SP-250



SWR & POWER METERS

SP-250

Low-profile, economy 2kW wattmeter. 1.6-60MHz band-width. 3W SWR sensitivity. Three ranges. A Best Buy! \$75.00

SP-15M

1.8-150MHz, 200 watt, low-profile wattmeter. VSWR, FWD PWR, REF PWR, 1.5W SWR sensitivity. Great for mobile HF. \$60.00

SP-45M

VHF-UHF to 100 watts. 3W sensitivity for SWR, 10 percent accuracy. All metal shielded construction. \$85.00

Distributed by

Encomm, Inc.

2000 Avenue G, Suite 800, Plano, Texas 75074 Phone (214) 423-0024 TLX 79-4783 ENCOMM DAL

V 135


VA 3 HVA


DUMMY LOADS



CT-300 Oil-less aircooled, 1kW peak for 3 min., 300W avg. DC-250MHz \$68.00

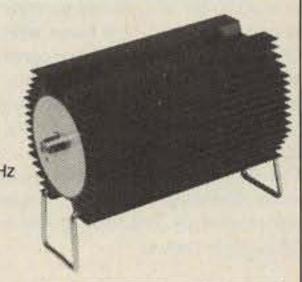
CT-150 Oil-less aircooled, 400W peak for 3 min., 150W avg. DC-250MHz \$46.00



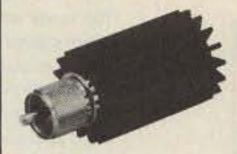


CT-15A 50W peak, 15W avg. S0-239 Screw-on dummy DC-500MHz, VSWR<1:1.2 \$12.00

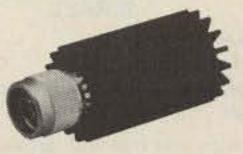CT-15N 50W peak, 15W avg., Type N Dummy Load. DC-500MHz, VSWR <1:1.1 \$21.00



SURGE SUPPRESSOR

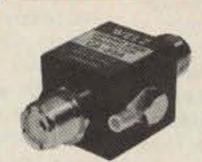

CA-35A Contains replaceable, chip-type surge voltage protector. Low loss, low VSWR. DC-500MHz, 350V breakdown. \$22.00

COAXIAL SWITCH

CH-20N Two-way coaxial switch. S0-239 type connector. DC-900MHz, IkW power. \$54.00




TERMINATION POWER METERS



TP-05X BNC connector, 5W talkie checker. Field calibratable, 3W avg. Dummy Load, 1W center. 50-500MHz. \$21.00

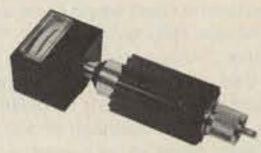TP-25A 25 watt version of TP-05X for mobile use. Larger Dummy Load. 50-500MHz \$40.00



All prices are suggested retail and subject to change.

Distributed by

Encomm, Inc.

2000 Avenue G, Suite 800, Plano, Texas 75074 Phone (214) 423-0024 TLX 79-4783 ENCOMM DAL station, A1, A3, A3A, A3J, A3H, F1, F2, F3, and A5 operations are permitted in the HF bands (with power limited to 150 W). Also, A1, A2, A3, A3A, A3J, F1, F2, F3, F4, A3H, A4, and A5 operations (with a power limit of 50 W for terrestrial and 100 W for satellite-working) are permitted.

VU2BEL

The Managing Director of Bharat Electronics Limited (BEL), Mr. N. L. Krishnan, has promised to help their club station (VU2BEL) with all facilities and equipment. There are more than 40 hams on the roll of the establishment. In addition to the club building, the establishment has provided their communications equipment, test equipment, antenna systems, etc. Now it is left to the inclination and interest of the hams to exploit and utilize the facilities openly offered by the Managing Director. He has whole-heartedly said that he is willing to help hams with projects for the design and development of new amateur equipment, especially ham gear which can be produced and marketed so that the national market for ham equipment can evolve.

The photograph shows the Managing Director operating one of the transceivers manufactured by BEL and given to the VU2BEL club station.



ISRAEL

Ron Gang 4Z4MK Kibbutz Urim Negev Mobile Post Office 85530 Israel

I hope that from the last few columns you haven't gotten the impression that the only amateur pioneering work being done here is in the VHF/UHF frontier. Yes, the lower end of the amateur spectrum is a new territory just beginning to be mapped here. You see, when in 1979 the World Administrative Radio Conference decided to expand the ham bands, the groundwork was laid for 160 meters to be opened up in this part of the world. So, for the hardy souls who brave the static-crash-torn reaches of the Top Band, we can now see what this band has to offer.

In the forefront of the pioneering effort here is Riki 4X4NJ of Gan Yavne on the Mediterranean coast about fifty kilometers south of Tel-Aviv. Riki's endeavors on 160 go back to pre-WARC years when, for the CQ Worldwide test in October, 1973, a special license was granted to set up a station. A full-size sloping dipole was hung from the top of the Four Seasons Hotel in Natanya, on a cliff overlooking the Mediterranean, and a Swan 160-meter transceiver on loan from VE3MR provided the means of exciting this effective antenna. From here on, Riki continued to experiment with this band from his own QTH, applying for special permission whenever an international contest would come up.

In October, 1982, along with 30, 17, and 12 meters, 160 became available to the Israeli radio amateur. 1810-1850 kHz may be used on a primary basis by Class A amateurs running a maximum of 100 Watts input and Class B operators with 10 Watts. 1850-200 kHz may be used by A IIcensees only on a secondary-non-interfering basis with 10 Watts input.

4X4NJ has since then worked all continents and run up the all-time record for Asia in the CQ WW contest. The credit must go to hard work, perseverance, and



The 1AØKM pictorial QSL card, showing the SMOM location, an ancient villa near the Tevere river which has been recognized as a national monument. For that reason, the tribander beam shown on the terrace (just right of the pine tree) had to be dismantled. A tilting-down five-bander vertical is now planned for the same terrace.

sparing no efforts on a good antenna system.

Riki began by loading the insulated guy wires of his 65-foot-high tower, resembling an inverted L sloping towards North America. Since then, the sky-wires have become more sophisticated, transmitting into a 100-foot wire hung from the top of the tower which is base loaded through a silver-plated coil. Sixteen 80-meter radials plus five quarter-wavelength 160-meter radials which are strung out temporarily over adjoining fields for contest weekends and assorted buried pipes comprise an effective ground system.

Receiving was at first the real problem: It was painstakingly difficult to dredge the far-off stations calling 4X4NJ out of the atmospheric noise. Thus, Riki switched between four different receiving antennas: the transmitting antenna plus attenuators, a horizontally-polarized omnidirectional dipole twelve feet up, a two-element vertical phased array composed of two twenty-foot elements with a rotatable pattern and remote transistor preamps, and an 80-foot-long non-terminated Beverage wire bi-directional to Europe and North America on one end and VK-ZL on the other. The Beverage, which Riki added last season, far outshone the previous receiving antennas, finding the North American stations, unreadable on the other antennas, were Q5 on this. This receiving antenna, added last winter, made it possible to hear better than Riki could ting effectiveness.

In early October, I got hold of Riki on the Tel Aviv repeater, and he told me of what appears to be his latest breakthrough. He recently completed a phased transmitting array with a very low angle of radiation and a rotary switch for selecting antenna direction. Construction details are being withheld until this antenna has been thoroughly tested out. Riki says that it appears to have a 15-to-20-dB front-to-back ratio and a forward gain of 6 to 10 dB. On receiving, it competes with the Beverage, and in certain instances actually outperforms it! Both G3BDQ and DJ8WL reported that he was coming in like a local, with a greatly improved signal, so Riki is ex-

On the equipment end (notice that we've left this for last, as on 160, the antenna is what really makes the difference), Riki is using the Drake C-line, with a combination of i-f and af filtering to squeeze the weak signals out of the noise. At this time, 4X4NJ has worked on Top Band 72 countries (53 confirmed), 25 US states,

We wish Riki best success on 160 this season, and hopefully some of you will have already made contact with him. There are other Israeli stations on 160 meters, but by far 4X4NJ is the most serious of all!

I would like to conclude this month by

be heard, so he decided that the next step in which to go was that of better transmit-

pecting big things out of this antenna.

and all continents.



The 1A0KM crew. From left, standing: I0MGM, I0JX, I0AMU, I0MXM. I0IJ is sitting at the mike. The atmosphere of the very exclusive ham shack is enhanced by ancient and valuable pictures on the walls.

thanking all those who have taken the time to respond to this column, either by letter or on the air. It has been heartening for me to know that so many people are interested in what's happening in this country outside of the tense headline news. This underlines the human aspect of amateur radio that makes possible people-topeople contacts, bypassing international boundaries and tensions.

Until next month, Shalom (peace) and 73.



ITALY

Giancarlo Martelli IOXXR Via Bevignani, 18 00162 Roma Italy

Mario Ambrosi I2MQP Via Stradella, 13 20129 Milano Italy

1A9KM—THE SOVEREIGN MILITARY ORDER OF MALTA HAM STATION

One of the most requested countries in the DXCC fan's world is the Sovereign Order of Malta, prefix 1A0. This political entity, founded in 1099, recognized by Pope Pascal II in 1310, and known as SMOM-Sovrano Militare Ordine di Maita-is fully independent from the Italian state, and under the provisions of international law, it maintains diplomatic relations with many countries and international organizations. The main activity of the tiny political and territorial entity, which is located in a beautiful spot of Rome near the Tevere River, is concerned with worldwide assistance in the sanitary and social fields.

The 1A0KM station was activated in November, 1980, when the Knights of Malta asked some amateurs to give their assistance in setting up radio contacts with their field hospitals located in the territory hit by the tremendous earthquake in Irpinia, South Italy. Just following that event, 1A0KM operated for some months, until January, 1981, raising savage pileups whenever it appeared on the bands. During that period, the station made about 8,000 QSOs. The DX Advisory Committee of the ARRL, after a complete survey of the documents submitted by SMOM through the station operators, recognized the independent political status of the territory governed by the Knights of Malta and added the 1A0 prefix to the DXCC list, giving credit to the 1A0KM cards starting from its earliest operations. The amateurs who started up the station and the new country, and who at present are the exclusive operators allowed to carry out ham-radio activity there, are Al IBAMU, Tony IBIJ, Tony IBJX, Mario IBMGM, and Mario IOMXM.

Due to the room shortage in the ancient villa which houses SMOM, the 1A0KM station does not yet have a fixed setup, and the rigs, as well as the antennas, are being taken inside and assembled whenever the station must operate; this is neither practical nor fast.

A tribander beam antenna which was mounted on the building roof had to be disassembled for esthetic reasons, since the villa is recognized as an antique and a valuable monument.

At the time of this writing, the 1AØKM crew is trying to get a corner to set up a permanent shack and a permanent antenna. The already-mentioned willing boys taxed themselves and bought a Yaesu FT-901DM transceiver, a Henry R2DK Classic amplifier, and a five-band 18AVT ground plane. They plan to put the antenna on the building terrace, with provisions to tilt it down on the floor when not in operation. This stable arrangement will allow the station crew to put the 1AØ sigs on the air more frequently, possibly entering some international contests as well.

The official QSL manager is Mario IØMGM, but due to the very heavy task involved with such a management, the cards for contacts made with the other operators (IØIJ, IØJX, IØAMU, and IØMXM) may be sent directly to these boys, who will manage their own QSLs: Antonio Privitera IØIJ, Via Ceresio, 34, 00199 Rome; Antonio Vernucci IØJX, Via G. C. Abba, 8, 00141 Rome; Mario Gallavotti IØMGM, Via Cassia, 929, 00189 Rome; Alfonso Porretta IØAMU, L.go S.Pio V, 16, 00165 Roma; and Mario Monaco IØMXM, Via R. Paolucci, 27/13, 00152 Rome.

HAM RADIO IN ITALY BEFORE WWII

It may be that the old-timers who started their activity before WWII are interested in knowing what amateur radio was like in Italy during the Fascist period. Italy had its own pioneers, like Adriano Ducati 1ACD, Giulio Salom 1MT, and others who broke the shortwave DX frontiers, establishing some world records in the roaring old times, around 1924-1925. They had government provisional permission then, as no laws or rules on amateur-radio activity had been issued in our country at that time. These laws or rules were never issued by the Fascist government, excluding one point of the Italian Postal Code where it was stated that "nobody shall exercise a transmitting radio station without the Post and Telegraph Ministry permission." Theoretically, ham radio was not forbidden, but on the other hand, the permission was not granted either. The reason for this was that the Fascists did not see with much pleasure every form of private contact between the Italian citizens and foreign democratic countries.

Naturally, radio had many fans in Italy, mostly devoted to home-brewing. There were three or four consumer magazines devoted to these fans, publishing descriptions, schematics, and advice on how to build BC radios, SW radios, and even amateur transmitters. There were also many good technicians, many of them very young, who home-brewed good SW receivers and listened to international BC stations and to foreign amateurs.

During that period, Ing. Ernesto Montu, an electronics engineer and university teacher who was famous in Italy for his Radiotecnique Manual, and who also had been one of the ham-radio pioneers many years before, founded the ARI, the association which still officially represents amateur radio in our country. At the same time, some amateur stations appeared on the bands in a clandestine way, with selfassigned callsigns. They did not communicate their names or QTHs, and they operated undisturbed. Their number started to grow, and in the meantime, Ing. Montu started a very small (but very dangerous in those times) QSL bureau in his own home, which also housed the ARI headquarters and a new magazine, Radio Giornale, the official journal of the association.

Year after year, the number of Italian hams increased. They tried to have a clean and purely technical kind of operation, in order not to raise any suspicion as to their intentions. The political police and the postal police played a very fair game and were highly tolerant as they apparently seemed to ignore that kind of activity.

I was almost a kid then and was deeply involved with radio, home-brewing receivers-at first simple crystal types, then regenerative sets with two or more tubes. When I first received shortwave, I was fascinated by the code transmissions and learned it in a hurry; then when I started to listen to the amateurs, I got really excited. I tried to get some information on how to get started, but the answers I got were vague. Some operators told me that they were Fascists, and that only Fascists could operate radio stations. Others warned me not to get involved in such a dangerous activity. I was 17 when I decided that I had to get on the air. My poor pocket (I was a student) permitted me to buy a '45 tube and an '80 rectifier, a supply transformer, and some other parts, all secondhand, and I started my activity with the 45' self-oscillating in a Hartley circuit and a Windom antenna.

I made a lot of DX contacts with that makeshift rig and got my WAC, which lived in my heart since I could not get the award from the ARRL! Although I did not declare my QTH and my name on the air, I found that some form of hidden intelligence, word after word, indication after indication, could be carried out in order to get in touch with other Italian fellows. That system worked, and I joined other friends and attended the annual meeting, a very clandestine one in Milano, where I knew Mr. Montu and had the chance to receive some QSL cards.

I had to rely only on that simple QRP rig and on a three-tube regenerative receiver, as my pocketbook did not permit much more. Many Italian hams were in possession of sophisticated transmitters, like crystal-controlled MOPAs with transmitting tubes in the power amplifier. Many of these tubes and components, like 807s and 813s, were coming into Italy through bootleggers from Switzerland. In Italy, we also had a very good commercially-produced receiver, with a six-band drum coil switching system, low-loss materials in the front end, S-meter, and optional bfo. It fit into a sumptuous mahogany cabinet like a BC receiver, but in reality, it was a real communication receiver. It was put out by IMCA, a firm owned by an underground Italian ham. That beautiful receiver was in many Italian shacks during the latter half of the thirties.

One day, I got an answer to a CQ from a very powerful station, presumably local, which gave a ham callsign and spoke perfect ham language. The operator, to my surprise, gave me an address in the same city where I lived-Bologna-and invited me to pay him a visit. His open style was very unusual in our community, but his invitation and his voice sounded so friendly that I decided to go. I turned pale when on the door I read: "Voluntary Militie for the National Security-Radio Center." I decided to turn back when a gentleman who was standing near the door asked me if I was I1PL. He sald, "I imagined your surprise and your fear, so I was waiting just to reassure you, Old Man." He cordially invited me inside.

Wow! For the first time in my life I saw an RCA AR88 and an RME 69! All around were racks filled with radio gear. "Boy, what is that strange key with two black paddles? What does 'Vibroplex' mean?" I felt myself getting faint when I saw some shelves filled with QSTs, ARRL handbooks, and bunches of QSLs from everywhere in the world. "What kind of QSL bureau are you using?" I asked him. "Direct mail" was the answer. My surprise was endless, as there was a tight censorship of mail to and from abroad.

I visited another room where I saw several AR88s and some operators typewriting. Nobody explained to me what they were watching. My new friend was a lieutenant colonel of the Fascist Militia, a military organization composed of members of the Fascist Party which cooperated with the regular army and supported the Fascist idea within Italian society. I visited my new friend very often and introduced him to other amateurs of Bologna.

Going back in my memory to these old days, I now realize that the funny situation which had seen outlaw radio amateurs becoming friends of the people who denied licenses and transmitting permission was the mirror of Italian society in the late thirties when the Fascist dictatorship became more of a formality than a reality in everyday life, due to the humanitarian philosophy of the Italian people.

Three years later, when the tragedy of WWII was approaching and the German Army invaded Belgium and Holland, the European radio amateurs were silent, since the administrations had revoked their licenses. Italian hams were still operating, mainly with hams on other continents. One evening, the postal police, together with the political police, paid a visit to Italian ham shacks all over the Italian territory. I must say that they "paid a visit," since when they came to my home they showed extremely good manners. They had a perquisition order, but they asked kindly for permission to take a look at my shack. I was alone at home, as my mother was out, and tried to deny them entrance. They reassured me that there was nothing to worry about, but that they had to confiscate the I1PL station. They took away the rig, the key, the log, and the QSLs. My mother, when she came back, found me sitting on the outdoor step with tears in my eyes.

I ran to my friend the morning after. "Don't worry," he said. "Let the waters settle for a few days and you will have your rig back, but you have to promise that you and your friends will disassemble everything. There will be no more ham radio." A few days later, I was invited to the office of the political police, where I learned that we had been monitored for a very long time. They said that since I carried out only experimental work, I had to pay only the minimum amount of a fine, due to the infringement of the Postal Code: "Nobody shall exercise a transmitting radio station without...", etc. A few days later, I got my gear back and disassembled everything.

That was amateur radio before WWII in Italy.

LIMITED ACTIVITY ON 3.5 MHZ

At present and in the near future, until the Italian administration makes up its mind on issuing new rules, it will be practically impossible to work Italian stations on the usual CW, RTTY, and SSB DX subbands recommended by the IARU.

The story starts long ago in 1968 when the last Italian law ruling radio-amateur activity was issued. On that occasion, the Italian administration gave a singular interpretation to the concept of "sharing" the 3.5-MHz band between the Radioamateur Service and other fixed and mobile services. Since amateurs had a secondary status according to WARC statements at that time, they obtained in Italy only the following thin frequency slices: 3.613-3.627 and 3.647-3.667. The rest of the band was assigned to the other services.

Many years passed during which that limiting rule was slowly forgotten. During this long period, amateurs spread out from their narrow subbands and joined their foreign fellows on the whole band.

After some years, Italian hams believed that the administration had issued new rules. The administration itself did not care much about this illegal operation, and that reinforced the conviction that everything was OK. I, like many others, never suspected that anything was wrong. In many instances, the ARI official magazine, Radio Rivista, published the amateur band plan for Italy, with the whole 3.5-MHz band assigned to amateurs according to the WARC frequency allocations, forgetting the principle that our administration had the right to forbid some frequencies to some services.

Suddenly, last spring, somebody inside these offices remembered the law. A tight monitoring started, and amateurs found outside legal subbands were warned, and some were fined. At the same time, another offensive started: Administration officers visited many ham shacks and fined all those who were found in possession of linear amplifiers, as the maximum legal power in Italy is 300 Watts input. Other minor discrepancies, like inaccurate logging, were verified and prosecuted, and some action was taken against amateurs working 144 MHz mobile from their cars. In fact, in Italy, any amateur mobile operation is forbidden, except for CBers who are authorized to carry radios in their cars.

From this perspective, other clouds could appear on the Italian amateur's horizon. The above-mentioned law does not take into consideration any unattended station outside the legal residence of the licensee: For that, all the VHF and UHF repeaters must be considered illegal and could be dismantled by administration officers. The same thing could be said about the SSB transmission mode: The old 1968 law authorizes only CW, AM, RTTY, and FM above 144 MHz; no further official act authorizing SSB has come since then.

Until today, our administration has closed both eyes; she could suddenly wake up, like she did about the 3.5-MHz band. We strongly hope that these archaic and out-of-date rules may be modified as soon as possible. But as a matter of fact, at present, Italian hams are at least out of the game as far as any 5-band activity is concerned, like contests, awards, etc.

Italian amateurs are still in shock after the withdrawal of the 3.5-MHz band. There are big discussions on the air and in the clubs. The ARI—Associazione Radioamatori Italiani—is accused of not having supported in due time the cause of Italian amateurs on that occasion. In fact, the ARI was absent when the Italian administration started its battle against amateurs. In addition, the ARI failed to warn amateurs about what was happening, so many of them continued to operate outside the permitted slices and were monitored and punished.

Italy is a very beautiful country. It is also a very contradictory one, due to its very young democracy and the problems raised by very fast growth. On one side, there is probably an excess of freedom due to a widely acclaimed liberalism—a clear reaction to the Fascist period. On the other side, most of the bureaucracy suffers from an old-fashioned paternalism to which they abdicate when in the counterpart they find power.

In the telecommunications field, the excess of freedom, unchained by a sentence of the Constitutional Court ("Everybody has the right, by any means, to express his thought"), led to an uncontrolled and abnormal growth of private TV and FM BC stations, operating unlicensed and unpermitted, with no technical control—a real jungle of interference with spurious radiation jamming other services, mainly the

aeronautical ones. The whole situation is absolutely inexpugnable due to the amount of political and commercial interests lying under it. The administration is also faced by other big problems, like the continuous increase of pirate stations. These stations work with amateur transceivers, often using linears and beams, and have invaded many frequencies allocated to the aeronautical mobile services, like 45 meters and segments of bands near 80 meters. An inestimable number of hand-held transceivers (which in Italy are sold with the same ease as a cigarette box) carry illegal private VHF and UHF communications. Due to the power underlying the TV and BC stations and the practical impossibility of locating thousands of illegal stations, the administration had to raise its hands. On the other hand, the administration, incapable of controlling the described mess and overloaded by the problems caused by the fast growth of the communications systems in our country, has a fair chance at repressing the amateurs who pose them further problems, since they are a weak and not a politically supported community.

At present, many Italian groups understand that their problems cannot be solved through traditional negotiation with the administration. They need a different platform. Maybe in the near future they will look for the support of the national media: TV, newspapers, and magazines. It may happen also that they decide to ask for support from fellow amateurs around the world and from ham magazines and foreign ham associations. We regret to inform the hams who read "73 International" around the world that, for the moment, Italian amateurs are cut out from the international path on the 3.5-MHz band and must disappear from the friendly competitions based on five-band communications. We do hope to be back with you very soon.

de IØXXR

SENATOR COSSIGA

At the end of last July, a telegram was received at the editorial office of the Italian League. The telegram was sent from the Senate—more specifically, from the secretary of the president of the Senate. The telegram said that the president required another copy of the July issue of the national radio magazine, since his copy was probably lost in the mail. It was with great pleasure that a second copy was sent to Francesco Cossiga IØFCG, president of the Senate, the second highest dignitary of the state.

IOFCG has been active since 1973 but hasn't had too much time to devote to radio, and in particular, to DXing-his favorite aspect of the hobby. He has been helped by the DXers of the Rome area with info and QSL routes. During a recent interview with one weekly magazine, he said: "I am a radio amateur and I am sorry not to have too much time to dedicate to it. In any case, during the weekends and holidays that I spend in Sardinia where I come from, I like to chat with friends and contact Alaska, the USA, and New Zealand." Senator Cossiga was born 55 years ago, and after a few years of teaching at Sassari University, he joined the Christian Democrats and won a seat in the House of Parliament in 1958. He has served in various positions in the government and has also been Prime Minister.

NEW DX RECORDS

New records from I@SYN were established during July. A DXpedition sponsored by the Italian DX Blue Team took place during the end of June and the beginning of July. The trip started on June 29

from Perugia, in the center of Italy. The destination was the north of Africa. The group consisted of three Italians: IOSNY, IØKBL, and IØRSC, plus EA5RK. Ceuta, EA9, was reached by car on July 2 after a trip of 3000 kilometers. On July 5, the first record was made with a contact on 1296 MHz with I8TUS/8, for a distance of 1914 kilometers. After giving new ones on 144 and 432 to all Europe, the group started working on 10 GHz, and on July 8, several contacts of more than 1500 kilometers were made. The record contact was 1663 kilometers, with IOYLI/IE9. Next year the group will try again to activate other countries on various frequencies and to break some records.

de I2MQP



MEXICO

Mark K. Toutjian XE1KMT Nandu 21 Vergel de Arboledas Cd. Lopez Mateos, Mex. 54500 Mexico

OPERATING IN MEXICO

I have received quite a few letters from foreign colleagues with regards to operating within Mexico while on vacation. No doubt the following information will be useful to many who may have wondered this as well.

Can You Operate In Mexico?

Sure you can! However, just as in all lands, papers are required. And where there are papers, paperwork is involved. Mexico is not the exception. Some call it "red tape." It all depends on how you look at it. This brings to mind an expression that my mother often helped me to appreciate: "What's worth getting is worth waiting for!" It has come in handy and helped me keep a proper perspective of things in life,

What Do You Need To Do?

Well, there are different factors involved. First of all, this depends on whether your country and Mexico have a bilateral or reciprocal agreement or not. The United States does not. But if your country does, then you can write to Mexico for an application at the following address: Secretaria de Communicaciones y Transportes, Subdireccion de Operacion de Sistemas Radioelectricos, Depto. de Normas y Reglamentos, Mexico 12, D.F.

The application will state what present requirements are in your case. This, of course, all depends on what details are covered in the reciprocal agreement between your country and Mexico. A photocopy of your present ham license will definitely be asked for upon submitting your application. All foreign visitors will be given a license not exceeding one year from the date it was issued and not longer than the expiration date on your visa. If your home license expires even earlier, don't expect to receive a permit to operate in Mexico for a longer term than what you were issued in your homeland.

No Reciprocal Agreement, You Say?

There still exists the possibility of your getting a limited ham license here, so don't fret. The Mexican FCC (Secretaria de Communicaciones y Transportes—SCT) will establish the requirements that should be satisfied in addition to those requirements that are already set for nation-

al amateurs-to-be. The tourist receives a visa for no more than six months, so his license could not be issued for more than that amount of time. The immigrant has to renew his visa (FM-2) each year for five years, so he can be issued a renewed license each year upon presenting a photocopy of his renewed immigration papers.

In either case, if your country does not have a reciprocal agreement with Mexico, then three tests are to be taken.

- 1) Morse code. If you apply for a firstclass license, you will be tested at 13 words per minute, second-class applicants will be tested at 10 words per minute, and the beginners will be tested at 5 words per minute. The restricted license (good for one year and not renewable) does not require the code test.
- 2) Theory. This includes electricity, magnetism, and radio communication. Yes, you guessed it! All in Spanish and in your own words! What better incentive could you have for brushing up on your Spanish, besides coming to Mexico?!
- Regulations. You could compare this to a written driver's test. You'll have to know the laws and regulations of the airwaves here in Mexico, just as in any country.

Whether your country has a reciprocal agreement with Mexico or not, you will be required to send in with your application a letter of responsibility, where a national amateur (one who has the same or higher grade license than what you are applying for) states that he will become responsible for you. Many of our 73 readers have already established long-term friendships with different experienced Mexican amateurs over the years and perhaps even had an "eyeball" or two together. So that should not present a problem for you.

Study Material for the Mexican Ticket?

Why don't you write to Pablo A. Mooser M. XE1SR, Av. Schiller #329, Mexico 5, D.F., and get his book: Guia de Estudios para la Licencia de Radioaficionado (Study Guide for the Ham Radio Amateur License) in Spanish and study up right away! He can also recommend to you some other real fine publications available in Spanish as well, being President of the Amateur Radio League here in Mexico.

Which Class License Do You Want?

Well, then again, that only depends on your personal skills and know-how. Class I and Class II are similar (the only difference being that you can transmit with 1 kW with the Class I license in certain areas and with 250 Watts with the Class II license in certain areas. This is all explained in detail in the above-recommended book and in Mexico's official regulations.

After applying for your license, the Mexican government will then advise you where you should go to take your tests; a few months will be given as a margin. So it would be best for you to apply as far in advance as possible for these tests if your country has no bilateral agreement with Mexico.

Since Mexico borders with the United States, I know that many amateurs from the US visit this country frequently and some may have assumed that there is no way to operate here in Mexico. Nevertheless, my idea here has been to help you realize that you can operate as a legal amateur here in Mexico upon fulfilling the proper requirements, even though there is no reciprocal agreement between the US and Mexico. A Mexican amateur cannot get his US license either, unless he fulfills requirements asked by the FCC. And when you think of it, isn't this part of

amateur radio? Don't forget that "what's worth getting is worth waiting for!" And thanks again for your many fine letters!



LIBERIA

Brother Donard Steffes, C.S.C. EL2AL/WB8HFY Brothers of the Holy Cross St. Patrick High School PO Box 1005 Monrovia Republic of Liberia

Did you ever hear of a fixed-frequency amateur net?

Anything can happen in Liberia! We are setting up a fixed-frequency net in the forty-meter band at 7.060 MHz. It is not limited to fixed-frequency radios and it is not limited to stations in Liberia. Actually, the net is in operation at the present time and DX stations, with or without traffic, are welcome to check in. It meets every Sunday morning at zero eight hundred zulu and on other days at zero seven hundred zulu.


Then why all this talk about the fixed frequency?

Well, the Liberia Radio Amateur Association is receiving some two dozen fixedfrequency radios. They are Heathkits and will be converted and crystalled for 7.060 MHz. They will remain Association property and will be rented out for five dollars a year (or less if necessary).

Our Novice-class operators are permitted phone at 7.060 MHz so that they can participate in the net activities. This is important for their encouragement and at the same time it makes our net communication system more effective. This is a very important factor for us here in Liberia where phones and postal service either do not exist or are not dependable. Novices (and in some cases, Generals) cannot afford to buy amateur-radio equipment, so these fixed-frequency radios are going to fill a real need.

The 7.060-MHz frequency is a kind of "get-together frequency" for Liberia and the countries within hearing distance, so our young operators should have ample opportunity to "get out." At the same time, they can talk to each other and they can practice code, on the air, communicating with each other by code. We are excited about this little venture.

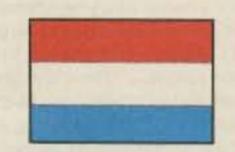The fixed-frequency net is not needed in many other countries, but for us it holds real promise.



THE NETHERLANDS

H. J. G. Meerman PD@DDV Zandvoorterweg 33 2111 GR Aerdenhout The Netherlands

RADIO-AMATEUR EXAMS

Twice a year, spring and fall, the Dutch amateur-radio exams are held. All persons who want to get a D license (145 MHz, no code) or upgrade to C class (145 and higher, no code) have to pass this exam.

The exam for the Dutch novice D li-

cense consists of 40 multiple-choice questions about transmitters, receivers, antennas, filters, radio regulations, and license conditions. Three answers are given for each question; you must have at least 29 correct answers to pass this exam with good results.

For the C license, you have to fill in 50 questions and you have the choice of four answers to each question, but you must have 35 answers correct to get a C license.

For the D exam, you have 75 minutes to complete all the questions. For the C exam, you have 30 minutes more time to finish.

The exam is held in a large hall normally used as an exhibition hall. Hundreds of tables and chairs are placed in this enormous hall, with space enough between each table so that it is impossible to look at your neighbor's exam papers.

The exam questions are bundled in a small 15-page booklet. The answers to the questions must be written down on a computer form, so that the forms can be calculated by a computer.

The Dutch amateur-radio exams are not free. The cost is 50 Dutch guilders and must be paid in advance to the account of the Dutch PTT.

After passing the C exam, you can upgrade to the A status (all bands, all modes). For this A status, you must pass a code exam of 12 words a minute.

The results of the exams are mailed to each person who takes the exam. It takes three weeks before the results are mailed. In the meantime, however, there is another way to know the results.

After the exams, National Dutch Amateur Radio Station PAØAA has a special broadcast about the exam results. The Dutch television also publishes the results on the "Dutch Teletekst System."

In 1982, a total of 1607 candidates came to the D exam. 2429 persons took the C exam. So it is plain to see that the interest in amateur radio is very much alive in Holland. Most of this interest is due to the code-free exam of the C and D licenses, but most of the amateurs try to master the code after some years working on VHF and UHF.

If you pass a Dutch amateur-radio exam with good results, you have to sign a paper, a kind of contract, which states that you agree with the license conditions and that you'll agree with rules to be taken by the authorities in the future. So you are agreeing with rules that you do not even know. Well, isn't that a bit strange?

On the day of the exam, the Dutch Radio Control Service has a very busy job. The reason for this is that some amateurs take their radio receivers with them into the exam building so they can receive the answers to all the questions. You can't believe it, but it is the truth. I'll tell you how this works out.

A person enters the exam room, takes his exam as quickly as possible, then goes away and walks to a parked car or a hotel room. In this car or hotel room, his friends are waiting for him and they sort out in no time the correct answers to the questions. They do this with the help of some smart guys and a couple of books. Now they transmit all the answers by radio into the exam room, where their friends are waiting with their receivers. Although the check-in at the exam room is very sharp, some manage to bring their receivers along.

You can imagine that the Dutch Radio Control Service does a lot of radio direction-finding at the exam. When I heard this story for the first time, I thought it was a joke! However, last year I heard it with my own ears on the FM band of my car radio.



NEW ZEALAND

D. J. (Des) Chapman ZL2VR 459 Kennedy Road Napier New Zealand

ZL PREFIX CHANGES

NZART made proposals to the regulatory body, the New Zealand Post Office, that separate prefixes should be allocated to the Chatham Islands, the Kermadecs, and the Auckland/Campbell Islands instead of the present /C, etc., method of identification.

The proposals were adopted, and from January 1, 1984, the ZLØ-9 series will be used as follows: ZLØ—for visitors to New Zealand (no change); ZL1-4—for mainland New Zealand, i.e., North Island, South Island, and Stewart Island (no change); ZL5—Antarctica (no change); ZL6—New Zealand Intruder Watch (no change); ZL7—Chatham Islands; ZL8—Kermadecs; ZL9—Auckland/Campbell Islands.

The ZK series will be as follows: ZK1— Cook Islands (no change); ZK2—Niue (no change); ZK3—Tokelau Islands (previously ZM7); ZK0, ZK4-9—reserved.

The ZM®-9 series will continue to be held in reserve and used on special occasions at the discretion of the Post Office. So, prefix hunters and all other interested amateurs, as of January 1, 1984, there will be a few more prefixes available by working the New Zealand off-shore islands under their new callsigns.

THE AREC STORY CONTINUED

AREC in ZL today consists of about 75 Sections and between 800 and 900 active members. Because there are more AREC Sections in Auckland and Wellington regions than there are callsigns in the ZL1E and ZL2E series, the New Zealand Post Office has approved the use of ZL6E calls in the Auckland region and ZL7E calls in the Wellington region. So when you hear such calls as ZL6EBA and ZL7ECA, they are not a pirate station or some rare DX, but Amateur Radio Emergency Corps stations in the Auckland and Wellington regional areas operating emergency communications networks. Who knows what the next 50 years will bring? A massive increase in the South Island population could mean ZL8E and ZL9E callsigns for AREC.

Two features of AREC in ZL are unique. Both stem from the Post Office recognition of the Radio Emergency Corps from its inception.

The first unique feature is the distinctive callsign series allocated for AREC stations in which the first letter of each callsign following the prefix is always an "E". The special "E" callsigns identify stations engaged in emergency communications and warn other amateurs not to interfere with what may be urgent or vital traffic. No other country has the advantage of such a system.

The other feature is the allocation of spot frequencies within or on the edge of the amateur bands specifically for AREC use. These are 3500 kHz, 3900 kHz, 7100 kHz, and the exclusive band of 1900–1925 kHz. Other frequencies may also be used for AREC communications when and as required.

In the early days of AREC, all equipment was home-built and performance varied considerably depending upon the skill of the constructor and the skill of the operator. Initially, all operation was on CW. All operators were amateurs who, when involved in field searches, had to be fit enough to travel with the search parties and carry the extra weight of their radio equipment, too!

The postwar years saw the adaption of war-surplus equipment for AREC use. Subsequently, special radio equipment was developed and produced for AREC use, initially AM and CW, and in the last few years, SSB, the present AREC sets for field work being TR 105s, while most base stations and field-search HQ stations are modern-day transceivers suitable for operation from emergency power supplies.

The advent of modern amateur equipment has revolutionized AREC operations, operators now being able to use complex equipment that was not dreamed of in years gone by. Just as HF equipment had become plentiful for amateurs, the migration of VHF amateurs to the 2-meter FM band and the establishment of repeaters has revolutionized mobile and portable operation.

The facilities for purely local communications are excellent, and because most VHF equipment is easily portable, its suitability for emergency and Civil Defense applications is obvious. With VHF links between the search teams and fieldsearch HQ, now the amateurs do not have to carry heavy equipment, but just a light hand-held with an additional battery supply, and they are good for several hours of search and rescue work.

Ished and developed along with AREC since 1948. The first of these, the Search and Rescue Organization, is sponsored primarily by the Civil Aviation Division of the Ministry of Transport and the Police Department. Any search for missing persons or for missing aircraft comes under the control of one or the other of these government departments, and AREC has the continuing role in the provision of communications to and from the field and frequently in the field as well. AREC is financed by an annual grant from the Search and Rescue Organization.

AREC also has a role in the Civil Defense Communications Network, providing the communication between Civil Defense Headquarters and the Sector Posts in most Civil Defense areas.

The present Officer Commanding of the ZL AREC, Ron Morgan ZL2GQ/ZL2EX, is quoted here to conclude this resume of the emergency amateur service as it exists in New Zealand:

"As the latest in the line of OCs of AREC, I am aware of the work, the planning, and the efforts that have been put into the development of the AREC of today by my predecessors and conscious of the need to continue to make every effort to preserve the good repute in which the Corps is held. To me, amateur radio is the greatest hobby in the world. AREC is the aspect of amateur radio that can be of service to the community, and in return for the privilege of enjoying the hobby, I believe that I, and every other ZL radio amateur, too, owes support to the Corps."

AWARDS

Remember the Hastings Centennial Award, 0001 hours GMT, February 1, 1984, until 2400 hours GMT, February 29, 1984. All bands, all modes; see last month's column for details of contacts required.

BITS 'N' PIECES

Recently, another World Communications Year activity took place at the Hawkes Bay Royal Show (County Fair) when the Napier and Hastings Branches of NZART combined to display amateur radio to the public. During the three days of the Royal Show, the combined Branches were allocated the special callsign of ZL9WCY and operated amateur stations from the display stand at the show. Also, they had static displays of AREC equipment, old and present day, some vintage radio equipment, and present-day transceivers.

There were three working amateur stations, one on 20/15/10 meters, one on 40 meters, and the other on 2 meters for local communications. Propagation was not good for the HF bands, but some excellent QSOs were made with US amateurs and others that helped to demonstrate amateur radio to the public.

There was a third section to the display where the public could touch special display items such as a vintage receiver tuned to the local broadcast station, with the output fed into a scope showing the patterns of the carrier and the sound/ speech. These "touch" display items proved very popular with young and old alike.

In an earlier column, when I described the national organization of amateur radio in ZL, it has been pointed out to me that I failed to indicate clearly the method by which our president is chosen.

NZART is probably one of the few national radio organizations where the members elect the president every two years. For the biennial elections, nominations are called for all offices, including that of the president, so here in ZL the members of NZART elect their president, unlike other national organizations which appoint from one of the elected council or executive.

February is the month when all NZART Branches are making feverish preparations for the National Field Day Contest. This year, so I'm told, there will be a special YL team operating one of the non-active Branches somewhere in the North Island.

Good luck to the YL team; the extra multiplier and contact points will be appreciated by all National Field Day participant teams.

More 50-year certificates to members of the ZL Old-Timers Club have been issued. Congratulations to the following: M. D. Mason ZL1NW, Tauranga; S. C. Baveystock ZL1NX, Tauranga; Watty Briden ZL1PN, Auckland; George Anderson ZL2JG, Waikanae; Jack Moore ZL2JM, Fielding.

Dates to remember: June 1-4, 1984—
the NZART Rose City Conference at
Palmerston North. If you are planning a
trip to ZL about that time, you will be most
welcome at our annual convention. Enquiries to the Rose City Conference, PO
Box 1718, Palmerston North, New Zealand, or to me at my home QTH.



NORWAY

Bjorn-Hugo Ark LA5YJ N-3120 Andebu Norway

Since my last column there have been some interesting activities in Norway. Of special interest was the yearly national convention of NRRL, held in Bodo, in northern Norway. This year's elections seemed both to underline the differences between the HQ members and the ordinary member and to smooth them out. I guess that's what democracy is all about, is it not?

Mr. Odd Andersen from the Norwegian Telecommunication Direktorat in Oslo gave a speech on the new license regulations expected to be issued. Word about a promised A license of 600 Watts output was very popular information for the nearly 100 members gathered—representing about a third of the total voting membership.

At a DX session earlier that morning, Alf Almedal LA5QK announced that they are at work getting Peter I Island recognized as a new DXCC country (which by now may already have been confirmed). He also said that a Norwegian Antarctic expedition will take place in late 1984, and that they were working to see that some of the members of that expedition will be ham operators. Rangnar Scholberg LA7FD and Mathias Bjerrang LA5NM, well-known operators from JX- and JW-land, held an interesting session about operation from the Arctic.

The convention was an absolute success, and the two local sections of NRRL, the Bodo and Fauske groups, could not have been praised more for their excellent planning and the smooth-running sessions.

DX CONVENTION

At the annual DX convention in Oslo, most of the eastern Norway members of the LADX group were gathered to elect a new president and members of the board. An unfortunate accident to Stig Lindblom LA7JO a week before kept members from central Norway away from the convention and kept the mood of the meeting rather low. Happily, LA7JO survived the fall from his 16-meter (48-foot) tower. He fell head first, and it is a mystery how he was able to survive without any greater harm than broken and crushed arms, although his condition was very serious for the first couple of days.

Svein Ovenstad LA3XI was elected as the new president of the LADX group. His predecessor was the late LA1KI, and the presidential chair had been empty for nearly a year since no one really wanted to touch the memory of our highly respected and beloved friend LA1KI, Norway's well-known top DXer for many years. The members of the board ran the LADX group in the meantime and did a good job.

Kare LA2GV was presented the trophy for being the top-score Norwegian operator in the SAC contest, 1982, in the single-operator/allband class. LA2GV had won the same trophy before, and I had the great pleasure of receiving the trophy on his behalf.

The LADX group is now looking into how to get SM@AGD to come over and talk



Odd Andersen speaks at the NRRL convention.

about his DXpeditions to our members; it also is involved with a couple of rather interesting projects which the board seems to be keeping secret!

MALPELO DXPEDITION

Hurray, Colombia! You did it! HK@TU (Malpelo) went on the air. The whole world was waiting, and you gave it to us. And congratulations for an excellent operation, which must have been very thoroughly prepared, with a touch of the good old days in it: not a foul word, no irritation over the often-too-eager operators trying to work them. This operation was something all the members of that crew could be proud of.

We here in Europe too well remember a certain PYØ operation not too long ago which will go into legend as one of the poorest SSB operations from a rare place in years. But a German group put that all right again. That group actually always does a good job, so anything else from that side would have been a shock. The Colombians did their effort to straighten this out in a tremendous manner. Thanks again, guys; good work.

DXers, well, it's time to look for Europe on the lower bands again.

40 has as always been very good, but when you are reading this, 80 and 160 will be at their peak to many areas. Remember, keep clear of the DX windows. You never know, day or night, when the bands will open. Most of the day and night there will be openings from Scandinavia both on 40 and 80 meters, toward North Amer-

ica and Japan. Listen in if you're interested in some good DX QSOs.

New countries we all are waiting for include Kermadec, Clipperton, China, Bouvet, Peter I Island, and San Felix. When will they come? Kermadec is due, China has been worked by many, but the rest? We'll wait and see, won't we? The thrill of a new one is always there, and the pleasure after working it, as well. Hours of strained listening, intensive calling, and then the feeling of your heart doing a couple of extra beats when your call is returned. And then the nervous tremble in your voice when confirming and giving your report, that's what it's all about! Thanks to the guys giving us that pleasure of working them.



PAPUA NEW GUINEA

Seigi Freymadi P29NSF PO Box 165 Rabaul Papua New Guinea

This will be my last contribution from Papua New Guinea. In fact, as I write this, the station has already been dismantled and the antennas have been taken down. All the ham gear is packed and en route to VK. P29NSF went QRT on October 3, 1983,

and will reemerge as VK4VSF from Brisbane.

We have spent 22 years in Papua New Guinea and been witness to great changes in the country. We have seen the peaceful transgression from Australian administration to self-government to independence in 1975. We have seen a people emerge from the Stone Age into the 20th century. I have been a P2 amateur for 31/2 years and enjoyed it immensely. An excellent location, good equipment, and a husband ready to indulge every whim connected with amateur radio made it a pleasure to operate. It has been fun being a DX station; being at the receiving end of pileups gives you a good feeling and it is very good experience. However, at times I have had to go QRT because some operators have no discipline or manners.

On September 20, 1983, at 0153 GMT, I worked VK4MAL aeronautical mobile, operator Barry, on 15m en route to Biak in West Irian, thence Manila and Hong Kong. There is quite a story attached to this one.

The aircraft, a 41-year-old DC3, saw service with the US Army during World War II and was bought by a retired pilot who flew it to Hong Kong for Cathay Pacific. It became that airline's first aircraft and flew the Hong Kong-to-Sydney run carrying passengers and mail.

In 1963, the old girl was sold to Mandated Territory Airline (MAL, hence the callsign) and flew in Papua New Guinea for 10 years. When Ansett Airlines of Papua New Guinea bought out MAL, the DC3 went to bush pilots of Queensland. The DC3 played a major role for bush pilots for another 10 years.

Now Cathay Pacific has bought the old bird back to display her in their museum in Hong Kong. A fitting retirement! The aircraft made a nostalgic flight into Port Moresby on September 19 under its original Cathay registration, VR-HDB, on one side and the Mandated Territory registration, VH-MAL, on the other side. The aircraft is painted in original Cathay Pacific colors.

After refueling in Port Moresby, the DC3 flew to Wewak and made an overnight stop there. I worked the station VK4MAL aeronautical mobile en route Wewak to Biak and consider myself privileged to have had the contact.

The aircraft was due in Hong Kong in time for the 37th anniversary of Cathay Pacific on September 23. Every "Territorian" has a soft spot for DC3 aircraft, as they gave wonderful service to the traveling public in this country in the past. Many a time have we flown "side-saddle" in a DC3! Nowadays Boeing 707s and F28s are used by Air Niugine, but several



The author has the pleasure of presenting a trophy to Kare LA2GV. He was the top-score Norwegian operator in the SAC contest in 1982.



Jorgen LASUF and Svein LA3XI were represented among the top ten DXers in Norway.

DC3s are still with the Papua New Guinea Defense Force.

What news from the P2 amateur scene? A new arrival is Bob P29PR, ex-VS5RP and -G3REP. Bob has just joined the Post and Telecommunication Corporation in Port Moresby. He has a Kenwood TS-180 and is active mainly on CW on all bands. Bob hopes to put P2 back on the CW map! His favorite band is 1.8 MHz, but he has found the noise level extremely high. Bob reports reasonable success on 80m, but as yet has not managed to get into W-land on that band.


No doubt the ranks of amateurs will be swelled in Papua New Guinea as the OK Tedi Mine becomes fully operational in the Western Province. Already on the air from Tabubil are John P29NJS and Stan P29SO.

The Papuan Motor Sports Club in Port Moresby held its annual independence Weekend Car Rally starting at 6 pm on September 14 and ending at 9 am on September 18. Throughout the event, communications were maintained by members of the Papua New Guinea Amateur Radio Society. The communications aspect was an unqualified success with stations working through the Moresby repeater and simplex, and as the rally moved further away from Port Moresby, on 40m during the day and on 80m at night.

Twenty-seven teams participated in the rally, amongst them six entries from Australia. Operating from O car was Peter P29NUK/ZUK, maintaining contact; the director of events, Wayne P29ZWW, upheld communications from another vehicle; the vehicle setting up control was manned by Bob P29BS. Finally, and bringing up the rear in the sweep vehicle, a sturdy 4WD to ensure that all cars had managed to get through safely, was Paul P29NPL. Manned relay stations were in operation, as well as field stations, and Rick P29ZFS was working as a manned 2m repeater. The complete success of the Independence Weekend Car Rally has convinced organizers to hold similar events throughout the year and Peter P29NUK intends to participate as navigator in the next one. Good work by the PNGARS!

The weekend of October 15-16 saw activity for the Jamboree of the Air and the Governor General of Papua New Guinea opened the event on P29JOA. Widespread interest was created, not only amongst guides and scouts, but also among police cadets with a view to forming a police radio club.

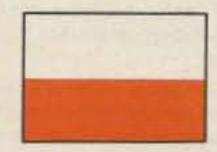So much from me and from Papua New Guinea and my best wishes to everyone.



POLAND

Jerry Scymczak 78-200 Bialogard Buczka 2/3 Poland

RADIO-LOCATION CONTEST

Amateur radio-location contests in Poland are becoming more and more popular. The Radio-Location Contest is organized in two bands, 3.5 MHz and 144 MHz. Competitions in each band are separate. Every entrant for the competition can compete in both bands or in only one of them. All participants of the contest are divided into the following categories:

(a) women irrespective of age;

(b) teenagers (boys and girls under 15 on January 1st of the year of the contest);



CT4UE in his shack.

(c) juniors under 18; (d) men more than 18; (e) seniors over 40.

Women, juniors, and men are appraised as a collective and as a team. The teams taking part in the top competition-the championship of Poland-represent provinces. The number of partakers from any province is to be limited to three in all categories. Individual contestants can take part in other competitions.

Every participant in the contest brings a radio receiver with antennas of one's own, a magnetic compass or the other one, a wristwatch, and a medical certificate of one's health. The use of a radio receiver with noises detectable at a distance of 10 meters is forbidden.

The organizer of the contest provides every participant with a map of the contest terrain. The terrain of the contest is to be predominantly arboreous and differences in its levels cannot be greater than 200 meters.

Five radio transmitters are to be placed at distances not less than 750 meters from each other. The overall length from the start through transmitter number 5 is to be 4-6 kilometers measured on the map. The transmitters are to be hidden so as not to be seen at a distance of 3 to 5 meters. The transmitters must not be placed in buildings or impenetrable places.

In each band, work the 5 transmitters successively: first minute-transmitter number 1, second minute-transmitter number 2..., fifth minute-transmitter number 5, sixth minute—transmitter number 1, and so on.

The emission A1 (telegraphy without modulation) is used in the 3.5-MHz band and A2 (telegraphy with modulation) is used in the 144-MHz band. Recommended keying rate is 30-45 marks /minute. All the transmitters are to operate best at the same frequency: 3500-3600 kHz in the 3.5-MHz band, and 144.500-144.845 kHz in the 144-MHz band. The power output of transmitters is to be 3-5 W and the stability of frequency not worse than 0.05%.

After a start signal one minute before the keying of the first transmitter, competitors in five-man groups run along alleyways 50-250 meters in length. When they are at the ends, their radio receivers are switched on and they begin to look for the transmitters. The sequence of detection is optional; however, transmitter number 5 must be found obligatorily and as the last. Transmitter number 5 ends its keying when all the competitors reach

their goal. The time of the race and the number of detected transmitters determine one's place in the contest.



PORTUGAL

Luiz Miguel de Sousa CT4UE PO Box 32 S. Joao do Estoril 2765 Portugal

It is with great pleasure and personal satisfaction that I write this first column for 73. I will emphasize some aspects of the oldest association of radio amateurs we have in Portugal, known as REP-Rede dos Emissores Portugueses.

REP was first founded in December of 1926 by Mr. D. Eugenio de Avilez, formerly CT1AE, and other enthusiasts. It now has approximately 1900 members, more than 50% of the Portuguese hams. In 1980, it was recognized as a public utility by the government.

According to REP's constitution, we have elections every two years to elect our Board of Directors, and an Annual General Meeting is held to present and approve reports of the past year, including the accounts.

Being a member of IARU, REP offers a lot of services to its members. These are a few of them: reception and shipment of QSL cards from and to other bureaus, handling the paperwork required for examinations and new licenses, renewal of fixed, mobile, or portable licenses, supply of technical books, and publication of the REP magazine or an informative sheet every three months. In either of these two publications, members have the latest news about DX, electronics, awards, telecommunications via satelite, and other important matters.

Every year, we celebrate our anniversary and have a regional contest on VHF and HF with all the Portugese regions (CT1/4, CT2, CT3).

On Mondays at 2230 local time, a radio bulletin is transmitted by CT1REP through the repeaters and also on 80-meter phone. In addition to this, REP gives assistance to all foreign hams who wish to operate from this country. For those interested, we only need a letter requesting this service.

Owing to the existence of reciprocal agreements with some countries, it is very

easy to operate from Portugal. At this time, we have reciprocity with the following countries: West Germany, Austria, Belgium, Denmark, Holland, Switzerland, Sweden, United States of America, England, Canada, Morocco, Brazil, Venezuela, South Africa, and Bolivia. More details about this will be given in the future.

The station that we have in REP is composed of a Yaesu transceiver (FT-902 DM), an FC-902 antenna coupler, an SP-901 external speaker, and an FV-901 DM, all this offered by Yaesu Musen in Japan. We also work on VHF using a Kenwood transceiver.

On the air, mostly around the DX frequencles, we might hear Portuguese hams using several modes of transmission—SSB, CW, SSTV, and RTTY. Some of them (very few) are also active through the satellites for ham use. It may be of interest to you to know that we have 15 repeaters on VHF and 2 on UHF.

We have our weekly meeting on Monday at 2100 local time. If you are in Lisbon, you are kindly invited to visit REP's headquarters, right in the heart of Lisbon. Last November, our good friend Frank Rose W1TIV came to see us and signed the Honour's Book.

Our address is Rua D. Pedro V, 7-4°, phone 361186. Just in case you forget the address, you may contact me at phone number 2688318 during the evenings.



TAIWAN

Tim Chen BV2A/BV2B PO Box 30-547 Taipei, Taiwan 107 Republic of China

To direct the attention of our people to the contribution of communications toward world peace and social developments, the Directorate General of Posts, Republic of China, has released a set of two stamps for commemorating the World Communications Year. Also, Chinese Posts and Telecommunications Department has finally granted permission to a group of Italian hams allowing them to operate in Taiwan.

The DXpedition group, consisting of three members (instead of four as previously reported) of the ARI DX Blue Team (I2MQP/BV, I2BVS/BV, and I2NYN/BV) arrived in Taipei on September 18 via KLM Airlines. They were settled in a new hotel, "Long Life," close to BV2A/BV2B.

On September 19, Mr. Hu, secretary of the China Radio Association, lent hands to take delivery of two transceivers (IC-740, IC-2KL) and accessories from the customs at the CKS International Airport, 45 kilometers from Taipei City. A deposit equivalent to US \$150 approximately instead of customs duty payment was placed for warranty of shipping all imported articles out of the country (ROC) within six months. As a matter of fact, all rigs after operation were duly reshipped out and the deposit money was refunded without any problem.

The imported equipment with a 2-element yagi and a vertical tribander were set up at a QTH near a public park on the roof on a 12-story building which is spacious for antenna installations and good for both receiving and transmitting purposes. The DXpedition station was dismantled on September 24, a half day earlier than the set schedule because of a strong developing and approaching typhoon.


This initial expedition activity was highly evaluated by us. Local authorities are glad to see that through amateur radio, we have done a lot in promoting international goodwill and friendship between people of the world. Making eyeball QSOs further enhances better understanding.

Some local important newspapers—The United Daily, The China News Agency, and The English China News—had good comments on the worldwide friendly movements of amateur radio. This has brought to the attention of the public the progressive quality and unique relations existing in this field.

All visitors were entertained by the China Radio Association at the Army Officers Club. They were introduced to many important officials at the party. Before their departure for home in Milan, a sight-seeing tour was arranged for them to visit the National Palace Museum, where they found great pleasure and relaxation.

I am pleased to have contacted I2MQP/BV, I2BVS/BV, and I2NYN/BV to offer them a new country credit; it also made my day to have the two-way communications domestically.

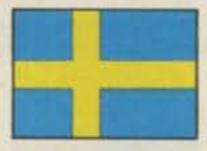I hear a group of JAs are planning to make a DXpedition to BV-land in January, 1984. I shall report in due course.



SWEDEN

Rune Wande SM®COP Frejavagen 10 S-155 00 Nykvarn Sweden

FOX HUNTING

Eskilstuna Sandare Amatorer, Club SK5LW, hosted the 1983 Swedish Championships in Amateur Radio Direction Finding (ARDF), popularly called fox hunting.

The championship is a combination of one daytime and one nighttime hunt. Winner in this combination was Christer Eriksson followed by Gunnar Svensson, a well-known name in these circles here. Neither of them is a ham; this is a sport for anybody. Leif SM5EZM was third but winner of the day event. The total number of participants was 50, of which there were two YLs. Kurt SM5OW, at 65 years of age an old-timer in ARDF, placed 39th and is still going strong.

The "foxes" were five very-low-powered transmitters on 80-meter CW hidden in the woods. The hunters were equipped with maps, compasses, and small ARDF receivers. At night, a flashlight was needed. Some hunters said that they preferred rainy weather because then they didn't hesitate when they crossed a swamp since they were already wet!

DX MEETING IN OREBRO

Club SK4BX, Orebro Sandaramatorer, arranged the popular annual gathering of Swedish DXers. SK4BX is a very active club some 150 km west of Stockholm. The club members always participate in major contests and the QSL cards on the walls show that SK4BK is successful in the DX pileups. The club runs one repeater on VHF 145.650 MHz, and one on UHF 437.650 MHz, as well as a UHF beacon on 432.960 MHz.

In early 1982, the club moved into a fine building (restored by the members) located just outside the city of Orebro. This QTH has great antenna possibilities and the lack of immediate neighbors minimizes the risk of TVI/RFI complaints. The an-



The ARI DX Blue Team in Taiwan. Left to right: I2BVS/BV, I2NYN/BV, BV2A/BV2B, and I2MQP/BV.

tenna tower is 40 meters high (130 ft.) with a TH5DX beam just under the 20-element Cue Dee yagi for 2 meters. Other antennas are for 160, 80, and 40 meters, and in the planning stage is an EME array for 70 centimeters.

Over 50 DXers got to meet in Orebro, some coming from as far away as the most southern part of SM7, an eight-hour drive by automobile. The top attraction was the talk and slide show by Erik SM@AGD, member of the DX Hall of Fame. During the last ten years, Erik has made quite a few very successful operations from the most rare spots throughout the DXworld.

Being a top-grade CW operator, he has made CW buffs as well as SSBers happy. During the last eight months of 1982, Erik toured the rare South Pacific Islands and worked 47,260 contacts.

He tried to limit the number of slides to less than 300, but his interesting and witty comments during the two-hour talk made everybody wish he had brought more. The last slides showed his QSL manager, Joergen SM3CXS, plodding his way to the mailbox through five feet of Nordic December snow to pick up the daily pounds of QSL cards. Joergen has now bought a snowblower to speed up future QSLing.

The club's own DXpedition last summer to OJØ Market Reef was shown by a professionally made film with authentic recorded sound. Goran SM4DHF, Kenneth SM4EMO, and Goran SM4HQO had to halt their operation after two days because of additional paperwork requested by the Finnish licensing authorities which luckily was resolved. During that silent period, they moved their rig and antenna a few feet east on the tiny reef and worked portable SM5! Market Reef is divided by the Finnish-Swedish national border.

SK4BX had furthermore managed to get a video recording from the Heard Island DXpedition slide show narrated by Jim VK9JKS himself.

SWEDISH HAMS DENIED SPECIAL WCY CALL

The United Nations declared 1983 as World Communications Year. In most countries, both the telecommunications authority and the radio amateurs have acknowledged the WCY by various special activities. One way of giving WCY publicity in many countries has been the issuing of special WCY callsigns. In Sweden, the league, SSA, applied for this kind of a call (suffix) to be used by club stations in each call area. However, the Swedish licensing authority, Televerket, has rejected this application.

MOTIONS TO IARU REGION 1 CONFERENCE

The International Amateur Radio Union (IARU) Region 1 Division was formed in 1950 to promote the special interests of the member societies in the International Telecommunication Union Region 1 (Europe, Africa, and parts of Asia) and to represent their interests at ITU conferences.

The Swedish amateur radio league, SSA (Sveriges Sandare Amatorer), has sent three motions to the IARU Region 1 Conference 1984. The first motion is about the Worldwide Grid-Locator System. In Europe, one system has been used for years, primarily in VHF/UHF traffic. It is extremely popular amongst VHF/UHF enthusiasts to collect locator squares in a manner similar to hunting for DXCC countries. The new worldwide locator system was accepted by Region 2 at the Cali Conference in Colombia in 1983, to be used in contests and for awards. Region 3 has also accepted this. The motion from SSA suggests an acceptance by Region 1 and Implementation on January 1, 1985. Basically, the world surface is divided into fields by 18 lines longitude and 18 lines latitude. These fields are divided into squares that are 2 degrees longitude and 1 degree latitude, which will give very good accuracy in determining QTH position.

The second motion concerns the timing system for EME traffic which is different on 144 MHz than on 432 and 1296 MHz. The SSA wants the IARU to recommend uniformity as well as a timing system with one-minute sequences.

The third motion: Because of the collision between the satellite traffic and the Region 1 VHF band plan for repeater channels R8 and R9 on 145.800 and 145.825 MHz respectively, the SSA suggests one solution: channel R9 should be moved to 145.575 MHz (output). The beacons that might be interfered with on 144.975 MHz (input) should be moved. If and when the satellite organizations move away from 145.825 MHz, R9 repeaters could move back to their original frequency.

Furthermore, the SSA suggests that each IARU member society issue an amateur-radio traffic handbook in their own language, in addition to articles about rules and regulations, to be published in the member magazines. The lack of obedience concerning international telecommunication rules and regulations might partly be due to lack of knowledge and understanding.

SSA MEMBERSHIP FEE

The 1984 membership fee is 195 Swedish kronor (approximately 25 US dollars). The league issues the membership magazine, QTC, eleven times a year, runs the QSL bureau, and serves Swedish radio amateurs in various important ways. The work for the club is done voluntarily. The only salaried employees are clerks at the headquarters in Stockholm.



WEST GERMANY

Ralf Beyer DJ3NW Opferkamp 14 3300 Braunschweig Federal Republic of Germany

INTERRADIO '83

On the world's largest fairgrounds, the Interradio '83 opened its gates from October 28-30, 1983, in Hannover, Germany.

Because of the size of the exhibition area and the various activities taking place at the same time, I first found myself at a poultry show. But finally I arrived at hall 19, the place to meet radio amateurs, computer freaks, electronics hobby enthusiasts, and a fair number of equipment and component manufacturers.

The approximately 50 booths were occupied by a dozen equipment manufacturers, half a dozen computer firms, a similar number of component manufacturers/distributors, and some firms offering software support, books, and miscellaneous material needed to organize the ham shack. More than a dozen institutions were represented, including the national radio-amateur organization DARC, AMSAT-DL, DIG, and others.

About 8500 people, including the presidents of national radio-amateur societies from England, Luxembourg, Sweden, Spain, and The Netherlands, visited the convention and many of them took the opportunity to join the presentations provided in two meeting rooms. Papers presented included AMTOR, EME, and OSCAR 10. An indoor "Bier-Garten" provided plenty of room for get-togethers with old and new friends and for the usual small talk.

The meeting of the DXers saw about 100 participants and Baldur Drobnica DJ6SI showed a film about his earlier Glorioso and Juan da Nova DXpedition. Baldur answered questions on the ill-fated tour to Spratly, of course, but fortunately he was not forced to dwell on the details over and over again.

About 250 young students were shown around and many of them joined classes held on fundamentals of electronics and hands-on exercises for the construction of small electronics projects. More than 100 kits for easy-to-build electronic circuits and 60 kits for experiments with a microprocessor were sold at the show.

I enjoyed the meeting very much because of the variety of stimulating impressions, but I could not find anything on the
international level which really turned me
on. However, at least one interesting idea
in this respect was the discussion of better support for future European DXpeditions. Existing plans to form national DX
foundations seem to be channeled more
and more towards a European DX foundation. A more sound financial support of
DXpeditions and a better service of European needs in this field could be desirable
outcomes of this move.

RAMSEY **ELECTRONIC'S**

PARTS WAREHOUSE

2575 Baird Rd. Penfield, NY 14526

716-586-3950

× 62

Inc.

We now have available a bunch of goodies too good to bypass. Items are limited so order today

MINI KITS - YOU HAVE SEEN THESE BEFORE NOW HERE ARE OLD FAVORITE AND NEW ONES TOO. GREAT FOR THAT AFTERNOON HOBBY.





A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna. battery and super instructions. This is the finest unit available

FM-3 Kit \$14.95 FM-3 Wired and Tested 19.95

FM Wireless Mike Kit

Transmits up to 300' to any FM broadcast radio. uses any type of mike Runs on 3 to 9V Type FM-2 has added sensitive mike preamp stage.

FM-1 kit \$3.95

FM-2 kit \$4.95

Universal Timer Kit

Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most timing needs

UT-5 Kit

\$5.95

Color Organ

See music come alive! 3 different lights flicker with music. One light each for, high, mid-range and lows Each individually adjust-

> Complete kit. ML-1 \$8.95

able and drives up

to 300 W. runs on

110 VAC

Video Modulator Kit

Converts any TV to video mohitor. Superstable, tunable over ch. 4-6. Runs on 5-15V accepts std video signal Best unit on the market! Complete kit. VD-1

Super Sleuth

Led Blinky Kit A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges. buttons, warning panel lights, anything! Runs on 3 to 15 volts. Complete kit. BL-1

\$2.95

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker

Complete kit. BN-9 \$5.95

CPO-1

Runs on 3-12 Vdc 1 wall out. 1 KHZ good for CPO Alarm, Audio Oscillator Complete kit \$2.95

Whisper Light Kit

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound the brighter the light Includes mike, controls up to 300 W. runs on 110 VAC.

\$6.95

Complete kit, WL-1

Mad Blaster Kit

Produces LOUD ear shattering and attention getting siren like sound. Can supply up to 15 watts of obnoxious audio Runs on 6-15 VDC

MB-1 Kit

Tone Decoder A complete tone deco-

der on a single PC board Features 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC Useful for touchtone burst detection. FSK, etc. Can also be used as a stable tone encoder Runs on 5 to 12 volts Complete kit TD-1 \$5.95

Siren Kit

Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts uses 3-45 ohm speaker.

Complete kit. SM-3

Crystals

AC Adapters

Good for clocks nicad

chargers, all 110 VAC plug

AC Outlet

Panel Mount with Leads

4/\$1.00

4 16V

1000 pF

047 16V

001 16V

DISK CERAMIC

Trimmer Caps

Sprague - 3-40 pf

Stable Polypropylene

50 ea.

Mini RG-174 Coax

10 ft. for \$1.00

01 16V disk 20/\$1.00

15/\$1.00

20/\$1.00

20/\$1.00

20/\$1.00

\$1.50

\$5.00

\$5.00

\$1.00

\$2.50

\$3.00

3 579545 MHZ

10 000000 MHZ

5 248800 MHZ

8 5 vdc @ 20 mA

16 vac @ 160mA

12 vac @ 250mA

Solid State Buzzers

one end

60 Hz Time Base Runs on 5-15 VDC Low current (2 5ma) 1 min month accuracy TB-7 Kit \$5. TB-7 Assy

Call your Phone Order in Today, TERMS: Satisfaction guaranteed or money refunded COD add \$2.50. Minimum order \$6.00. Orders under \$10.00 add \$1.50. Add 6% for postage, insurance, handling. Overseas add 15% N.Y. residents add 7% tax

CLOCK KITS

Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today!



Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six 4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify).

Clock kit, 12/24 hour, DC-5

Clock with 10 min. ID timer, 12/24 hour, DC-10

\$24.95 \$29.95

For wired and tested clocks add \$10.00 to kit price. SPECIFY 12 OR 24 HOUR FORMAT

SATELLITE TV KIT

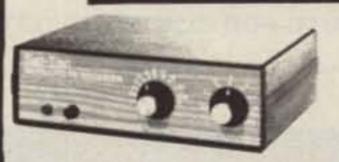


image rejection, fully tunable audio to recover 'hidden' subcarriers, divide by two PLL demodulator for excellent threshold performance, tight tracking AFC to assure drift free reception, and of course, full 24 channel tunable coverage.

Build your satellite TV system around the R2B. close to ten thousand others already have and now It's available in kit form at a new low price. Order THE POPULAR SAT-TEC RECEIVER IN KIT-FORM! yours today.

NEW, LOWER PRICES!

Featured in a Radio Electronics magazine cover story (May 82), the reliable R2B Sat-tec TV receiver is now operating in thousands of locations. The R2B is easy to build; pre-etched, plated boards with screened component layout assures accurate component placement and the critical IF section and local oscillator are preassembled and aligned! All parts are included for the R2B; attractive case, power supply. descriptive operating manual as well as complete assembly instructions. Features of the receiver include: dual conversion design for best A complete Satellite TV System requires a dish antenna, LNA (low noise amplifier). Receiver and Modulator. R2B Receiver Kit R2B Receiver, Wired and Tested \$395.00 \$295.00 120°K LNA \$49.95 RM3 RF Modulator

Prices include domestic UPS shipping

PARTS PARADE

IC SPECIALS LINEAR 74500

\$.35 \$1.50 \$2.95

\$1.50 \$.45 \$1.00 \$1.00 \$1.00 \$1.25 10/\$2.00 \$ 50 \$.50 \$2.95

50 50 .50 \$9.00 \$2.00 \$1.35 \$1.75

READOUTS

FND 359 4" C C

FND 507/510 5 C A

MAN 72/HP7730 33°C A HP 7651 43 C A TRANSISTORS 2N3904 NPN C+F 15/\$1.00 2N3906 PNP C+F 15/\$1.00 2N4403 PNP C+F 15/\$1.00 2N441D NPN C-F 15/\$1.00 2N4916 FET C+F 4/\$1.00 2N5401 PNP C+F 5/\$1.00 2N6028 C+F 4/\$1.00 2N3771 NPN Silicon \$1.50 2N5179 UHF NPN 3/\$2.00 Power Tab NPN 40W 3/\$1.00

Power Tab PNP 40W 3/1.00 MPF 102/2N5484 \$.50 NPN 3904 Type T+R 50/\$2.50 PNP 3906 Type T+R 50/\$2.50 2N3055 2.80 3/\$2.00 2N2646 UJT

\$.40 \$.65 7.447 7475 \$.50 7490 \$.50 74196 \$1.35

SPECIAL \$15.00 11090 \$ 1.25 10116 \$17.50 7208 7207A \$ 5.50

7216D \$21.00 7107C \$12.50 5314 \$ 2.95 5375AB/G \$ 2.95 7001 \$ 6.50

FERRITE BEADS With info and specs 15/\$1.00 6 Hole Balun Beads

Sockets 8 Pin 10/\$2.00 14 Pin 10/\$2.00 16 Pin 10/\$2.00 24 Pin 4/\$2.00 28 Pin 4/\$2.00 40 Pin 3/\$2.00

Diodes 5 1 V Zener 20/\$1.00 1N914 Type 50/\$1.00 8/\$1.00 TKV 2Amp 100V 1Amp 15/\$1.00

25 AMP 100V Bridge \$1.50 each

Mini-Bridge 50V 1 AMP 2 for \$1.00

Resistor Ass't

Assortment of Popular values - 1/4 watt. Cut lead for PC mounting. center. "" leads, bag of 300 or more

\$1.50 Switches Mini toggle SPDT \$1.00 Red Pushbuttons N.O. 3/\$1.00

Earphones 3 leads 8 ohm, good for small tone speakers alarm clocks etc 5 for \$1.00

Mini 8 ohm Speaker Approx 2' diam Round small buzzer 450 Hz. 86 dB sound output on 5-12 vdc at 10-30 mA TTL type for radios mike etc. 3 for \$2.00 compatible

Slug Tuned Coils Small 3/16" Hex Slugs turned coil 3 turns

10 for \$1.00 CAPACITORS TANTALUM ALUMINUM

Dipped Epoxy Electrolytic 1000 uF 16V Radial \$.50 1.5 uF 25V 3/\$1.00 500 uF 20V Axial \$.50 1.8 uF 25V 3/\$1.00 150 uf 16V Axial 5/\$1.00 22 uF 25V 3/\$1.00 10 uF 15V Radial 10/\$1.00 Ceramic IF Filters B.W SOLD OUT , KHZ

DC-DC Converter +5 vdc input prod -9 vdc @ 30ma +9 vdc produces -15 vdc @ 35ma \$1.25

25K 20 Turn Trim Pot \$1.00 tK 20 Turn Trim Pot \$.50 Crystal Microphone

Small 1" diameter 1/4" thick crystal mike cartridge \$.75 Coax Connector

Chassis mount BNC type \$1.00 Parts Bag Asst of chokes disc caps tant resistors

transistors diodes MICA caps etc.

Nice quality clips 5 for \$1.00 * Rubber Grommets 10 for \$1.00 Connectors 6 pin type gold contacts for mA-1003 car clock module sm bag (100 pc) \$1.00 lg bag (300 pc) \$2.50

9 Volt Battery Clips

Leds - your choice, please specify Mini Red, Jumbo Red, High Intensity Red, Illuminator Red 8/\$1 Mini Yellow, Jumbo Yellow, Jumbo Green

Motorola MV 2209 30 PF Nominal cap 20-80 PF - Tunable range -.50 each or 3/\$1.00


Audio Prescaler

Make high resolution audio measurments, great for musical instrument tuning. PL tones, etc. Multiplies audio UP in frequency. selectable x10 or x100, gives 01 HZ resolution with 1 sec gate time! High sensitivity of 25 mv. 1 meg input z and built-in filtering gives great performance. Runs on 9V battery, all CMOS

PS-2 kit \$29.95 PS-2 wired \$39.95

600 MHz PRESCALER

and insurance.

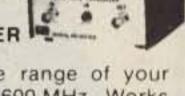

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 my sensitivity, specify -10 or -100

Wired, tested, PS-1B \$59.95 Kit. PS-1B \$44.95

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 W in for 15 out, 4W in for 30 out. Max output of 35 W. incredible value, complete with all parts, less case and T-R relay PA-1, 30 W pwr amp kit \$22.95 6.95 TR-1, RF sensed T-R relay kit

MRF-238 transistor as used in PA-1 8-10db gain 150 mhz

RF actuated relay senses RF (1W) and closes DPDT relay For RF sensed T-R relay

TR-1 Kit \$6.95 **OP-AMP Special**

Complete triple regulated power

Power Supply Kit

supply provides variable 6 to 18 volts at 200 ma and +5 at 1 Amp Excellent load regulation, good filtering and small size. Less transformers, requires 6.3 V ra 1 A and 24 VCT Complete kit. PS-3LT \$6.95

BI-FET LF 13741 - Direct pin for pin 741 cm OV a but 500,000 MEG 50 for only \$9.00 SOLD power drain 10 for \$2.00 **78MG** \$1.25 7812 \$1.00 Regulators 79MG \$1.25 7815 \$1.00 7905 723 \$.50 \$1.25 7912 309K \$1.15 \$1.25 \$1.00 7915 \$1.25

Shrink Tubing Nubs Nice precut poes of shrink size 1" x "4" shrink to "4" Great for splices 50/\$1.00 Opto Isolators - 4N28 type

Molex already precut in length of 7. Perfect

for 14 pin sockets 20 strips for \$1.00

To-220 Heat Sinks

over 3 meg

Mini TO-92 Heat Sinks Thermalloy Brand 5 for \$1.00 3 for \$1.00 \$.50 ea.

Opto Reflectors - Photo diode + LED Molex Pins

\$1.00 ea. CDS Photocells Resistance varies with light, 250 ohms to

3 for \$1.00

THE MOST AFFORDABLE REPEATER

ALSO HAS THE MOST IMPRESSIVE PERFORMANCE FEATURES

(AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!)

JUST LOOK AT THESE PRICES!

Band	Kit	Wired/Tested
10M,6M,2M,220	\$680	\$880
440	\$780	\$980

Both kit and wired units are complete with all parts, modules, hardware, and crystals.

CALL OR WRITE FOR COMPLETE DETAILS.

Also available for remote site linking, crossband, and remote base.




FEATURES:

- SENSITIVITY SECOND TO NONE; TYPICALLY 0.15 uV ON VHF, 0.3 uV ON UHF.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH
 8 POLE CRYSTAL FILTER & CERAMIC FILTER FOR GREATER THAN 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS. SEE R144, R220, AND R451 SPECS IN RECEIVER AD BELOW.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY TUNE TRANSMITTER; UP TO 20 WATTS OUT (UP TO 50W WITH OPTIONAL PA).

HIGH QUALITY MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.


HIGH-PERFORMANCE RECEIVER MODULES

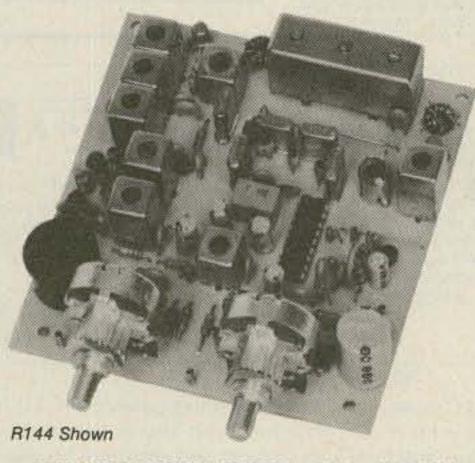


- R144/R220 FM RCVRS for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity, more than -100 dB at ±12 kHz, best available today. Flutter-proof squelch. AFC tracks drifting xmtrs. Xtal oven avail. Kit only \$138.
- R451 FM RCVR Same but for uhf. Tuned line front end, 0.3 uV sens. Kit only \$138.
- R76 FM RCVR for 10M, 6M, 2M, 220, or commercial bands. As above, but w/o AFC or hel. res. Kits only \$118.
 Also avail w/4 pole filter, only \$98/kit.
- R110 VHF AM RECEIVER kit for VHF aircraft band or ham bands. Only \$98.
- R110-259 SPACE SHUTTLE RECEIVER, kit only \$98.

hamlronics®

TRANSMITTERS

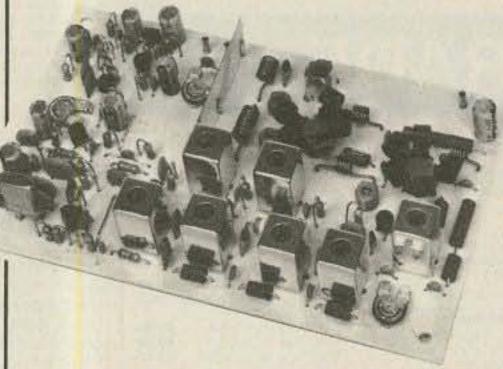


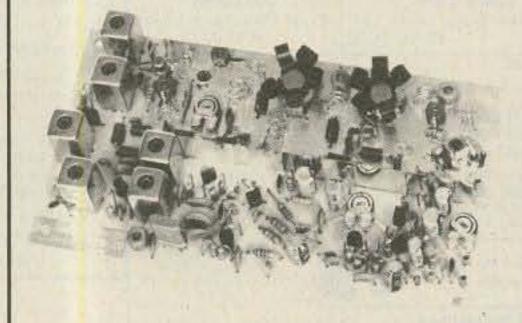 T51 VHF FM EXCITER for 10M, 6M, 2M, 220 MHz or adjacent bands. 2 Watts continuous, up to 2½ W intermittent. \$68/kit.





- T451 UHF FM EXCITER 2 to 3 Watts on 450 ham band or adjacent freq. Kit only \$78.
- VHF & UHF LINEAR AMPLIFIERS. Use on either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Several models. Kits from \$78.
- A16 RFTIGHT BOX Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Designed especially for repeaters, \$20.

ACCESSORIES

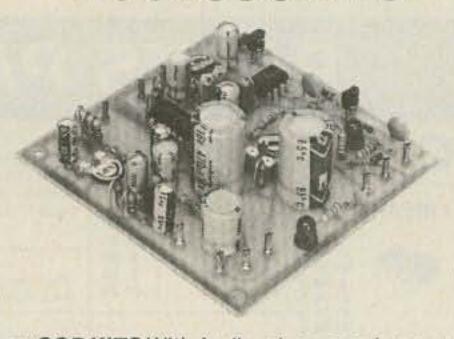

- COR KITS With Audio mixer, speaker amplifier, tail & time out timers. Kit only \$38.
- CWID KITS 158 bits, field programmable, clean audio, rugged TTL logic. Kit only \$68.
- DTMF DECODER/CONTROLLER KITS.
 Control 2 separate on/off functions with touchtones®, e.g., repeater and autopatch.
 Use with main or aux. receiver or with Autopatch.
 Only \$90
- AUTOPATCH KITS. Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control via repeater receiver. Many other features. Only \$90. Requires DTMF Module.

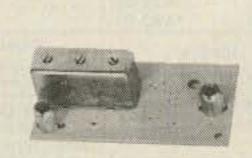

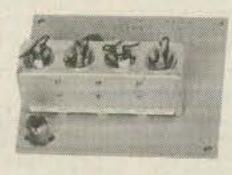

 HELICAL RESONATOR FILTERS available separately on pcb w/connectors.

HRF-144 for 143-150 MHz \$38 HRF-220 for 213-233 MHz \$38 HRF-432 for 420-450 MHz \$48

NEW LOW-NOISE PREAMPS RECEIVING CONVERTERS TRANSMIT CONVERTERS

New low-noise microwave transistors make preamps in the 0.9 to 1.0 dB noise figure range possible without the fragility and power supply problems of gas-fet's. Units furnished wired and tuned to ham band. Can be easily retuned to nearby freq.



Models LNA(), P30, and P432 shown

Model	Tunable Freq Range	Noise Figure	Gain	Price
LNA 28	20-40	0.9 dB	20 dB	\$39
LNA 50	40-70	0.9 dB	20 dB	\$39
LNA 144	120-180	1.0 dB	18 dB	\$39
LNA 220	180-250	1.0 dB	17dB	\$39
LNA 432	380-470	1.0 dB	18dB	\$45
LNA 800	470-960	1.2dB	15dB	\$45


ECONOMY PREAMPS

Our traditional preamps, proven in years of service. Over 20,000 in use throughout the world. Tuneable over narrow range. Specify exact freg. band needed. Gain 16-20 dB. NF = 2 dB or less. VHF units available 27 to 300 MHz. UHF units available 300 to 650 MHz.

P30K, VHF Kit less case	\$18
P30W, VHF Wired/Tested	\$33
P432K, UHF Kit less case	\$21
P432W, UHF Wired/Tested	\$36

P432 also available in broadband version to cover 20-650 MHz without tuning. Same price as P432; add "B" to model #.

HELICAL RESONATOR PREAMPS

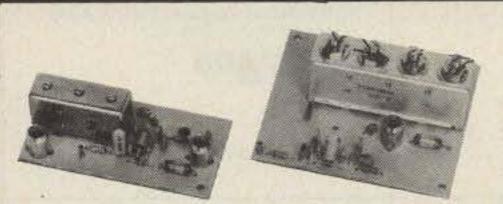

Our lab has developed a new line of low-noise receiver preamps with helical resonator filters built in. The combination of a low noise amplifier similar to the LNA series and the sharp selectivity of a 3 or 4 section helical resonator provides increased sensitivity while reducing intermod and cross-band interference in critical applications. See selectivity curves at right. Noise figure = 1 to 1.2 dB. Gain = 12 to 15 dB.

Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49
HRA-220	213-233 MHz	\$49
HRA-432	420-450 MHz	\$59
HRA-()	150-174MHz	\$69
HRA-()	450-470 MHz	\$79



Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

	Antenna Input Range	Receiver
VHF MODELS Kit with Case \$49 Less Case \$39 Wired \$69	28-32 50-52 50-54 144-146 145-147 144-144.4 146-148 144-148 220-222 220-224	144-148 28-30 144-148 28-30 28-30 27-27.4 28-30 50-54 28-30 144-148
	222-226 220-224 222-224	144-148 50-54 28-30
UHF MODELS Kit with Case \$59 Less Case \$49 Wired \$75	432-434 435-437 432-436 432-436 439.25	28-30 28-30 144-148 50-54 61.25

SCANNER CONVERTERS Copy 72-76, 135-144, 240-270, 400-420, or 806-894 MHz bands on any scanner. Wired/tested Only \$88.

SAVE A BUNDLE ON **VHF FM TRANSCEIVERS!**

FM-5 PC Board Kit - ONLY \$178 complete with controls, heatsink, etc. 10 Watts, 5 Channels, for 2M or 220 MHz.



with speaker, knobs, connectors, hardware. Only \$60.

REPEAT OF A SELLOUT! While supply lasts, get \$60 cabinet kit free when you buy an FM-5 Transceiver kit.


Where else can you get a complete transceiver for only \$178

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 Watts output vhf, 1 Watt uhf.

	Exciter Input Range	Antenna Output		
For VHF, Model XV2 Kit \$79 Wired \$149 (Specify band)	28-30 28-29 28-30 27-27.4 28-30 50-54 144-146 50-54 144-146	144-146 145-146 50-52 144-144.4 220-222* 220-224 50-52 144-148 28-30		
For UHF,	28-30 28-30	432-434 435-437		


Model XV4 50-54 432-436 61.25 439.25 Kit \$99 144-148 432-436* Wired \$169

*Add \$20 for 2M input

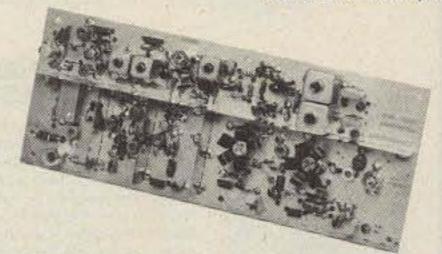

VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Several models, kits from \$78.

LOOK AT THESE ATTRACTIVE CURVES!

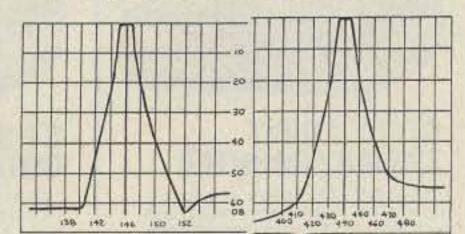

Typical Selectivity Curves of Receivers and Helical Resonators.

IMPORTANT REASONS WHY YOU SHOULD BUY FROM THE **VALUE LEADER:**

- 1. Largest selection of vhf and uhf kits in the world.
- 2. Exceptional quality and low prices due to large volume.
- 3. Fast delivery; most kits shipped same day.
- professional instruction 4. Complete, manuals.
- 5. Prompt factory service available and free phone consultation.
- 6. In business 21 years.
- 7. Sell more repeater modules than all other mfrs. and have for years. Can give quality features for much lower cost.

Call or Write for FREE CATALOG

- (Send \$1.00 or 4 IRC'c for overseas mailing)
- Order by phone or mail Add \$3 S & H per order 233 (Electronic answering service evenings & weekends) Use VISA, MASTERCARD, Check, or UPS COD.

hamlronics, inc.

65-A MOUL RD. ● HILTON NY 14468 Phone: 716-392-9430

Hamtronics ® is a registered trademark


THE FIRST NAME IN ELECTRONIC TEST GEAR



NEW FROM RAMSEY 20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit that will allow you to easily test resistors, capacitors, digital circuits and diodes . TV video sync filter . wide bandwidth & high sensitivity . internal graticule . high quality rectangular CRT front panel trace rotator
 Z axis
 high sensitivity x-y mode
 very low power consumption • regulated power supply • built-in calibrator · rock solid triggering · high quality hook-on probes

high quality hook-on probes included

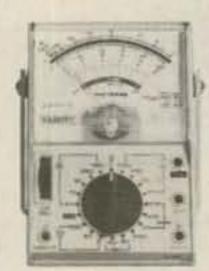

RAMSEY D-1100 **VOM-MULTITESTER**

Compact and reliable, designed to service a wide variety of equipment. Features include . mirror back scale

· double-jeweled precision moving coil . double overload protection . an ideal low cost unit for the beginner or as a spare back-up unit.

test leads and battery included




RAMSEY D-2100 **DIGITAL MULTITESTER**

A compact easy to use unit designed to operate like a pro. Featuring • 3½ digit LCD • low BAT, indicator . all range overload protection . overrange indication · auto-polarity Transistor tester • dual-slope

integration • vinyl carrying case

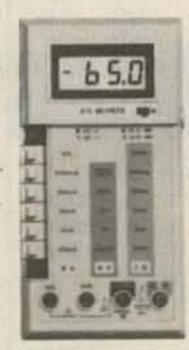
hee test leads, battery & vinyl carrying case included



RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost . In-line color coded push buttons, speeds range selection * abs plastic tilt stand . recessed input jacks . overload protection on all ranges . 3% digit LCD display with auto zero, auto polarity & low BAT, indicator

test leads and battery included

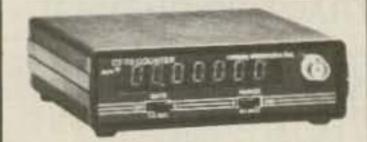


CT-70 7 DIGIT **525 MHz COUNTER**

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp . dual selectable gate times . gate activity indicator

 50mV @ 150 MHz typical sensitivity wide frequency range
 1 ppm accuracy

wired includes AC adapter

CT-70 kit \$99.95

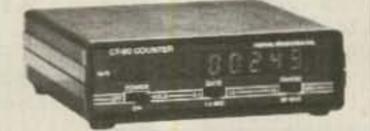

CT-90 9 DIGIT **600 MHz COUNTER**

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits . gate indicator . display hold 25mV @ 150 MHz typical sensitivity

 10 MHz timebase for WWV calibration . 1 ppm accuracy

wired includes AC adapter

CT-90 kit	\$129.95
OV-1 0.1 PPM over timebase	\$59.95
BP-4 nicad pack	8.95



CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. . gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy . display hold . dual inputs with preamps

wired includes AC adapter

CT-125 kit .		 5	149.95
BP-4 nicad	pack	 29250	8.95



CT-50 8 DIGIT **600 MHz COUNTER**

A versatile lab bench counter with optional receive frequency adapter. which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display . 1 ppm accuracy

wired

CT-50 kit	 	\$ 139.95
RA-1 receiver		. 14.95



DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions . 3% digit, % inch LED display . automatic decimal placement . automatic polarity

wired includes AC adapter



PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency . great for PL tone measurements . multiplies by 10 or 100 . 0.01Hz resolution & built-in signal preamp/conditioner

wired includes AC adapter

PS-2 kit \$39.95



PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain . BNC connectors . great for sniffing RF . ideal receiver/TV preamp

wired includes AC adapter

PR-2 kit \$34.95

warranty.



PS-1B 600 MHz **PRESCALER**

Extends the range of your present counter to 600 MHz . 2 stage preamp divide by 10 circuitry • sensitivity:
 25mV @ 150 MHz • BNC connectors · drives any counter

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased

return in original form for refund • add 6% for shipping and insurance to a

maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50

wired includes AC adapter

PS-1B kit \$49.95

ACCESSORIES FOR RAMSEY COUNTERS

Telescopic whip antenna—BNC plug ... \$ 8.95 High impedance probe, light loading . . . 16.95 Low pass probe, audio use 16.95 Direct probe, general purpose use 13.95 Tilt bail, for CT-70, 90, 125 3.95



BANKAMERICARD VISA

PHONE ORDERS CALL 716-586-3950

TELEX 466735 RAMSEY CI >62

• orders under \$10.00 add \$1.50 • NY residents add 7% sales tax • all kits have a 90 day parts warranty. Wired units have a one year parts & labor RAMSEY ELECTRONICS, INC. 2575 Baird Rd.

Penfield, N.Y. 14526

John J. Meshna Jr., Inc.

19 Allerton Street • Lynn, MA 01904 • Tel: (617) 595-2275

SELF STANDING COMPUTER TERMINALS


We acquired a small number of these beautifully made computer terminals which were made by a major U. S. manufacturer. We do not know all the details about them at press time, but we can tell you that someone lost over \$2000 on each of them. They lose you win. The terminals feature 3 micro-processors for powerful capabilities, 106 key, Hall Effect ASCII keyboard, 10 user defineable keys, EAROMs, 16K RAM, 48K ROM, serial RS 232 asynchronous data communications, (synchronous optional), selectable baud rates of 75-38.4K BPS, high resolution, 12" green screen, composite video monitor, 80 X 25 line scrolling display, built-in reverse video option, self-contained, lightweight, tightly regulated switching power supply & more than can be fit in this space. The terminals were designed to be daisy chained around a central host computer and used as individual work stations. The host system could then selectively address any machine in the network for any message it may have. All units are visually inspected prior to shipment. An operators manual is provided w/ each unit. Shpg. wt. 55 lb. model no. MT 686 \$289.00 With the addition of our TP 420 dual FDD system below, you can

create your own office system.

We offer the following as options: schematic pac. 3 lb. USRT for synchronous data comm. w/ installation data

25' RS 232 cable, 1 male & 1 female DB 25 connector

\$ 10.00 \$ 10.00 \$ 20.00

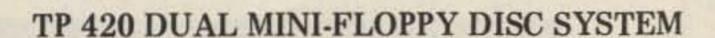

The TP 420 is an extremely versatile mini floppy disc drive system. It consists of 2 Shugart SA 400 51/4" floppy disc drives, associated logic, controller card, power supply, cooling fan, and case. The TP 420 has a built in controller card which features: Z 80 A CPU, Z 80A DMA, Z 80A CTC, Intel 8271 controller chip, 6K RAM, ROM, plus other goodies. We have been told that the serial interface controller card within the TP 420 will support up to 48" drives from the unused port on it. The con troller card can be easily removed should you wish to use it on some other system. Also built in is a tightly regulated, switching power supply which runs on 115/230 v 50/60 hz.. The TP 420 is shipped w/ the interface cable for the MT 686, data, & schematics. Shpg. wt. 22 lb. Stock no. TP 420 \$300.00

PDR-27 NAVY RADIATION METER

Just released by the US Navy. They appear to be in excellent condition and include the fitted aluminum transit case. Batteries not furnished but are available in most electronic supply houses. 4 ranges 0.5 to 500 mr/hr. Removeable hand probe, detection of Beta and Gamma radiation. With todays world conditions and perhaps proximity to a nuke power station, it might provide a little insurance to own one of these instruments. With no facilities to check or test, we offer AS IS, visually OK Schematic provided with each. We have some accessories and offer as an option although not required for operation. Shipping wgt. 22 lb. PDR-27 Rad Meter \$50.00


PDR-27 phones \$7.00 Hi Sensitivity GM tube \$10.00


Approx. 100 page Instr. Book \$10.00 Low Sensitivity GM tube \$5.00

The above listed tubes are already installed in the meter. We are offering these as spares if desired.

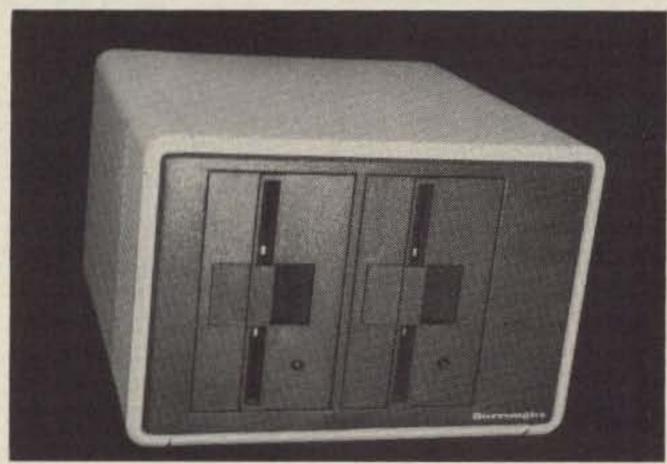PHONE ORDERS accepted on MC, VISA, or AMEX No COD's. Shpg. extra on above. Send for free 72 page catalogue jam packed w/ bargains.





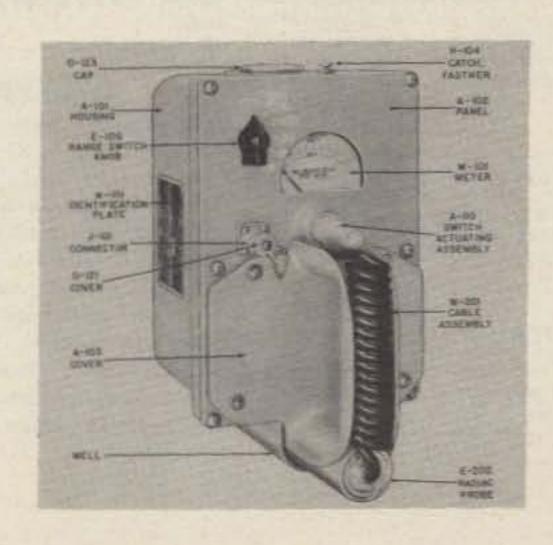

DEALER DIRECTORY

Culver City CA

Jun's Electronics, 3919 Sepulveda Blvd., Culver City CA 90230, 390-8003. Trades 463-1886 San Diego, 827-5732 (Reno NV).

Fontana CA

Complete lines ICOM, DenTron, Ten-Tec, Mirage, Cubic, Lunar, over 4000 electronic products for hobbyist, technician, experimenter. Also CB radio, landmobile. Fontana Electronics, 8628 Sierra Ave., Fontana CA 92335, 822-7710.

San Jose CA

Bay area's newest amateur radio store. New & used amateur radio sales & service. We feature Kenwood, ICOM, Azden, Yaesu, Ten-Tec, Santec & many more. Shaver Radio, Inc., 1378 So. Bascom Ave., San Jose CA 95128, 998-1103.

New Castle DE

Factory Authorized Dealer! Yaesu, ICOM, Ten-Tec, KDK, Azden, AEA, Kantronics, Santec. Full line of accessories. No sales tax in Delaware. One mile off 1-95. Delaware Amateur Supply, 71 Meadow Road, New Castle DE 19720, 328-7728.

Bloomington IL

Rohn Towers—Wholesale direct to users. 23% to 34% discount from dealer price. All products available. Write or call for price list. Also we are wholesale distributors for Antenna Specialists, Regency, and Hy-Gain. Hill Radio, 2503 G.E. Road, PO Box 1405, Bloomington IL 61701-0887, 663-2141.

Boise ID

Rocky Mountain area's newest ham dealer. Call RJM first for AEA, Azden, KDK, Ten-Tec, Butternut, Cushcraft, and morel RJM Electronics, 4204 Overland, Boise ID 83705. 343-4018.

Preston ID

Ross WB7BYZ has the largest stock of amateur gear in the Intermountain West and the best prices. Call me for all your ham needs. Ross Distributing, 78 So. State, Preston ID 83263, 852-0830.

Littleton MA

The reliable ham store serving NE. Full line of ICOM & Kenwood. Yaesu HTs, Drake, Daiwa, B&W accessories. Curtis & Trac keyers. Larsen, Hustler, Telex/Hy-Gain products. Mirage amps., Astron P.S., Alpha Delta protectors, ARRL & Kantronics instruction aids. Whistler radar detectors. Full line of coax fittings. TEL—COM Electronic Communications, 675 Great Rd. (Rt. 119), Littleton MA 01460, 486-3400/3040.

Ann Arbor MI

See us for products like Ten-Tec, R. L. Drake, DenTron and many more. Open Monday through Saturday, 0830 to 1730. WB8VGR, WB8UXO, WD8OKN, and W8RP behind the counter. Purchase Radio Supply, 327 E. Hoover Ave., Ann Arbor MI 48104, 668-8696.

Livonia MI

Complete photovoltaic systems. Amateur radio, repeater, satellite, and computer applications! Call Paul WD8AHO. Encon Photovoltaics, 27600 Schoolcraft Road, Livonia MI 48150, 523-1850.

Hudson NH

Look!—hams, SWLs, and experimenters: parts, books, gear, antennas, towers. Call for quotes. Polcari's ELECTRONICS CENTER, 61 Lowell Road (Route 3A), Hudson NH 03051, 883-5005.

Albany, New York UPSTATE NEW YORK

Kenwood, ICOM, Ten-Tec, Belden, Cushcraft, Larsen, Hustler, ARRL, Hy-Gain, B&W, MFJ, Mirage. New and used equipment. Serving the amateur community since 1942. Adirondack Electronics, Inc., 1991 Central Avenue, Albany NY 12205, 456-0203 (one mile west of Northway exit 2W).

Columbus OH

The biggest and best ham store in the Midwest featuring Kenwood and other quality products with working displays. We sell only the best. Authorized Kenwood service. Universal Amateur Radio, Inc., 1280 Aida Dr., Reynoldsburg (Columbus) OH 43068, 966-4267.

Scranton PA

ICOM, Bird, Cushcraft, Beckman, Fluke, Larsen, Hustler, Antenna Specialists, Astron, Avanti, Belden, W2AU/W2VS, AEA, Vibroplex, HamKey, Amphenol, Sony, B&W, Coax-Seal, Cover Craft, J.W. Miller/Daiwa, ARRL, Ameco, Shure. LaRue Electronics, 1112 Grandview St., Scranton PA 18509, 343-2124.

Dallas TX

IBM PC/Apple aftermarket products; hobbyists' electronics project kits: \$50.00 complete modem kit, subscription/satellite TV decoder kits, EPROM programmer/duplicator, popular memory IC testers, data sheets, application notes, and more than 6000 parts in stock. Semiconductors, discretes, video products, tools Please write for your free literature/catalog. Independent Electronics, 6415-06 Airline Rd., Dallas TX 75205.

Baltimore/Washington

Avantek transistors, amplifiers, oscillators, and LNAs. Coaxial cable and connectors. Blonder Tongue dealer with Microwave laboratory. Applied Specialties, Inc., 10101G Bacon Drive, Beltsville MD 20705. Wash. 595-5393, Balt. 792-2211. 7:30 am to 6:00 pm, Monday thru Friday.

DEALERS

Your company name and message can contain up to 25 words for as little as \$150 yearly (prepaid), or \$15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the May '84 issue must be in our hands by March 1st. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Nancy Ciampa.

PROPAGATION

J. H. Nelson 4 Plymouth Dr. Whiting NJ 08759

EASTERN UNITED STATES TO:

- Late A. R. S.	M. S.P.		-	-	_		٠.	40.1	-		-	0.00
GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	7	7	3A	3A	3A	3A	3A	7A	14	21	21
ARGENTINA	14	7	7	7B	7B	7	14	21A	21A	21A	21A	14/
AUSTRALIA	21	14	7B	7B	7B	7B	7B	14B	14B	14	21A	21A
CANAL ZONE	14	7	7	7	7	7	14	14A	21	21A	21	14/
ENGLAND	7	7	3A	3A	3A	3AB	14	21	21A	14	14B	7
HAWAII	21	14	7B	7	7	7	3A	14B	14	21	21A	21A
INDIA	14B	7B	7B	7B	7.B	7B	14	14A	14	14B	14B	14B
JAPAN	14A	14B	7B	7B	7	7	7	7B	7B	7B	7B	14A
MEXICO	14A	7	7	7	7	7	7	14	14A	21A	21A	21
PHILIPPINES	14A	7B	7B	7B	7B	7B	7B	7B	14B	14B	14B	14
PUERTO RICO	14	7	7	7	7	7	14	14A	21A	21A	21	14A
SOUTH AFRICA	14	7	7	7	7B	7A	21	21A	21A	21A	21	14A
U. S. S. R.	7	3A	3A	3A	7	7B	14	21	14	14B	7B	7B
WEST COAST	21	14	7	7	7	3A .	7	14	21A	21A	21A	21
CENTR	A		U	TIV	E	D	ST	A	TE	S	TO) :
ALASKA	14A	14	7	3A	ЗА	3A	3A	3A	7A	14	21	21
ARGENTINA	14	7	7в	7B	7B	7	7A	21	21A	21A	21A	21
AUSTRALIA	21	14A	7B	7B	7B	7B	7B	7B	14B	14	21A	21A
CANAL ZONE	14	7	7	7	7	先	7A	14A	21	21A	21	21
ENGLAND	7	7	3A	3A	3A	3AB	7.B	14	21A	14	14B	7B
HAWAII	21A	14A	7	7	7	7	3A	7	14	21	21A	21A
INDIA	14B	14B	7B	7B	7B	7B	7B	14B	14B	14B	14B	14B
JAPAN	21	14	7B	7B	7	7	7	7	7B	7B	14B	14A
MEXICO	14A	7	7	7.	7	7	7	14	14A	21A	21A	21
PHILIPPINES	21	14	7B	7B	7B	7B	7B	7	14B	14B	14B	14A
PUERTO RICO	14	7	7	7	7	7	7A	14A	21A	21A	21	14A
SOUTH AFRICA	14	7	7	7	7B	7B	14	21	21A	21A	21	14A
U. S. S. R.	7B	3A	3A.	3A .	7	7B	7B	14	14	14B	7B	7B
WESTE	RI	V	U	רוע	ΓEI	D	ST	A	ΤE	S	TO) :
ALASKA	2.1	14	74	34	34	34	34	34	7.4	14	21	2.1

ALASKA 78 38 38 3A 3A 3A 7A 14 21 21 7B 14A 14 7B 7B 7B 14 21A 21A 21A 21 **ARGENTINA** AUSTRALIA 21A 21 14 7B 14B 14 21A 21A 14B 7B 7B 7B CANAL ZONE 14A 7A 21A 21A 21 14 21 ENGLAND 7B 3A 3AB 3AB 14B 3A 7.B 14A 14 14B 7B 21A 21 14 HAWAII 7A 14 21 21A 21A INDIA 14 14A 14B 7B 7B 7B 7B 7B 14B 14B 14B 14B JAPAN 21A 21 14B 7B 7B MEXICO 21 14 14A 21 21A 21A 21 14B 7B 7B 7B PHILIPPINES 14B 14B 14B 21 14 21 **PUERTO RICO** 14A 21A 21A 21 SOUTH AFRICA 14 7B 7B 7B 14 21 21A 21 14 14B 7B U. S. S. R. 7B 3AB 3AB 3AB 3AB 7B 7B 14B EAST COAST 14 21A 21A 21A

A = Next higher frequency band may also be useful. B = Difficult circuit this period.

First letter = night waves. Second = day waves.

G = Good, F = Fair, P = Poor. * = Chance of solar flares.

= Chance of aurora.

NOTE THAT NIGHT WAVE LETTER NOW COMES FIRST.

February SUN MON TUE WED THU FRI SAT F/F F/G F/G G/G 5 6 F/F G/G G/G F/G G/G G/G F/G 12 13 15 16 18 F/G P/F P/F F/G F/F F/G F/G 19 23 F/G G/G G/G G/G G/G F/F P/F 28 26 P/F F/F F/F F/F

FT-77 The Rig for All Seasons!

Answering the call for an HF rig that goes everywhere, sounds great, and is cost-effective, Yaesu proudly introduces the FT-77 Compact HF Transceiver System.



Computerized Design and Manufacture

The FT-77 design engineers utilized the latest computerized circuit board layout methods, resulting in a compact, reliable transceiver with maximum utilization of available space. Automated insertion techniques are used in assembly, providing improved reliability and quality control over earlier designs.

Operating Versatility

The FT-77 is equipped for operation on all amateur bands between 3.5 and 29.7 MHz, including the three new WARC bands. Fully operational on SSB and CW, the FT-77 includes a dual width noise blanker (designed to minimize the "Woodpecker" or ignition noise), full SWR metering, R.I.T., and optional CW filter with wide/narrow selection. The optional FM-77 permits operation on the FM mode, with front panel squelch sensitivity control.

Expandable Station Concept

Ideal for mobile operation because of its compact size and light weight, the FT-77 forms the nucleus of a versatile base station. Available as options for the FT-77 are the FP-700 AC Power Supply, FV-700DM Synthesized External VFO and Memory System, FTV-707 VHF/UHF Transverter, and FC-700 Antenna Coupler, providing top performance at an extraordinarily low price.

Best of All, It's a Yaesu!

With most experience in transceiver design and manufacture, the Yaesu trademark is your guarantee of quality and durability. We've got all-new technology and an all-new warranty policy to back it up.

See the FT-77 and the all new line of Yaesu HF, VHF, and UHF transceivers, receivers and accessories at your Yaesu Dealer today! It's time you tried a Yaesu!

Price And Specifications Subject To Change Without Notice Or Obligation





0283

YAESU ELECTRONICS CORPORATION, 6851 Walthall Way, Paramount, CA 90723 ● (213) 633-4007 YAESU Cincinnati Service Center, 9070 Gold Park Dr. Hamilton, Ohio 45011 ● (513) 874-3100

Digital DX-terity...



General coverage, Superior dynamic range, 2 VFO's, 8 memories, Scan, Notch...COMPACT!

TS-430S

The TS-430S combines the ultimate in compact styling with advanced circuit design and performance. An all solid-state SSB, CW, and AM transceiver, with FM optional, covering the 160-10 meter Amateur bands, it also incorporates a 150 kHz-30 MHz general coverage receiver having a superior dynamic range, dual digital VFO's, 8 memories, memory scan, programmable band scan, IF shift, notch filter, all-mode squelch, and built-in speech processor.

TS-430S FEATURES:

• 160-10 meter operation, with general coverage receiver

With 160-10 meter Amateur band coverage, including WARC 30, 17, and 12 meter bands, it also features a 150 kHz-30 MHz general coverage receiver. Innovative UP-conversion digital PLL circuit, for superior frequency stability and accuracy. UP/DOWN band switches for Amateur bands or 1-MHz steps across entire 150 kHz-30 MHz range. Two digital VFO's continuously tuneable from band to band. Band information output on rear panel.

- USB, LSB, CW, AM, with optional FM
 Operates on USB, LSB, CW, and AM, with optional FM, internally installed. AGC time constant automatically selected by mode.
- Compact, lightweight design
 Measures only 10-5/8 (270) W x 3-3/4 (96)
 H x 10-7/8 (275) D, inches (mm), weighs only 14.3 lbs. (6.5 kg.).
- Superior receiver dynamic range
 Use of 2SK125 junction-type FET's in
 the Dyna-Mix high sensitivity, balanced,
 direct mixer circuit provides superior
 dynamic range.
- 10-Hz step dual digital VFO's
 10-Hz step dual digital VFO's operate independently, include band and mode information. Different band and mode cross operation possible. Dial torque adjustable. STEP switch for tuning in 10-Hz or 100-Hz steps. A=B switch quickly shifts "B" VFO

to the same frequency and mode as "A" VFO, or vice-versa. VFO LOCK switch provided. RIT control tunes VFO or memory. UP/DOWN manual scan possible using optional microphone.

 Eight memories store frequency, mode, and band data

Memories store frequency, mode, and band data. Eighth memory stores receive and transmit frequencies independently. M.CH switch for operation of memory as independent VFO, or fixed frequency.

- Lithium battery memory back-up Estimated five-year life.
- Memory scan
 Scans memories in which data is stored.
- Programmable automatic band scan
 Scans programmed band width. Scan
 speed adjustable. HOLD switch interrupts
 band or memory scan.
- IF shift circuit for minimum QRM.
 IF passband may be moved to place interferring signals outside the passband, for best interference rejection.
- Tuneable notch filter built-in Deep, sharp, tuneable, audio notch filter.
- Narrow-wide filter selection
 NAR-WIDE switch for IF filter selection on
 SSB and CW when optional filters are in stalled. (2.4 kHz IF filter built-in.)
- Speech processor built-in Improves intelligibility, increases average "talk-power."
- Fluorescent tube digital display Indicates frequency to 100 Hz (10 Hz modifiable).
- All solid-state technology
 Input rated 250 W PEP on SSB, 200 W
 DC on CW, 120 W on FM (optional), 60 W
 on AM. Built-in cooling fan, multi-circuit
 final protection. Operates on 12 VDC, or
 120/220/240 VAC with optional
 PS-430 AC power supply.
- · All-mode squelch circuit, built-in
- · Noise blanker, built-in
- RF attenuator (20 dB)
- Vox circuit, plus semi break-in with side-tone



Optional AT-250 Automatic Antenna Tuner

Designed to match the TS-430S in size, color, and appearance. Functionally compatible with any HF transceiver of 200 watts PEP or lower. (Requires manual bandswitching.)

- · Covers 160-10 meter incl. WARC
- ABC Automatic Band Changing System (when used with TS-430S)
 SWR/Power meter
 4 antenna terminals
 Built-in AC Power Supply.

Other optional accessories:

- · PS-430 compact AC power supply.
- PS-30 or KPS-21 AC power supplies.
- * SP-430 external speaker.
- · MB-430 mobile mounting bracket.
- AT-130 compact antenna tuner, 80-10 m incl. WARC.
- FM-430 FM unit.
- YK-88C (500 Hz) or YK-88CN (270 Hz)
 CW filters.
- YK-88SN (1.8 kHz) narrow SSB filter.
- YK-88A (6 kHz) AM filter.
- MC-42S UP/DOWN hand microphone.
- MC-55 (8P) mobile microphone.
- MC-60A deluxe desk microphone.
- MC-80 UP/DOWN desk microphone.
- MC-85 multi-function desk microphone.

More information on the TS-430S is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220



Specifications and prices are subject to change without notice or obligation